

## Short circuit Admittance parameters (Y-parameters) :-

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$

$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

$$Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$

$$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$

where,  $Y_{11}$  = input driving point admittance.


$Y_{22}$  = output driving point admittance.

$Y_{12}$  = Reverse transfer admittance.


$Y_{21}$  = Forward transfer admittance.
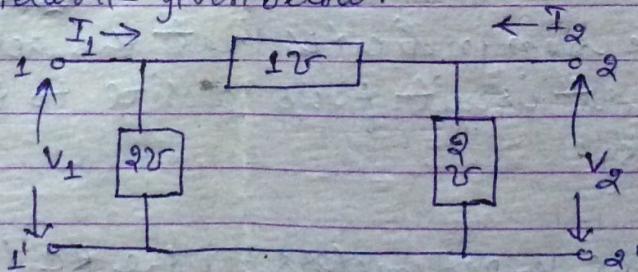
### Examples:-

- Compute the short circuit admittance parameters for the resistive  $\pi$ -network given below:



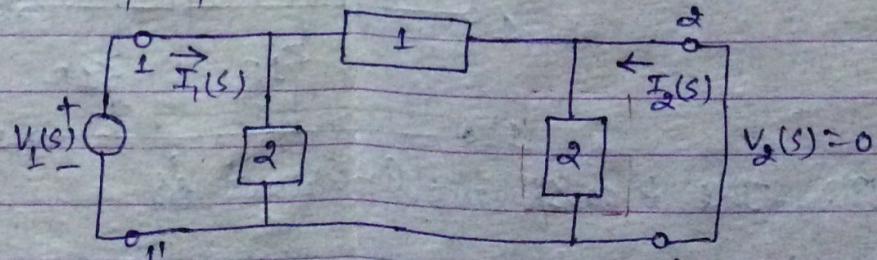Soln: with output port of short circuit i.e.  $V_2(s)=0$




$$Y_{11} = \frac{I_1(s)}{V_1(s)} \Big|_{V_2(s)=0} = \frac{V_1(s) \cdot Y_2(s)}{V_1(s)} = (2+1)\Omega = 3\Omega$$

$$Y_{21} = \frac{I_2(s)}{V_1(s)} \Big|_{V_2(s)=0} = \left( -\frac{1}{2+1} \right) I_2(s) = -\frac{1}{3} \cdot 3V_1 = -1V$$

The -ve sign indicates that the actual current through the short circuit flows opposite to the reference direction of  $I_2(s)$ .

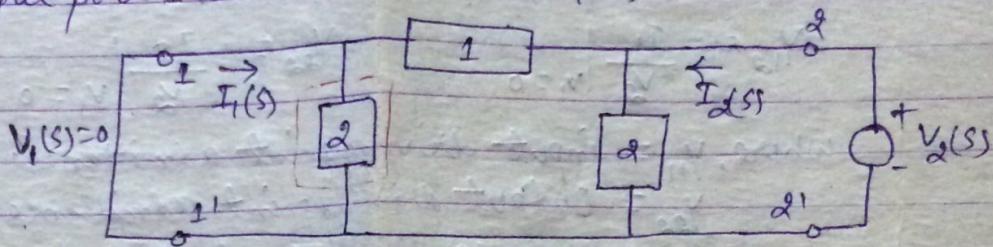With input port 1 short circuit i.e.  $V_1(s)=0$




$$Y_{22} = \frac{I_2(s)}{V_2(s)} \Big|_{V_1(s)=0} = \frac{V_2(s) - Y_2(s)}{V_2(s)} = (2+1)V = 3V$$


$$Y_{12} = \frac{I_1(s)}{V_2(s)} \Big|_{V_1(s)=0} = \left( -\frac{1}{1+2} \right) I_2(s) = -\frac{1}{3} \cdot 3V_2 = -1V$$

The -ve sign indicates that the actual current through the short circuit flows opposite to the reference direction of  $I_1(s)$ .

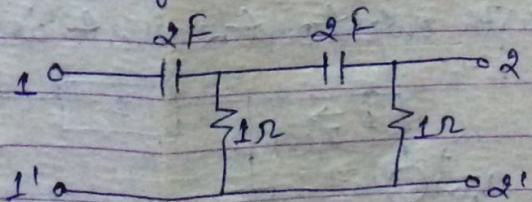- ⑪ Find the y-parameters for the RC Ladder network.




Soln: The transformed circuit is

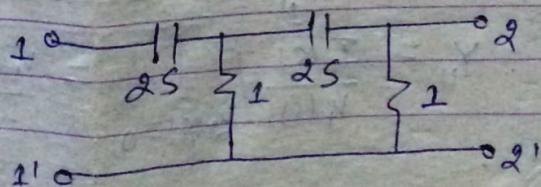

Bhattarai ③

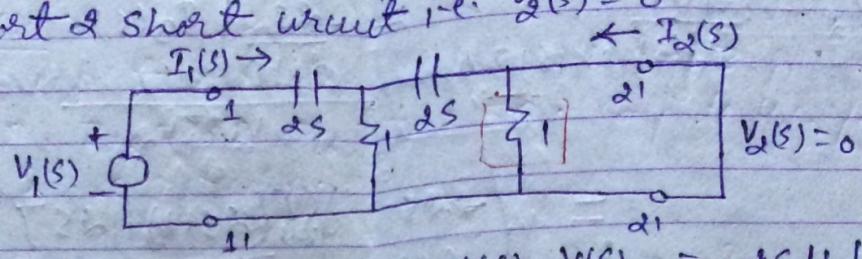With port 2 short circuit i.e.  $V_2(s) = 0$



$$Y_{11} = \frac{I_1(s)}{V_1(s)} \Big|_{V_2(s)=0} = \frac{V_1(s) \cdot V_2(s)}{V_1(s)} = \frac{\omega s}{\omega s + 1}$$

$$= \left( \frac{\omega s(\omega s + 1)}{4s + 1} \right)$$


$$Y_{21} = \frac{I_2(s)}{V_1(s)} \Big|_{V_2(s)=0} = - \frac{(\omega s)}{1 + \omega s} \cdot I_1(s)$$

$$\frac{V_1(s)}{V_1(s)}$$

$$= \left( -\frac{\omega s}{\omega s + 1} \right) \times \frac{\omega s(\omega s + 1)}{4s + 1} \times V_1$$

$$= \left( -\frac{4s^2}{4s + 1} \right) V_1$$

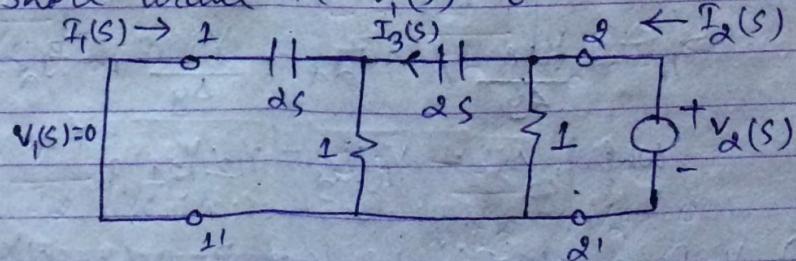With port 1 short circuit i.e.  $V_1(s) = 0$



$$Y_{22} = \frac{I_2(s)}{V_2(s)} \Big|_{V_1(s)=0} = \frac{V_2(s) \cdot [(2s+1) || 2s] + 1}{V_2(s)}$$

$$= \left( \frac{\omega s(\omega s + 1)}{4s + 1} + 1 \right) = \left( \frac{4s^2 + 6s + 1}{4s + 1} \right)$$

$$\begin{aligned}
 Y_{12} &= \frac{I_1(s)}{V_2(s)} \Big|_{V_1(s)=0} = \frac{\left( \frac{-2s}{2s+1} \right) I_3(s)}{V_2(s)} \\
 &= \frac{\left( \frac{-2s}{2s+1} \right) \left\{ \frac{[(2s+1)(12s)]}{[(2s+1)(12s)+1]} \right\} I_2(s)}{V_2(s)} \\
 &= \frac{\left( \frac{-2s}{2s+1} \right) \left[ \frac{2s(2s+1)}{(4s+1)} \times \frac{(4s+1)}{(4s^2+6s+1)} \right] \left( \frac{4s^2+6s+1}{4s+1} \right) V_2}{V_2} \\
 &= \left( \frac{-4s^2}{4s+1} \right)
 \end{aligned}$$

Expressions for Z-parameters in terms of Y-parameters and vice-versa:-

(i) Z-parameters in terms of Y-parameters:-

$$Z_{11} = \frac{Y_{22}}{\Delta_y}, \quad Z_{22} = \frac{Y_{11}}{\Delta_y}, \quad Z_{12} = -\frac{Y_{21}}{\Delta_y} \text{ and } Z_{21} = -\frac{Y_{12}}{\Delta_y}$$

$$\text{where, } \Delta_y = Y_{11}Y_{22} - Y_{12}Y_{21}$$

(ii) Y-parameters in terms of Z-parameters:-

$$Y_{11} = \frac{Z_{22}}{\Delta_Z}, \quad Y_{22} = \frac{Z_{11}}{\Delta_Z}, \quad Y_{12} = -\frac{Z_{21}}{\Delta_Z} \text{ and } Y_{21} = -\frac{Z_{12}}{\Delta_Z}$$

$$\text{where, } \Delta_Z = Z_{11}Z_{22} - Z_{12}Z_{21}$$

Example:-

① A two-port network has the following Z-parameters:  
 $Z_{11} = 10\Omega$ ,  $Z_{22} = 12\Omega$ ,  $Z_{12} = Z_{21} = 5\Omega$ . Compute the Y-parameters for the same network.

Soln:

$$\Delta_Z = Z_{11} \cdot Z_{22} - Z_{12} \cdot Z_{21} = Z_{11} \cdot Z_{22} - (Z_{12})^2 = 10 \times 12 - 5^2 = 95$$

Now,

$$Y_{11} = \frac{Z_{22}}{\Delta_Z} = \frac{12}{95} = 0.1263 \text{ V}$$

$$Y_{22} = \frac{Z_{11}}{\Delta_Z} = \frac{10}{95} = 0.1053 \text{ V}$$

$$Y_{12} = Y_{21} = -\frac{Z_{12}}{\Delta_Z} = -\frac{5}{95} = -0.0526 \text{ V}$$

Transmission Parameters (A, B, C, D) :-

$$V_1 = A \cdot V_2 - B \cdot I_2$$

$$I_1 = C \cdot V_2 - D \cdot I_2$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0}$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$


$$B = \left. -\frac{V_1}{I_2} \right|_{V_2=0}$$

$$D = \left. -\frac{I_1}{I_2} \right|_{V_2=0}$$

Here, A, B, C and D are the transmission parameters / ABCD parameters / chain parameters / general circuit parameters.

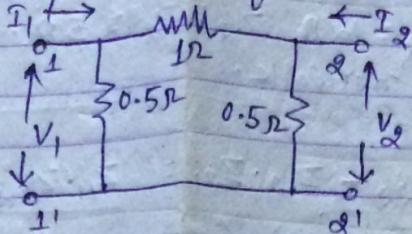
Example:-

- ① Find out ABCD parameters for the resistive  $\pi$ -network:



Soln:

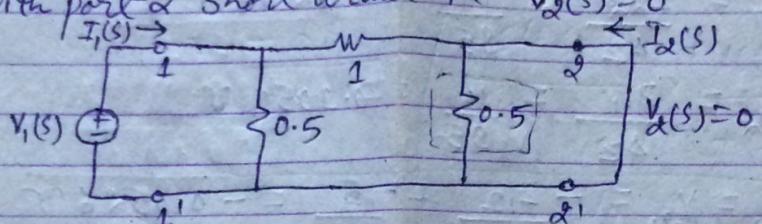
With port 2 short circuit i.e.  $V_2(s) = 0$



$$B = - \frac{V_1(s)}{I_2(s)} \Big|_{V_2(s)=0} = - \frac{(1+0.5) I_1(s)}{I_2(s)} = - \frac{1.5 I_1(s)}{I_2(s)} = - \frac{0.5}{1.5} \times \frac{I_1(s)}{I_2(s)} = 1\Omega$$

$$D = - \frac{I_1(s)}{I_2(s)} \Big|_{V_2(s)=0} = - \frac{I_1(s)}{-0.5 \times I_1(s)} = 3$$

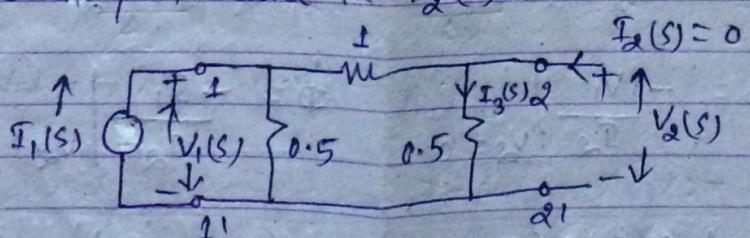With port 2 open circuit i.e.  $I_2(s) = 0$




$$A = \frac{V_1(s)}{V_2(s)} \Big|_{I_2(s)=0} = \frac{(1+0.5) / 1.5 I_1(s)}{I_3(s) \times 0.5} = \frac{0.75 I_1(s)}{\frac{0.5}{2} \times I_1(s) \times 0.5} = 3$$


Q8 Lattices (4)

$$C = \frac{I_1(s)}{V_2(s)} \Big|_{V_2(s)=0} = \frac{I_1(s)}{\frac{I_3(s) \times 0.5}{2}} = \frac{I_1(s)}{\frac{0.5}{2} \times I_1(s) \times 0.5} = 8 \text{ V}$$

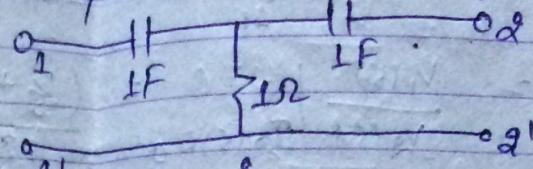
② Find the transmission parameters for the given RC network:



Soln: The transformed circuit is

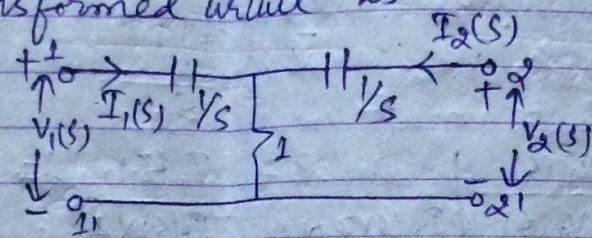

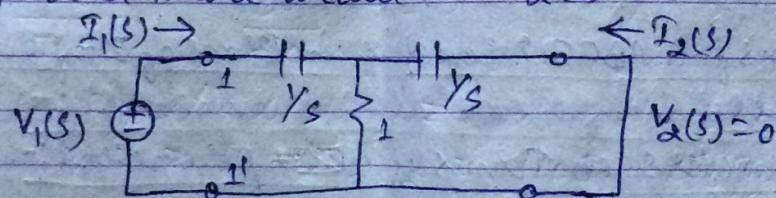
With port 2 short circuit i.e.  $V_2(s) = 0$



$$B = -\frac{V_1(s)}{I_2(s)} \Big|_{V_2(s)=0} = \frac{[(1+Y_S) + Y_S] I_1(s)}{-\left(\frac{1}{1+Y_S}\right) I_1(s)} = \frac{2s+1}{\frac{s(s+1)}{(s+1)}} = \frac{2s+1}{s^2}$$

$$D = -\frac{I_1(s)}{I_2(s)} \Big|_{V_2(s)=0} = \frac{-I_1(s)}{-\left(\frac{1}{1+Y_S}\right) I_1(s)} = \left(\frac{s+1}{s}\right)$$

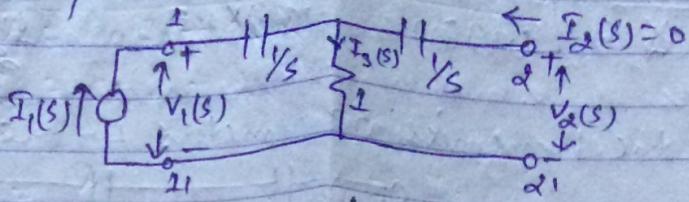With port 2 open circuit i.e.  $I_2(s) = 0$



$$A = \left. \frac{V_1(s)}{V_2(s)} \right|_{I_2(s)=0} = \frac{(1/s + 1) I_1(s)}{I_3(s) \times 1} = \frac{(s+1)}{s} \frac{I_1(s)}{I_1(s)}$$

$$= \frac{(s+1)}{s}$$

$$C = \left. \frac{I_1(s)}{V_2(s)} \right|_{I_2(s)=0} = \frac{I_1(s)}{I_1(s) \times 1} = 1$$

Expressions for ABCD parameters in terms of Z-parameters and Y-parameters :-

i) ABCD parameters in terms of Z-parameters :-

$$A = \frac{Z_{11}}{Z_{21}}, \quad B = \frac{\Delta Z}{Z_{21}} = \frac{Z_{11} \cdot Z_{22} - Z_{21} \cdot Z_{12}}{Z_{21}}$$

$$C = \frac{1}{Z_{21}} \text{ and } D = \frac{Z_{22}}{Z_{21}}$$

ii) ABCD parameters in terms of Y-parameters :-

$$A = -\frac{Y_{22}}{Y_{21}}, \quad B = -\frac{1}{Y_{21}}$$

$$C = -\frac{\Delta Y}{Y_{21}} = -\left( \frac{Y_{11} \cdot Y_{22} - Y_{12} \cdot Y_{21}}{Y_{21}} \right) \text{ and } D = -\frac{Y_{11}}{Y_{21}}$$

Example:- The Z-parameters for a two port network are:  
 $Z_{11} = 40 \Omega$ ,  $Z_{22} = 30 \Omega$ ,  $Z_{12} = Z_{21} = 20 \Omega$ . Compute the transmission parameters for the network. Hence, write the network equations using these two types of parameters.

Soln:

$$A = \frac{Z_{11}}{Z_{d1}} = \frac{40}{20} = 2$$

$$B = \frac{b_2}{Z_{d1}} = \frac{Z_{11}Z_{22} - Z_{d1}Z_{12}}{Z_{d1}} = \frac{40 \times 30 - 20^2}{20} = \frac{800}{20} = 40 \Omega$$

$$C = \frac{1}{Z_{d1}} = \frac{1}{20} = 0.05 V$$

$$D = \frac{Z_{22}}{Z_{d1}} = \frac{30}{20} = 1.5$$

Network equations using Z-parameters are:

$$V_1 = Z_{11}I_1 + Z_{12}I_2 = 40I_1 + 20I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2 = 20I_1 + 30I_2$$

Similarly, network equations using ABCD parameters are:

$$V_1 = AV_2 - BI_2 = 2V_2 - 40I_2$$

$$I_1 = CV_2 - DI_2 = 0.05V_2 - 1.5I_2$$

Note:-

① Z-parameters in terms of ABCD parameters:-

$$Z_{11} = A/C, Z_{12} = \frac{AD - BC}{C}, Z_{21} = 1/C \text{ and } Z_{22} = D/C$$

② Y-parameters in terms of ABCD parameters:-

$$Y_{11} = \frac{D}{B}, Y_{12} = -\left(\frac{AD - BC}{B}\right), Y_{21} = -1/B \text{ and } Y_{22} = A/B$$

Hybrid parameters (h-parameters) :-

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} \frac{V_2}{Z}$$

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0}, \quad h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} \quad \text{and} \quad h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0}$$

Here,  $h_{11}$ ,  $h_{21}$ ,  $h_{12}$  and  $h_{22}$  are the h-parameters.

$h_{11}$  = input impedance.

$h_{21}$  = forward current gain.

$h_{12}$  = reverse voltage gain.

$h_{22}$  = output admittance.

Inverse Hybrid parameters (g-parameters) :-

$$I_1 = g_{11} \cdot V_1 + g_{12} I_2$$

$$V_2 = g_{21} \cdot V_1 + g_{22} \frac{I_2}{Z}$$

$$g_{11} = \left. \frac{I_1}{V_1} \right|_{I_2=0} = \text{open circuit input admittance.}$$

$$g_{21} = \left. \frac{V_2}{V_1} \right|_{I_2=0} = \text{open circuit forward voltage ratio/gain.}$$

$$g_{12} = \left. \frac{I_1}{I_2} \right|_{V_1=0} = \text{short circuit reverse current gain.}$$

$$g_{22} = \left. \frac{V_2}{I_2} \right|_{V_1=0} = \text{short circuit output impedance.}$$

Note: STREAM

SUBJECT

① h-parameters in terms of z-parameters:-

$$h_{11} = \frac{z_{11}z_{22} - z_{21}z_{12}}{z_{22}}, \quad h_{12} = \frac{z_{12}}{z_{22}}$$

$$h_{21} = -\frac{z_{21}}{z_{22}} \text{ and } h_{22} = \frac{1}{z_{22}}$$

② h-parameters in terms of y-parameters:-


$$h_{11} = \frac{1}{y_{11}}, \quad h_{12} = -\frac{y_{12}}{y_{11}}, \quad h_{21} = \frac{y_{21}}{y_{11}} \text{ and}$$

$$h_{22} = \frac{y_{11}y_{22} - y_{12}y_{21}}{y_{11}}$$

③ h-parameters in terms of ABCD parameters:-

$$h_{11} = B/D, \quad h_{12} = \frac{AD - BC}{D}, \quad h_{21} = -1/D \text{ and } h_{22} = C/D$$

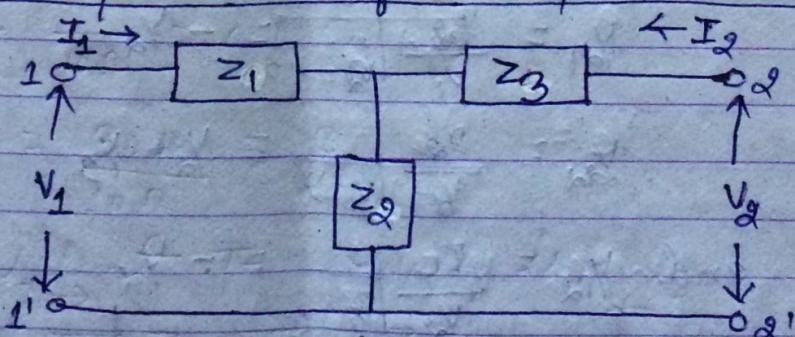T-section Representation of a Two-port Network:-



Z-parameters:-

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = z_1 + z_2$$

$$z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = z_2$$

$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} = z_2 + z_3$$

$$\text{and } Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0} = Z_2$$


Conversely,

$$Z_2 = Z_{12} = Z_{21}$$

$$Z_1 = Z_{11} - Z_{12} \text{ and}$$

$$Z_3 = Z_{22} - Z_{12}$$

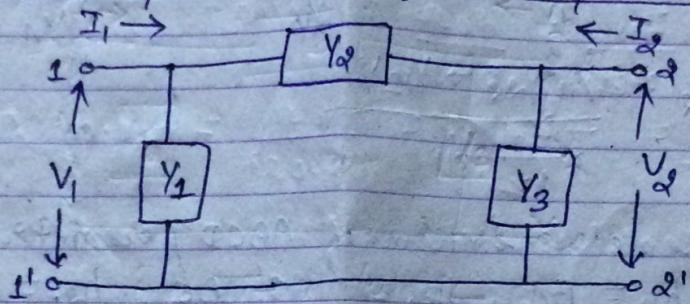π-section representation of a Two-port network :-



Y-parameters:-

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} = Y_1 + Y_2$$

$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0} = -Y_2$$

$$Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0} = Y_1 + Y_3$$

$$\text{and } Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0} = -Y_3$$

Conversely,

$$Y_1 = Y_{11} + Y_{21}$$

$$Y_2 = -Y_{21} \text{ and}$$

$$Y_3 = Y_{12} + Y_{22}$$

Example:-

The Z-parameters of a two-port network are:  $Z_{11} = 20 \Omega$ ,  $Z_{22} = 30 \Omega$ ,  $Z_{12} = Z_{21} = 10 \Omega$ . Find the Y and ABCD parameters of the network. Also, find its equivalent T-network.

Soln:

Y-parameters:-

$$Y_{11} = \frac{Z_{22}}{\Delta Z} = \frac{Z_{22}}{Z_{11}Z_{22} - Z_{12}Z_{21}} = \frac{30 \Omega}{(20 \times 30 - 10^2) \Omega^2} = \frac{30 \Omega}{500 \Omega^2} = 0.06 \text{ V}$$

$$Y_{22} = \frac{Z_{11}}{\Delta Z} = \frac{20 \Omega}{500 \Omega^2} = 0.04 \text{ V}$$

$$Y_{12} = Y_{21} = -\frac{Z_{21}}{\Delta Z} = -\frac{10 \Omega}{500 \Omega^2} = -0.02 \text{ V}$$

ABCD parameters:-


$$A = \frac{Z_{11}}{Z_{21}} = \frac{20 \Omega}{10 \Omega} = 2$$

$$B = \frac{b_2}{Z_{21}} = \frac{500 \Omega^2}{10 \Omega} = 50 \Omega$$

$$C = \frac{1}{Z_{21}} = \frac{1}{10 \Omega} = 0.1 \text{ V}$$

$$D = \frac{Z_{22}}{Z_{21}} = \frac{30 \Omega}{10 \Omega} = 3$$

The equivalent T-network is,

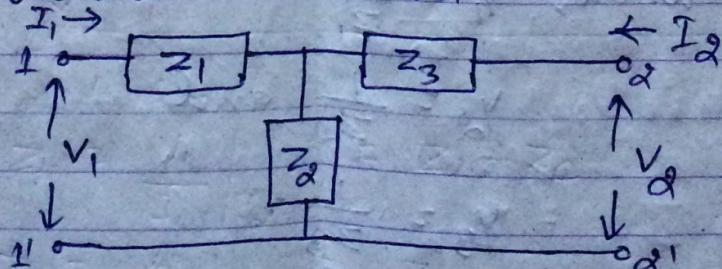

$$\text{Where, } Z_1 = Z_{11} - Z_{12} = 20 - 10 = 10 \Omega$$

$$Z_2 = Z_{12} = Z_{21} = 10 \Omega \text{ and}$$

$$Z_3 = Z_{22} - Z_{12} = 30 - 10 = 20 \Omega$$

T to  $\pi$  and  $\pi$  to T Transformation:-

i) T to  $\pi$  Transformation:-

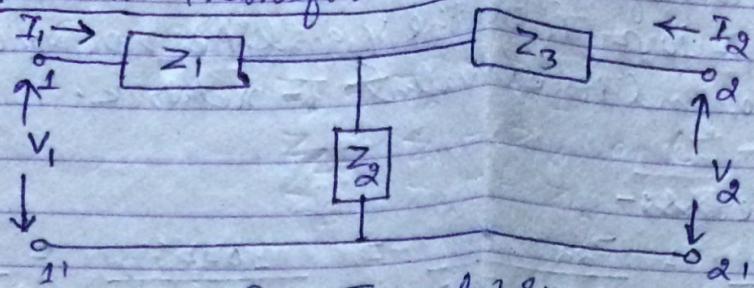


Fig. T-network

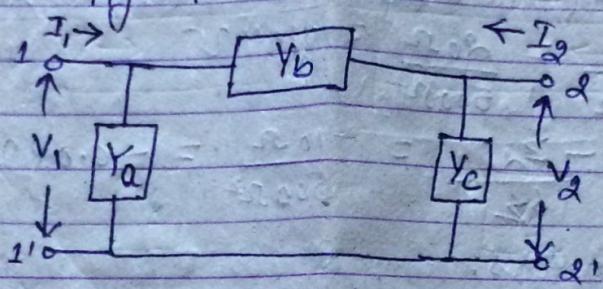


Fig.  $\pi$ -network

$$Y_a = \frac{Y_1 Y_2}{Y_1 + Y_2 + Y_3}$$

$$Y_b = \frac{Y_1 Y_3}{Y_1 + Y_2 + Y_3}$$

$$Y_c = \frac{Y_2 Y_3}{Y_1 + Y_2 + Y_3}$$


$$\text{Where, } Y_i = \frac{1}{Z_i}$$

$$Y_2 = \frac{1}{Z_2} \text{ and}$$

$$Y_3 = \frac{1}{Z_3}.$$

Blettarai ⑥

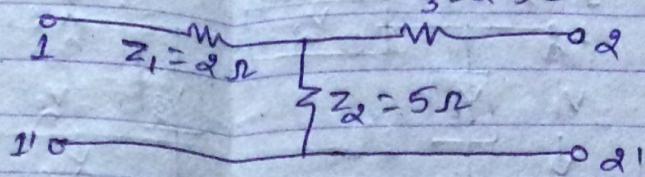Example:- Find the equivalent  $\pi$ -network for the given T-network.



Soln:

Let the equivalent  $\pi$ -network has  $y_b$  as the series admittance and  $y_a$  and  $y_c$  as the shunt/parallel admittances of ports 1 and 2 respectively i.e.

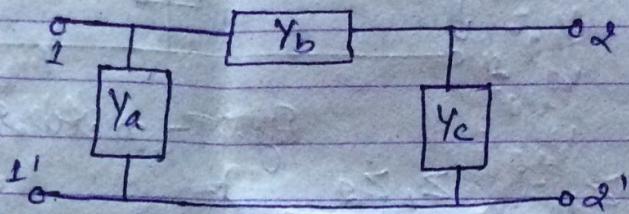


Fig.  $\pi$ -network.

$$\text{Then, } y_1 = \frac{1}{z_1} = \frac{1}{2} = 0.5 S$$

$$y_2 = \frac{1}{z_2} = \frac{1}{5} = 0.2 S$$

$$y_3 = \frac{1}{z_3} = \frac{1}{2.5} = 0.4 S$$

$$\text{Now, } y_a = \frac{y_1 y_2}{y_1 + y_2 + y_3} = \frac{0.5 \times 0.2}{0.5 + 0.2 + 0.4} = \frac{0.1}{1.1} = \frac{1}{11} S$$

$$y_b = \frac{y_1 y_3}{y_1 + y_2 + y_3} = \frac{0.5 \times 0.4}{1.1} = \frac{0.2}{1.1} = \frac{2}{11} S$$

$$y_c = \frac{y_2 y_3}{y_1 + y_2 + y_3} = \frac{0.4 \times 0.2}{1.1} = \frac{0.8}{1.1} = \frac{8}{11} S$$

i)  $\Pi$  to  $T$  Transformation :-

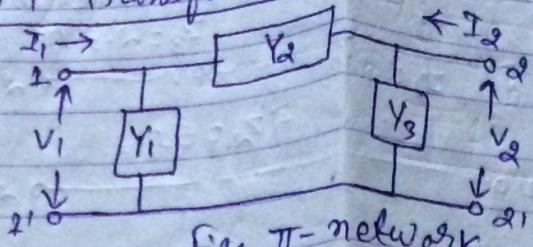


Fig.  $\Pi$ -network

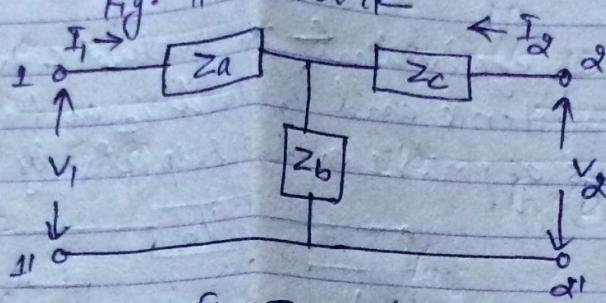


Fig. T-network

$$Z_a = \frac{Z_1 Z_2}{Z_1 + Z_2 + Z_3}$$

$$Z_b = \frac{Z_1 Z_3}{Z_1 + Z_2 + Z_3}$$

$$Z_c = \frac{Z_2 Z_3}{Z_1 + Z_2 + Z_3}$$


where,  $Z_1 = \frac{1}{Y_1}$

$$Z_2 = \frac{1}{Y_2} \text{ and}$$

$$Z_3 = \frac{1}{Y_3}$$

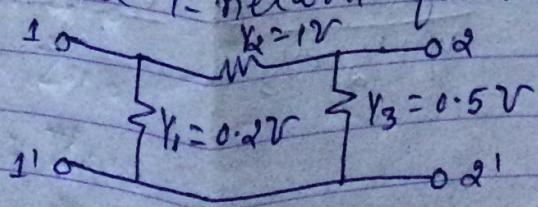Example:-

① Find the equivalent T-network for the given  $\Pi$ -network.



Soln:

Let the equivalent T-network has impedance  $Z_b$  in the parallel/shunt arm and impedances  $Z_a$  and  $Z_c$  in the series arm of ports 1 and 2 respectively i.e.

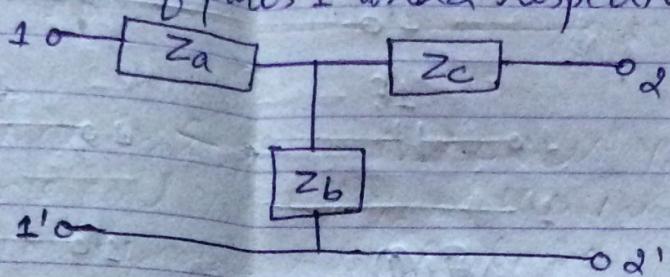


Fig. T-network

Then,

$$Z_1 = \frac{1}{Y_1} = \frac{1}{0.25} = 4 \Omega$$

$$Z_2 = \frac{1}{Y_2} = \frac{1}{1.5} = 0.667 \Omega$$


$$Z_3 = \frac{1}{Z_3} = \frac{1}{0.5} = 2 \Omega$$

$$\text{Now, } Z_a = \frac{Z_1 Z_2}{Z_1 + Z_2 + Z_3} = \frac{4 \times 0.667}{4 + 0.667 + 2} = \frac{2.667}{6.667} = 0.4 \Omega$$

$$Z_b = \frac{Z_1 Z_3}{Z_1 + Z_2 + Z_3} = \frac{4 \times 2}{4 + 0.667 + 2} = \frac{8}{6.667} = 1.2 \Omega$$

$$Z_c = \frac{Z_2 Z_3}{Z_1 + Z_2 + Z_3} = \frac{0.667 \times 2}{4 + 0.667 + 2} = \frac{1.334}{6.667} = 0.2 \Omega$$

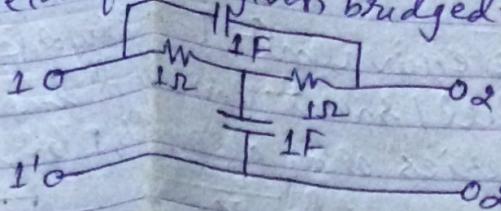II) Find the  $y$ -parameters for the given bridged-T RC network.



Soln:

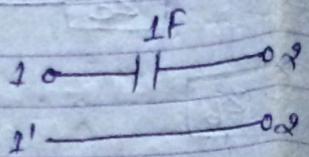


Fig (a)

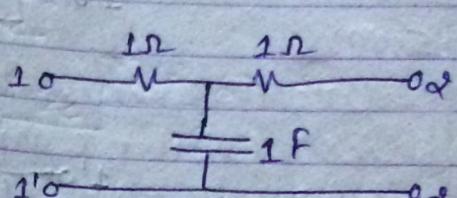


Fig (b)

$$Y_{11a} =$$

$$Y_{21a} =$$

$$Y_{22a} =$$

$$Y_{12a} =$$

$$Y_{11b} =$$

$$Y_{21b} =$$

$$Y_{22b} =$$

$$Y_{12b} =$$

$$\therefore Y_{11eq} = Y_{11a} + Y_{11b}$$

$$Y_{21eq} = Y_{21a} + Y_{21b}$$

$$Y_{22eq} = Y_{22a} + Y_{22b}$$

$$Y_{12eq} = Y_{12a} + Y_{12b}$$

Note:-

In Fig (a) since  $I_1$  and  $I_2$  are not independent i.e. as soon as  $V_1$  will be applied,  $I_1$  will flow causing  $I_2$  to flow as  $(-I_1)$ ,  $Z$ -parameters cannot be determined.

$$\text{Hence, } Z_{11eq} = Z_{11b}$$

$$Z_{21eq} = Z_{21b}$$

$$Z_{22eq} = Z_{22b}$$

$$Z_{12eq} = Z_{12b}$$