

Chapter : 1 REVIEW OF NETWORK Analysis

There are two techniques:

D) Mesh analysis/ loop analysis

USES KVL

② Nodal Analysis


USES KCL

Q.1 Finding the current I_1 and I_2

Sol: From given circuit,

$$I_1 - I_2 = 3 \text{ A}$$
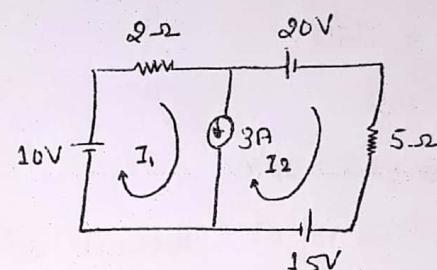
$$\Rightarrow I_1 = I_2 + 3 \quad \dots \dots \dots \textcircled{1}$$



Now, applying KVL to the supermesh corresponding to the current source, we get

$$10 - 2I_1 - 20 - 5I_2 - 15 = 0$$

$$\text{or, } -2I_1 - 5I_2 - 25 = 0$$

$$\text{or, } -2I_1 - 5I_2 = 25$$

$$\text{or, } -2(I_2 + 3) - 5I_2 = 25 \quad [\because \text{From eq. } \textcircled{1}, I_1 = I_2 + 3]$$

$$\text{or, } -2I_2 - 6 - 5I_2 = 25$$

$$\text{or, } -7I_2 = 31$$

$$\text{or, } I_2 = -\frac{31}{7} = -4.43 \text{ A}$$


$$\text{and, } I_1 = -4.43 + 3 = -1.43 \text{ A}$$

Q.2 Find V_1 and V_2

Sol: From given circuit

$$\Rightarrow V_1 - V_2 = 20 \text{ V}$$
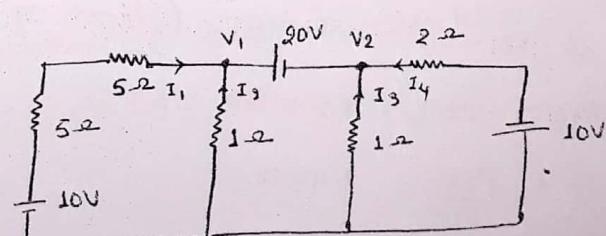
$$V_1 = 20 + V_2 \quad \dots \dots \textcircled{1}$$



Now, applying KCL to the supernode corresponding to the voltage source, we get

$$\frac{v}{10} + \frac{v-10}{1} + \frac{v-10}{1} + \frac{-10-v}{2} = 0$$

$$\text{or, } \frac{10-v}{10} - v_1 - v_2 + \frac{(-10-v)}{2} = 0$$

$$\text{or, } 10-v - 10v_1 - 10v_2 - 50 - 5v_2 = 0$$

$$\text{or, } -11v_1 - 15v_2 = 40$$

$$\text{or, } -11(20+v_2) - 15v_2 = 40 \quad \dots \quad [\text{from eqn. } ①, v_1 = v_2 + 20]$$

$$\text{or, } -220 - 11v_2 - 15v_2 = 40$$

$$\text{or, } -26v_2 = 260$$


$$\therefore v_2 = -10\text{V}$$

$$\text{and, } v_1 = -10 + 20 = 10\text{V}$$

Q.3: Find I_1 and I_2

Soln:

From loop 1st,

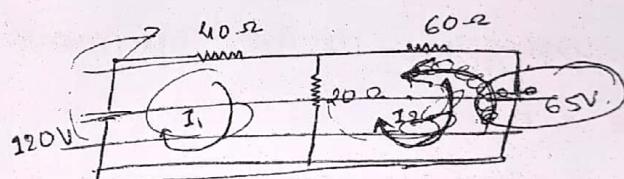

$$120 - 40I_1 - 20(I_1 - I_2) = 0$$

$$\text{or, } 120 - 40I_1 - 20I_1 + 20I_2 = 0$$

$$\text{or, } 60I_1 - 20I_2 = 120$$

$$\text{or, } 30I_1 - I_2 = 6$$

$$\therefore I_2 = 3I_1 - 6 \quad \dots \quad ①$$

Now, from loop 2nd,

~~$$-20(I_2 - I_1) + 60I_2 + 65 = 0$$~~

$$\text{or, } -20I_2 + 20I_1 + 60I_2 - 65 = 0$$

$$\text{or, } 80I_2 - 20I_1 = 65$$

$$\text{or, } 80(3I_1 - 6) - 20I_1 = 65 \quad (\text{from eqn. } ①, I_2 = 3I_1 - 6)$$

$$\text{or, } 240I_1 - 20I_1 = 65 + 480$$



$$\text{or, } I_1 = \frac{545}{220} = 2.48\text{A}$$

$$\text{and, } I_2 = 3 \times 2.48 - 6 = 1.43\text{A.}$$

$$120 - 40I_1 - 20(I_1 - I_2) = 0$$

$$-60I_1 - 65 - 20(I_2 - I_1) = 0$$

$$65 - 60I_2 - 20(I_2 - I_1) = 0$$

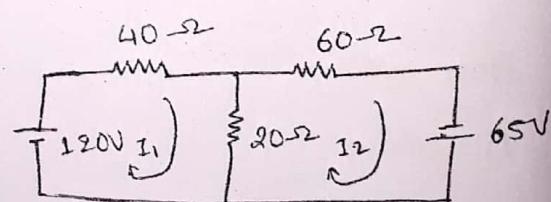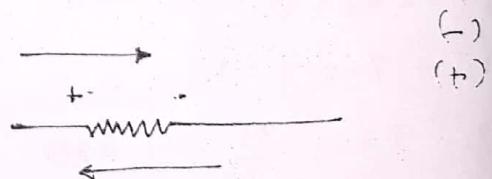

Chapter 2 Circuit differential equations
(Formulation and solutions)

(2)

Electronic circuit

Electronic circuit is the combination of the electronic components connected to form a network providing desired output terms of voltage or current. Three major components of circuit

Sources of energy

Circuit elements

Destination or load [can also be included in circuit elements]

Classification of elements:

Circuit elements can be classified as:

- i) Active and passive
- ii) Linear and non-linear
- iii) Unilateral and Bilateral

Active and passive elements:

Active:

With the ability to control flow of electron (diode, transistor, vacuum tubes, silicon controlled rectifiers)


Passive:

Passive electronic components are those that don't have the ability to control current by means of another electrical signal.
Examples: capacitors, resistors, inductors etc.

i) Linear and non-linear:


Linear:



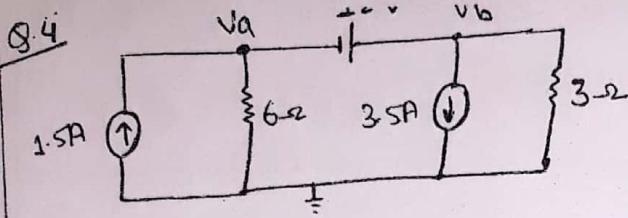

Determine the values of the node voltages, V_a and V_b .

[Ans: $V_a = -12V$, $V_b = 0V$]

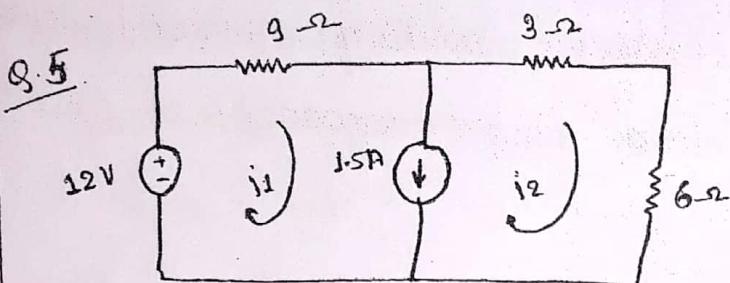

Find i_1 and i_2


[Ans: $I_1 = 1.4167A$ and $I_2 = -83.3mA$]

The relationship between current and voltage will be linear i.e. current or voltage increases in a constant proportion with respect to time. It follows ohms law ($V = IR$)

examples:

- Resistance, capacitor, inductor

Non-linear:

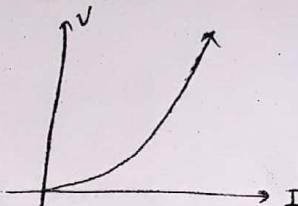

The output characteristics is not linear. It does not follow the ohm law.

examples:


- diode, transistor, transformer, inductor (When the core is saturated)

iii) Unilateral and Bilateral

unilateral:

current flows in only one direction.


e.g. diode

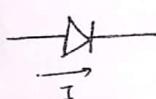

bilateral


current flows in both directions

e.g. Resistance

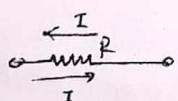

Inductance and capacitance behaviour:


A. Inductance Behaviour:

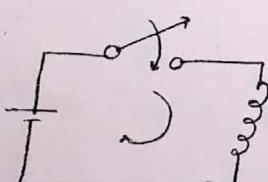

\rightarrow mmf

$N \geq$ No. of turns of coil

It produces magnetic field

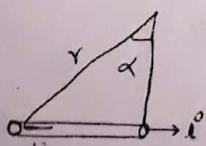

Magnetic field, $dB = \mu_0 cos \alpha dt$ where,

We know,

$$V = \frac{d\psi}{dt}, \quad \psi = \text{Magnetic Flux}$$
$$V = \text{induced voltage}$$

$t = 0^-$ open
 $t = 0$
 $t = 0^+$ closed

NOTE: Permeability, the degree of magnetization of a material in response to a magnetic field]

where, Magnetic flux.

$$\psi = Li \dots \textcircled{1}$$

L is inductance of inductor.

Now,

$$V = \frac{d(Li)}{dt} = L \frac{di}{dt} (\because \text{from } i)$$

$$i = \frac{1}{L} \int_{-\infty}^t V dt$$


$$= \frac{1}{L} \int_{-\infty}^0 V dt + \frac{1}{L} \int_0^t V dt$$

$$i = i(0^-) + i(t > 0)$$

Thus, closing the switch at the instant $t = 0$, maintains the same flux linkage before and after the switch is changed. Thus, "current cannot change instantaneously across inductor."

i.e. At, $t = 0^-$ and $t = 0^+$, current remains same.

For example,

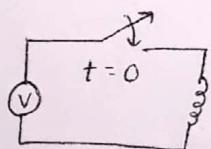


For above circuit, switch is open at $t = 0^-$ and is closed at $t = 0^+$

i.e. $i(0^-) \rightarrow$ current at time $t = 0^- = 0(\text{zero})$

Then, $t = 0^+$

B. Capacitive behaviour:

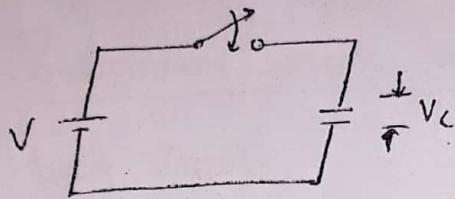

We have, relationship between charge and current

$$i = \frac{dq}{dt} \quad \dots \textcircled{1}$$

Also, $q = CV$ where, C = capacitance

Differentiating on both side w.r.t. t,

$$\frac{dq}{dt} = \frac{d}{dt}(CV) = C \frac{dv}{dt}$$

$$\text{Thus, } \frac{dv}{dt} = \frac{i}{C} \quad (\because \text{from (i)})$$

$$\text{or, } V = \frac{1}{C} \int_{-\infty}^t idt + \frac{1}{C} \int_0^t idt$$


$$V = V_C(0^-) + V_C(t > 0)$$

so, "Voltage cannot change instantaneously across across the capacitor"

$$\text{i.e. } V_C(0^-) = V_C(0^+)$$

Capacitive Behaviour:

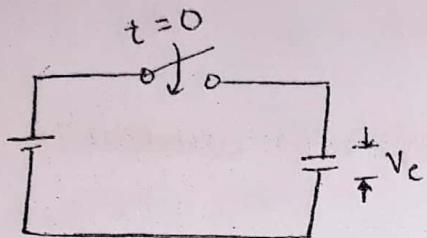- * current and charge relationship : $i = \frac{dq}{dt}$
 - * Voltage and charge relationship : $q = C(V - V_0)$



A diagram of a parallel plate capacitor. Two horizontal lines represent the plates. On the left plate, there are six '+' signs indicating positive charge. On the right plate, there are three '-' signs indicating negative charge. Between the plates, a vertical line labeled 'dielectric' is positioned, representing a dielectric slab. The text 'electric field produces' is written to the right of the diagram.

For capacitor, we have

$$g = cv$$

Differentiating with respect to t , we get

$$\frac{dq}{dt} = c \frac{dv}{dt}$$

For, instantaneous change $dt = 0$ i.e. $(t = 0^-) - (t = 0^+) = 0$

Now, equation ① becomes, $dv = 0$




Thus, "Voltage across capacitor can not change instanteneo
i.e. $V(t=0^-) = V(t=0^+)$.

At, $t = 0^-$, let switch is open

and, at $t = 0$, switch closes


at $t = 0^+$, switch closes

at $t = \infty$ (fully energised)

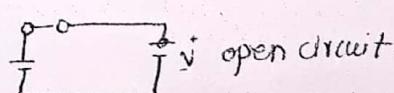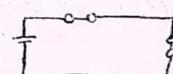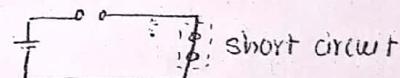

As t increases voltage across capacitor also increases and acts as voltage source. At $t = \infty$, capacitance is fully charged and acts as open circuit i.e. like voltage source.

Inductive Behaviour:

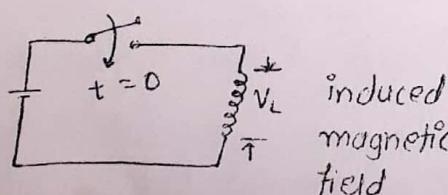

For Inductor, flux ϕ is related with Voltage by the relation

Where,
 $\psi = Li$ Where, $L = \text{inductance}$

$$\text{For } K=1, \quad V = \frac{d\psi}{dt}$$

$$V = \frac{d(Li)}{dt} = L \frac{di}{dt}$$




$$\text{or, } di = \frac{V}{L} dt \dots \textcircled{1}$$

For instantaneous change, $dt = 0$, and if $dt = 0$, $di = 0$.

Thus, "Current across inductor can not change instantaneously"

$$\text{i.e. } i(t=0^-) = i(t=0^+)$$

Let, switch is open at $t = 0^-$

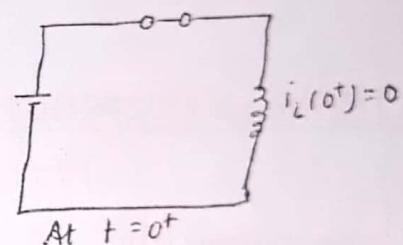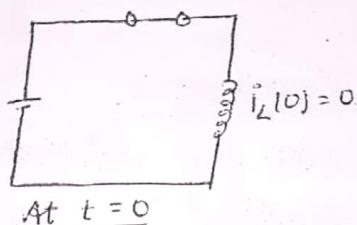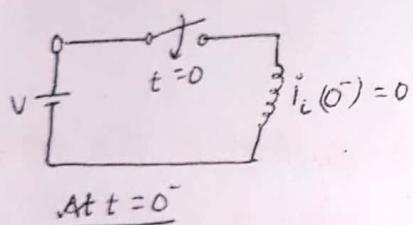


As, t increases, $i_L(t)$ also increases and acts as a current source.

And, at $t = \infty$, inductor is fully energised and acts as short circuit.

Circuit differential equation

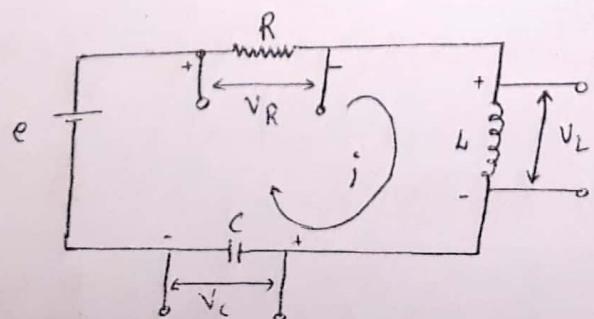Let us consider a circuit with resistor of resistance R , inductor of inductance L and capacitor of capacitance C .



$$\text{Here, } V_R = iR, \quad V_L = L \frac{di}{dt} \quad \text{and, } V_C = \frac{1}{C} \int i dt$$

Now, apply KVL in above circuit, we get

$$e = V_R + V_L + V_C$$

$$\Rightarrow e = IR + L \frac{di}{dt} + \frac{1}{C} \int_{-\infty}^{\infty} i dt$$

This equation is known as integro-differential equation.

Differentiating above equation with respect to t, we get

$$\Rightarrow 0 = R \frac{di}{dt} + L \frac{d^2 i}{dt^2} + \frac{1}{C} i$$

$$\Rightarrow \boxed{L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = 0} \quad \dots \dots \textcircled{a}$$

which is called differential equation.

Differential operator / P operator:

It changes the differential equation to the algebraic expression and is defined by,

$$P() = \frac{d}{dt} () \quad \dots \textcircled{1}$$

For any function $f(t)$

$$Pf(t) = \frac{d}{dt} f(t) \quad \dots \dots \textcircled{2}$$

$$\text{Similarly, } \frac{d^n f(n)}{dt^n} = P^n f(t) \quad \dots \dots \textcircled{3}$$

The above differential equation \textcircled{a} becomes,

$$\boxed{L P^2 i + R P i + \frac{i}{C} = 0}$$

Similarly


$$\int_0^t i dt = \frac{i}{P} \quad (\text{only for finite})$$

NOTE: Inverse operator is defined for finite integral only.
i.e. $\int_0^t i dt \neq \underline{i}$

Driving point operational impedance:

The total impedance of circuit viewed from voltage source is called driving point operational impedance.

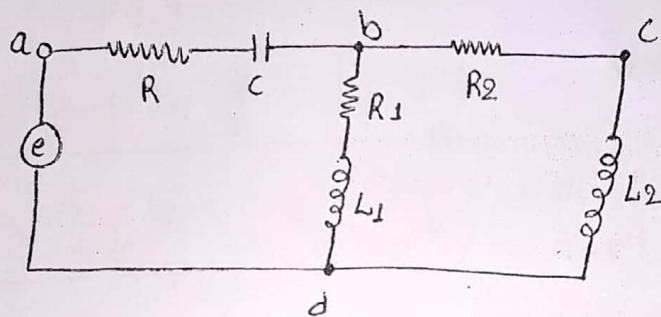Write the equation for the operational impedance for each branch of circuit and determine the expression for driving point operational impedance through terminal pair a-d.




$$\text{For branch } ab \rightarrow Z(P) = R + \frac{1}{PC}$$

$$\text{branch } bd \rightarrow Z_1(P) = R_1 + PL_1$$

$$\text{branch } bc \rightarrow Z_2(P) = R_2 + L_2 P$$

NOW,

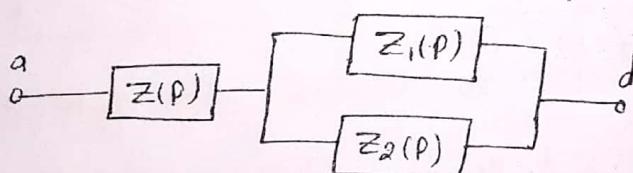


Thus, driving point impedance across terminal ad is,

$$\begin{aligned} Z_{ad} &= Z_p + Z_1(P) // Z_2(P) \\ &= R + \frac{1}{PC} + \left\{ (R_1 + L_1 P) // (R_2 + L_2 P) \right\} \\ &= R + \frac{1}{PC} + \frac{(R_1 + L_1 P)(R_2 + L_2 P)}{R_1 + L_1 P + R_2 + L_2 P} \end{aligned}$$

$$Z_{ad} = R + \frac{1}{PC} + \frac{R_1 R_2 + R_1 L_2 P + R_2 L_1 P + L_1 L_2 P^2}{R_1 + R_2 + L_1 P + L_2 P}$$

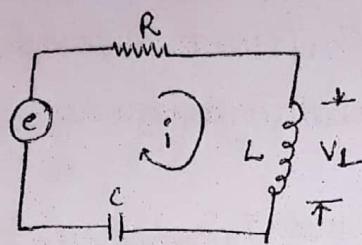Q.2 Find the differential equation that relate v_L and e in the circuit:



Sol: Method I

Applying KVL in the above circuit:

$$e = v_R + v_L + v_C$$

$$\Rightarrow e = iR + v_L + \frac{1}{C} \int i dt \quad \dots \textcircled{1}$$

$$\text{we have, } i = \frac{1}{L} \int v_L dt$$

Now, equation 1 becomes

$$e = \frac{R}{L} \int v_L dt + v_L + \frac{1}{LC} \int \int v_L dt dt \quad \dots \textcircled{11}$$

Differentiating eq 11 w.r.t to t

$$\frac{d\varphi}{dt} = \frac{R}{L} v_L + \frac{dv_L}{dt} + \frac{1}{LC} \int v_L dt$$

Again, differentiating w.r.t t

$$\frac{d^2\varphi}{dt^2} = \frac{R}{L} \frac{dv_L}{dt} + \frac{d^2v_L}{dt^2} + \frac{1}{LC} v_L$$

$$\Rightarrow \boxed{\frac{d^2e}{dt^2} = \frac{d^2v_L}{dt^2} + \frac{R}{L} \frac{dv_L}{dt} + \frac{v_L}{LC}}, \text{ which is the required differential equation.}$$

Method II:

$$\text{we have, } Z_R = R, Z_L = LP, Z_C = \frac{1}{PC}$$

NOW, using Voltage dividing rule, we get,

$$v_L = \frac{e * Z_L}{Z_L + Z_0 + Z_R}$$

$$V_L = \frac{e * L P}{R + L P + \frac{1}{P C}}$$

$$V_L = \frac{e L P * P C}{R P C + L C P^2 + 1} = \frac{P^2 e L C}{P^2 L C + P R C + 1}$$


$$P^2 L C V_L + P R C V_L + V_L = P^2 e L C$$

$$P^2 V_L + \frac{R}{L} P V_L + \frac{1}{L C} V_L = P^2 e$$

Replacing, P by $\frac{d}{dt}$ we get

$$\boxed{\frac{d^2(V_L)}{dt^2} + \frac{R}{L} \frac{d}{dt} V_L + \frac{1}{L C} V_L = \frac{d^2(e)}{dt^2}}, \text{ which is required differential equation}$$

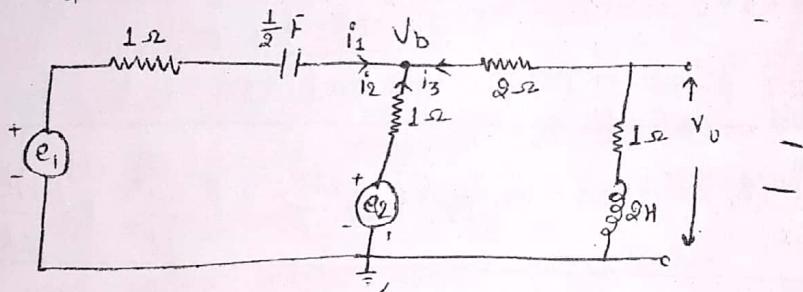3. Find the differential equation that relate V_0 to the source voltage e_1 and e_2 .



Soln: Applying nodal analysis at node b

$$i_1 + i_2 + i_3 = 0$$

$$\frac{e_1 - V_b}{1 + \frac{2}{P}} + \frac{e_2 - V_b}{1} + \frac{0 - V_b}{3 + 2P} = 0$$

$$\Rightarrow \frac{P(e_1 - V_b)}{P+2} + (e_2 - V_b) + \left(\frac{-V_b}{3+2P} \right) = 0$$

$$\Rightarrow P(e_1 - V_b)(3+2P) + (P+2)(3+2P)(e_2 - V_b) - V_b(P+2) = 0$$

$$\Rightarrow (Pe_1 - PV_b)(3+2P) + (P+2)(3e_2 - 3V_b + 2Pe_2 - 2PV_b) - V_bP + 2V_b = 0$$

$$\Rightarrow 3Pe_1 + 2P^2e_1 - 3PV_b - 2P^2V_b + 3Pe_2 - 3PV_b + 2P^2e_2 - 2P^2V_b + 6e_2 - 6V_b + 10PV_b = 0$$

$$3) \Rightarrow -3PV_b - 2P^2V_b - 3PV_b - 2P^2V_b - 6V_b - 4PV_b - V_bP - 2V_b = -3Pe_1 - 3Pe_2 - 2P^2e_2 - 6e_2 + 4Pe_2$$

$$\Rightarrow -4P^2V_b - 11PV_b - 8V_b = -e_1(2P^2 + 3P) - e_2(2P^2 + 7P + 6)$$

$$\Rightarrow V_b = \frac{e_1(2P^2 + 3P) + e_2(2P^2 + 7P + 6)}{4P^2 + 11P + 8} = \frac{e_1P(3+2P) + e_2(3+2P)}{4P^2 + 11P + 8}$$

Now, using voltage dividing rule,

$$V_o = \frac{V_b \times (1+2P)}{(3+2P)} = \frac{e_1P(3+2P) + e_2(3+2P)(P+2)}{(3+2P) \times (4P^2 + 11P + 8)} \times (1+2P)$$

$$V_o = \frac{e_1P(1+2P) + e_2(P+2)(1+2P)}{4P^2 + 11P + 8}$$

$$\text{or, } 4P^2V_o + 11PV_o + 8V_o = 2P^2e_1 + Pe_1 + e_2(2P^2 + 5P + 2)$$

$$\text{or, } 4P^2V_o + 11PV_o + 8V_o = 2P^2e_1 + Pe_1 + 2P^2e_2 + 5Pe_2 + 2e_2$$

Now, Replacing P by $\frac{d}{dt}$

$$4 \frac{d^2}{dt^2}(V_o) + 11 \frac{d}{dt}(V_o) + 8V_o = 2 \frac{d^2}{dt^2}e_1 + \frac{de_1}{dt} + 2 \frac{d^2}{dt^2}e_2 + 5 \frac{de_2}{dt} + 2e_2$$

General formulation of Differential equation

General equation for differential equation is defined as,

$$a_0 \frac{d^n}{dt^n} + a_1 \frac{d^{n-1}}{dt^{n-1}} + a_2 \frac{d^{n-2}}{dt^{n-2}} + \dots = c$$

Where, n = Order of circuit and

if $c=0$, the differential equation is called homogeneous equation.
and, if $c \neq 0$, the differential equation is called non homogeneous eq.

For any electric circuit,

Response function = Network function * Source function

$$\text{i.e. } Y(t) = H(P) \cdot f(t)$$

$= \frac{N(P)}{D(P)} \cdot f(t)$, where $f(t)$ = response function
 $G(P) = \text{network function}$
 $N(P) = \text{Numerator function}$
 $D(P) = \text{Denominator function}$

Solution of non-homogeneous differential equations:

General differential non-homogeneous equation is,

$$y(t) = G(P) \cdot f(t)$$

$$\Rightarrow y(t) = \frac{N(P)}{D(P)} \cdot f(t)$$

$$\Rightarrow y(t) \cdot D(P) = N(P) \cdot f(t)$$

Its solution consists of two parts:

Particular solution / forced solution / steady-state response

Complementary solution / Transient solution / Natural solution

Homogeneous solution.


Forced solution or particular solution

Let $f(t)$ be the applied source function to the network and $y(t)$ be its forced response. It is termed as forced because it remains in existence as long as the source function is applied. It is also called steady state response since it remains in the circuit long after the transient part disappears.

Math review:

<u>Form of $f(t)$</u>	<u>Form of $y(t)$</u>
Exponential Ae^{st}	$D'e^{st}$
Sinusoidal $A\sin \omega t$	$D\sin \omega t + B\cos \omega t$
	$A\cos \omega t$
Constant K	K'
Polynomial t^n	$a_0 + a_1 t_1 + a_2 t_2 + \dots + a_n t_n$

Force response to the constant source:

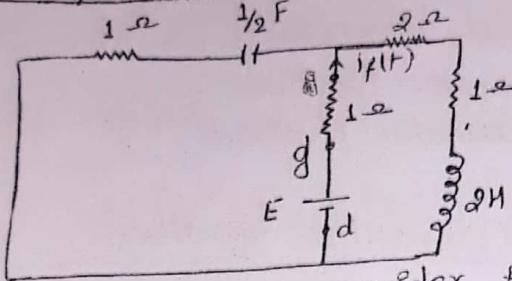

Let us consider the given circuit. Here, E is constant source and let us find force battery current $i_f(t)$, Corresponding the constant source E . The driving point impedance $Z_{gd}(P)$ is found by looking into the circuit through terminal g and d.

$$Z_{gd}(P) = \left[\left(1 + \frac{2}{P} \right) \parallel (3 + 2P) \right] + 1$$

$$= \frac{\left(\frac{P+2}{P} \right) * (3+2P)}{\frac{P+2}{P} + 3+2P} + 1$$

$$= \frac{3P + 2P^2 + 6 + 4P}{P+2 + 3P + 2P^2} + 1$$

$$= \frac{2P^2 + 7P + 6 + 2P^2 + 4P + 2}{2P^2 + 4P + 2} = \frac{4P^2 + 11P + 8}{2P^2 + 4P + 2}$$

$$\text{Then, } i_f(t) = \frac{E}{Z_{gd}(P)} = \frac{2P^2 + 4P + 2}{4P^2 + 11P + 8} E$$

$$\Rightarrow (4P^2 + 11P + 8) i_f(t) = (2P^2 + 4P + 2) E$$

Replace P by $\frac{d}{dt}$ we get

$$4 \frac{d^2}{dt^2} i_f(t) + 11 \frac{d}{dt} i_f(t) + 8 i_f(t) = 2 \frac{d^2 E}{dt^2} + 4 \frac{d E}{dt} + 2E$$

$\because E$ is constant so,

$$4 \frac{d^2}{dt^2} i_f(t) + 11 \frac{d}{dt} i_f(t) + 8 i_f(t) = 2E \quad \dots \textcircled{1}$$

Let, the solution of differential equation is K , i.e. i_f

Then equation $\textcircled{1}$ becomes

$$4 \frac{d^2}{dt^2} K + 11 \frac{d}{dt} K + 8K = 2E$$

$$\Rightarrow K = \frac{E}{4} \quad \therefore i_f(t) = \frac{E}{4}$$

Alternative - method :

We have,

$$i_f(t) = \frac{dP^2 + 4P + 2}{4P^2 + 11P + 8} E$$

$$\text{Let, } P=0, \text{ then } i_f(t) = \frac{E}{4}$$

Conclusion :

Thus, The force response due to constant source can be found as.


$$y_f(t) = [G(P)]_{P=0} f(t)$$

concept :

AS, $t \rightarrow \infty$ capacitor \Rightarrow Open circuit
inductor \Rightarrow short circuit


at, $t \rightarrow \infty$, the above circuit becomes,

$$i_f(t) = \frac{E}{4}$$

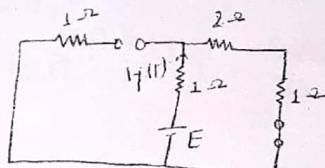

forced response of the exponential source :

Let us consider the following circuit:

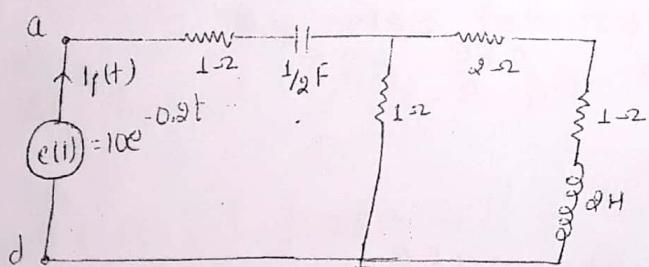

Here, $e(t) = 10e^{-0.9t}$ is the exponential source defined by equation, $e(t) = Ae^{-st}$... ①

Differentiating ① with respect to t

$$\frac{de(t)}{dt} = \frac{d}{dt} Ae^{-st} = -Ase^{-st} = -se(t)$$

$$\therefore Pe(t) = se(t)$$

i.e. differentiating to exponential function leads to algebraic multiplication by s . AS, integration is the inverse operation of differentiation

y

Now, we have

$$y(t) = G(p) \cdot f(t)$$

$$\Rightarrow i_f(t) = \frac{e(t)}{Z_{ad}(p)} \quad \text{... (i)}$$

and,

$$Z_{ad}(p) = \left(1 + \frac{2}{p} \right) + \left\{ 1 / (3 + 2p) \right\} = \frac{4p^2 + 11p + 8}{2p^2 + 4p} \quad \text{... (ii)}$$

from (i) and (ii)

$$i_f(t) = \left(\frac{2p^2 + 4p}{4p^2 + 11p + 8} \right) e(t) = \left(\frac{2p^2 + 4p}{4p^2 + 11p + 8} \right) 10e^{-0.2t}$$

$$\text{or, } (4p^2 + 11p + 8) i_f(t) = (2p^2 + 4p) 10e^{-0.2t}$$

now, replace p by $\frac{d}{dt}$)

$$4 \frac{d^2}{dt^2} i_f(t) + 11 \frac{d}{dt} i_f(t) + 8 i_f(t) = 2 \frac{d^2}{dt^2} (10e^{-0.2t}) + 4 \frac{d}{dt} (10e^{-0.2t})$$

~~we have~~, $i_f(t) = Ae^{-0.2t}$ be the forced response.

Let,

Then,

$$4 \frac{d^2}{dt^2} (Ae^{-0.2t}) + 11 \frac{d}{dt} (Ae^{-0.2t}) + 8Ae^{-0.2t} = 20 \times (-0.2) \frac{d}{dt} e^{-0.2t} + 4 \times (-0.2)^2 A e^{-0.2t}$$

$$\text{or, } 4A(-0.2)(-0.2)e^{-0.2t} + 11A(-0.2)e^{-0.2t} + 8Ae^{-0.2t} = (-4 \times 0.2) e^{-0.2t} + (-0.8) \times 10$$

$$\text{or, } 0.16Ae^{-0.2t} - 2.2Ae^{-0.2t} + 8Ae^{-0.2t} = 0.8e^{-0.2t} - 8e^{-0.2t}$$

$$\text{or, } 5.96Ae^{-0.2t} = -7.2e^{-0.2t}$$

$$\therefore A = -1.21$$

Thus, Required solution is, $i_f(t) = -1.21e^{-0.2t}$

Alternative method,

$$\text{we have, } i_f(t) = \frac{2p^2 + 4p}{4p^2 + 11p + 8} \times 10e^{-0.2t}$$

replace, p by s and put $s = -0.2$

$$i_f(t) = \frac{2s^2 + 4s}{4s^2 + 11s + 8} 10e^{-0.2t} = \frac{2 \times (-0.2)^2 + 4 \times (-0.2)}{4 \times (-0.2)^2 + 11(-0.2) + 8} \times 10e^{-0.2t}$$

$$\frac{0.08 - 0.8}{0.16 - 2.2 + 8} \times 10 e^{-0.2t}$$

$$\frac{-0.72 \times 10}{5.96} \times e^{-0.2t}$$

$$f(t) = -1.21e^{-0.2t}$$

Conclusion:


In general way, if source function is exponential i.e. e^{st} , then corresponding response function $y_f(t)$ is given by

$$y_f(t) = [G(p)] f(t)$$

$$y_f(t) = G(s) \Big|_{s=s_g} f(t)$$

Forced response to sinusoidal source:

Let us consider the following circuit:

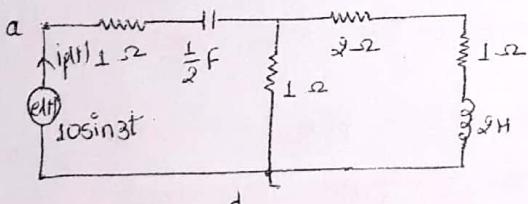

If $I_f(t)$ be the forced response due to sinusoidal function $10\sin 3t$ then $i_f(t) = \frac{e(t)}{Z_{ad}(p)}$. As from the circuit,

$$Z_{ad}(p) = \left(1 + \frac{2}{p}\right) + \left\{ 1 \parallel (3 + 2p) \right\} = \frac{4p^2 + 11p + 8}{2p^2 + 4p}$$

$$\text{Now, } i_f(t) = \frac{\omega p^2 + 4p}{4p^2 + 11p + 8} e(t) = \frac{\omega p^2 + 4p}{4p^2 + 11p + 8} * 10\sin 3t$$

$$\text{or, } (4p^2 + 11p + 8) i_f(t) = (\omega p^2 + 4p) 10\sin 3t$$

$$\text{Now, } (\omega p^2 + 4p) 10\sin 3t = \frac{d}{dt}^2 (10\sin 3t) + 4 \frac{d}{dt} (10\sin 3t)$$

$$= 20 \times 3 \times 3 (-\sin 3t) + 40 \times 3 \cos 3t$$

$$= -180\sin 3t + 120\cos 3t$$

5)

Thus, we get

$$(4P^2 + 11P + 8) i_f(t) = -180 \sin 3t + 120 \cos 3t \quad \dots \dots \textcircled{1}$$

Let, $i_f(t) = A \sin 3t + B \cos 3t$ be the form of solution.

$$\text{Then, } 4P^2 i_f(t) = 4 \frac{d^2}{dt^2} (A \sin 3t + B \cos 3t) = -36 \sin 3t - 36B \cos 3t$$

$$11P i_f(t) = 11 \frac{d}{dt} (A \sin 3t + B \cos 3t) = 33A \cos 3t - 33B \sin 3t$$

Then, equation $\textcircled{1}$ becomes,

$$\text{or, } -36A \sin 3t - 36B \cos 3t + 33A \cos 3t - 33B \sin 3t + 8A \sin 3t + 8B \cos 3t = -180 \sin 3t + 120 \cos 3t$$

$$\text{or, } (-36A - 33B + 8A) \sin 3t + (-36B + 33A + 8B) \cos 3t = -180 \sin 3t + 120 \cos 3t$$

Comparing coefficient of $\sin 3t$ and $\cos 3t$

$$-28A - 33B = -180 \quad \dots \dots \textcircled{2}$$

$$-28B + 33A = 120 \quad \dots \dots \textcircled{3}$$

Solving $\textcircled{2}$ and $\textcircled{3}$, we get

$$A = 4.8 \text{ and } B = 1.38$$

Thus,

$$i_f(t) = 4.8 \sin 3t + 1.38 \cos 3t$$

Alternative method :

$$\text{We have, } i_f(t) = \frac{\omega P^2 + 4P}{4P^2 + 11P + 8} 10 \sin 3t$$

$$= \left[\frac{\omega P^2 + 4P}{4P^2 + 11P + 8} \times 10e^{j3t} \right]^*$$

Now, replacing P by s and $s = 3j$ we get

$$i_f^*(t) = \frac{\omega s^2 + 4s}{4s^2 + 11s + 8} 10e^{j3t} = \frac{\omega (3j)^2 + 4(3j)}{4(3j)^2 + 11(3j) + 8} * 10e^{j3t}$$

$$= \frac{-18 + 12j}{-28 + 33j} * 10e^{j3t} = \frac{21.6 \angle 146.3}{48.3 \angle 130.3} * 10e^{j(3t + 16)}$$

$$= 0.5 \angle 16^\circ * 10e^{j3t} = 5e^{j(3t + 16)}$$

$$\text{or } i_f(t) = \text{Im}(i_f^*(t)) = 5 \sin(3t + 16) = 4.8 \sin 3t + 1.38 \cos 3t$$

Forced response of polynomial source:

Consider the following source:

$$i_f(t) = \frac{e(t)}{Z_{eq}(P)} \quad \dots \textcircled{1}$$

$$\text{here, } Z_{eq}(P) = 1 + \left\{ \left(1 + \frac{2}{P} \right) / (3 + 2P) \right\}$$

$$= \frac{4P^2 + 11P + 8}{4P^2 + 4P + 2}$$

NOW, eq. \textcircled{1} becomes

$$i_f(t) = \frac{2P^2 + 4P + 2}{4P^2 + 11P + 8} e(t)$$

$$\text{or, } (4P^2 + 11P + 8) i_f(t) = (2P^2 + 4P + 2) e(t)$$

Let, $i_f(t) = A + Bt$, be the forced solution then,

$$\Rightarrow 4 \frac{d^2}{dt^2}(A+Bt) + 11 \frac{d}{dt}(A+Bt) + 8(A+Bt) = 2 \frac{d^2}{dt^2}(Bt) + 4 \frac{d}{dt}(Bt) + 4t$$

$$\text{or, } 0 + 11B + 8A + 8Bt = 0 + 8 + 4t$$

$$\text{or, } (11B + 8A) + (8B)t = 8 + (4)t$$

comparing constant and coefficient of t

$$\therefore 8B = 4 \Rightarrow B = \frac{1}{2}$$

$$\therefore 11B + 8A = 8$$

$$\text{or, } 5.5 + 8A = 8$$


$$\text{or, } 8A = 2.5$$

$$A = \frac{2.5}{8} = \frac{5}{16}$$

$\therefore i_f(t) = \frac{5}{16} + \frac{1}{2}t$ is the forced response due to Source $e(t)$.

The natural Response or Transient Response:

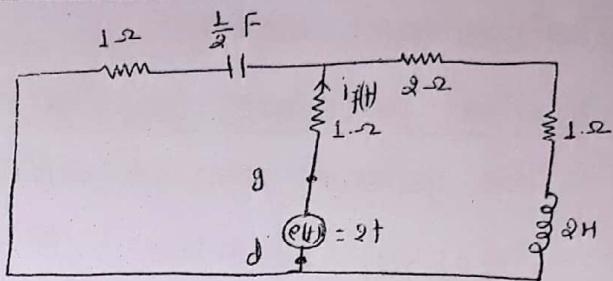→ Transient response represents the characteristic of current or voltage for the circuit having energy storing elements. The transient response is obtained as the solution of homogeneous



5

→ The source is made to zero then the differential equation to homogeneous version.

Generalised procedure for finding transient solution:

The general form of differential is given by

$$D(P) \cdot Y(t) = N(P) \cdot F(t) \quad \dots \textcircled{1}$$


Equation ① represents the non-homogeneous differential equation operator form.

The homogeneous version of the differential equation is obtained by setting $F(t) = 0$ i.e. $D(P) \cdot Y(t) = 0 \quad \dots \textcircled{11}$

Since, Only exponential function qualifies as a solution to differential equation, the P operator can be replaced by the all multiplier's so, $D(S)Y(t) = 0 \quad \dots \textcircled{111}$

$D(S)$ is the denominator polynomial of the network function and $D(S) = 0$ represents the characteristics equation.

Let us consider the following circuit:

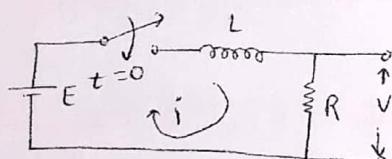

Applying KVL when switch is closed, i.e. at $t = 0^+$

$$E = L \frac{di}{dt} + RI \quad \dots \textcircled{1}$$

$$\text{Now, } V = \frac{E * R}{L \frac{di}{dt} + RI} \Rightarrow VL + VR = ER \Rightarrow \frac{L}{R} VP + V = E$$

$$\Rightarrow \frac{L}{R} \frac{dv}{dt} + V = E \quad \dots \textcircled{111}, \text{ which is non-homogeneous equation}$$

At steady state (i.e. $t \rightarrow \infty$), for constant source, put $p=0$ i.e. $\frac{dv}{dt} = 0$

$$V_f = E \quad \dots \textcircled{111}$$

$$[\text{At } t = 0^-, i_L(0^-) = 0 = i_L(0^+)$$

$$V(0^+) = i_L(0^+) * R = 0, \text{ so eq? } \textcircled{111} \text{ is not for time } t = 0^+$$

Thus, equation ① is not the solution for all the time.

Now, for transient response, the homogeneous version of differ-

$$\frac{L}{R} \frac{dV}{dt} + V = 0 \quad \text{... (iv)}$$

Since, only the exponential form satisfies the above condition so,
let, $V_t = ke^{st}$ be the transient solution.

Then from eq? (iv)

$$\frac{L}{R} \frac{d(ke^{st})}{dt} + ke^{st} = 0$$

$$\frac{L}{R} kse^{st} + ke^{st} = 0 \quad \text{or, } ke^{st} \left(\frac{L}{R}s + 1 \right) = 0$$

$$\text{i.e. } ke^{st} \neq 0 \text{ so, } \frac{L}{R}s + 1 = 0$$

$$\Rightarrow s = -\frac{R}{L}$$

$$\therefore V_t = ke^{-\frac{R}{L}t}$$

$$\text{Then, total solution would be, } V = V_f + V_t \\ = E + ke^{-\frac{R}{L}t} \quad \text{... (v)}$$

Here, k is unknown and it can be found by using initial conditions.

Initial condition:

At ($t = 0^-$)

$$i(0^-) = 0, V(0^-) = 0 \quad [\text{since switch is open}]$$

$$\text{At } (t = 0^+), i(0^+) = i(0^-) = 0 \quad [\text{since, current through conductor inductor can not change instantaneously}] \\ \Rightarrow V(0^+) = 0$$

Now, for $t = 0^+$, eq? (v) becomes

$$V(0^+) = E + ke^{-\frac{R}{L}(0^+)} \Rightarrow 0 = E + k \quad \therefore k = -E$$

Hence, equation (v) becomes,

$$V = E - Ee^{-\frac{R}{L}t} = E(1 - e^{-\frac{R}{L}t})$$

This is the required solution.

Initial conditions:

The calculation of current (i) and voltage (v) and their derivative at $t = 0^+$ are the initial conditions.

Negative (-) and positive (+) sign with time are used to differentiate between the time immediately before and immediately after the operation of the switch.

Initial conditions in elements

① Resistor:

$$V = IR$$

The current through resistance changes instantaneously if voltage across it changes instantaneously.
i.e. $i(0^-) \neq i(0^+)$ and, $V(0^-) \neq V(0^+)$

② Inductor:

$$V = L \frac{di}{dt}$$

The current through the inductor can not change instantaneously.

$$i(0^-) = i(0^+)$$

③ Capacitor:






$$V = \frac{1}{C} \int_0^t i(t) dt$$

The voltage through the capacitor can not change instantaneously.






$$\text{so, } V(0^-) = V(0^+).$$

Summary:






elements and initial conditions

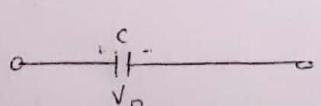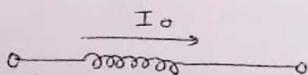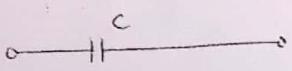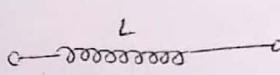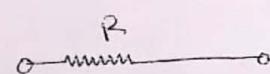

equivalent at $t = 0^+$

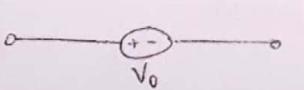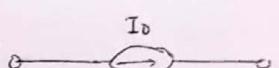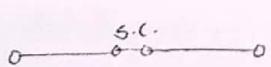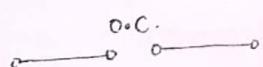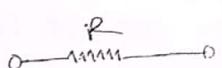

equivalent at $t = 0^-$

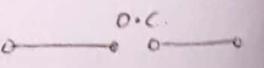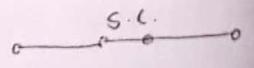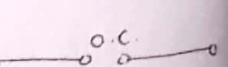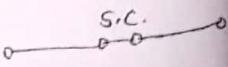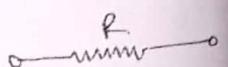

Procedure to find initial conditions

- ① Draw an equivalent circuit for $t = 0^+$, based on the following rule:

→ If there is an inductor in the circuit, then it is an open terminal pair with zero initial current.

current source if there is initial current.


Replace all capacitor by short circuit or by voltage source depending on whether there is initial voltage or not.

Find the values of initial current and voltage i.e. at $t = 0^+$ from equivalent circuits.


To find higher derivatives of initial values we need to write integral differential equation using KVL or KCL for original circuit.

Ques:
① In the circuit shown below: $V = 10V$, $R = 10\Omega$, $L = 1H$, $C = 10\mu F$.

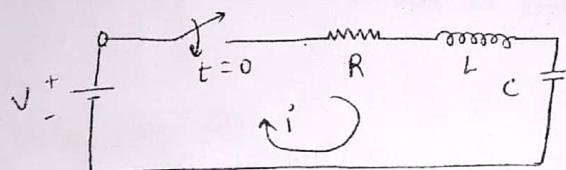Find $i(0^+)$, $\frac{di(0^+)}{dt}$, $\frac{d^2i(0^+)}{dt^2}$:



At $t = 0^+$, the equivalent circuit is

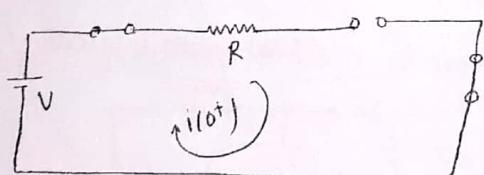

Here,

$$i(0^+) = 0$$

Using, KVL for $t > 0^+$

$$V = iR + L \frac{di}{dt} + V_C \quad \dots \textcircled{1}$$

At, $t = 0^+$,

$$10 = i(0^+) R + L \frac{di(0^+)}{dt} + V_C(0^+)$$


Here, $V_C(0^+) = V_C(0^-) = 0$ since, Voltage across capacitor can not change instantaneously.

Now,

$$10 = \frac{di(0^+)}{dt}$$

$$\therefore \frac{di(0^+)}{dt} = 10 \text{ amp/sec.}$$

Equivalent circuit for $t > 0^+$

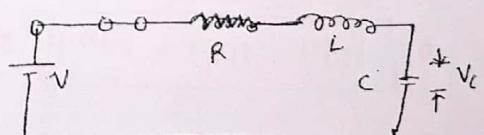

Equation ① can be written as,

$$v = iR + L \frac{di}{dt} + \frac{1}{C} \int i dt \quad \dots \dots \textcircled{1}$$

Differentiating eq. ① w.r.t t, we get

$$R \frac{di}{dt} + L \frac{d^2 i}{dt^2} + \frac{i}{C} = 0$$


At, $t = 0^+$

$$R \frac{di(0^+)}{dt} + L \frac{d^2 i(0^+)}{dt^2} + \frac{i(0^+)}{C} = 0$$

$$10 \times 10 + \frac{d^2 i(0^+)}{dt^2} + 0 = 0$$

$$\therefore \frac{d^2 i(0^+)}{dt^2} = -100 \text{ amp/sec}^2$$

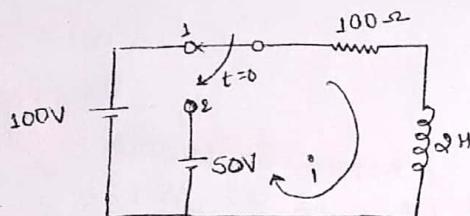- ② Find the total response for $t > 0$ for i. If switch was initially on steady state is reached and moved to position 2 at time $t = 0$.




Soln: When the switch is at position 1.

At $t = 0^-$ (i.e. steady state condition is reached), equivalent circuit

$$\text{i.e. } 100 = 100i \Rightarrow i = 1 \text{ amp}$$

$$\therefore i(0^-) = 1 \text{ amp}$$

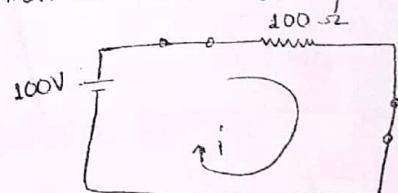

so, $i(0^+) = i(0^-) = 1 \text{ amp}$ since, current through inductor can not change instantene-


At $t > 0$ i.e. switch is at position 2

Applying KVL,

$$50 = 100i + 2 \frac{di}{dt} \dots \textcircled{1}$$

$$\text{or, } 50 = 100i + 2pi$$

$$\Rightarrow i = \frac{50}{100 + 2p}$$

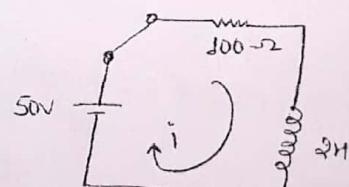

For, forced response, since source is constant, replace $i \cdot 1 + i = \frac{50}{100 + 2p} = 0.5 \text{ amp}$

or transient response.

Homogeneous version of equation ① is,

$$100i + 2\frac{di}{dt} = 0$$

$$\text{Let, } i = Ke^{st}$$

$$\therefore 100Ke^{st} + 2\frac{d}{dt}Ke^{st} = 0$$

$$\therefore 100Ke^{st} + 2sKe^{st} = 0$$

$$\therefore Ke^{st}(100+2s) = 0$$

$$\therefore Ke^{st} \neq 0$$

$$\text{so, } 100+2s = 0 \Rightarrow s = -50$$

$$\therefore i_t(t) = Ke^{-50t}$$

$$\begin{aligned} \text{The total response would be, } i(t) &= i_f(t) + i_t(t) \\ &= 0.5 + Ke^{-50t} \end{aligned}$$

Using initial condition:


$$i(0^+) = 0.5 + Ke^{-50(0^+)}$$

$$\text{or, } 1 = 0.5 + K \Rightarrow K = 0.5$$

$$\text{Hence, Total response is, } i(t) = 0.5 + 0.5e^{-50t}$$

$$\boxed{i = 0.5(1 + e^{-50t})}$$

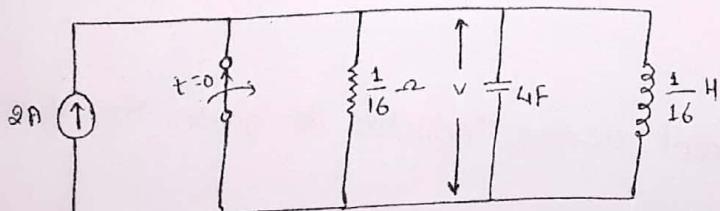Find $V(0^+)$, $\frac{dv(0^+)}{dt}$ and $\frac{d^2v(0^+)}{dt^2}$ for circuit below: [2011 Fall] 14F VC
[2012 Spring]




At $t = 0^-$, switch is closed i.e. $i_R(0^-) = i_C(0^-) = i_e(0^-) = 0$ amp

At, $t = 0^+$, switch is opened. The equivalent circuit is

Then,
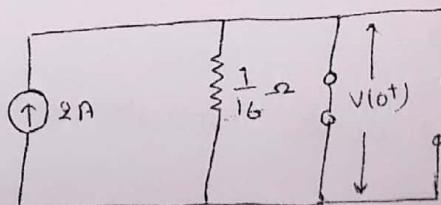
$$V(0^+) = 2A \times \frac{1}{16} \Omega = \frac{1}{8} V$$



$$\boxed{V(0^+) = \frac{1}{8} V}$$


1)

At $t > 0$, circuit is

using KCL;

$$\Delta A = i_R + i_C + i_L$$
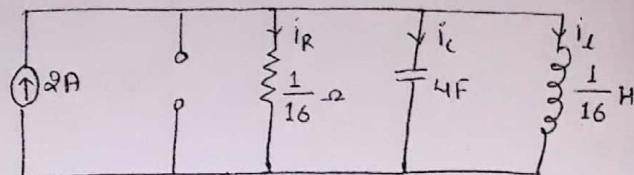
$$\text{or, } \Delta A = 16V + 4 \frac{dV}{dt} + i_L \quad \dots \dots \textcircled{1}$$



For $t = 0^+$

$$\Delta = 16V(0^+) + 4 \frac{dV(0^+)}{dt} + i_L(0^+)$$

$$\text{or, } \Delta = 16 \times 0 + 4 \frac{dV(0^+)}{dt} + 0$$

$$\text{or, } \frac{dV(0^+)}{dt} = \frac{1}{2} \text{ V/sec}$$

Now, differentiating (i) with respect to t ,

$$0 = 16 \frac{dV}{dt} + 4 \frac{d^2V}{dt^2} + \frac{V}{L} \quad \left[\because i_L = \frac{1}{L} \int V dt \right]$$

At $t = 0^+$

$$0 = 16 \frac{dV(0^+)}{dt} + 4 \frac{d^2V(0^+)}{dt^2} + \frac{V(0^+)}{1/16}$$

$$\text{or, } 0 = \frac{16 \times 1}{2} + 4 \frac{d^2V(0^+)}{dt^2} + 0 \times \frac{16}{1} \quad \Rightarrow -8 = 4 \frac{d^2V(0^+)}{dt^2}$$

$$\therefore \frac{d^2V(0^+)}{dt^2} = -2 \text{ V/sec}^2$$

Summary:

1. The voltage and current across inductor is given by, $V_L = L \frac{di_L}{dt}$
 $i_L = \frac{1}{L} \int V_L dt$
2. The current and voltage across capacitor is given by, $i_C = C \frac{dV_C}{dt}$
 $V_C = \frac{1}{C} \int i_C dt$
3. The voltage across capacitor and current across inductor can not instantaneous.
4. The driving point operational impedance of a network is the overall

expressed in terms of p-operator and viewed across source.
The circuit equation for network having energy storing elements is
non-homogeneous differential equation and the characteristics of circuit
(i.e. current and voltage) is determined by solving non-homogeneous
differential equation.

The solution of non homogeneous differential equation consists of two
parts i.e. Forced solution and transient solution.

Forced solution represents the steady state behaviour of the circuit
and nature of the source determines the nature of the forced response.
Transient solution is obtained by solving the homogeneous version of
differential equation and represents the changing characteristics of
current or voltage.

Total solution is the summation of forced response and transient response
e. $i(t) = i_L(t) + i_f(t)$

and the solution is complete when we use initial condition to determine
the value of constant.


Initial condition gives the value of current and voltage and their
derivatives at time $t = 0^+$.

Chapter . 5 Circuit Dynamics

It is the study of dynamic behaviour of linear circuits and systems containing one or more energy storing elements. It gives the information about how long it takes to the circuit respond to a source function. The period of adjustment during which the stored energy changes from some initial level to commanded final level is called the settling time of the circuit.

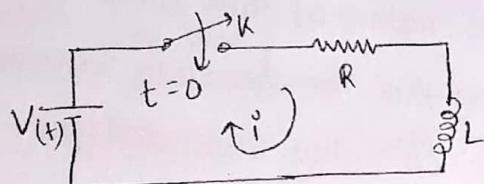
1. Step response to RL circuit

Let us consider the RL circuit as given below



Here, Switch is initially opened and at $t = 0$, it is closed. We apply step response to above circuit.
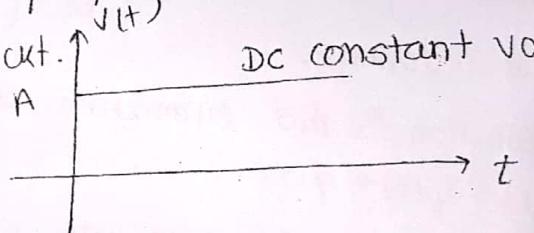
$$\text{i.e. } V(t) = \begin{cases} 0 & \text{at } t < 0 \\ A & \text{otherwise} \end{cases}$$



At, $t = 0^-$, $i(0^-) = 0$ amp and,

$$i(0^+) = i(0^-) = 0 \text{ amp} \quad \dots \textcircled{1}$$

[Since, current through inductor can not change instantaneously.]

Now, at $t > 0$ apply KVL

$$V = iR + L \frac{di}{dt} \quad \dots \textcircled{II}$$

For forced response, above equation using p-operator is

$$V = iR + LPi$$

$$\text{or, } i = \frac{V}{R+LP}$$

For constant source, put $p = 0$

$$\Rightarrow i_f(t) = \frac{V}{R} \quad \dots \textcircled{III}$$

For transient response,

The characteristic equation for above differential equation is,

$$R + LS = 0$$

$$\Rightarrow s = -\frac{R}{L} \dots \textcircled{iv}$$

And, homogeneous form of equation \textcircled{ii} is,

$$L \frac{di}{dt} + iR = 0$$

Then,

transient solution, $i_t(t)$ is given by,

$$i_t(t) = Ke^{st} = Ke^{-\frac{R}{L}t}$$


Thus, total response becomes,

$$\begin{aligned} i(t) &= i_p(t) + i_t(t) \\ &= \frac{V}{R} + Ke^{-\frac{R}{L}t} \dots \textcircled{v} \end{aligned}$$

Now, using initial conditions, at $t = 0^+$

$$\begin{aligned} i(0^+) &= \frac{V}{R} + Ke^{-\frac{R}{L}(0^+)} \\ i(0^+) &= \frac{V}{R} + K \end{aligned}$$

$\Rightarrow K = \frac{V}{R}$

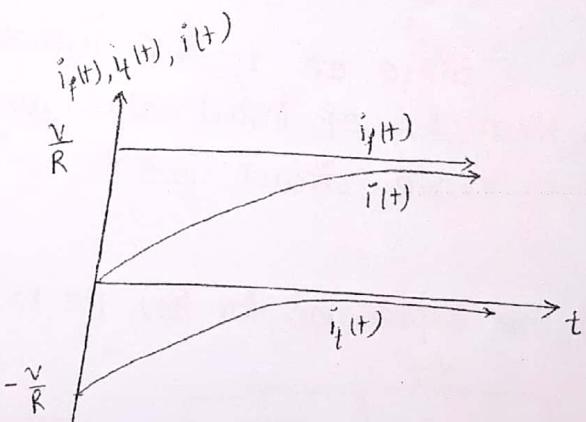

Time constant

At, $t = 0$, $i(t) = 0$

At, $t = \infty$, $i(t) = \frac{V}{R} - \frac{R}{L} \cdot \frac{L}{R}$

$$\begin{aligned} t, t = \frac{L}{R}, i(t) &= \frac{V}{R} - \frac{V}{R} \cdot e^{-\frac{R}{L} \cdot \frac{L}{R}} \\ &= \frac{V}{R} - \frac{V}{R} \cdot e^{-1} = \frac{V}{R} (1 - e^{-1}) \\ &= 0.632 \frac{V}{R} \end{aligned}$$

$\Rightarrow T = \frac{L}{R}$ is known as the time constant of the circuit and is defined as the interval after which current or voltage changes of its total change. OR,

Time constant is defined as time taken by the total response to 63.2% of the steady state value. It is represented by T .

Again for,

$$i_t(t) \text{ at } t = \frac{L}{R}, i_t(t) = -\frac{V}{R} e^{-\frac{t}{T}} = -\frac{V}{R} e^{-1} = -0.37 \frac{V}{R}$$

So, time constant is also defined as time taken by the transient response to decay to 37% of its initial value.

Settling time:

$$\text{At, } t = T, i_t(t) = -0.37 \frac{V}{R} =$$

$$t = 2T, i_t(t) = -0.135 \frac{V}{R}$$

$$t = 3T, i_t(t) = -0.0498 \frac{V}{R}$$


$$t = 4T, i_t(t) = -0.0183 \frac{V}{R}$$

$$t = 5T, i_t(t) = -0.0067 \frac{V}{R}$$

Since, at $t = 5T$, transient response has almost to less than 1% of initial value and then circuit settles. So, time for above circuit is $5T$.

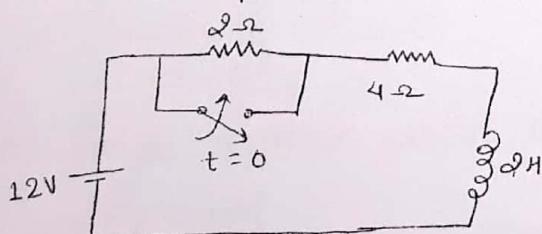Q.1

Find the expression for $i(t)$ for $t > 0$




Also, find time constant and settling

Soln: At $t = 0^-$,

Equivalent circuit is,

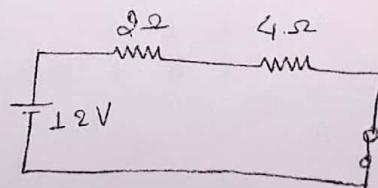
$$i(0^-) = \frac{12V}{6\Omega} = 2 \text{ amp}$$



At $t = 0^+$, equivalent circuit is, $\therefore i(0^-) = i(0^+) = 2 \text{ amp}$ (\because current

using KVL at $t > 0$
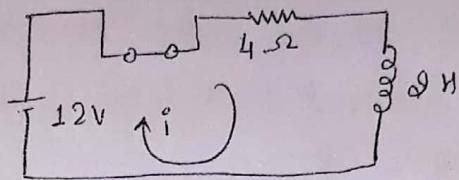
$$12 - 4i - \frac{2di}{dt} = 0 \quad \dots \textcircled{1}$$



In P operator form

$$12 = 4i + 2pi \Rightarrow i = \frac{12}{4+2p}$$

for forced response,

$$i_f(t) = \frac{12}{4+2p}$$

Being DC source of 12V, i.e. constant replace p by 0.

$$i_f(t) = 3 \text{ amp.}$$

For transient response,

Homogeneous equation is, $4i + 2\frac{di}{dt} = 0$

Characteristic equation is, $4+2s=0$

$$\Rightarrow s = -2$$

Thus, $i_t(t) = Ke^{st} = Ke^{-2t}$

Then, total solution $i(t) = i_f(t) + i_t(t)$
 $= 3 + Ke^{-2t}$

Now, using initial condition,

At $t = 0^+$

$$i(0^+) = 3 + Ke^{-2(0^+)}$$

$$2 = 3 + K \quad \therefore K = -1$$

Thus, $i(t) = 3 - e^{-2t}$

Since, $i_t(t) = -e^{-2t}$ compare it with $e^{-\frac{t}{\tau}}$ we get, $\tau = \frac{1}{2}$

\therefore Time constant (τ) = 0.5 sec.

$$\therefore$$
 Setting time, $t = 5\tau = 5 \times \frac{1}{2} = 2.5 \text{ sec.}$

$\Rightarrow \tau = \frac{L}{R}$ is known as the time constant of the circuit and is defined as the interval after which current or voltage changes by 36.8% of its total change. OR,

Time constant is defined as time taken by the total response 63.2% of the steady state value. It is represented by T .

Again for,

$$i_t(t) \text{ at } t = \frac{L}{R}, i_t(t) = -\frac{V}{R} e^{-\frac{t}{T}} = -\frac{V}{R} e^{-1} = -0.37 \frac{V}{R}$$

So, time constant is also defined as time taken by the transient response to decay to 37% of its initial value.

Settling time:

$$\text{At, } t = T, i_t(t) = -0.37 \frac{V}{R}$$

$$t = 2T, i_t(t) = -0.135 \frac{V}{R}$$

$$t = 3T, i_t(t) = -0.0498 \frac{V}{R}$$


$$t = 4T, i_t(t) = -0.0183 \frac{V}{R}$$

$$t = 5T, i_t(t) = -0.0067 \frac{V}{R}$$

Since, at $t = 5T$, transient response has almost reduced to less than 1% of initial value and then circuit settles. So, settling time for above circuit is $5T$.

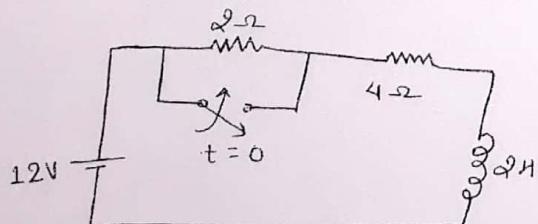Q1

Find the expression for $i(t)$ for $t > 0$




Also, find time constant and settling time.

Sol:

At $t = 0^-$,

Equivalent circuit is,

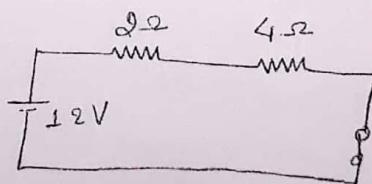
$$i(0^-) = \frac{12V}{6\Omega} = 2 \text{ amp}$$



~~At $t = 0^+$, equivalent circuit is,~~ $\therefore i(0^-) = i(0^+) = 2 \text{ amp}$ (\because current

Op response to series RC circuit:


Consider the following circuit,

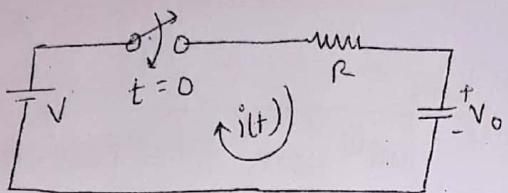

At, $t = 0^-$, $V_c(0^-) = V_0$ and $i(0^-) = 0$

At, $t = 0^+$: Voltage across capacitor can not change instantaneously.
 $V_c(0^+) = V_c(0^-) = V_0$

Equivalent circuit is,

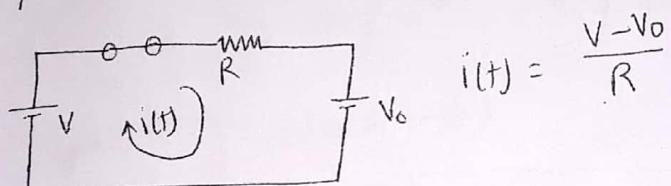

At, $t > 0$

using KVL

$$V = iR + \frac{1}{C} \int_{-\infty}^t idt$$

$$V = iR + \frac{1}{C} \int_{-\infty}^0 idt + \frac{1}{C} \int_0^t idt$$

$$V = iR + V_0 + \frac{1}{C} \int_0^t idt \dots \textcircled{1} \quad \left[\begin{array}{l} \text{Here, } V \text{ is step response} \\ \text{i.e. constant DC source} \end{array} \right]$$

Differentiating with respect to t ,

$$0 = R \frac{di}{dt} + 0 + \frac{1}{C}$$

$$\text{or, } R \frac{di}{dt} + \frac{1}{C} = 0$$

Using P-operator form,

$$RP\dot{i} + \frac{1}{C} = 0$$

This is the homogeneous equation.

So, forced response, $i_f(t) = 0$.

Now, for transient solution/response;

characteristic equation is,

$$SR + \frac{1}{C} = 0 \Rightarrow S = -\frac{1}{RC}$$

$$\text{Thus, } i_f(t) = Ke^{st} = Ke^{-\frac{1}{RC}t}$$

Total response,

$$i(t) = i_f(t) + i_t(t) = Ke^{-\frac{1}{RC}t}$$

Note: Here, time constant

$$T = RC \text{ at, } t = RC$$

$$i(t) = \left(\frac{V-V_0}{R}\right) e^{-1}$$

$$= 0.368 \left(\frac{V-V_0}{R}\right)$$

Now, using initial condition at $t = 0^+$

$$i(0^+) = Ke^{-\frac{1}{RC}(0^+)}$$


$$\text{or, } \frac{V-V_0}{R} = K$$

∴ Thus, total solution,

$$i(t) = \left(\frac{V-V_0}{R}\right) e^{-\frac{1}{RC}t}$$

Response of RL circuit to sinusoidal driving function:

Consider the following circuit:

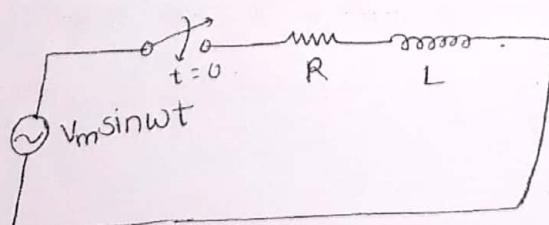

At, $t = 0^-$, $i(0^-) = 0 \text{ amp}$

At, $t = 0^+$, $i(0^+) = i(0^-) = 0$ Since current through inductor can change instantaneously.

NOW,

Apply KVL for $t > 0$,

$$V_m \sin \omega t = iR + L \frac{di}{dt} \dots \dots \dots \textcircled{1}$$

in ρ operator form,

$$V_m \sin \omega t = i\rho + L\rho i$$

$$\frac{V_m \sin \omega t}{R+Ls} \dots \textcircled{1}$$

equation $\textcircled{1}$ is non-homogeneous equation. Its solution has 0 parts.

$$\text{Forced response : } i_f(t) = \frac{\text{Im} [V_m e^{j\omega t}]}{R+Ls}$$

Replace s by $j\omega$ we get

Then,

$$i_f(t) = \frac{\text{Im} [V_m e^{j\omega t}]}{R+j\omega L} = \text{Im} \left(\frac{V_m e^{j\omega t}}{z} \right)$$

$$\text{where, } z = \sqrt{R^2 + \omega^2 L^2} \text{ and, } \phi = \tan^{-1} \left(\frac{\omega L}{R} \right)$$

$$= \frac{V_m}{z} \text{Im} \left(e^{j(\omega t - \phi)} \right)$$

$$\therefore i_f(t) = \frac{V_m}{z} \sin(\omega t - \phi)$$

② Transient response:

Homogeneous form of equation $\textcircled{1}$ is,

$$iR + L \frac{di}{dt} = 0$$

characteristic equation is,

$$R + Ls = 0$$

$$s = -\frac{R}{L} - \frac{R}{L}t$$

$$\therefore i_t(t) = K e^{st} = K e^{-\frac{R}{L}t}$$

$$\text{Total response, } i(t) = i_f(t) + i_t(t) = \frac{V_m}{z} \sin(\omega t - \phi) + K e^{-\frac{R}{L}t}$$

$$\text{using initial values, i.e. at } t=0^+, i(0^+) = \frac{V_m}{z} \sin(\omega(0^+) - \phi) + K e^{-\frac{R}{L}(0^+)}$$

$$i(0^+) = \frac{V_m}{z} \sin(-\phi) + K$$


$$\text{or, } 0 = \frac{V_m}{z} (\sin(-\phi)) + K$$

$$\therefore K = \frac{V_m}{z} \sin \phi$$

$$\boxed{i(t) = \frac{V_m}{z} \left\{ \sin(\omega t - \phi) + \sin \phi e^{-\frac{R}{L}t} \right\}}$$

3)

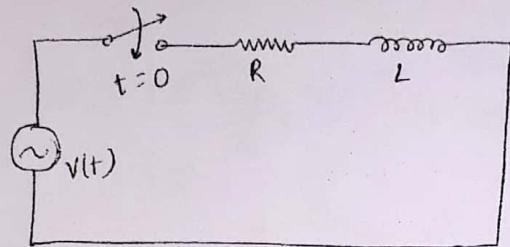8. For series RL circuit $V(t) = 10 \sin(10^4 t + \frac{\pi}{6})$, $R = 2 \Omega$, and $L = 0.1$. Voltage $v(t)$ is applied at $t = 0$, calculate $i(t)$ for $t > 0$. Assume $i_L(0^-) = 0$.



Q1: At, $t = 0^-$

$$i(0^-) = 0$$

Now, $i(0^+) = i(0^-) = 0 \because$ Current through inductor can not change immediately

Apply KVL, at $t > 0$

$$V(t) = Ri + L \frac{di}{dt}$$

$$\text{or, } 10 \sin\left(10^4 t + \frac{\pi}{6}\right) = 2i + 0.01 \frac{di}{dt} \quad \dots \dots \textcircled{1}$$

using p-operator

$$10 \sin\left(10^4 t + \frac{\pi}{6}\right) = 2i + 0.01 pi \quad \dots \dots \textcircled{2}$$

Equation ① is non-homogeneous equation. So, its solution contains two parts

① Forced solution

from equation ②

$$\begin{aligned} i &= \frac{10 \sin\left(10^4 t + \frac{\pi}{6}\right)}{2 + 0.01p} \\ &= I_m \left[10 e^{j\left(10^4 t + \frac{\pi}{6}\right)} \right] \end{aligned}$$

NOW, Replace p by s and put $s = j10^4$

$$i(t) = I_m \left[10 e^{j\left(10^4 t + \frac{\pi}{6}\right)} \right]$$

$$= I_m \left\{ \frac{10 e^{j(10^4 t + \frac{\pi}{6})}}{100 \cdot 488.85} \right\}$$

$$= I_m \left\{ 0.1 e^{j(10^4 t + \frac{\pi}{6} - 88.85)} \right\}$$

$$i = 0.1 \sin \left(10^4 t + \frac{\pi}{6} - 88.85 \right)$$

For transient solution

Homogeneous form of equation ① is,

$$di + 0.01 \frac{di}{dt} = 0$$

characteristic equation is,

$$s + 0.01s = 0$$

$$\Rightarrow s = -200$$

∴ Transient solution, $i_t(t) = K e^{st} = K e^{-200t}$

Thus,

$$i(t) = i_p(t) + i_t(t)$$

$$= 0.1 \sin \left(10^4 t + \frac{\pi}{6} - 88.85 \right) + K e^{-200t}$$


at, $t = 0^+$

$$i(0^+) = 0.1 \sin \left(\frac{\pi}{6} - 88.85 \right) + K$$

$$\therefore K = 0.08526$$

Thus, total response, $i(t) = 0.08526 e^{-200t} + 0.1 \sin \left(10^4 t + \frac{\pi}{6} - 88.85 \right)$

Step response of series RLC circuit

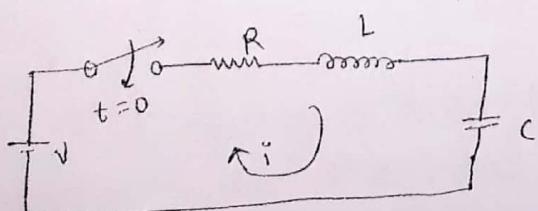

Let us consider a series RLC circuit as shown in figure above.

At $t = 0^-$

$$i(0^-) = 0 \text{ amp.}$$

at, $t = 0^+$, $i(0^+) = i(0^-) = 0$ (\because current through inductor cannot change instantaneously)

Apply KVL for $t > 0$.

$$V = iR + L \frac{di}{dt} + \frac{1}{C} \int_0^t i dt \quad \dots \dots \textcircled{1}$$

Differentiation with respect to t ,

$$0 = R \frac{di}{dt} + L \frac{d^2i}{dt^2} + \frac{i}{C}$$

$$\Rightarrow L \frac{d^2i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = 0$$

$$\Rightarrow \frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = 0 \quad \dots \dots \textcircled{2}$$

Being homogeneous equation, forced response

$$i_f(t) = 0$$

For transient response,

$$\text{characteristic equation is: } s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \quad \dots \dots \textcircled{3}$$

equation $\textcircled{3}$ is quadratic equations and it has two roots. Let s_1 and s_2 be their roots.

$$\text{i.e. } s_1, s_2 = \frac{-\frac{R}{L} \pm \sqrt{\left(\frac{R}{L}\right)^2 - \frac{1}{LC}}}{2 \cdot 1}$$

$$= -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \left(\frac{1}{LC}\right)} \quad \dots \dots \textcircled{4}$$

Then, transient equation is,

$$\begin{aligned} i_t(t) &= K_1 e^{s_1 t} + K_2 e^{s_2 t} \\ &= \left\{ -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 - \left(\frac{1}{LC}\right)} \right\} t + \left\{ -\frac{R}{2L} - \sqrt{\left(\frac{R}{2L}\right)^2 - \left(\frac{1}{LC}\right)} \right\} t \end{aligned}$$

The current in equation $\textcircled{5}$ depends upon the value of s_1 and s_2 which might be

- Complex-conjugate
- Real and equal

The system which has real and equal roots is called critically damped system. The value of resistance which makes system critically damped is called critical resistance and denoted by R_c .

From equation ④ roots will be equal if,

$$\left(\frac{R}{2L}\right)^2 - \left(\frac{1}{LC}\right) = 0$$

Then, Critical resistance R_c is given by

$$\left(\frac{R_c}{2L}\right)^2 = \frac{1}{LC}$$

$$R_c^2 = \frac{4L}{C}$$

$$\therefore R_c = 2\sqrt{\frac{L}{C}} \quad \text{--- ⑥}$$

In order to put the second order system in standard form, we define two parameters called damping ratio and damped natural frequency.

Damping ratio is defined as the ratio of actual resistance to critical resistance of the circuit and denoted by zeta (ξ) then,

$$\xi = \frac{R}{R_c} = \frac{R}{2\sqrt{\frac{L}{C}}} = \frac{R}{2}\sqrt{\frac{C}{L}} \quad \text{--- ⑦}$$

The second parameter is defined as the frequency at which response oscillates and is denoted by ω_n .

$$\omega_n = \frac{1}{\sqrt{LC}} \quad \text{--- ⑧}$$

Now,

$$2\xi\omega_n = 2 \times \frac{R}{2}\sqrt{\frac{C}{L}} \times \frac{1}{\sqrt{LC}} = \frac{R}{L} \quad \text{--- ⑨}$$

From equation ⑧, ⑨ and ② we can represent second order differential equation in standard form as:

$$\frac{d^2i}{dt^2} + 2\xi\omega_n \frac{di}{dt} + \omega_n^2 i = 0 \quad \text{--- ⑩}$$

Now, characteristic equation for above differential equation is,

Roots are,

$$s_1, s_2 = \frac{-2\zeta\omega_n \pm \sqrt{4(\zeta\omega_n)^2 - 4\omega_n^2}}{2} = -\zeta\omega_n \pm \sqrt{\omega_n^2(\zeta^2 - 1)}$$
$$= -\zeta\omega_n \pm \omega_n\sqrt{\zeta^2 - 1} \quad \text{..... (12)}$$

CASE I :

If $\zeta > 1$

For, $\zeta > 1$, roots are real and distinct and such system called over damped system. Then, $i(t)$ is given by,

$$i(t) = k_1 e^{s_1 t} + k_2 e^{s_2 t}$$
$$\left\{ -\zeta\omega_n - \omega_n\sqrt{\zeta^2 - 1} \right\} t \quad \left\{ -\zeta\omega_n + \omega_n\sqrt{\zeta^2 - 1} \right\} t$$
$$= k_1 e^{\left\{ -\zeta\omega_n - \omega_n\sqrt{\zeta^2 - 1} \right\} t} + k_2 e^{\left\{ -\zeta\omega_n + \omega_n\sqrt{\zeta^2 - 1} \right\} t} \quad \text{..... (13)}$$

Now, value of k_1 and k_2 are determined by using initial condition. We have, $i(0^+) = 0$ Amp. (14)

and, for $\frac{di(0^+)}{dt}$ from equation (13), $V = iR + L \frac{di}{dt} + \frac{1}{C} \int_0^t i dt$

at, $t = 0^+$

$$V = i(0^+) R + L \frac{di(0^+)}{dt} + v_c(0^+)$$

$$\therefore \frac{di(0^+)}{dt} = \frac{V}{L} \quad \text{..... (15)}$$

From equation (13), at $t = 0^+$

$$i(0^+) = k_1 e^0 + k_2 e^0 \Rightarrow k_1 = -k_2 \quad \text{..... (16)}$$

Now, differentiating equation (13) with respect to t , we get

$$\frac{di(t)}{dt} = \left(-\zeta\omega_n - \omega_n\sqrt{\zeta^2 - 1} \right) k_1 e^{\left\{ -\zeta\omega_n - \omega_n\sqrt{\zeta^2 - 1} \right\} t} + \left(-\zeta\omega_n + \omega_n\sqrt{\zeta^2 - 1} \right) k_2 e^{\left\{ -\zeta\omega_n + \omega_n\sqrt{\zeta^2 - 1} \right\} t}$$

at, $t = 0^+$

$$\begin{aligned} i(0^+) &= (-\xi w_n - w_n \sqrt{\xi^2 - 1}) k_1 e^0 + (-\xi w_n + w_n \sqrt{\xi^2 - 1}) k_2 e^0 \\ \frac{V}{L} &= -\xi w_n k_1 - w_n \sqrt{\xi^2 - 1} k_1 + \xi w_n k_2 - w_n \sqrt{\xi^2 - 1} k_2 \quad [\because k_2 = -k_1] \\ \frac{V}{L} &= k_1 (-2w_n \sqrt{\xi^2 - 1}) \end{aligned}$$

$$k_1 = -\frac{V}{2Lw_n \sqrt{\xi^2 - 1}} = -k_2$$

Therefore,

$$i(t) = \frac{-V}{2Lw_n \sqrt{\xi^2 - 1}} e^{(-\xi w_n - w_n \sqrt{\xi^2 - 1})t} + \frac{V}{2Lw_n \sqrt{\xi^2 - 1}} e^{(-\xi w_n + w_n \sqrt{\xi^2 - 1})t} \quad (17)$$

e II IF $\xi = 1$,

For $\xi = 1$, roots are real and equal. Then $i(t)$ becomes,

$$i(t) = k_1 e^{st} + k_2 t e^{st} = (k_1 + k_2 t) e^{st} \quad (18)$$

NOW, root will be,

from equation 12,

$$s = -\omega_n$$

$$\text{Then, } i(t) = (k_1 + k_2 t) e^{-\omega_n t} \quad (19)$$

Differentiating w.r.t. to t ,

$$\frac{di(t)}{dt} = -\omega_n (k_1 + k_2 t) e^{-\omega_n t} + k_2 e^{-\omega_n t} \quad (20)$$

using initial condition at $t = 0^+$, from equation (19) and (20) we get

$$i(0^+) = \{k_1 + k_2(0^+)\} e^{-\omega_n \times 0}$$

$$0 = k_1$$

$$\text{Then, } \frac{di(0^+)}{dt} = -\omega_n \{k_1 + k_2(0^+)\} e^{-\omega_n \times 0} + k_2 c = -\omega_n k_2 c$$

$$\Rightarrow \frac{V}{L} = 0 + k_2 \quad \Rightarrow k_2 = \frac{V}{L}$$

Hence, total solution,

$$i(t) = (K_1 + K_2 t) e^{-\omega_n t} = \frac{V}{L} t e^{-\omega_n t} \quad \text{--- (22)}$$

Case III : IF $\xi < 1$,

For $\xi < 1$, roots are imaginary and complex conjugate. Hence roots are given as,

$$s_1, s_2 = -\xi \omega_n \pm \omega_n \sqrt{\xi^2 - 1} \quad \text{--- (23)}$$

$$= -\xi \omega_n \pm \omega_n \sqrt{1 - \xi^2}$$

$$= -\xi \omega_n \pm j \omega_n \sqrt{1 - \xi^2}$$

$$= -\xi \omega_n \pm j \omega_d \quad \text{where, } \omega_d = \omega_n \sqrt{1 - \xi^2} \quad \text{--- (24)}$$

damped frequency of oscillation.

Then,

transient response,

$$\begin{aligned} i_t(t) &= K_1 e^{s_1 t} + K_2 e^{s_2 t} \\ &= K_1 e^{(-\xi \omega_n + j \omega_d)t} + K_2 e^{(\xi \omega_n - j \omega_d)t} \end{aligned}$$

$$\text{Hence, } i_t(t) = e^{-\xi \omega_n t} [K_1 e^{j \omega_d t} + K_2 e^{-j \omega_d t}] \quad \text{--- (25)}$$

Differentiating eqⁿ. (25) w.r.t. t we get

$$\frac{di(t)}{dt} = e^{-\xi \omega_n t} [K_1 j \omega_d e^{j \omega_d t} + K_2 (-j \omega_d) e^{-j \omega_d t}] + \frac{(-\xi \omega_n) e^{-\xi \omega_n t}}{[K_1 e^{j \omega_d t} + K_2 e^{-j \omega_d t}]} \quad \text{--- (26)}$$

using initial condition, at $t = 0+$, from eqⁿ. (25) and (26) we get

$$i(0+) = e^{-\xi \omega_n t} [K_1 + K_2] \quad \text{--- (27)}$$


$$\Rightarrow K_1 + K_2 = 0 \quad \text{or} \quad K_1 = -K_2$$

$$\text{and, } \frac{di(0+)}{dt} = e^{-\xi \omega_n t} [-K_2 j \omega_d e^0 - j \omega_d K_2 e^0] - \xi \omega_n \cdot e^0 [K_1 + K_2].$$

$$\frac{V}{L} = e^{-\xi \omega_n t(0)} \cdot -2 K_2 j \omega_d \quad \Rightarrow \quad K_2 = -\frac{V}{2 j L \omega_d} = -K_1$$

$$\text{Hence, } i(t) = e^{-\xi \omega_n t} \left[\frac{V}{2 j L \omega_d} e^{j \omega_d t} - \frac{V}{2 j L \omega_d} e^{-j \omega_d t} \right]$$

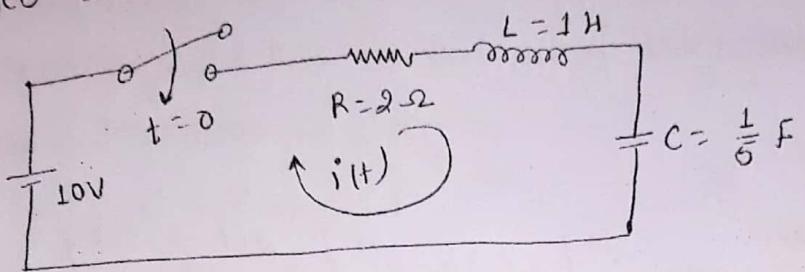For the given circuit calculate $i(t)$ for $t > 0$. Assume initial charges and current zero.



∴ Here, $i(0^-) = 0 = i(0^+)$ ∵ since, current through inductor can not change instantaneously.

Now, apply KVL at $t > 0$, we have

$$10 = Ri + L \frac{di}{dt} + \frac{1}{C} \int i dt \quad \dots \dots \dots \textcircled{1}$$

Differentiating w.r.t. t ,

$$0 = R \frac{di}{dt} + L \frac{d^2i}{dt^2} + \frac{i}{C}, \quad \dots \dots \dots \textcircled{2}$$

equation. ② is homogeneous second order differential equation. So, forced response becomes zero.

$$\text{Thus, } i(t) = i_f(t) + i_t(t) = i_t(t)$$

$$LS^2 + RS + \frac{1}{C} = 0$$

Now, For transient response, characteristic equation is, $S^2 + 2S + 5 = 0$

$$S_1, S_2 = -\frac{2 \pm \sqrt{4 - 20}}{2} = -\frac{2 \pm 4j}{2} = -1 \pm 2j$$

$$\begin{aligned} \text{Thus, } i(t) &= K_1 e^{S_1 t} + K_2 e^{S_2 t} \\ &= K_1 e^{(-1+2j)t} + K_2 e^{(-1-2j)t} \\ &= e^{-t} [K_1 e^{2jt} + K_2 e^{-2jt}] \end{aligned} \quad \dots \dots \dots \textcircled{3}$$

Using initial condition, at $t = 0^+$

$$i(0^+) = e^0 [K_1 e^0 + K_2 e^0] \Rightarrow 0 = K_1 + K_2$$

∴ $K_1 = -K_2$

From equation ⑤ and ④

$$i(t) = e^{-t} [k_1 e^{2jt} - k_1 e^{-2jt}]$$

$$i(t) = k_1 e^{-t} [e^{2jt} - e^{-2jt}]$$

differentiating w.r.t t,

$$\frac{di(t)}{dt} = k_1 e^{-t} [2je^{2jt} + 2je^{-2jt}] + (-)k_1 e^{-t} [e^{2jt} - e^{-2jt}]$$

Now, from equation ① at $t = 0^+$

$$10 = R i(0^+) + L \frac{di(0^+)}{dt} + v_c(0^+)$$

$$10 = 0 + \frac{di(0^+)}{dt}$$

$$\frac{di(0^+)}{dt} = 10 \text{ amp/sec.}$$

at $t = 0^+$ eq. ⑤ gives,

$$\frac{di(0^+)}{dt} = k_1 [2j + 2j] - k_1 [1 - 1]$$

$$10 = k_1 [4j] \Rightarrow k_1 = \frac{10}{4j} = -\frac{10}{4} j$$

$$\therefore k_1 = -2.5j = -k_2$$

Required solution,

$$i(t) = e^{-t} [-2.5j e^{2jt} + 2.5j e^{-2jt}]$$

A LAPLACE transform is mathematical tool that is widely used to find the solution of differential equations without exactly solving the differential equation by classical method.


Mathematically, If $f(t)$ be the given function which is defined for $t \geq 0$ Laplace transform is given by

$$L[f(t)] = F(s) = \int_0^\infty f(t) e^{-st} dt \quad \dots \dots \textcircled{1}$$

Where, $s = \sigma + j\omega$, is called complex frequency. Similarly, Inverse Laplace transform is $F(s)$ and is given by,

$$L^{-1}[F(s)] = f(t) = \int_{-\infty}^{\infty} F(s) e^{st} ds \quad \dots \dots \textcircled{2}$$

Flowchart for Laplace transform:

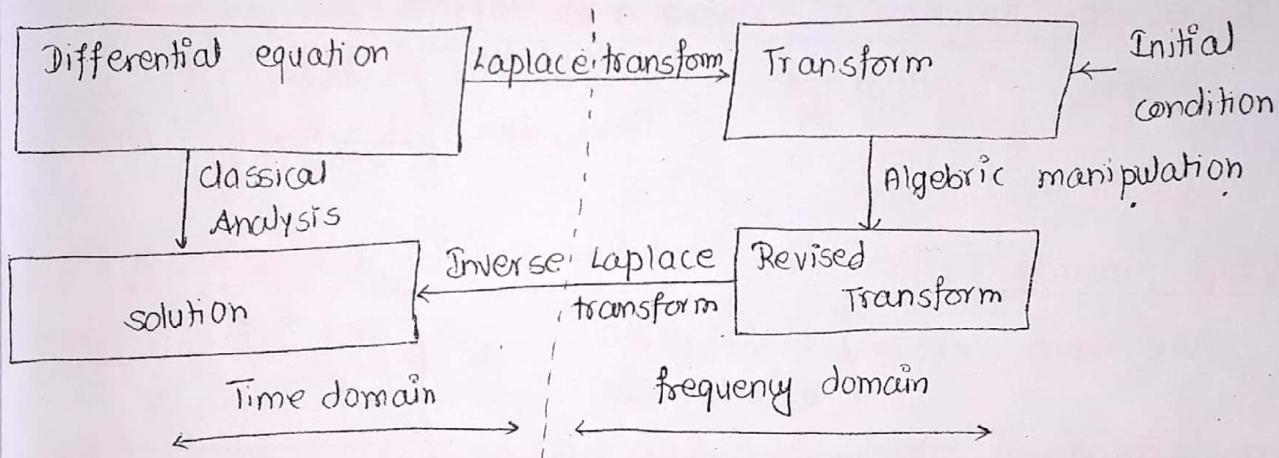

Steps:

1. We start with an integro-differential equation and find corresponding Laplace transform
2. Transform is manipulated algebraically after the initial conditions are applied.
3. We perform an inverse Laplace transform to find the complete solution

Advantages:


- 1) It yields the complete information about the sustained (steady) and transient solution rather than the three part solution procedure of classical method.
- 2) Solution gets highly simplified.
- 3) Gives a single solution (complete solution) rather than in parts.

) Initial conditions are automatically specified on transformed and are applied in first step rather than in last step.

Laplace transform of some basic function

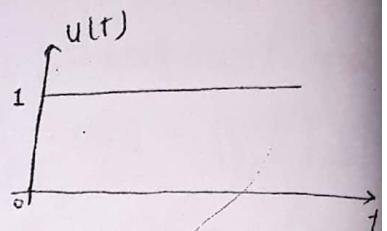1) Unit step function

We have, $u(t) = \begin{cases} 1 & \text{for } t \geq 0 \\ 0 & \text{otherwise} \end{cases}$



Then,

$$L[u(t)] = \int_0^\infty e^{-st} u(t) dt = \int_0^\infty e^{-st} dt = \left[\frac{e^{-st}}{-s} \right]_0^\infty = \frac{1}{s}$$


$u(t) \xleftrightarrow{L.T.} \frac{1}{s}$

2) Exponential function e^{at} where a is constant:

$$L[e^{at}] = \int_0^\infty e^{-st} e^{at} dt = \int_0^\infty e^{-(s-a)t} dt = \left[\frac{e^{-(s-a)t}}{-(s-a)} \right]_0^\infty = \frac{1}{s-a}$$

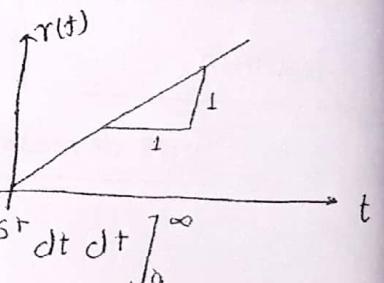3) Ramp function

We have, $r(t) = \begin{cases} t & \text{for } t \geq 0 \\ 0 & \text{otherwise} \end{cases}$



Then, $L[r(t)] = \int_0^\infty e^{-st} t dt = \left[t \int e^{-st} dt - \int \int e^{-st} dt dt \right]_0^\infty$

$$= \left[t \frac{e^{-st}}{-s} - \frac{e^{-st}}{s^2} \right]_0^\infty = \frac{1}{s^2}$$

) similarly,

$$t^2 \xleftrightarrow{L.T.} \frac{2}{s^3} \quad \text{and} \quad t^n \xleftrightarrow{L.T.} \frac{n!}{s^{n+1}}$$

4) $\sin wt$ and $\cos wt$

$$L[f(t)] = \int_0^\infty e^{-st} f(t) dt$$

We have, $e^{jwt} = \cos wt + j \sin wt$

Then, $L[e^{jwt}] = L[\cos wt + j \sin wt]$

$\therefore +$ $L[\cos wt + j \sin wt] = \frac{1}{s} + \frac{j}{s^2 + w^2}$

$$\frac{s+j\omega}{s^2+\omega^2} = L[\cos \omega t] + j L[\sin \omega t]$$

$$\frac{s}{s^2+\omega^2} + j \frac{\omega}{s^2+\omega^2} = L[\cos \omega t] + j L[\sin \omega t]$$

$$[\sin \omega t] = \frac{\omega}{s^2+\omega^2} \text{ and, } L[\cos \omega t] = \frac{s}{s^2+\omega^2}$$


unit impulse function

Impulse function is defined as,

$$\delta(t) = 0 \text{ for } t \neq 0 \\ \infty \text{ for } t = 0$$

unit impulse function,
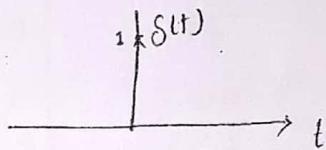
$$\delta(t) = 0 \text{ for } t \neq 0 \\ 1 \text{ for } t = 0$$



$$L\{\delta(t)\} = \int_0^\infty e^{-st} \delta(t) dt = e^{-st} \Big|_{t=0} = 1.$$

Laplace transform of derivatives:

$$\left[\frac{df(t)}{dt} \right] = \int_0^\infty \frac{df(t)}{dt} e^{-st} dt = \int_0^\infty u dv$$

for, $u = e^{-st}$ and, $dv = \frac{df(t)}{dt}$. Then, $du = -se^{-st}$ and $v = f(t)$

$$\int_a^b u dv = [uv]_a^b - \int_b^a v du$$

$$\text{Then, } \int_0^\infty \frac{df(t)}{dt} e^{-st} dt = \left[e^{-st} f(t) \right]_0^\infty + \left[s \int_0^\infty e^{-st} f(t) dt \right]_0^\infty \\ = sF(s) + \cancel{\left[e^{-\infty} f(\infty) \right]} - \cancel{\left[e^0 f(0) \right]} \\ = sF(s) - F(0)$$

Where, $f(0)$ is the value of $f(t)$ at $t = 0^+$ and given by initial condition of the circuit.

$$\text{Similarly, } L\left[\frac{d^2 f(t)}{dt^2} \right] = s^2 F(s) - sF(0) - F'(0)$$

$$L\left[\frac{d^n f(t)}{dt^n} \right] = s^n F(s) - s^{n-1} F(0) - s^{n-2} F'(0) + \dots F^{n-1}(0)$$

8) Laplace transform of integrals

$$L \left[\int_0^t f(t) dt \right] = \frac{F(s)}{s} \text{ and}$$

$$L \left[\int_{-\infty}^t f(t) dt \right] = \int_{-\infty}^0 f(t) dt + \int_0^t f(t) dt = \frac{f(0)}{s} + \frac{F(s)}{s}$$

Some formulas:

$f(t)$	$F(s)$	$f(t)$	$F(s)$
1	$\frac{1}{s}$	$t e^{at}$	$\frac{1}{(s-a)^2}$
t	$\frac{1}{s^2}$	$t^n e^{at}$	$\frac{n!}{(s-a)^{n+1}}$
t^2	$\frac{2!}{s^3}$	$t \sin at$	$\frac{2as}{(s^2+a^2)^2}$
t^n	$\frac{n!}{s^{n+1}}$	$t \cos at$	$\frac{s^2-a^2}{(s^2+a^2)^2}$
e^{at}	$\frac{1}{s-a}$	$e^{-at} \sin wt$	$\frac{w}{(s+a)^2+w^2}$
$\cos at$	$\frac{s}{s^2+a^2}$	$e^{-at} \cos wt$	$\frac{s+a}{(s+a)^2+w^2}$
$\sin at$	$\frac{a}{s^2+a^2}$	e^{-at}	$\frac{1}{s+a}$
$\sinh at$	$\frac{a}{s^2-a^2}$	$t e^{-at}$	$\frac{1}{(s+a)^2}$
$\cosh at$	$\frac{s}{s^2-a^2}$		

Ex Solve for $i(t)$ using L.T method.

$$\frac{d^2 i}{dt^2} + 4 \frac{di}{dt} + 3i = 0, \quad i(0) = 3, \quad \frac{di(0)}{dt} = 1$$

Sol:

We have,

$$\frac{d^2 i}{dt^2} + 4 \frac{di}{dt} + 3i = 0$$

Taking Laplace transform on both side,

$$L \left\{ \frac{d^2 i}{dt^2} \right\} + 4 L \left\{ \frac{di}{dt} \right\} + 3 L \{ i \} = 0$$

$$s^2 + us + 3] I(s) - s \cdot 3 - 1 - 12 = 0$$

$$(s^2 + us + 3) I(s) = 3s + 13$$

$$I(s) = \frac{3s + 13}{s^2 + us + 3} = \frac{3s + 13}{(s+3)(s+1)} = \frac{A}{s+3} + \frac{B}{s+1}$$

$$= \frac{3s + 13}{(s+3)(s+1)} \Big|_{s=-3} = \frac{3 \times -3 + 13}{-3+1} = \frac{4}{-2} = -2$$

$$= \frac{3s + 13}{(s+3)(s+1)} \Big|_{s=-1} = \frac{3 \times -1 + 13}{-1+3} = \frac{10}{2} = 5$$

$$I(s) = -\frac{2}{s+3} + \frac{5}{s+1}$$

Now, taking inverse L.T

$$i(t) = L^{-1}\{I(s)\} = -2e^{-3t} + \cancel{5e^{-t}}$$

Solve by Laplace transform method

$$\frac{d^2 i}{dt^2} + 2 \frac{di}{dt} + 5i = 0, \quad i(0) = 2, \quad i'(0) = -4$$

i.e. we have, $\frac{d^2 i}{dt^2} + 2 \frac{di}{dt} + 5i = 0$

Taking Laplace transform on both side,

$$L\left[\frac{d^2 i}{dt^2}\right] + 2L\left[\frac{di}{dt}\right] + 5L[i] = 0$$

$$[s^2 I(s) - si(0) - i'(0)] + 2[sI(s) - i(0)] + 5I(s) = 0$$

$$s^2 I(s) - 2s + 4 + 2sI(s) - 4 + 5I(s) = 0$$

$$(s^2 + 2s + 5) I(s) = 2s$$

$$I(s) = \frac{2s}{s^2 + 2s + 5} = \frac{2s}{s^2 + 2s + 1 + 4} = \frac{2s}{(s+1)^2 + (2)^2}$$

$$I(s) = \frac{2(s+1)}{(s+1)^2 + (2)^2} - \frac{2}{(s+1)^2 + (2)^2}$$

Now taking inverse Laplace transform

$$i(t) = L^{-1}\{I(s)\} = 2 \cdot e^{-t} \cos 2t - e^{-t} \sin 2t$$

3.3 solve by L.T. method.

$$\frac{d^2 i}{dt^2} + 10 \frac{di}{dt} + 25i = 0, \quad i(0^+) = 2, \quad \frac{di(0^+)}{dt} = 0$$

Taking Laplace transform on both side,

$$L\left[\frac{d^2 i}{dt^2}\right] + 10 L\left[\frac{di}{dt}\right] + 25 L[i] = 0$$

$$\Rightarrow s^2 I(s) - si(0^+) - i(0^+) + 10sI(s) - 10i(0^+) + 25I(s) = 0$$

$$\Rightarrow (s^2 + 10s + 25) I(s) - 2s - 20 = 0$$

$$\Rightarrow (s^2 + 10s + 25) I(s) = 2s + 20$$

$$\Rightarrow I(s) = \frac{2s + 20}{(s+5)(s+5)} = \frac{A}{(s+5)} + \frac{B}{(s+5)^2}$$

$$\text{Now, } B = \left. \frac{2s + 20}{(s+5)(s+5)} \times (s+5)^2 \right|_{s=-5} = 10$$

$$\text{and, } 2s + 20 = (s+5)A + B$$

$$\text{or, } 2s + 20 = As + 5A + B$$

comparing coefficient of s ,

$$A = 2$$

$$\text{so, } I(s) = \frac{2}{s+5} + \frac{10}{(s+5)^2}$$

Using Inverse Laplace transform, we get

$$i(t) = L^{-1}[I(s)] = L^{-1}\left[\frac{2}{s+5}\right] + L^{-1}\left[\frac{10}{(s+5)^2}\right]$$

$$\boxed{i(t) = 2e^{-st} + 10te^{-st}}$$

Properties of Laplace transform:

① Linear Combination:

$$\text{If } L[f_1(t)] = F_1(s) \text{ and } L[f_2(t)] = F_2(s)$$

Then, $L[af_1(t) + bf_2(t)] = aF_1(s) + bF_2(s)$ where a and b are constants.

change of scale

If $L[f(t)] = F(s)$ then,




$$L[f(at)] = \frac{1}{a} F\left(\frac{s}{a}\right)$$

shift in time domain

If $L[F(t)] = F(s)$ then,

$$\cancel{L[f(t)]} L[f(t-a)] = e^{-as} F(s)$$

samples:

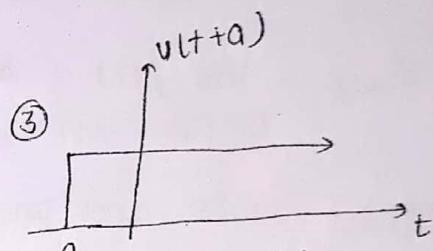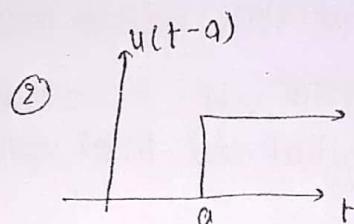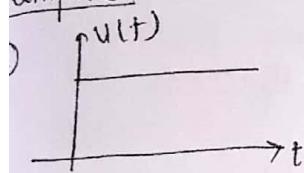

$$L[u(t)] = \frac{1}{s} \quad L[u(t-a)] = \frac{e^{-as}}{s}$$

$$L[u(t+a)] = \frac{e^{as}}{s}$$

shifting in s-domain:

If $f(t) \xleftrightarrow{\text{L.T.}} F(s)$ then

$$L\{e^{at} f(t)\} = F(s-a)$$

Eg: find L.T. of $e^{-4t} \sin 10t$

$$\text{we have, } L[\sin 10t] = \frac{10}{s^2 + 10^2} = F(s)$$

$$\text{Then, } L[e^{-4t} \sin 10t] = F(s+4) = F(s)|_{s=s+4} = \frac{10}{(s+4)^2 + 100}$$

5) Multiplication by t:

If $L[f(t)] = F(s)$ then,

$$L[t f(t)] = -F'(s) \text{ and}$$

$$L[t^n f(t)] = (-1)^n \frac{d^n F(s)}{ds^n}$$

Eg: Find, L.T. of $t \sin 3t$

$$\text{we have, } L[\sin 3t] = \frac{3}{s^2 + 9}$$

$$\text{Then, } L[t \sin 3t] = (-1)^1 \frac{d}{ds} \left(\frac{3}{s^2 + 9} \right) = -1 \cdot \frac{3 \cdot (-1) \cdot 2s}{(s^2 + 9)^2} = \frac{6s}{(s^2 + 9)^2}$$

⑥ Initial value theorem and final value theorem:

Initial value theorem

If $f(t)$ and its first derivative $f'(t)$ are Laplace transform then,

$$f(0) = \lim_{t \rightarrow 0} f(t) = \lim_{s \rightarrow \infty} s F(s)$$

Final value theorem

If $f(t)$ and its first derivative $f'(t)$ are Laplace transform then,

$$f(\infty) = \lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} s F(s)$$

Assignment: State and prove initial and final value theorem.

Q. Find the Laplace transform of $5 + 5e^{-2t} + 10e^{-4t}$. And verify initial and final value theorem.

Sol: Here,

$$f(t) = 5 + 5e^{-2t} + 10e^{-4t}$$

Taking Laplace transform on both sides, we get

$$L[f(t)] = L(5) + L[5e^{-2t}] + L[10e^{-4t}]$$

$$F(s) = \frac{5}{s} + \frac{5}{s+2} + \frac{10}{s+4}$$

NOW, ① initial value theorem,

$$\lim_{t \rightarrow 0} f(t) = \lim_{t \rightarrow 0} [5 + 5e^{-2t} + 10e^{-4t}] = 5 + 5 + 10 = 20$$

$$\begin{aligned} \lim_{s \rightarrow \infty} s F(s) &= \lim_{s \rightarrow \infty} s \left[\frac{5}{s} + \frac{5}{s+2} + \frac{10}{s+4} \right] = \lim_{s \rightarrow \infty} \left(5 + \frac{s}{s+2} + \frac{10s}{s+4} \right) \\ &= 5 + 5 + 10 = 20 \end{aligned}$$

Here, $\lim_{t \rightarrow 0} f(t) = \lim_{s \rightarrow \infty} s F(s)$. Hence, initial value theorem is verified.

Again, ② final value theorem,

$$\lim_{t \rightarrow \infty} f(t) = \lim_{t \rightarrow \infty} [5 + 5e^{-2t} + 10e^{-4t}] = 5 + 5e^{-\infty} + 10e^{-\infty} = 5$$

$$\lim_{s \rightarrow 0} s F(s) = \lim_{s \rightarrow 0} s \left[\frac{5}{s} + \frac{5}{s+2} + \frac{10}{s+4} \right] = \lim_{s \rightarrow 0} \left[5 + \frac{5s}{s+2} + \frac{10s}{s+4} \right] = 5$$

∴ $\lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} s F(s)$. Hence, final value theorem is verified.

Inverse Laplace transform:

We use partial fraction expansion to find $f(t)$ from $F(s)$.
Laplace transform equation is polynomial of s . i.e.

$$F(s) = \frac{N(s)}{D(s)}$$

For partial expansion, order of $N(s)$ should be always less than $D(s)$, otherwise we divide $N(s)$ by $D(s)$.

Next, we factorize $D(s)$ in terms of its roots.

$$\begin{aligned} D(s) &= a_0 s^d + a_1 s^{d-1} + \dots + a_d \\ &= a_0 (s-s_1)(s-s_2) \dots (s-s_d) \end{aligned}$$

Case 1

If roots are real and distinct

$$\frac{N(s)}{(s-s_1)(s-s_2) \dots (s-s_d)} = \frac{k_1}{(s-s_1)} + \frac{k_2}{(s-s_2)} + \dots + \frac{k_d}{(s-s_d)}$$

Where, $k_d = \left. \frac{N(s)}{D(s)} \times (s-s_d) \right|_{s=s_d}$

Case 2

If roots are equal and real.

$$\frac{N(s)}{(s-s_1)^r} = \frac{k_1}{(s-s_1)} + \frac{k_2}{(s-s_1)^2} + \dots + \frac{k_n}{(s-s_1)^r}$$

Where, $k_n = \frac{1}{(r-n)!} \left[\frac{d^{r-n}}{ds^{r-n}} \left\{ \frac{N(s)}{D(s)} (s-s_1)^r \right\} \right]_{s=s_1}$

Case 3

If roots are complex conjugate

$$\frac{N(s)}{(s-\alpha+j\beta)(s-\alpha-j\beta)} = \frac{k_1}{(s-\alpha+j\beta)} + \frac{k_2}{(s-\alpha-j\beta)}$$

Where, k_2 or $k_1 = \left[\frac{N(s)}{D(s)} \times (s-\alpha \pm j\beta) \right] \Big|_{s=\alpha \pm j\beta}$

Analysis of R, L, C, network using Laplace transform:

General methods:

Step 1: Find initial condition from the circuit


Step 2: Use KVL or KCL to form differential equation

Step 3: Use Laplace transform to find polynomial in s-domain

Step 4: Use inverse Laplace transform to obtain solution in time

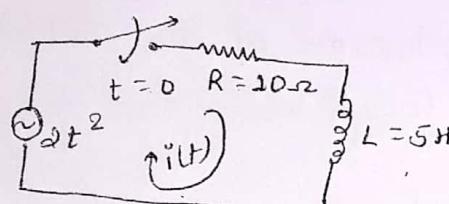Q.1

Solve for $i(t)$ for the following circuit:



Sol: At, $t = 0^-$

$$i(0^-) = 0$$

$i(0^+) = i(0^-) = 0$ [∴ Current through inductor can not change instantaneously.]
For, $t > 0$, using KVL.

$$\frac{dt^2}{dt} = 10i(t) + 5\frac{di(t)}{dt}$$

Taking Laplace transform on both sides,

$$L[2t^2] = L[10i(t)] + L[5\frac{di(t)}{dt}]$$

$$2 \cdot \frac{2}{s^3} = 10I(s) + 5[sI(s) - I(0^+)]$$

$$\text{or, } \frac{4}{s^3} = 10I(s) + 5sI(s) - 5 \times 0$$

$$\text{or, } I(s)[10 + 5s] = \frac{4}{s^3}$$

$$\text{or, } I(s) = \frac{4/s^3}{s^3(s+2)}$$

Using partial fraction,

$$I(s) = \frac{4/s^3}{s^3(s+2)} = \frac{A}{s} + \frac{B}{s^2} + \frac{C}{s^3} + \frac{D}{s+2}$$

$$\frac{4}{5} = As^2(s+2) + Bs(s+2) + Cs + Ds^3$$

$$\frac{4}{5} = As^3 + 2s^2A + s^2B + 2sB + Cs + 2C + s^3D$$

$$\frac{4}{5} = (A+D)s^3 + (2A+B)s^2 + (2B+C)s + 2C$$

Comparing coefficient,

$$e.d \quad \partial C = \frac{4}{5} \Rightarrow C = \frac{2}{5}$$

$$2B+C=0 \Rightarrow B = -\frac{C}{2} = -\frac{1}{5}$$

$$2A+B=0 \Rightarrow A = -\frac{B}{2} = \frac{1}{10}$$

$$A+D=0 \Rightarrow D=-A = -\frac{1}{10}$$

Thus,


$$I(s) = \frac{1}{10s} + \frac{1}{5s^2} + \frac{2}{5s^3} - \frac{1}{10(s+2)}$$

Taking inverse laplace transform,

$$\dot{i}(t) = \frac{1}{10} - \frac{1}{5}t + \frac{1}{5}t^2 - \frac{1}{10}e^{-2t}$$

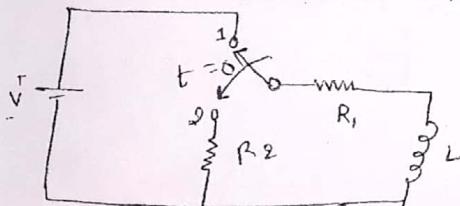Q.2 2005 fall 3(b)


Solve for $i(t)$ for the following circuit.



i: For $t=0^-$

Equivalent circuit is,

$$i(0^-) = \frac{V}{R_1}$$

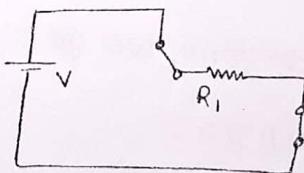


$\therefore i(0^+) = i(0^-) = \frac{V}{R_1}$ (\because Current through inductor can not change instantaneously,

Now, using KVL for $t > 0$.

At, $t > 0$, equivalent circuit is

$$R_1 i(t) + R_2 i(t) + L \frac{di(t)}{dt} = 0$$
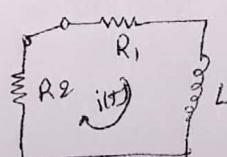
$$\text{or}, i(t) (R_1 + R_2) + L \frac{di(t)}{dt} = 0$$



Using, Laplace transform we get

$$(R_1 + R_2) I(s) + LS I(s) - L I(0) = 0$$

5

$$\Rightarrow I(s) = \frac{V}{R_1(R_1 + R_2 + Ls)}$$


$$\Rightarrow I(s) = \frac{V}{R_1(R_1 + R_2 + s)}$$

Taking inverse Laplace transform, we get

$$i(t) = \frac{V}{R_1} e^{-\left(\frac{R_1+R_2}{L}\right)t}$$

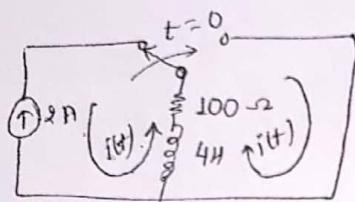Q3 2005 Spring

In the circuit shown, the switch is moved from position 1 at $t = 0$. Find the solution for $i(t)$.



sofⁿ: At, $t = 0^+$,

$$i(0^+) = -2 \text{ A}$$

$i(0^+) = i(0^-) = -2 \text{ A}$ [Current through inductor can not change instantaneously]

using KVL for $t > 0$, we get

$$4 \frac{di(t)}{dt} + 100i(t) = 0$$

Taking Laplace transform, we get

$$4sI(s) - 4i(0^+) + 100I(s) = 0$$

$$I(s)(4s + 100) = 4 \times -2 = -8$$

$$I(s) = \frac{-8}{4(s+25)} = -\frac{2}{s+25}$$


Taking inverse Laplace transform, we get

$$i(t) = -2e^{-25t}$$

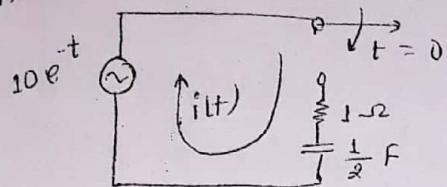Q4 2006 Fall

For series circuit having $R = 1\Omega$, $C = \frac{1}{2}\text{F}$, with no initial

expression for the resulting current in the circuit for $t > 0$. Use Laplace transform.



$$\text{At } t = 0^-$$

$$V_C(0^-) = 0$$

$\therefore V_C(0^+) = V_C(0^-) = 0$ (\because Voltage across capacitor can not change instantaneously)

for, $t > 0$, using KVL

$$10e^{-t} = i(t) + \frac{1}{C} \int_{-\infty}^t i(t) dt$$

$$\Rightarrow 10e^{-t} = i(t) + \frac{1}{C} \int_{-\infty}^0 i(t) dt + \frac{1}{C} \int_0^t i(t) dt$$

$$10e^{-t} = i(t) + V_C(0^+) + \frac{1}{C} \int_0^t i(t) dt$$

Taking Laplace transform, we get

$$\frac{10}{s+1} = I(s) + \frac{1}{1/2} \frac{I(s)}{s}$$

$$\frac{10}{s+1} = I(s) \left(1 + \frac{2}{s} \right)$$

$$\frac{10}{s+1} = I(s) \left(\frac{s+2}{s} \right)$$

$$I(s) = \frac{10s}{(s+1)(s+2)}$$

NOW, using partial fraction,

$$\frac{10s}{(s+1)(s+2)} = \frac{A}{s+1} + \frac{B}{s+2}$$

$$A = \frac{10s}{(s+1)(s+2)} \times (s+1) \Big|_{s=-1} = -\frac{10}{1} = -10$$

$$B = \frac{10s}{(s+1)(s+2)} \times (s+2) \Big|_{s=-2} = -\frac{20}{-1} = 20$$

Then,

$$I(s) = -\frac{10}{s+1} + \frac{20}{s+2}$$

Taking inverse Laplace transform, we get $\boxed{\dots, 10e^{-t}, 20e^{-2t}}$

Analysis of R, L, C

① For capacitor

Voltage across capacitor is given by,

$$V_C = \frac{1}{C} \int_{\infty}^t i dt = \frac{1}{C} \int_{\infty}^0 i dt + \frac{1}{C} \int_0^t i dt \\ = V_C(0^+) + \frac{1}{C} \int_0^t i dt$$

Now,

Taking L.T. of V_C , we get

$$L[V_C] = L[V_C(0^+)] + \frac{1}{C} \frac{i(s)}{s}$$

For inductor

$$V_L = L \frac{di}{dt} \quad \text{and}, \quad L[V_L] = L [s I(s) - i(0^+)]$$

3) for resistance

$$V_R = RI \quad \text{and}, \quad L[V_R] = R I(s)$$


transform impedance and transformed circuit:

The ratio of voltage and current in s domain is called transformed impedance.

$$\text{i.e. Transformed impedance, } Z(s) = \frac{V(s)}{I(s)}$$

Resistance

In time domain, we have $v = iR$

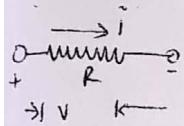

Taking Laplace transform we have


$$L[v] = L[iR]$$

$$V(s) = R I(s) \Rightarrow R = \frac{V(s)}{I(s)}$$

ductor

(with no initial current)
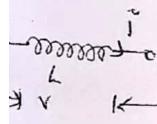
$$\text{In time domain, } v = L \frac{di}{dt}$$



Taking L.T., we get

$$V(s) = L s I(s) - L I(0^+)$$

$$L s = \frac{V(s)}{I(s)}$$

(with initial current)

$$V(s) = L s I(s) - L I(0^+)$$

apacitance


(with no initial charge)

$$\text{In time domain, } v = \frac{1}{C} \int i dt$$

$$\Rightarrow i = C \frac{dv}{dt}$$

Taking L.T. we get,

$$I(s) = C s V(s) - C V(0^+)$$

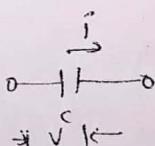


$$\frac{V(s)}{I(s)} = \frac{1}{C s}$$

(with initial charge)


$$I(s) = C s V(s) - C V(0^+)$$

When all the elements in time domain along with source are converted to s-domain then newly formed circuit is called transformed circuit.

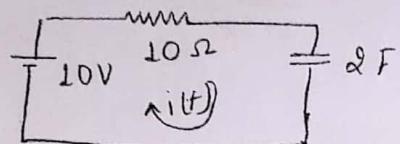Ex 1 Find $i(t)$ by transformed circuit method.



Sol: In s-domain, above circuit becomes

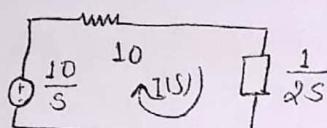

using, KVL

$$\frac{10}{s} = 10I(s) + \frac{1}{2s} I(s)$$

$$\Rightarrow I(s) \left[10 + \frac{1}{2s} \right] = \frac{10}{s}$$


$$\Rightarrow I(s) \left[\frac{20s+1}{2s} \right] = \frac{10}{s}$$

$$\Rightarrow I(s) = \frac{20}{20s+1} = \frac{1}{s + \frac{1}{20}}$$

Taking, inverse L.T., we get

$$i(t) = e^{-\frac{1}{20}t}$$

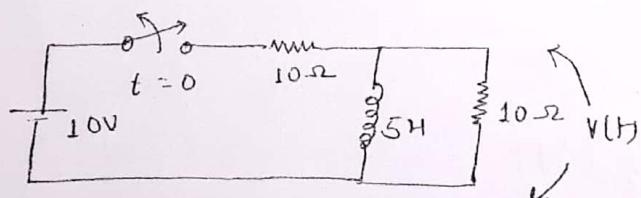Ex 2 Find $v(t)$ using transformed circuit:




Sol:

Here,

At, $t = 0^-$


$$i(0^-) = \frac{10}{10} = 1A$$

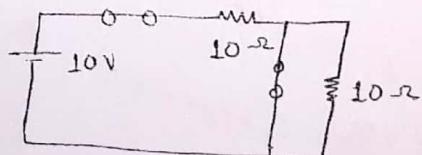

$\therefore i(0^+) = i(0^-) = 1A$ [∴ Current through inductor can not change instantaneously.]


For, $t = 0^+$

∴ Equivalent circuit is,

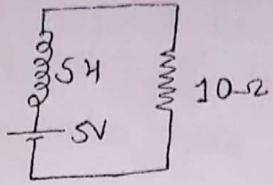

NOW, Taking KVL, In s-domain,

$$sV = \frac{dI}{dt} + 10$$

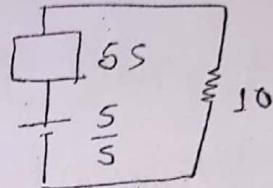

using voltage dividing rule

$$V(s) = \frac{5}{s} \cdot \frac{10}{10+5s} = \frac{10}{s(s+2)}$$

$$= \frac{5}{s} - \frac{5}{s+2}$$

Taking inverse L.T. we get

$$v(t) = 5 - 5e^{-2t}$$


Transfer Function

Transfer function is a mathematical expression in s-domain which relates input and output characteristics of transform circuit. It can also be defined as the ratio of Laplace transform of output to the Laplace transform of the input, under the assumption that all initial conditions are zero.

Mathematically, let $x(t)$ be the input function and $y(t)$ be the output function. Then network function $H(s)$ is given by,

$$H(s) = \frac{L[y(t)]}{L[x(t)]} = \frac{Y(s)}{X(s)}$$

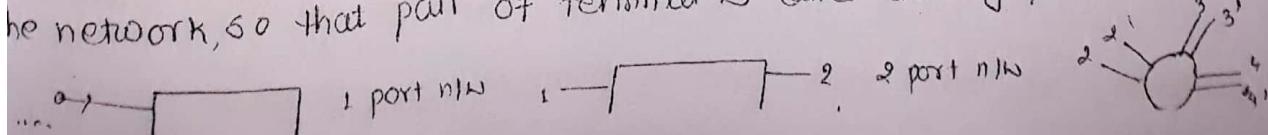For any electronic circuit two terminals are associated which are called terminal pair or port. In one port network, terminal pair is connected to an energy source which is the driving force for the network, so that pair of terminal is called driving point of the n/w.



In two port network, 1-1' port is connected to driving force port 2-2' is connected to the load. For one port network the function that relates the voltage and current at the same port is called driving point impedance $Z(s)$ or driving point admittance $Y(s)$.

$$\text{i.e. } Z(s) = \frac{V(s)}{I(s)}, Y(s) = \frac{I(s)}{V(s)}$$

Where, $V(s)$ (voltage) is the response parameter and $I(s)$ (current source or vice-versa.

For two port network

There are two pairs of driving point impedance and two driving point admittance for two port network, given by

$$Z_{11}(s) = \frac{V_1(s)}{I_1(s)}, Y_{11}(s) = \frac{I_1(s)}{V_1(s)}$$

$$Z_{22}(s) = \frac{V_2(s)}{I_2(s)}, Y_{22} = \frac{I_2(s)}{V_2(s)}$$

The network function which relates the transform of a quantity at one port to the transform of another quantity at the other port is called transfer function. Thus, the transfer function which relates voltage and current for two port n/w has the following cases:

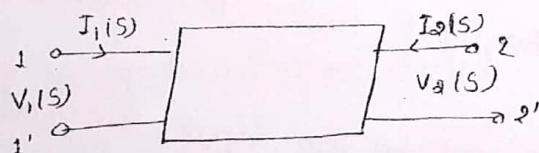


Fig: of port n/w.

(a) Voltage transfer Function (ratio):

It is defined as the ratio of Laplace transform voltages at two ports and is given by,

$$G_{12}(s) = \frac{V_2(s)}{V_1(s)}$$

(b) Current transfer function (ratio):

It is defined as the ratio of Laplace transform currents at two ports and is given by, $\alpha_{12} = I_2(s)$

Transfer admittance

It is defined as the ratio of transform of current at one port to transform of voltage at next point port.

$$\text{i.e. } Y_{12}(S) = \frac{I_2(S)}{V_1(S)} \quad \text{and, } Y_{21}(S) = \frac{I_1(S)}{V_2(S)}$$

Transfer impedance:

ratio of transform of voltage at one port to transform of current at next port.

$$\text{i.e. } Z_{12}(S) = \frac{V_1(S)}{I_2(S)} \quad \text{and, } Z_{21}(S) = \frac{V_2(S)}{I_1(S)}$$

Driving Impedance

It is the ratio of Laplace transform of voltage and currents at the same port.


$$Z_{11}(S) = \frac{V_1(S)}{I_1(S)} \quad \text{and, } Z_{22}(S) = \frac{V_2(S)}{I_2(S)}$$

Driving admittance


It is the ratio of Laplace transform of current and voltage at the same port.

$$Y_{11}(S) = \frac{I_1(S)}{V_1(S)} \quad \text{and, } Y_{22}(S) = \frac{I_2(S)}{V_2(S)}$$

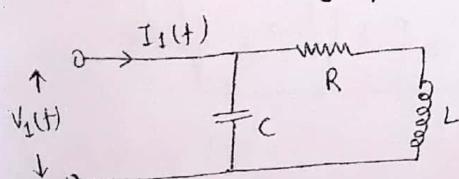1. Find the driving point impedance for the following one port network.



Soln: The transform circuit is,

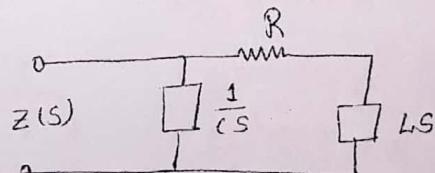


$$\text{Now, } Z(S) = \frac{1}{CS} // (R + LS)$$


$$= \frac{\frac{1}{CS} (R + LS)}{\frac{1}{CS} + R + LS} = \frac{R + LS}{1 + RCS + LCS^2} = \frac{R + LS}{LCS^2 + RCS + 1}$$

$$\boxed{Z(S) = \frac{R}{LC} + \frac{1}{CS}}$$

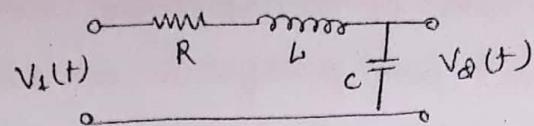Q.2 Find the transfer function $\frac{V_2(s)}{V_1(s)}$ in the following circuit



Soln: Transform circuit is,

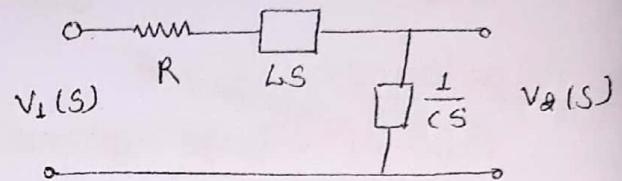



By using voltage dividing rule, we get

$$V_2(s) = \frac{\frac{1}{Cs} \times V_1(s)}{R + LS + \frac{1}{Cs}}$$

$$\Rightarrow \frac{V_2(s)}{V_1(s)} = \frac{\frac{1}{Cs}}{\frac{1}{Cs} [RCS + LCS^2 + 1]} = \frac{1}{LCS^2 + RCS + 1}$$

$$\therefore \frac{V_2(s)}{V_1(s)} = \frac{\frac{1}{LC}}{S^2 + \frac{R}{L}s + \frac{1}{LC}}$$

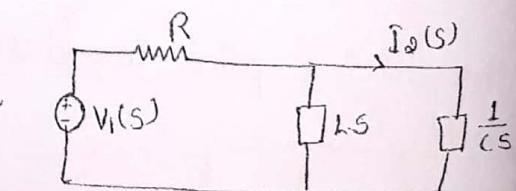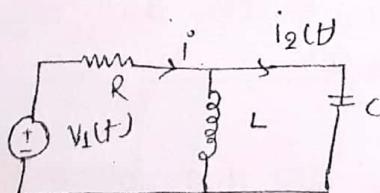Q3 Find transfer admittance $\frac{I_2(s)}{V_1(s)}$ in the following circuit



Soln: The transform circuit is,

$$Y(s) = \frac{V_1(s)}{R + (LS) // \frac{1}{Cs}}$$

$$= \frac{V_1(s)}{R + \frac{LS \times \frac{1}{Cs}}{LS + \frac{1}{Cs}}}$$

$$= \frac{V_1(s)}{R + \frac{L/C}{LCS^2 + 1}}$$

$$= \frac{V_1(s)}{RLCS^2 + R + LS}$$


$$= \frac{(LCS^2 + 1)}{(RLCS^2 + LS + R)} V_1(s)$$

$$I_2(S) = \frac{LS}{LS + \frac{1}{CS}} \times I(S)$$


$$= \frac{LCS^2}{(LCS^2 + 1)} \cdot \frac{(LCS^2 + 1) V_1(S)}{(RLCS^2 + LS + R)}$$

$$\frac{I_2(S)}{V_1(S)} = \frac{LCS^2}{RLCS^2 + LS + R} = \frac{s^2/R}{s^2 + \frac{1}{RC}s + \frac{1}{LC}}$$

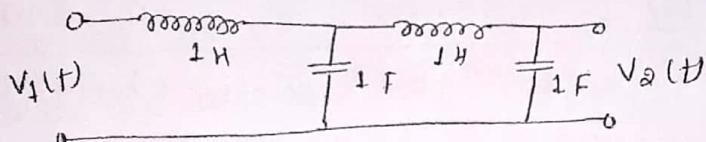Find the transfer function $\frac{V_2(S)}{V_1(S)}$ of the following circuit.



1: The transform circuit is,

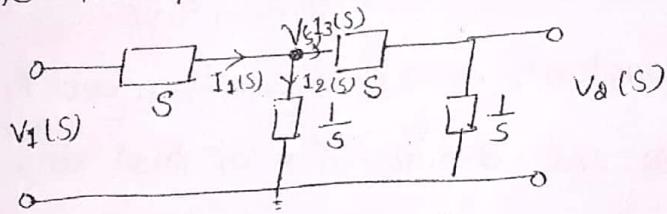

Using nodal analysis,

$$I_1(S) = I_2(S) + I_3(S)$$

$$\frac{V_1(S) - V(S)}{S} = \frac{V(S) - 0}{1/S} + \frac{V(S) - V_2(S)}{S}$$

$$\frac{V_1(S)}{S} - \frac{V(S)}{S} = SV(S) + \frac{V(S)}{S} - \frac{V_2(S)}{S}$$

$$V(S) \left[\frac{1}{S} + S + \frac{1}{S} \right] = \frac{V_1(S) + V_2(S)}{S}$$

$$V(S) \left[\frac{S + S^2}{S} \right] = \frac{V_1(S) + V_2(S)}{S}$$

$$V(S) = \frac{V_1(S) + V_2(S)}{(S^2 + 2)}$$

Using voltage dividing rule

$$V_2(S) = \frac{\frac{1}{S} \times V(S)}{S + \frac{1}{S}} = \frac{V_1(S) + V_2(S)}{(S^2 + 2)} \times \frac{1}{(S^2 + 1)} = \frac{V_1(S) + V_2(S)}{S^4 + 3S^2 + 2}$$

$$\text{or, } (s^4 + 3s^2 + 2) V_2(s) - V_2(s) = V_1(s)$$

$$\text{or, } (s^4 + 3s^2 + 1) V_2(s) = V_1(s)$$

$$\therefore \frac{V_2(s)}{V_1(s)} = \frac{1}{s^4 + 3s^2 + 1}$$

Poles and zeros of network functions (Transfer functions)

All the network function can be written as the of polynomial as a function of s .

$$\text{Mathematically, } N(s) = \frac{P(s)}{Q(s)} = \frac{a_0 s^n + a_1 s^{n-1} + \dots + a_{n-1} s + a_n}{b_0 s^m + b_1 s^{m-1} + \dots + b_{m-1} s + b_m}$$
$$= \frac{a_0}{b_0} \frac{(s-z_1)(s-z_2)(s-z_3)\dots(s-z_n)}{(s-p_1)(s-p_2)(s-p_3)\dots(s-p_m)}$$

where, $\frac{a_0}{b_0}$ is constant, $z_1, z_2, z_3, \dots, z_n$ and p_1, p_2, \dots, p_m are factors of numerator and denominator of $N(s)$ and are frequencies.

When the variable s has the value equals to z_1, z_2, \dots, z_n , polynomial $N(s)$ equals zero. Then such complex frequencies $N(s)=0$ are called zeros of transfer function $N(s)$.

Similarly, when the variable s has the value equal p_1, p_2, \dots, p_m , polynomial $N(s)$ equals infinity (∞). Then such frequencies for which $N(s)=\infty$ are called poles of transfer $N(s)$.

For any network functions zeros are represented by (o), and poles are represented by (*).

amples


Draw poles and zeros for network function:

$$N(s) = \frac{s(s+1)}{(s+2)(s^2+2s+5)}$$

sol: Given, $N(s) = \frac{s(s+1)}{(s+2)(s^2+2s+5)}$

$$= \frac{s(s+1)}{(s+2)((s+1)^2 - (2j)^2)}$$
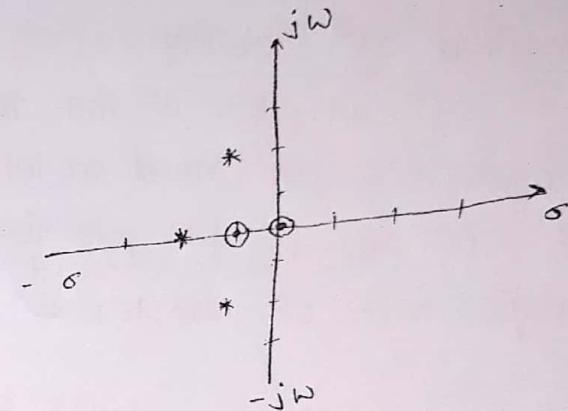
$$= \frac{s(s+1)}{(s+2)(s+1-2j)(s+1+2j)}$$



Then, zeros are at, $s = 0, s = -1$


poles are at, $s = -2, -1 \pm 2j$

② $N(s) = \frac{s^2(s+3)}{(s+1)(s^2+4s+5)}$

Given, $N(s) = \frac{s^2(s+3)}{(s+1)(s^2+4s+5)}$

$$= \frac{s^2(s+3)}{(s+1)((s+2)^2 - j^2)}$$

$$= \frac{s^2(s+3)}{(s+1)(s+2 \pm j)}$$

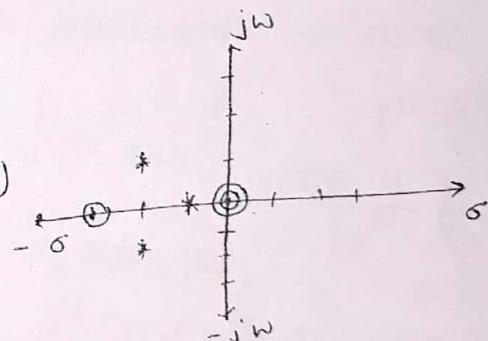

Then, zeros are at, $s = 0, 0, -3$


and, poles are at, $s = -1, -2 \pm j$

③ $f(t) = e^{-3t} \cos 5t$

sol: Given, $f(t) = e^{-3t} \cos 5t$

Taking Laplace transform
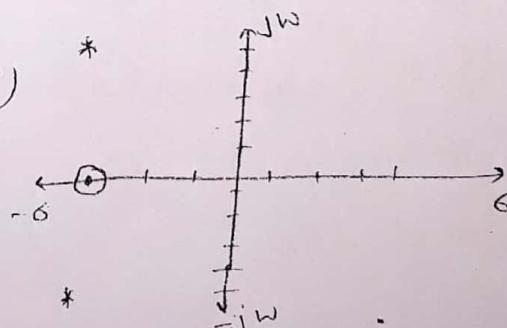
$$F(s) = \frac{s+3}{(s+3)^2 + 5^2} = \frac{s+3}{(s+3 \pm 5j)} *$$



zeros are at, $s = -3$

poles are at, $s = -3 \pm 5j$

2)

Network stability:

Network is said to be stable if its response is finite at any time and system implies that small changes in system input initial condition ^{or in system parameter} does not result in large change in output.

Condition of stability:

- If all poles of the transfer function relating the output to input are confirmed on left half of s-plane, the system is stable.
- If any of the pole that lies on jω is repeated or lie in right half of complex s plane, then the system is unstable.

Routh - Hurwitz criteria for stability (R-H criteria)

It states that "The network or system describes a transfer function for which p(s) is the denominator polynomial. The system is stable if there are no changes of sign in first column of array."

R-H array :

Consider a system with characteristic equation,

$$p(s) = a_0 s^n + a_1 s^{n-1} + \dots + a_n = 0$$

Thus, we construct R-H array as below:

$$\begin{array}{cccc}
 s^n & a_0 & a_2 & a_4 \\
 s^{n-1} & a_1 & a_3 & a_5 \\
 s^{n-2} & b_1 & b_2 & b_3 \\
 s^{n-3} & c_1 & c_2 & \\
 s^{n-4} & d_1 & & \\
 \vdots & & & \\
 s^0 & & &
 \end{array}$$

Where, $b_1 = -\frac{1}{a_1} \begin{vmatrix} a_0 & a_4 \\ a_1 & a_3 \end{vmatrix}$

$b_2 = -\frac{1}{a_2} \begin{vmatrix} a_0 & a_4 \\ a_1 & a_5 \end{vmatrix}$

$c_1 = -\frac{1}{b_1} \begin{vmatrix} a_1 & a_3 \\ b_1 & b_2 \end{vmatrix}$

$c_2 = -\frac{1}{b_2} \begin{vmatrix} a_1 & a_5 \\ b_1 & b_3 \end{vmatrix}$

$d_1 = -\frac{1}{c_1} \begin{vmatrix} b_1 & b_2 \\ c_1 & c_2 \end{vmatrix}$

Now, we count the number of sign changes as we go from $a_0, a_1, b_1, c_1, \dots$. The no. of sign changes of the coefficient in the first column gives the number of the roots of the characteristic equation that are right half of the s -plane.

so, for stable system all the coefficients $a_0, a_1, b_1, c_1, \dots$ should be of same sign.

Example

check stability of the system with transfer function

$$G(s) = \frac{s^2 + s + 1}{s^5 + 15s^4 + 85s^3 + 225s^2 + 274s + 120}$$

(Q1): R-H array for above transfer function is,

$$s^5 \quad 1 \quad 85 \quad 274$$

$$b_1 = -\frac{1}{15} \begin{vmatrix} 1 & 85 \\ 15 & 225 \end{vmatrix} = 70$$

$$s^4 \quad 15 \quad 225 \quad 120$$

$$b_2 = -\frac{1}{15} \begin{vmatrix} 1 & 274 \\ 15 & 120 \end{vmatrix} = 266$$

$$s^3 \quad b_1 = 70 \quad b_2 = 266 \quad \times \quad c_1 = 168 \quad c_2 = 120$$

$$c_1 = -\frac{1}{70} \begin{vmatrix} 15 & 225 \\ 70 & 266 \end{vmatrix} = 168$$

$$s^2 \quad d_1 = 216 \quad \times \quad c_2 = 120$$

$$c_2 = -\frac{1}{70} \begin{vmatrix} 15 & 120 \\ 70 & 0 \end{vmatrix} = 120$$

Since, The first column

of R-H array has no sign

$$d_1 = -\frac{1}{168} \begin{vmatrix} 70 & 266 \\ 168 & 120 \end{vmatrix} = 216$$

change i.e. none of the poles

$$e_1 = -\frac{1}{216} \begin{vmatrix} 168 & 120 \\ 216 & 0 \end{vmatrix} = 120$$

lies in the right half of the

s -plane. Thus, the system is

stable.

$$s^4 + 3s^3 + 4s^2 + 4s + 40 = 0$$

(Q2): R-H array of above transfer function is,

$$\begin{array}{ccccc}
 s^4 & 1 & 4 & 40 & \\
 s^3 & 3 & 42 & 0 & \\
 s^2 & b_1 = -10 & b_2 = 40 & & \\
 s^1 & c_1 = 54 & 0 & & \\
 s^0 & 40 & & &
 \end{array}$$

$$b_1 = -\frac{1}{3} \begin{vmatrix} 1 & 4 \\ 3 & 42 \end{vmatrix} = -10$$

$$b_2 = -\frac{1}{3} \begin{vmatrix} 1 & 40 \\ 3 & 0 \end{vmatrix} = 40$$

$$c_1 = +\frac{1}{10} \begin{vmatrix} 3 & 42 \\ -10 & 40 \end{vmatrix} = 54$$

Since, the first column of R-H array has sign change. There is a pole in right half of s-plane. Thus, the system is unstable.

Q3 Find the value of A for which

$$s^3 + 2s^2 + 2s + A = 0 \text{ is stable.}$$

Sol: R-H array:

$$\begin{array}{ccc}
 s^3 & 1 & 2 \\
 s^2 & 2 & A \\
 s & -\frac{1}{2}(A-4) \\
 s^0 & \frac{2}{A-4} \left\{ \frac{1}{2}A(A-4) \right\} = A
 \end{array}$$

The system will be stable if A is greater than zero or

i.e. $4 > A$.

But for $A = 4$, third row seems to be zero and other elements can not be determined. So, in such cases we replace zero by very small number near to zero represented by ϵ .

For $A = 4$,

R-H array becomes,

$$\begin{array}{ccc}
 s^3 & 1 & 2 \\
 s^2 & 2 & 4 \\
 s & 0 \\
 s^0 & \text{can not be calculated}
 \end{array}$$

special case :

When element of 1st row is zero

decide the stability depending on values of ϵ .

Now, R-H array becomes:

$$\begin{array}{cccc} s^3 & 1 & 2 \\ s^2 & 2 & 4 \\ s^1 & 6 \\ s^0 & 4 \end{array}$$

Thus, for $A = 4$, System is stable if ϵ is greater than zero and system is unstable if ϵ is less than zero.

Check the stability for $s^4 + s^3 + 2s^2 + 2s + 3$.

R-H array

$$\begin{array}{cccc} s^4 & 1 & 2 & 3 \\ s^3 & 1 & 2 & 0 \end{array} \quad b_1 = -\frac{1}{1} \begin{vmatrix} 1 & 2 \\ 1 & 2 \end{vmatrix} = 0$$

$$\begin{array}{cccc} s^2 & 0 & 3 \\ s^1 & \text{can not be determined} \\ s^0 & \text{can not be determined} \end{array}$$

Since, first column has zero in third row. Fourth row becomes infinity so we can not find stability. In such cases we replace zero by small number ϵ and stability depends on ϵ .

Now, Replacing 0 by ϵ above R-H array becomes

$$\begin{array}{cccc} s^4 & 1 & 2 & 3 \\ s^3 & 1 & 2 & \epsilon \\ s^2 & \epsilon & 3 \\ s^1 & c_1 = 2 - \frac{3}{\epsilon} & 0 \\ s^0 & 3 \end{array} \quad c_1 = -\frac{1}{\epsilon} \begin{vmatrix} 1 & 2 \\ \epsilon & 3 \end{vmatrix} = \frac{2\epsilon - 3}{\epsilon}$$

for ϵ greater than zero, $2 - \frac{3}{\epsilon}$ is negative. So, system is unstable.

Also, for ϵ less than zero first element of third row is negative. So, system is again unstable. Hence, the system defined by above equation is unstable.

Check the stability for:

Q17: R-H array 1^os.

$$\begin{array}{cccccc}
 s^6 & 1 & 11 & 36 & 36 & b_1 = -\frac{1}{5} \left| \begin{array}{ccc} 1 & 11 \\ 5 & 25 \end{array} \right| = \frac{55-25}{5} \\
 s^5 & 5 & 25 & 30 & 0 & b_2 = -\frac{1}{5} \left| \begin{array}{ccc} 1 & 36 \\ 5 & 30 \end{array} \right| = \frac{36 \times 5 - 30}{5} \\
 s^4 & b_1 = 6 & b_2 = 30 & 36 & & \\
 s^3 & c_1 = 0 & c_2 = 0 & 0 & c_1 = -\frac{1}{6} \left| \begin{array}{ccc} 5 & 25 \\ 6 & 30 \end{array} \right| = \frac{150 - 150}{6} = 0 \\
 s^2 & \text{can not be determined} & & & & \\
 s^1 & & & & c_2 = -\frac{1}{6} \left| \begin{array}{ccc} 5 & 30 \\ 6 & 36 \end{array} \right| = \frac{180 - 180}{6} = 0 \\
 s^0 & & & & &
 \end{array}$$

If entire row is zero then we take the polynomial of e row and divide the system polynomial by that polynomial to find quotient then stability is determined by quotient.

$$\begin{array}{r}
 \frac{\frac{1}{6}s^2 + \frac{5}{6}s + 1}{6s^4 + 30s^2 + 36} \left(\begin{array}{c} 5s^8 + 5s^5 + 11s^4 + 25s^3 + 36s^2 + 30s + 36 \\ - 5s^8 - 5s^4 - 6s^2 \\ \hline 5s^8 + 6s^4 + 28s^3 + 30s^2 + 30s + 36 \\ - 5s^8 - 28s^3 - 30s \\ \hline 6s^4 + 30s^2 + 36 \\ - 6s^4 + 30s^2 + 36 \\ \hline 0 \end{array} \right)
 \end{array}$$

Here, quotient is, $\frac{\frac{1}{6}s^2 + \frac{5}{6}s + 1}{6s^4 + 30s^2 + 36}$ then R-H array is

$$\begin{array}{cccc}
 s^2 & \frac{1}{6} & 1 & \\
 s^1 & \frac{5}{6} & 0 & b_1 = -\frac{6}{5} \left| \begin{array}{cc} \frac{1}{6} & 1 \\ \frac{5}{6} & 0 \end{array} \right| = 1 \\
 s^0 & b_1 = 1 & &
 \end{array}$$

Since, the first column of R-H array for quotient has no sign changes. So, the system is stable.

3.6 Check the stability

$$s^5 + s^4 + 4s^3 + 24s^2 + 3s + 63 = 0$$

R-H array is

$$s^5 \quad 1 \quad 4 \quad 3$$

$$b_1 = -\frac{1}{1} \begin{vmatrix} 1 & 4 \\ 1 & 24 \end{vmatrix} = -20$$

$$s^4 \quad 1 \quad 24 \quad 63$$

$$b_2 = -\frac{1}{1} \begin{vmatrix} 1 & 3 \\ 1 & 63 \end{vmatrix} = -60$$

$$s^3 \quad -20 \quad -60 \quad 0$$

$$c_1 = \frac{1}{20} \begin{vmatrix} 1 & 24 \\ -20 & -60 \end{vmatrix} = 21$$

$$s^2 \quad 21 \quad 63 \quad 0$$

$$c_2 = \frac{1}{20} \begin{vmatrix} 1 & 63 \\ -20 & 0 \end{vmatrix} = 63$$

$$s^1 \quad 0 \quad 0 \quad 0$$

$$s^0 \text{ can not be determined}$$

$$D_1 = -\frac{1}{21} \begin{vmatrix} -20 & -60 \\ 21 & 63 \end{vmatrix} = 0$$

$$D_2 = -\frac{1}{21} \begin{vmatrix} -20 & 0 \\ 21 & 0 \end{vmatrix} = 0$$

Here, the entire row for s^1 is zero. So we take polynomial just above that row

$$\text{i.e. } P(s^2) = 21s^2 + 63$$

Then, taking derivatives

$$P'(s^2) = 2 * 21s = 42s$$

Now, R-H array becomes

$$\begin{array}{cccc} s^5 & 1 & 4 & 3 \\ s^4 & 1 & 24 & 63 \\ s^3 & -20 & -60 & 0 \\ s^2 & 21 & 63 & 0 \\ s^1 & 42 & 0 & 0 \\ s^0 & 63 & & \end{array}$$

Limitation of R-H Criteria:

1. Valid only if characteristic equation is algebraic with real coefficients. If any of coefficient is complex or if equation is not algebraic R-H criteria can not be applied.
2. Gives information about roots only with respect to left half or right half of s -plane i.e. does not give information about roots on jw -axis.
3. Can not be applied to discrete time system.

Here, first column of R-H array has two sign changes. So, the system is unstable.

Time domain behaviour of circuit from pole and zero plot:

Consider a transfer function $G_{12}(s)$ that relates response function $V_2(s)$ with source function $V_1(s)$. Thus, relation will be as.

$$V_2(s) = G_{12}(s) * V_1(s)$$

Let the transfer function $G_{12}(s)$ has m poles i.e. P_1, P_2, P_3 , and $V_1(s)$ has n poles $P_{m+1}, P_{m+2}, \dots, P_{m+n}$, then using the partial

" Fraction expansion, the response $V_2(s)$ can be expressed as

$$V_2(s) = \frac{k_1}{s-p_1} + \frac{k_2}{s-p_2} + \dots + \frac{k_m}{s-p_m} + \frac{k_{m+1}}{s-p_{m+1}} + \dots + \frac{k_{m+n}}{s-p_{m+n}}$$

The poles $p_1, p_2, p_3, \dots, p_m$ contributes to the transient response and the poles $p_{m+1}, p_{m+2}, \dots, p_{m+n}$ contributes to force response.


Taking inverse Laplace transform of the above equation:

$$V_2(t) = k_1 e^{p_1 t} + k_2 e^{p_2 t} + \dots + k_m e^{p_m t} + k_{m+1} e^{p_{m+1} t} + \dots + k_{m+n} e^{p_{m+n} t}$$

The poles therefore determines the waveform of the time variation of the response, the o/p voltage. The zeros determine the magnitude of each part of the response i.e. responsible values k_1, k_2, \dots, k_{m+n} .

In time domain, we see that the real part of each pole appears with an exponential term. If this real part is -ve, exponential form decays to 0 as time increases.

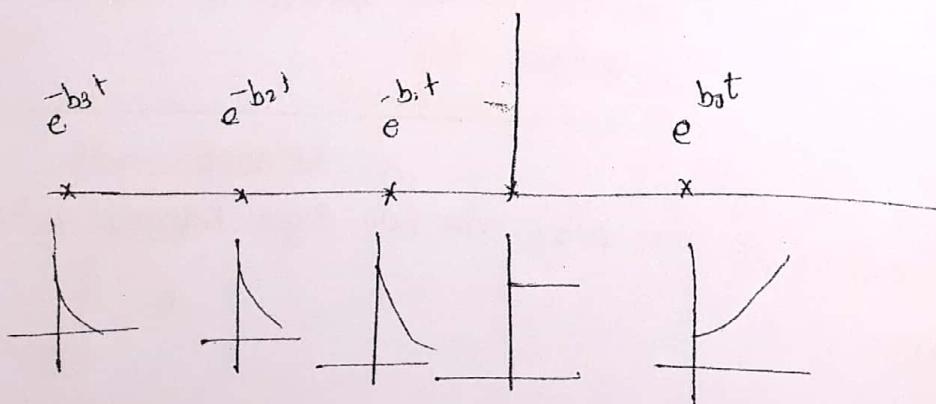Hence, for a system all poles of network functions lie on left half of s-plane but zeros are not so restricted.



Complex conjugate pole corresponds to oscillatory nature in time domain.

(1)

Time-Domain Response from pole-zero plot:

The time-domain response can be obtained from the pole-zero plot of a network function. Consider a network function given by

$$H(s) = \frac{N(s)}{D(s)} = K \frac{(s-z_1)(s-z_2) \dots (s-z_n)}{(s-p_1)(s-p_2) \dots (s-p_m)}$$

Where, z_1, z_2, \dots, z_n are zeros and $p_1, p_2, p_3, \dots, p_m$ are poles of the function $H(s)$.

Assume that poles and zeroes are distinct. Using partial fraction expansion,

$$H(s) = \frac{k_1}{s-p_1} + \frac{k_2}{s-p_2} + \dots + \frac{k_m}{s-p_m}$$

where,


$$k_i = [(s-p_i) H(s)]_{s=p_i}; i=1, 2, \dots, m$$

$$\text{or, } k_i = \frac{K (p_i - z_1)(p_i - z_2) \dots (p_i - z_n)}{(p_i - p_1)(p_i - p_2) \dots (p_i - p_m)}$$

If $H(s) = \frac{s(s+1)}{(s+4)(s^2+6s+18)}$; find $h(t)$ using the pole-zero diagram of the function.

Sol: Here, $H(s) = \frac{s(s+1)}{(s+4)(s^2+6s+18)}$
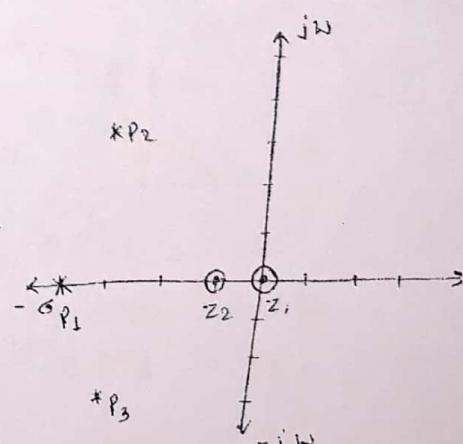
$$= \frac{s(s+1)}{(s+4)\{(s+3)^2 + 3^2\}} = \frac{s(s+1)}{(s+4)(s+3 \pm 3j)}$$



Zeros are at, $s = 0, -1$

Poles are at, $s = -4, -3 \pm 3j$

$$H(s) = \frac{k_1}{s+4} + \frac{k_2}{(s+3+3j)} + \frac{k_3}{(s+3-3j)}$$

For pole $p_1 = -4$

$$k_1 = K \frac{(p_1 - z_1)(p_1 - z_2)}{(p_1 - p_2)(p_1 - p_3)} = \frac{1(-4-0)(-4+1)}{(-4+3+3j)(-4+3-3j)} = \frac{12}{12+3^2} = 1.2$$

For the pole, $P_2 = -3 + 3j$

$$\begin{aligned}
 K_2 &= \frac{(P_2 - Z_1)(P_2 - Z_2)}{(P_2 - P_1)(P_2 - P_3)} = \frac{(-3 - j3 - 0)(-3 - j3 + 1)}{(-3 - j3 + 4)(-3 - j3 + 3 - j3)} \\
 &= \frac{(-3 - j3)(-2 - j3)}{(1 - j3)(-j6)} = \frac{6 + 9j + 6j - 9}{-6j - 18} = \frac{-3 + 15j}{-6(j + 3)} \\
 &= \frac{1 - 5j}{6 + 2j} = \frac{1 - 5j}{6 + 2j} \times \frac{6 - 2j}{6 - 2j} = \frac{6 - 2j - 30j - 10}{36 + 4} \\
 &= -\frac{4 - 32j}{40} = \frac{1}{10} (-1 - j8)
 \end{aligned}$$

For the pole, $P_3 = -3 + 3j$

$$K_3 = K_2^* = \frac{1}{10} (-1 + j8)$$

$$H(s) = \frac{1 \cdot 2}{s - 4} + \frac{1}{10} (-1 - j8) \frac{1}{s + 3 + 3j} + \frac{1}{10} (-1 + j8) \frac{1}{s + 3 - 3j}$$

Taking inverse Laplace transform:

$$\begin{aligned}
 h(t) &= 1 \cdot 2 e^{-4t} + \frac{1}{10} (-1 - j8) e^{(-3 - 3j)t} + \frac{1}{10} (-1 + j8) e^{(-3 + 3j)t} \\
 &= 1 \cdot 2 e^{-4t} + e^{-3t} \left[-\frac{1}{10} (e^{j3t} + e^{-j3t}) + \frac{8}{10} j (e^{j3t} - e^{-j3t}) \right] \\
 &= 1 \cdot 2 e^{-4t} + e^{-3t} \left[-\frac{1}{10} (2 \cos 3t) - \frac{8}{10} (2 \sin 3t) \right]
 \end{aligned}$$

$$h(t) = 1 \cdot 2 e^{-4t} - \frac{1}{5} e^{-3t} [\cos 3t + 8 \sin 3t]$$

periodic signals

A signal $f(t)$ is said to be periodic with time period T if $f(t) = f(t+T)$ for all value of t and T is a constant time known as time period.

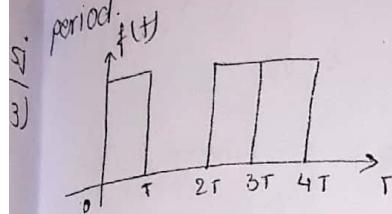


fig: non-periodic signal

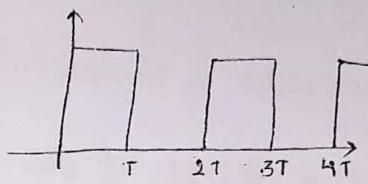


fig: periodic signal

Fundamental or Time period

Minimum positive, non-zero value of T , for which $f(t) = f(t+T)$ is satisfied.

$$\text{Fundamental frequency } (\omega_0) = \frac{\omega_0}{T}$$

Even and odd signals:

A Function is said to be even function if it ~~satisfies~~ satisfies $f(t) = f(-t)$ and a function is said to be odd function if it satisfies $f(t) = -f(-t)$.

Example: t^n for even value of n , $\cos nt$, cost are even function whereas t^n for odd value of n , $\sin nt$ are odd function.

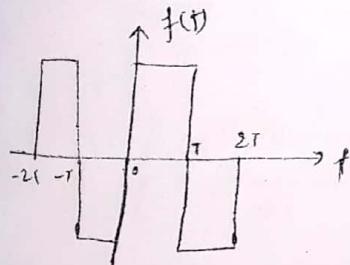


fig: odd function

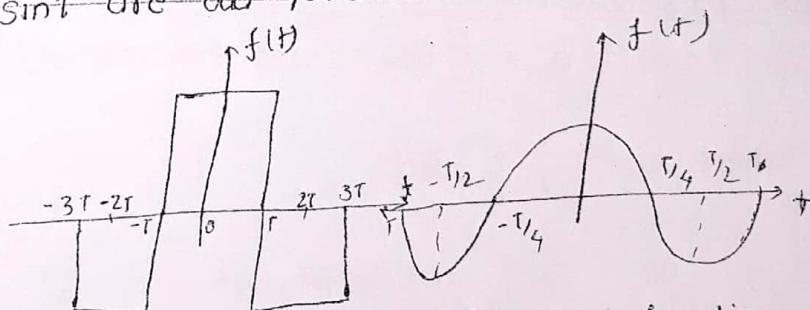


fig: even function

fig: even function

Fourier Series

Fourier series is the representation of any periodic signal in terms of complex exponential as given by following equation.

$$x(t) = \sum_{n=-\infty}^{\infty} a_n e^{j n \omega_0 t}$$

where, $\omega_0 = \frac{\omega_0}{T}$ is fundamental frequency.

$$x(t) = a_0 + \sum_{n=1}^{\infty} [a_n e^{j n \omega_0 t} + a_n^* e^{-j n \omega_0 t}]$$

Where a_n is complex fourier coefficient.

Any periodic signal $f(t)$ can be represented by the infinite sum of sine wave representation components which is called fourier series expansion.

$$\text{i.e. } f(t) = a_0 + \sum_{n=1}^{\infty} \left[a_n \cos \frac{2\pi n t}{T_0} + b_n \sin \frac{2\pi n t}{T_0} \right]$$

$$= a_0 + \sum_{n=1}^{\infty} [a_n \cos \omega_0 n t + b_n \sin \omega_0 n t] \quad \dots \dots \dots \quad ①$$

where, T_0 is the time period of $f(t)$ and $\omega_0 = \frac{2\pi}{T_0}$ where f_0 is the fundamental frequency and $n f_0$ are harmonics of f_0 . a_0, a_n and b_n of equation ① are called trigonometric fourier series coefficients.

Determination of fourier coefficient:

(a) for complex exponential functions:

$$x(t) = \sum_{n=-\infty}^{\infty} a_n e^{jn\omega_0 t}$$

$$\text{where, } a_n \text{ is given by, } a_n = \frac{1}{T} \int_0^T x(t) e^{-jn\omega_0 t} dt$$

$$\text{for } n=0, \quad a_0 = \frac{1}{T} \int_0^T x(t) dt.$$

(b) For trigonometric function

$$x(t) = a_0 + \sum_{n=1}^{\infty} (a_n \cos n\omega_0 t + b_n \sin n\omega_0 t)$$

$$\text{where, } a_0 = \frac{1}{T} \int_0^T x(t) dt$$


$$a_n = \frac{2}{T} \int_0^T x(t) \cos n\omega_0 t dt$$

$$b_n = \frac{2}{T} \int_0^T x(t) \sin n\omega_0 t dt$$

$$\text{For even function : } b_n = 0, \quad a_n = \frac{4}{T} \int_0^{T/2} x(t) \cos n\omega_0 t dt, \quad a_0 = \frac{2}{T} \int_0^{T/2} x(t) dt$$

$$\text{For odd function : } a_0 = 0 \quad \text{and} \quad a_n = 0, \quad b_n = \frac{4}{T} \int_0^{T/2} x(t) \sin n\omega_0 t dt$$

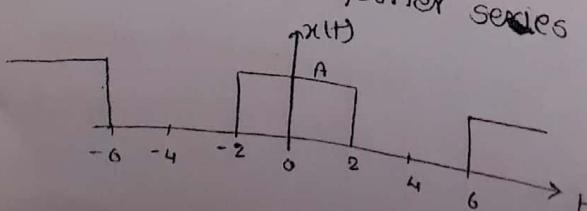Q.1 Find the exponential fourier series coefficient for the signal



$$T = 8$$

$$\omega_0 = \frac{2\pi}{T} = \frac{2\pi}{8} = \frac{\pi}{4}$$

Now, $x(t) = \begin{cases} A & \text{for } -2 \text{ to } 2 \\ 0 & \text{for } 2 \text{ to } 6 \end{cases}$

$$\sin \theta = \frac{e^{j\theta} - e^{-j\theta}}{2j}$$

$$\cos \theta = \frac{e^{j\theta} + e^{-j\theta}}{2}$$

We have, $x(t) = \sum_{n=-\infty}^{\infty} a_n e^{jn\omega_0 t}$

$$\text{where, } a_n = \frac{1}{T} \int_0^T x(t) e^{-jn\omega_0 t} dt$$

$$= \frac{1}{8} \int_{-2}^2 A e^{-jn\omega_0 t} dt$$

$$= \frac{A}{8} \left[\frac{e^{-jn\omega_0 t}}{-jn\omega_0} \right]_{-2}^2$$

$$= \frac{A}{8} \left[\frac{e^{-2jn\omega_0} - e^{2jn\omega_0}}{-jn\omega_0} \right]$$


$$= \frac{A}{8} \left[\frac{e^{-jn\frac{\pi}{2}} - e^{jn\frac{\pi}{2}}}{-jn\frac{\pi}{4}} \right]$$

$$= \frac{A}{8} \left[\frac{e^{jn\frac{\pi}{2}} - e^{-jn\frac{\pi}{2}}}{2j} \right] \times \frac{2}{n\frac{\pi}{4}}$$

$$= \frac{A}{2} \frac{\sin n\frac{\pi}{2}}{n\frac{\pi}{2}}$$

$$= \frac{A}{2} \operatorname{sinc} \frac{n\pi}{2}$$

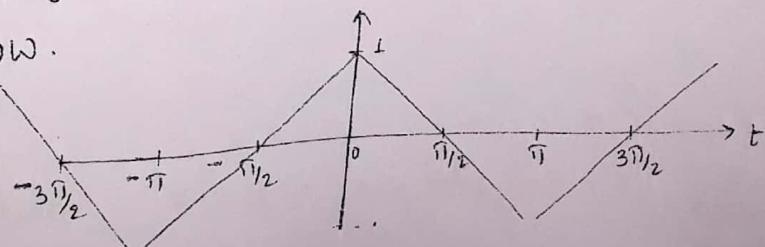Q.2. Obtain the trigonometric Fourier-series representation for the signal shown below.



SOLN: Here,

$$f(t) = \begin{cases} \frac{2}{\pi}t + 1 & \text{for } -\pi \text{ to } 0 \\ -\frac{2}{\pi}t + 1 & \text{for } 0 \text{ to } \pi \end{cases}$$

$$T = 2\pi, \omega_0 = \frac{2\pi}{T} = 1$$

Since function $f(t)$ is an even function. Hence, $b_n = 0$

NOW,

$$a_0 = \frac{2}{T} \int_0^{\pi/2} f(t) dt$$

$$= \frac{2}{2\pi} \int_0^{\pi} \left(-\frac{2}{\pi}t + 1 \right) dt$$

$$= \frac{1}{\pi} \left[-\frac{2}{\pi} \left[\frac{t^2}{2} \right]_0^{\pi} + [t]_0^{\pi} \right]$$

$$= \frac{1}{\pi} \left[-\frac{2}{\pi} \times \frac{\pi^2}{2} + \pi \right] = 0$$

$$a_n = \frac{4}{T} \int_0^{\pi/4} f(t) \cos n\omega_0 t dt$$

$$= \frac{4}{2\pi} \int_{-\pi}^0 \left(\frac{2}{\pi}t + 1 \right) \cos n\omega_0 t dt$$

$$= \frac{2}{\pi} \left[\int_{-\pi}^0 \frac{2}{\pi}t \cos n\omega_0 t dt + \int_{-\pi}^0 \cos n\omega_0 t dt \right]$$
~~$$= \frac{2}{\pi} \left[\left\{ \frac{\sin n\omega_0 t}{n\omega_0} \right\}_{-\pi}^0 + \left\{ \frac{2}{\pi} \left[\left(\frac{ts \sin n\omega_0 t}{n\omega_0} \right)_{-\pi}^0 - \int_{-\pi}^0 \frac{\sin n\omega_0 t}{n\omega_0} dt \right] \right\} \right]$$

$$= \frac{2}{\pi} \left[\left[\frac{\sin nt}{n} \right]_{-\pi}^0 + \left[\frac{2}{\pi} \frac{t \sin nt}{n} \right]_{-\pi}^0 - \frac{2}{n\pi} \left[\frac{\cos nt}{n} \right]_{-\pi}^0 \right]$$


$$= \frac{2}{\pi} \left[0 + 0 + \frac{2}{n^2\pi} [1 - (-1)^n] \right]$$~~

$$a_n = \frac{4}{n^2\pi^2} [1 - (-1)^n]$$

Therefore,

$$a_n = 0 ; \text{ if } n \text{ is even i.e. } 2, 4, 6$$
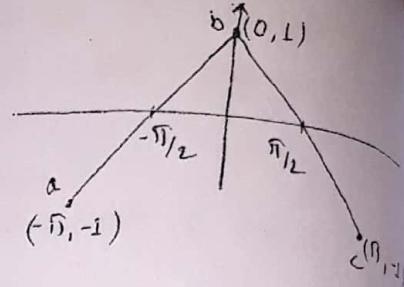
$$a_n = \frac{8}{n^2\pi^2} ; \text{ if } n \text{ is odd i.e. } 1, 3, 5, 7 \quad \text{and } b_n = 0$$



$$\text{Eq' of ab} \Rightarrow y+1 = \frac{2}{\pi}(x+\pi)$$

$$y = \frac{2}{\pi}x + 2 - 1 = \frac{2}{\pi}x$$


$$\text{Eq' of bc} \Rightarrow y-1 = -\frac{2}{\pi}(x)$$

$$y = -\frac{2}{\pi}x + 1$$

$$f(t) = \sum_{n=1}^{\infty} \frac{8}{n^2 \pi^2} \cos nt ; n \text{ is odd}$$

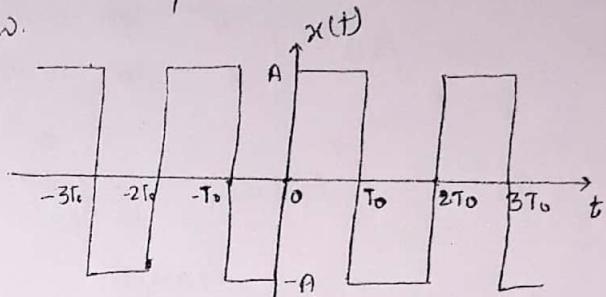Q3. Obtain the trigonometric Fourier series representation of the periodic signal as shown in figure below.

Ans: Here, $x(t) = \begin{cases} A & \text{for } 0 \leq t < T_0 \\ -A & \text{for } T_0 \leq t < 2T_0 \end{cases}$



Time period, $T = 2T_0$

$$\omega_0 = \frac{2\pi}{2T_0} = \frac{\pi}{T_0}$$

Since, the function is an odd function, hence $a_0 = 0, a_n = 0$.

$$\text{Now, } b_n = \frac{4}{T} \int_0^{T_0} x(t) \sin n\omega_0 t dt$$

$$\begin{aligned} &= \frac{4}{2T_0} \int_0^{T_0} A \sin n\omega_0 t dt \\ &= \frac{2A}{T_0} \int_0^{T_0} \sin \frac{n\pi t}{T_0} dt \\ &= \frac{2A}{T_0} \left[-\frac{\cos \frac{n\pi t}{T_0}}{\frac{n\pi}{T_0}} \right]_0^{T_0} \\ &= \frac{2A}{n\pi} \left[-\cos n\pi + 1 \right] \\ &= \frac{2A}{n\pi} [1 - (-1)^n] \end{aligned}$$

Therefore, $b_n = 0$; if n is even

$$= \frac{4A}{n\pi} ; \text{ if } n \text{ is odd}$$

$$\therefore x(t) = \sum_{n=1}^{\infty} \frac{4A}{n\pi} \sin \frac{n\pi t}{T_0} ; n \text{ is odd.}$$

3.4 Determine the exponential form of fourier series expansion for the periodic waveform shown in figure below.

Sol: Here, $f(t) = \begin{cases} 1 & \text{for } 0 \text{ to } a \\ 0 & \text{for } a \text{ to } T \end{cases}$

$$a_0 = \frac{1}{T} \int_0^T f(t) dt = \frac{1}{T} \int_0^a dt = \frac{a}{T}$$

$$a_n = \frac{1}{T} \int_0^T f(t) e^{-jnw_0 t} dt$$

$$= \frac{1}{T} \int_0^T e^{-jnw_0 t} dt = \frac{1}{T} \left[\frac{e^{-jnw_0 t}}{-jnw_0} \right]_0^a$$

$$= \frac{1}{T} \left[\frac{e^{-jnw_0 a}}{-jnw_0} - 1 \right]$$

$$= \frac{1 - e^{-jnw_0 a}}{jn w_0 T}$$

$$\therefore f(t) = \frac{a_0 + \sum_{n=-\infty}^{\infty} \left(\frac{1 - e^{-jnw_0 a}}{jn w_0 T} \right) e^{jnw_0 t}}{T}$$


3.5 obtain the trigonometric fourier series of waveform shown below:

Sol: Here,

$$T = T$$

$$w_0 = \frac{2\pi}{T}$$
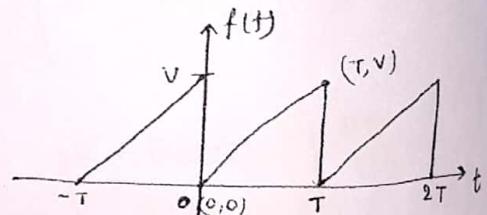
$$\text{and, } f(t) = \frac{V}{T} t \quad \text{for } t = 0 \text{ to } T$$



$$\text{Eq: } \Rightarrow y = \frac{V}{T} x$$

NOW, Trigonometric fourier series expansion is given as,

$$f(t) = a_0 + \sum_{n=1}^{\infty} [a_n \cos n w_0 t + b_n \sin n w_0 t]$$

$$\text{where, } a_0 = \frac{1}{T} \int_0^T f(t) dt = \frac{1}{T} \int_0^T \frac{V}{T} t dt = \frac{V}{T^2} \left[\frac{t^2}{2} \right]_0^T = \frac{V}{2}$$

$$a_n = \frac{1}{T} \int_0^T f(t) \cos n w_0 t dt = \frac{1}{T} \int_0^T \frac{V}{T} t \cos n w_0 t dt$$

$$= \frac{V}{T^2} \left\{ \left[\frac{t \sin n w_0 t}{n w_0} \right]_0^T - \int_0^T \frac{\sin n w_0 t}{n w_0} dt \right\} = \frac{V}{T^2} \left\{ \frac{T \sin n 2\pi}{n 2\pi} - \frac{1}{n w_0} \right\}$$

$$\frac{V}{T} \left\{ \frac{1}{n^2 \omega_0^2} (\cos 2n\pi - 1) \right\}$$

$$\frac{V}{T} \cdot \frac{1}{n^2 \cdot 4\pi^2} (1-1)$$

$$a_0 \text{ and } b = \frac{2}{T} \int_0^T f(t) \sin n\omega_0 t dt$$

$$= \frac{2}{T} \int_0^T \frac{V}{T} t \sin \frac{2\pi n t}{T} dt$$

$$= \frac{2V}{T^2} \left\{ \left[\frac{t \cos \frac{2\pi n t}{T}}{\frac{2\pi n}{T}} \right]_0^T - \int_0^T \left(-\frac{\cos \frac{2\pi n t}{T}}{\frac{2\pi n}{T}} \right) dt \right\}$$

$$= \frac{2V}{T^2} \left\{ -\frac{\cos 2\pi n}{\frac{2\pi n}{T}} + 0 + \frac{1}{\frac{2\pi n}{T}} \left[\frac{\sin \frac{2\pi n t}{T}}{\frac{2\pi n}{T}} \right]_0^T \right\}$$

$$= \frac{V}{T} \frac{1}{\frac{2\pi n}{T}} + \frac{2V}{(\frac{2\pi n}{T})^2} \left[\frac{\sin 2\pi n}{\frac{2\pi n}{T}} \right] \xrightarrow{0}$$

$$= -\frac{V}{n\pi}$$

$$\therefore f(t) = \frac{V}{2} + \sum_{n=1}^{\infty} \left[-\frac{V}{n\pi} \sin \frac{2\pi n}{T} t \right].$$

Fourier transform:

Fourier transform is approach to develop the frequency domain representation of a non-periodic signal.

Let, $x(t)$ be non-periodic signal then its Fourier transform or Fourier integral is given as,

$$x(t) \xleftarrow{\text{F.T.}} X(j\omega)$$

$$X(j\omega) = F(x(t)) = \int_{-\infty}^{\infty} x(t) e^{-j\omega t} dt$$

and Inverse Fourier transform is,

$$x(t) = F^{-1}[X(j\omega)] = \frac{1}{2\pi} \int_{-\infty}^{\infty} X(j\omega) e^{j\omega t} d\omega$$

Fourier transform is complex function so it has both magnitude and direction

Existence of fourier transform

A function $x(t)$ is said to be fourier transformable, if it is satisfied following Dirichlet conditions:

- The function $x(t)$ is absolutely integrable i.e. $\int_{-\infty}^{\infty} |x(t)| dt < \infty$
- The function has finite number of maxima and minima, if any, within a finite interval of time.
- The function is single valued and has finite number of discontinuities, if any, within a finite interval of time.

Q1. Obtain the fourier transform of a single-sided exponential function $e^{-at} u(t)$ as shown in figure below. Also draw the spectrum. (where $a > 0$).

Sol:

$$x(t) = e^{-at} u(t)$$


NOW,

$$X(j\omega) = F[x(t)]$$

$$= \int_{-\infty}^{\infty} x(t) e^{-j\omega t} dt = \int_0^{\infty} e^{-at} e^{-j\omega t} dt$$

$$= \int_0^{\infty} e^{-(a+j\omega)t} dt = \frac{e^{-(a+j\omega)t}}{-a-j\omega} \Big|_0^{\infty}$$

$$= \frac{1}{a+j\omega}$$

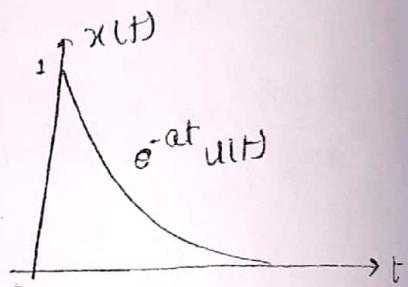

Since, Fourier transform is complex, both amplitude and phase spectrums are necessary i.e.


$$X(j\omega) = |X(j\omega)| e^{j\phi(\omega)}$$

Amplitude spectrum: $|X(j\omega)| = \frac{1}{\sqrt{a^2 + \omega^2}}$

and, phase spectrum, $\phi(\omega) = -\tan^{-1}\left(\frac{\omega}{a}\right)$

w	$-a$	0	a	
$(j\omega)$	$\frac{1}{\sqrt{3}}a$	$\frac{1}{a}$	$\frac{1}{\sqrt{2}}a$	

w	$-a$	b	a
(\sin)	$\pi/4$	0	$-\pi/20$

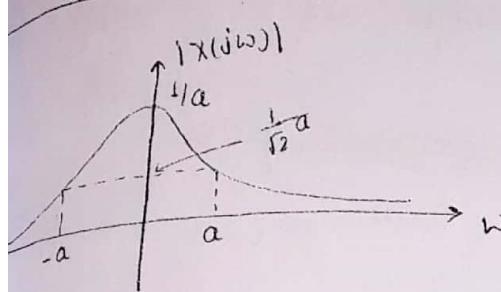

a) Amplitude spectrum


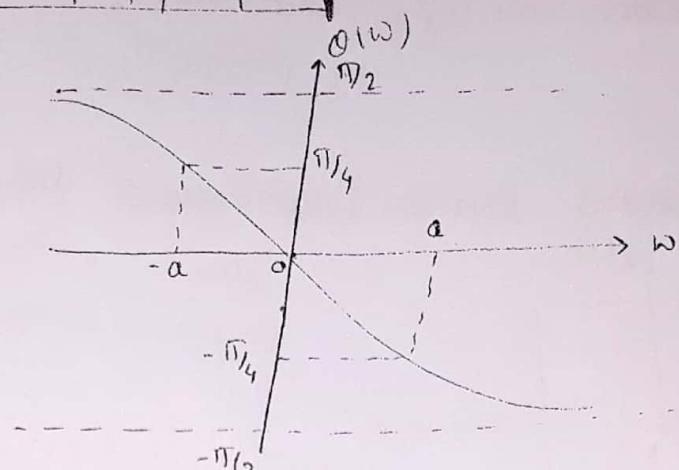


fig: phase spectrum.

Find the fourier transform of the gate function shown in figure below.

1^o: Here,
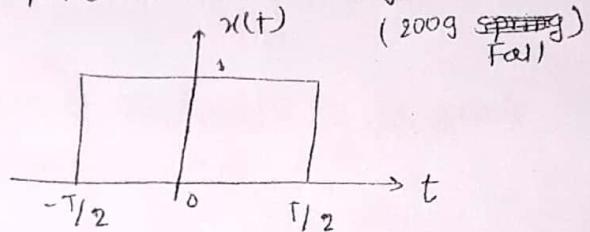
$$x(t) = \begin{cases} 1 & ; \text{ for } -\frac{T}{2} < t < \frac{T}{2} \\ 0 & ; \text{ otherwise} \end{cases}$$




$$X(j\omega) = F[x(t)] = \int_{-\infty}^{\infty} x(t)e^{-j\omega t} dt$$

$$= \int_{-\infty}^{T/2} e^{-j\omega t} dt = \left. \frac{e^{-j\omega t}}{-j\omega} \right|_{-\infty}^{T/2}$$

$$= \frac{e^{-j\omega \left(\frac{T}{2}\right)} - e^{-j\omega \left(-\frac{T}{2}\right)}}{-j\omega} = \frac{e^{j\omega \frac{T}{2}} - e^{-j\omega \frac{T}{2}}}{-j\omega}$$


$$= \frac{2}{\omega} \left[\frac{e^{j\omega T/2} - e^{-j\omega T/2}}{2j} \right] = \frac{2}{\omega} \sin(\omega T/2)$$
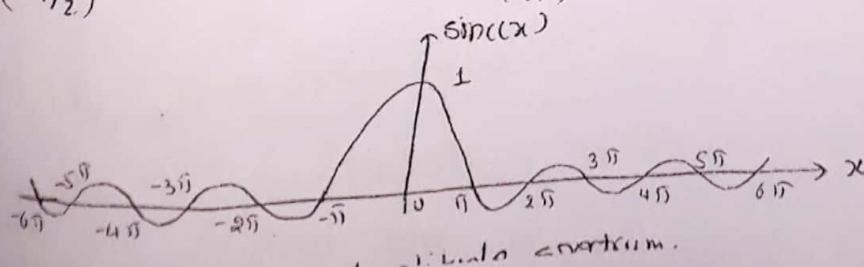
$$= \frac{T}{(\omega T/2)} \sin(\omega T/2) = T \text{sinc}\left(\frac{\omega T}{2}\right)$$




Now, since $\text{sinc}(x) = 0$ when $x = \pm n\pi$

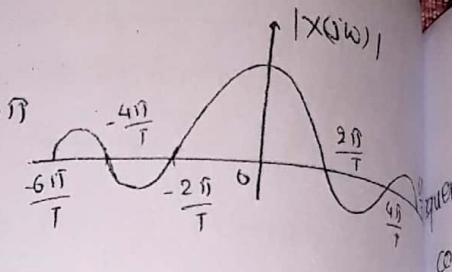Therefore, $\text{sinc}\left(\frac{\omega T}{2}\right) = 0$ when, $\frac{\omega T}{2} = \pm n\pi$
 $\omega = \pm \frac{2n\pi}{T}$.



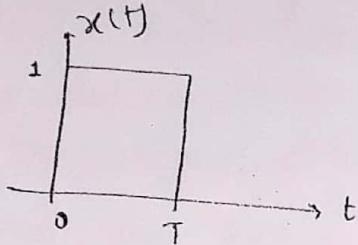Q.3. Find the Fourier Transform of the rectangular pulse.



Soln: Here,

$$x(t) = \begin{cases} 1 & \text{for } 0 \text{ to } T \\ 0 & \text{otherwise} \end{cases}$$

$$\begin{aligned} X(j\omega) &= F[x(t)] = \int_{-\infty}^{\infty} x(t)e^{-j\omega t} dt \\ &= \int_0^T e^{-j\omega t} dt = \frac{e^{-j\omega t}}{-j\omega} \Big|_0^T \\ &= \frac{e^{-j\omega T} - 1}{-j\omega} = \frac{1 - e^{-j\omega T}}{j\omega} = \frac{e^{-j\omega T/2} - j\omega T/2}{j\omega} \times \frac{e^{-j\omega T/2} + j\omega T/2}{j\omega} \\ &= \frac{2e^{-j\omega T/2}}{\omega} \left[e^{j\omega T/2} - e^{-j\omega T/2} \right] = \frac{2e^{-j\omega T/2}}{\omega} \frac{\sin(\omega T/2)}{\omega T/2} \times (\omega T/2) \\ &= \frac{2}{\omega} T e^{-j\omega T/2} \text{sinc}\left(\frac{\omega T}{2}\right) \end{aligned}$$

Amplitude response/spectrum is same as previous and phase spectrum is,

$$\angle X(j\omega) = -\left(\frac{\omega T}{2}\right)$$

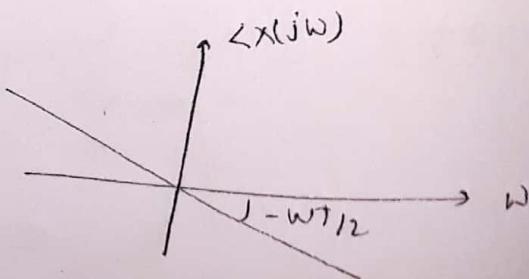


Fig: phase spectrum

If is the study of circuit behaviour according to the change in frequency. Let $H(s)$ be any network function where, $s = \sigma + j\omega$, since frequency contributed by ω , we consider only imaginary part.

Thus, for $s = j\omega$,

$H(s)$ becomes complex network function $H(j\omega)$. In general

$$\text{we have, } H(s) = \frac{a_0 s^n + a_1 s^{n-1} + \dots + a_n}{b_0 s^m + b_1 s^{m-1} + \dots + b_m}$$

on factorizing,

$$H(s) = \frac{a_0 (s - z_1)(s - z_2) \dots (s - z_n)}{b_0 (s - p_1)(s - p_2) \dots (s - p_m)}$$

$$\text{for } s = j\omega, \quad H(j\omega) = \frac{a_0}{b_0} \left[\frac{(j\omega - z_1)(j\omega - z_2) \dots (j\omega - z_n)}{(j\omega - p_1)(j\omega - p_2) \dots (j\omega - p_m)} \right]$$

Thus, frequency response is the curve response for magnitude and phase of transfer function for different values of ω .

Bode plot:

The scientist H.W. Bode Suggested a specific method to obtain the frequency response in which logarithmic values are used. It is the graphical representation of transfer function and used to determine stability of transfer function at various frequency.

In general, Bode plot consists of two plots:

Magnitude plot

logarithmic value of magnitude are plotted against logarithmic values of ω .

We have, $H(j\omega) = R(\omega) + jX(\omega)$

$$\phi = \tan^{-1} \frac{X(\omega)}{R(\omega)}, \quad |H(j\omega)| = \sqrt{R(\omega)^2 + X(\omega)^2}$$

In dB,

$$|H(j\omega)|_{\text{in dB}} = 20 \log \sqrt{R^2(\omega) + X^2(\omega)}$$

Therefore, we plot $|H(j\omega)|_{\text{in dB}}$ vs $\log \omega$

Phase plot

phase angle in degrees are plotted against logarithmic values of ω

$$\phi = \tan^{-1} \left[\frac{X(\omega)}{R(\omega)} \right]$$

We plot, ϕ vs. $\log \omega$.

ω ,

Bode plot:

$H(s)$ is expressed as:

$$H(s) = \frac{K (1+sT_a)(1+sT_b)}{s^n (1+sT_1)(1+sT_2)}$$

For $s = j\omega$

$$H(j\omega) = \frac{K (1+j\omega T_a)(1+j\omega T_b)}{(j\omega)^n (1+j\omega T_1)(1+j\omega T_2)}$$

$$\begin{aligned} \text{The magnitude } |H(j\omega)|_{\text{indB}} &= 20 \log K + 20 \log \sqrt{1+\omega^2 T_a^2} + 20 \log \sqrt{1+\omega^2 T_b^2} \\ &\quad - 20 \log \omega^n - 20 \log \sqrt{1+\omega^2 T_1^2} - 20 \log \sqrt{1+\omega^2 T_2^2} \end{aligned}$$

$$\begin{aligned} \text{d. phase, } \phi &= \tan^{-1} \left(\frac{0}{K} \right) + \tan^{-1} (\omega T_a) + \tan^{-1} (\omega T_b) - \tan^{-1} \left(\frac{\omega^n}{0} \right) - \tan^{-1} (\omega T_1) \\ &\quad - \tan^{-1} (\omega T_2) \\ &= \tan^{-1} (\omega T_a) + \tan^{-1} (\omega T_b) - 90^\circ - \tan^{-1} (\omega T_1) - \tan^{-1} (\omega T_2) \end{aligned}$$

Bode plot for common polynomials

1) Constant, K

$$|H(j\omega)|_{\text{indB}} = 20 \log K$$

$$\phi = 0^\circ$$

2) Differentiator, s^n

$$|H(j\omega)|_{\text{indB}} = 20 \log (\omega^n)$$

$$\phi = 90^\circ$$

3) Integrator, $\frac{1}{s^n}$

$$|H(j\omega)|_{\text{indB}} = 20 \log \left(\frac{1}{\omega^n} \right)$$

$$= 20 \log 1 - 20 \log \omega^n$$

$$= -20 \log \omega^n$$

$$\phi = -90^\circ$$

4) $(1+sT)$

$$\begin{aligned} |H(j\omega)|_{\text{indB}} &= 20 \log \sqrt{1+\omega^2 T^2} \\ &= 20 \log \sqrt{1 + \left(\frac{\omega}{\omega_m} \right)^2} \quad \left(\because T = \frac{1}{\omega_m} \right) \end{aligned}$$

for $\omega < < \omega_m$

$$|H(j\omega)|_{\text{indB}} = 20 \log 1 = 0$$

$$\text{for } \omega = \omega_m, |H(j\omega)|_{\text{indB}} = 30 \text{ dB}$$

$$P > \omega_m$$

$$|H(j\omega)| \text{ in dB}$$

20 dB

40 dB

60 dB;

Similarly, for $\frac{1}{1+ST}$ magnitude decreases at slope of -20 dB/dec.

phase is given by $\phi = -\tan^{-1}\left(\frac{\omega}{\omega_m}\right)$

Factor	Coupling Frequency	$ H(j\omega) \text{ in dB}$	ϕ
K	none	$20 \log K$	0°
$S = (j\omega)$	none	+20 dB/dec line with 0 dB at $\omega = 1$	$+90^\circ$
$\frac{1}{S} = \frac{1}{j\omega}$	none	-20 dB/dec line with 0 dB at $\omega = 1$	-90°
$(1+ST)$	$\omega_m = \frac{1}{T}$	+20 dB/dec line with ≈ 0 dB at $\omega \gg \omega_m$ For -20 dB/dec line with ≈ 0 dB at $\omega \gg \omega_m$	$\tan^{-1}(WT)$
$\frac{1}{1+ST}$	$\omega_m = \frac{1}{T}$	≈ 0 dB at $\omega \gg \omega_m$ For +40 dB/dec line with ≈ 0 dB at $\omega \gg \omega_m$ For	$-\tan^{-1}\left(\frac{\omega}{\omega_m}\right)$
$\omega_m^2 + 2\zeta\omega_m S + S^2$	ω_m	≈ 0 dB at $\omega \gg \omega_m$ For	$\tan^{-1} \frac{2\zeta\omega/\omega_m}{1 - (\frac{\omega}{\omega_m})^2}$
$\frac{S^2}{\omega_m^2} + \frac{2\zeta S}{\omega_m} + 1$	ω_m	≈ 0 dB at $\omega \gg \omega_m$ For	$-\tan^{-1} \frac{2\zeta\omega/\omega_m}{1 - (\frac{\omega}{\omega_m})^2}$
$\left(\frac{j\omega}{\omega_m}\right)^2 + \frac{2\zeta j\omega}{\omega_m} + 1$	ω_m	-40 dB/dec line with ≈ 0 dB at $\omega \gg \omega_m$ For	$-\tan^{-1} \frac{2\zeta\omega/\omega_m}{1 - (\frac{\omega}{\omega_m})^2}$
$\left(\omega_m^2 + 2\zeta\omega_m S + S^2\right)^{-1}$	ω_m	≈ 0 dB at $\omega \gg \omega_m$ For	

Example:

plot magnitude and phase for

$$G(S) = \frac{20(0.15+1)(0.0025+1)}{S^2(S+100)}$$

$$= \frac{20(0.15+1)(0.0025+1)}{100 S^2 (0.015+1)}$$

$$= \frac{0.2(0.15+1)(0.0025+1)}{S^2 (0.015+1)}$$

For $s = j\omega$


$$G(j\omega) = \frac{0.2 (0.1j\omega + 1) (0.002j\omega + 1)}{(j\omega)^2 (0.01j\omega + 1)}$$


Table to plot magnitude of $G(j\omega)$

S.N.	Factor	c.f.	$ M \text{dB}$
1.	0.2	none	$20 \log(0.2) = -14 \text{ dB}$
2.	$0.1j\omega + 1$	10	+20 dB/dec line with ods at $\omega > 10$ radian
3.	$0.002j\omega + 1$	500	+20 dB/dec line with ods For $\omega > 500$ radian
4.	$\frac{1}{\omega^2}$	none	-40 dB/dec line with ods at $\omega = 1$
5.	$\frac{1}{0.01j\omega + 1}$	100	-20 dB/dec line with ods at $\omega > 100$ radian. For

Phase plot
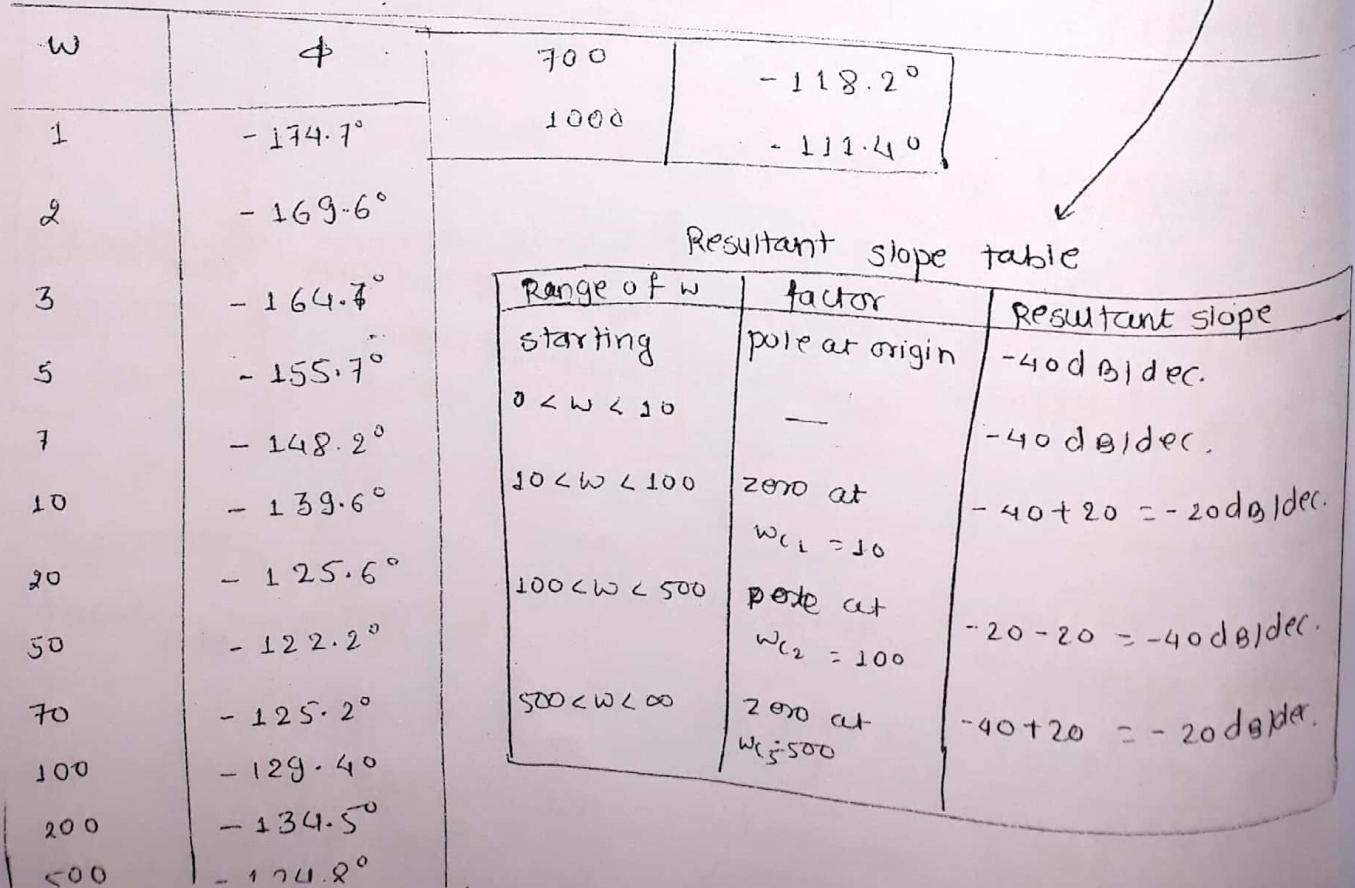
$$\phi = \tan^{-1}(0.1\omega) + \tan^{-1}(0.002\omega) - 180^\circ - \tan^{-1}(0.01\omega)$$



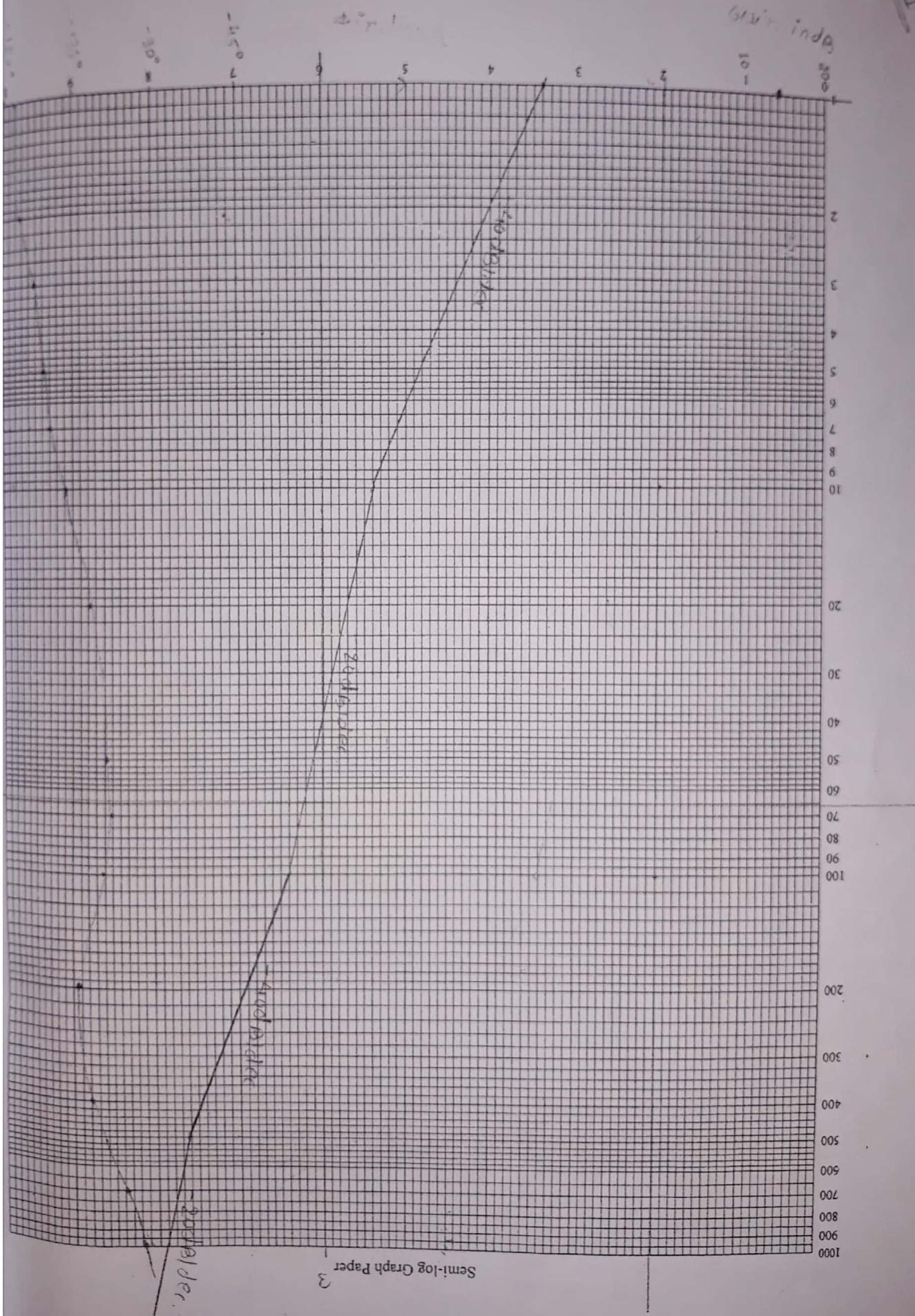

Example 2 Draw asymptotic Bode plot for the following function:

$$G(s) = \frac{20(s+2)}{s(s^2 + 4s + 16)}$$

$$\begin{aligned} G(s) &= \frac{20(s+2)}{s(s^2 + 4s + 16)} \\ &= \frac{20(1 + 0.5s)}{16s\left(\frac{s^2}{16} + \frac{1}{4}s + 1\right)} \\ &= \frac{2.5(1 + 0.5s)}{s\left(\frac{1}{16}s^2 + \frac{1}{4}s + 1\right)} \end{aligned}$$

For, $s = j\omega$

$$G(j\omega) = \frac{2.5(1 + 0.5j\omega)}{j\omega\left(\frac{1}{16}(j\omega)^2 + \frac{1}{4}j\omega + 1\right)} = \frac{2.5(1 + 0.5j\omega)}{(j\omega)\left\{\left(1 - \frac{1}{16}\omega^2\right) + \frac{1}{4}j\omega\right\}}$$

Table to plot magnitude of $G(j\omega)$

S.N.	Factor	C.F.	$ M \text{dB}$
1	2.5	none	$20 \log(2.5) = 7.95 \text{ dB}$
	$1 + 0.5s$	2	+20 dB/dec line with odB at $\omega > 2 \text{ radian}$ For
	$\frac{1}{s}$	none	-20 dB/dec line with odB at $\omega = 1$
	$\frac{1}{16s^2 + \frac{1}{4}s + 1}$	4	-40 dB/dec line with odB at $\omega > 100 \text{ radian}$ For

Table for phase plot $\phi \approx \tan^{-1}(0.5\omega) - 90^\circ - \tan^{-1}\left\{\frac{\omega}{1 - \frac{1}{16}\omega^2}\right\}$

ϕ	ω	ϕ
-88.57°	10	-88.57°
-87.16°	20	-87.16°
-83.2°	50	-83.2°
-80.9°	70	-80.9°
-78.4°	100	-78.4°
-78.7°	200	-78.7°
-78.7°	500	-78.7°
-82.9°	700	-82.9°
-155.64°	1000	-155.64°

Range of ω	Factor	Resultant slope
Starting	pole at origin	-20 dB/decade
$0 < \omega < 2$	—	-20 dB/dec.
$2 < \omega < 4$	zero pole at $\omega_{c1} = 2$	-20 + 20 = 0 dB/dec.
$\omega > 4$	pole at $\omega_{c2} = 4$	0 - 40 = -40 dB/dec.

Phase crossover frequency

The frequency at which the angle of the system function -180° is called phase-crossover frequency. It is denoted by ω_p .

Gain crossover frequency

The frequency at which the magnitude of the system function 0 dB is called gain-crossover frequency. It is denoted by ω_g .

Gain Margin (GM)

As the system gain changes, the system stability gets effected. As gain K is increased, the system becomes less and less stable.

The gain margin is the amount of gain in dB that can be added to the system before the system becomes unstable.

The gain margin is the reciprocal of the magnitude of the system function at the frequency where the phase angle is -180° or the phase-crossover frequency. Mathematically,

$$GM = \frac{1}{|G(j\omega_p)|}$$

In terms of dB ,

$$GM \text{ in } \text{dB} = 20 \log_{10} \frac{1}{|G(j\omega_p)|} = -20 \log_{10} |G(j\omega_p)|$$

The positive gain margin means increase in gain is allowable and system is stable. On the otherhand, the negative gain margin means the gain limit has been crossed and system is unstable.

Phase margin (PM)

The phase margin is the amount of phase lag in degree that can be added to the system before the system becomes unstable.


The phase margin is 180° plus the phase angle ϕ at the gain-crossover frequency. Mathematically,

$$PM = 180^\circ + \phi$$

$$\text{where, } \phi = \angle G(j\omega_g)$$

The positive phase margin means increase in phase lag is allowed.

Semi-log Graph Paper

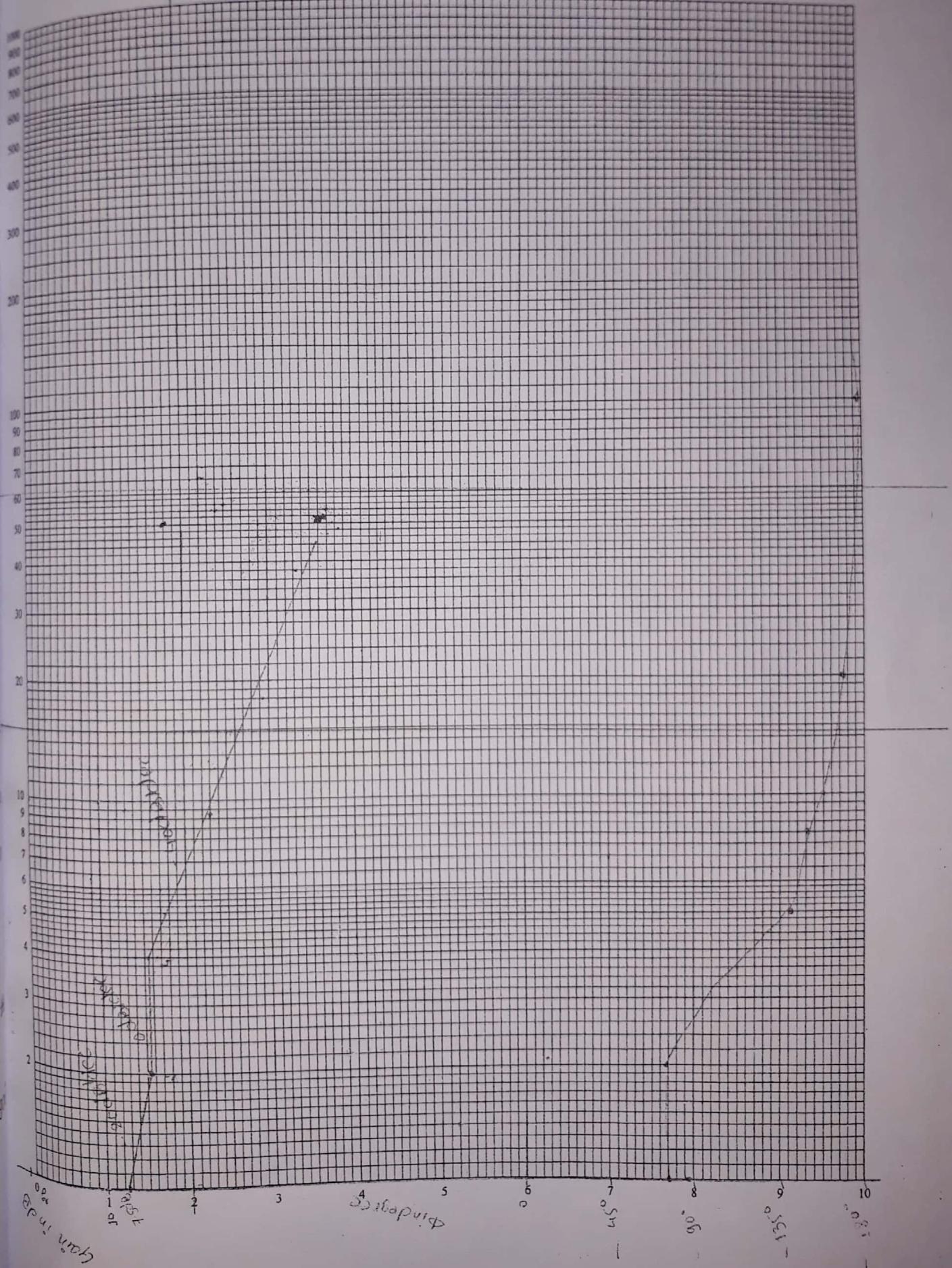

The system is stable. On the other hand, the negative phase margin means the phase lag limit has been crossed and system is unstable.

IE: If PM is positive, GM must be positive and vice-versa. and if PM is negative, GM must be negative and vice-versa.

Draw the Bode plot for

$$G(s) = \frac{20}{s(s+2)(s+10)}$$

From the Bode plot, also determine (i) phase-cross over frequency (ii) gain-cross over frequency (iii) gain margin (iv) phase margin (v) stability.

Solution:

Arrange $G(s)$ in time constant form

$$G(s) = \frac{1}{s\left(1 + \frac{s}{2}\right)\left(1 + \frac{s}{10}\right)}$$

Table to plot magnitude of $G(s)$

N.	Factor	c.F.	$ M $ dB
1	none		$20\log(1) = 0$ dB
2	s	none	-20 dB/dec line with 0 dB at $\omega = 1$
3	$1 + \frac{s}{2}$	2	-20 dB/dec line for $\omega > 2$
4	$1 + \frac{s}{10}$	10	-20 dB/dec line for $\omega > 10$

resultant slope table

range of ω	factor	Resultant slope
starting	pole at origin	-20 dB/dec.
$\omega < 2$	—	-20 dB/dec.
$\omega < 10$	pole at $\omega_c = 2$	$-20 - 20 = -40$ dB/dec.
$\omega < \infty$	pole at $\omega_c = 10$	$-40 - 20 = -60$ dB/dec.

Phase

$$G(j\omega) = \frac{1}{j\omega\left(1 + \frac{j\omega}{2}\right)\left(1 + \frac{j\omega}{10}\right)}$$

ω	ϕ
0.1	-93.43°
1	-122.27°
2	-146.3°
0	-213.69°
00	-263.14°
0	-270°

From Bode plot,

phase - crossover frequency, $\omega_p = 4.7 \text{ rad/sec}$.

gain - crossover frequency, $\omega_g = 1 \text{ rad/sec}$.

gain - margin, GM = +20dB

phase - margin, PM = +57°


Since, both GM and PM are positive, the given system is stable in nature.

Filters

- Filters are the combination of electrical components which pass or allows the un-attenuated transmission of electric signals with certain frequency range and stops transmission of electric signals outside the range.
- Band, in which ideal filters have to pass all frequencies without reduction in magnitude are referred to as pass band.
- Band, in which ideal filters have to attenuate (or stop) frequencies are referred to as stop band.
- The frequency which separates the pass-band and stop-band is defined as the cut-off frequency of the filter.

Classification of filters:

There are four common types of filters:

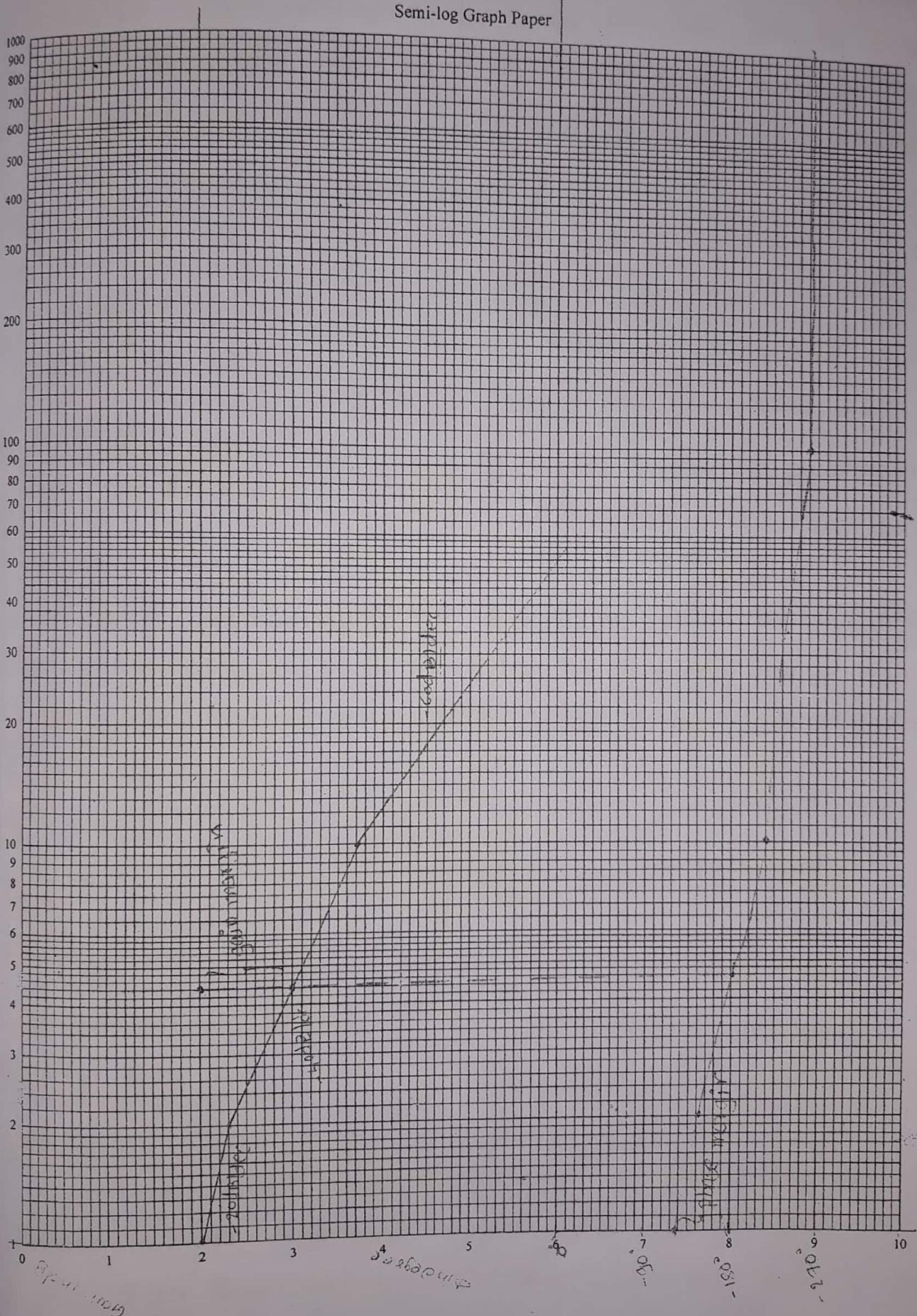

① Low pass filter

These filters reject all frequencies above cut-off frequency. The attenuation characteristics of an ideal low pass filter is shown in figure below. Thus, the pass band or transmission band for the LP filter is the frequency range 0 to f_c and the stop band or attenuation band is the frequency range above f_c .

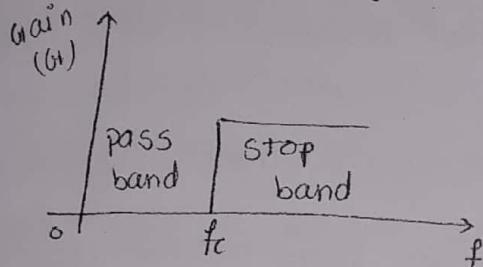


fig: Ideal characteristic of low pass filter.

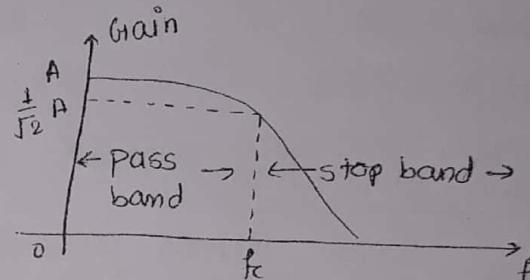


fig: characteristic of practical low pass filter.

② High pass filter

These filters reject all frequencies below cut-off frequency f_c . Thus, the pass band for HP filter is frequency range above f_c and the stop band or attenuation band is the frequency range below f_c .

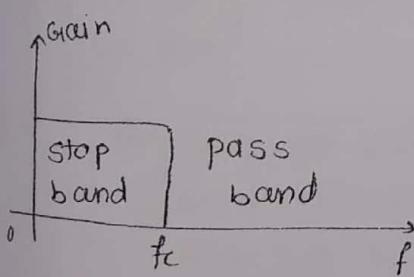


fig: Ideal characteristic of High pass filter

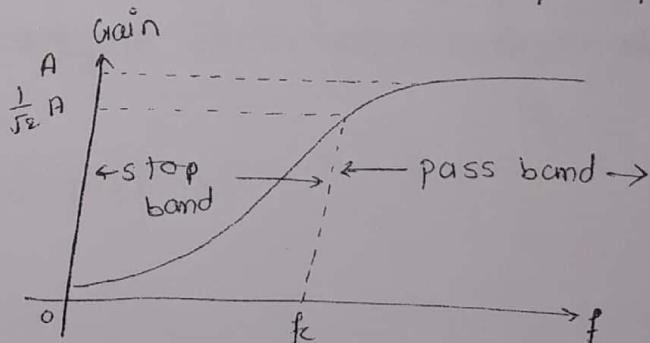


fig: characteristic of High pass filter.

③ Band pass filter

These filters allow transmission of frequencies between two designated cut off frequencies and reject all other frequencies. Band pass filter has two cut-off frequencies and will have the pass band $f_{c2} - f_{c1}$. f_{c1} is called lower cut-off frequency while f_{c2} is higher cut-off frequency.

The range between higher/upper and lower cut-off frequency is called width.

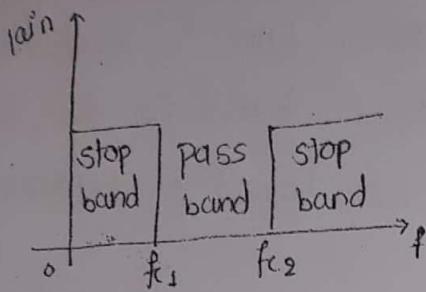


fig: Ideal response of Band pass filter.


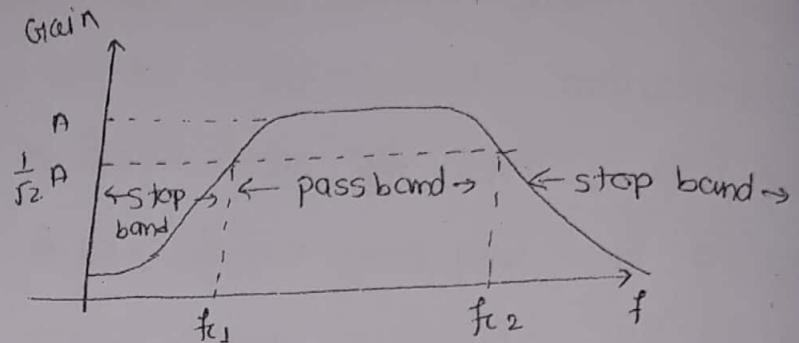
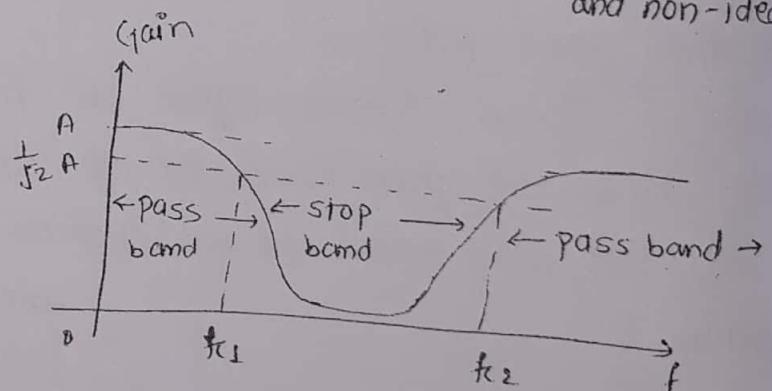


fig: non-ideal response of band pass filter.

④ Band-stop filter

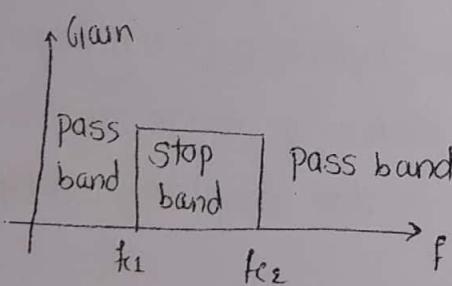These filters pass all frequencies lying outside a certain range, while it attenuates all frequencies between the two frequencies f_{c1} and f_{c2} . The characteristic of an ideal, band stop filter is shown in below



OTEI * Roots of $p(s)$ are not permitted at the origin except in case of odd function (polynomial) since one root of odd part $N(s)$ of polynomial is always present at the origin.

Hurwitz polynomial

A polynomial $P(s)$ is said to be Hurwitz polynomial if the following conditions are satisfied:

- $P(s)$ is real when s is real
- The roots of $p(s)$ have real parts which are zero or negative.

If the polynomial $P(s)$ can be written as

$$P(s) = a_n s^n + a_{n-1} s^{n-1} + \dots + a_1 s + a_0$$

then, All the coefficients a_i must be positive and none of the coefficients may be zero. except odd and even polynomial.

The continued fraction expansion of the ratio of the odd to even parts $[M(s)/N(s)]$ or the even to odd parts $[M(s)/N(s)]$ of a Hurwitz polynomial yields positive quotient terms. In case of odd or even polynomial, ratio of $p(s)$ and s is taken.

Check whether the given polynomial $P(s) = s^4 + s^3 + 5s^2 + 3s + 4$ is Hurwitz or not.

$$\text{Here, } P(s) = s^4 + s^3 + 5s^2 + 3s + 4$$

Condition 1: Since all coefficients of $P(s)$ are positive and none of the coefficients are zero.

Condition 2: The even and odd parts of $P(s)$ are

$$M(s) = s^4 + 5s^2 + 4$$

$$N(s) = s^3 + 3s$$

Continued fraction expansion of $\Psi(s) = \frac{M(s)}{N(s)}$ is given by

$$\begin{aligned} & s^3 + 3s \overline{s^4 + 5s^2 + 4} (s \\ & \quad - s^4 - 3s^2) \\ & \quad \overline{2s^2 + 4} s^3 + 3s \left(\frac{1}{2}s \right) \\ & \quad - s^3 - 2s \\ & \quad \overline{s} 2s^2 + 4 (2s) \\ & \quad - 2s^2 \\ & \quad \overline{4} s \left(\frac{1}{4}s \right) \\ & \quad - s \end{aligned}$$

So that, the continued fraction expansion of $\Psi(s)$ is

$$\begin{aligned}\Psi(s) &= \frac{M(s)}{N(s)} \\ &= s + \frac{1}{\frac{s}{2} + \frac{1}{2s + \frac{1}{\frac{s}{4}}}}\end{aligned}$$

Since, all the quotient terms of the continued fraction expansion are positive, $p(s)$ is Hurwitz.

2. Check whether the given polynomial $p(s) = s^4 + s^3 + 2s^2 + 4s + 1$ is Hurwitz or not.

Solution: Here, $p(s) = s^4 + s^3 + 2s^2 + 4s + 1$

Condition 1: Since, all the coefficients of $p(s)$ are positive and none of the coefficient are zero.

Condition 2: Even and odd parts of $p(s)$ are

$$M(s) = s^4 + 2s^2 + 1$$

$$N(s) = s^3 + 4s$$

So, continued fraction expansion of $\Psi(s) = \frac{M(s)}{N(s)}$ is given as,

$$\begin{aligned}s^3 + 4s \Big) s^4 + 2s^2 + 1 \left(s \right. \\ \frac{s^4 + 4s^2}{-2s^2 + 1} \Big) s^3 + 4s \left(-\frac{1}{2}s \right. \\ \frac{s^3 - \frac{s}{2}}{-\frac{s}{2}} \Big) -2s^2 + 1 \left(-\frac{4}{9}s \right. \\ \frac{+2s^2}{-\frac{9}{2}s} \Big) \frac{9}{2}s \left(\frac{9}{2}s \right. \\ \frac{\frac{9}{2}s}{x} \Big)\end{aligned}$$

Since, all the quotient terms of the continued fraction expansion are not positive, $p(s)$ is not Hurwitz.

Positive Real Function

A Function (polynomial) is said to be positive real function if it satisfies the following conditions:

Condition 1: The polynomial should be Hurwitz polynomial i.e. function must have no poles on right half of s-plane. This condition can be checked through a continued fraction expansion of the odd to even parts or even to odd parts of $T(s)$ in which quotients must be positive.

Condition 2: If poles of given function are on jw axis, then residue of poles on jw axis should be positive.

(This condition is tested by making partial fraction expansion of given polynomial.)

Condition 3: $\operatorname{Re}[T(j\omega)] \geq 0$ for all ω

$$\text{Let, } T(s) = \frac{N(s)}{D(s)} = \frac{M_1(s) + N_1(s)}{M_2(s) + N_2(s)}$$

Where, $M_i(s)$ are even polynomial and $N_i(s)$ are odd polynomials.

Finalizing:

$$T(s) = \frac{M_1(s) + N_1(s)}{M_2(s) + N_2(s)} \times \frac{M_2(s) - N_2(s)}{M_2(s) - N_2(s)} = \frac{M_1 M_2 - M_1 N_2 + N_1 M_2 - N_1 N_2}{M_2^2 - N_2^2}$$
$$= \frac{M_1 M_2 - N_1 N_2}{M_2^2 - N_2^2} + \frac{N_1 M_2 - M_1 N_2}{M_2^2 - N_2^2}$$

Here, $M_1 M_2$ and $N_1 N_2$ are even function while $N_1 M_2$ and $M_1 N_2$ are functions. So, even part of $T(s) = \frac{M_1 M_2 - N_1 N_2}{M_2^2 - N_2^2}$ and odd part of $s = \frac{N_1 M_2 - M_1 N_2}{M_2^2 - N_2^2}$

So, if we let, $s = j\omega$, we see that even parts of the polynomial is while the odd part of the polynomial is imaginary.

$$\text{i.e. } \operatorname{Re}[T(j\omega)] = \text{Even}[T(s)]_{s=j\omega}$$

$$\operatorname{Im}[T(j\omega)] = \text{odd}[T(s)]_{s=j\omega}$$

So, to test the condition $\operatorname{Re}[T(j\omega)] \geq 0$, we determine the part of $T(s)$ by finding even part of $T(s)$ and put $s = j\omega$

then we check whether $\operatorname{Re}[T(jw)] \geq 0$ for all w or not.

$$\therefore A(w^2) = M_1(jw) \cdot M_2(jw) - N_1(jw) \cdot N_2(jw) \geq 0 \text{ for all } w \text{ or not.}$$

Properties of PRF:

If $F(s)$ is PRF then $\frac{1}{F(s)}$ is also PRF.

The sum of two PRF is also PRF but difference may not be

The poles/zeros of PRF can not have positive real parts.

The poles/zeros of PRF occurs either in real or in complex conjugate.

Highest power of numerator and denominator may differ at most by unity.

lowest power of denominator and numerator polynomial may differ at most by unity.

3.1 Test whether the following function is PRF or not

$$Z(s) = \frac{s^2 + 5}{s(s^2 + 1)}$$

Soln: For given function, $D(s) = s^3 + s$

Condition 1: Then, odd polynomial $= s^3 + s$ so,

$$D'(s) = 3s^2 + 1$$

Then, continue fraction is,

$$\begin{array}{r} 3s^2 + 1 \Big) s^3 + s \left(\frac{1}{3}s \right. \\ \underline{-} s^3 + \frac{1}{3}s \\ \hline \frac{2s}{3} \Big) 3s^2 + 1 \left(\frac{9}{2}s \right. \\ \underline{-} 3s^2 \\ \hline 1 \Big) \frac{2s}{3} \left(\frac{2s}{3} \right. \\ \underline{-} \frac{2s}{3} \\ \hline x \end{array}$$

Since, all the quotients are positive,

$D(s)$ is Hurwitz polynomial.

Condition 2

$Z(s)$ has poles at $s = 0$ and $s = \pm j$

Now, to find residues taking partial fraction we get

$$\frac{ds^2 + 5}{s(s+1)} = \frac{ds^2 + 5}{s(s-j)(s+j)} = \frac{A}{s} + \frac{B}{s+j} + \frac{C}{s-j}$$

$$A = \left. \frac{ds^2 + 5}{s(s-j)(s+j)} \right|_{s=0} = \frac{5}{-j^2} = 5$$

$$B = \left. \frac{ds^2 + 5}{s(s-j)(s+j)} \right|_{s=-j} = \frac{3}{2} = -\frac{3}{2}$$

$$C = \left. \frac{ds^2 + 5}{s(s-j)(s+j)} \right|_{s=j} = -\frac{3}{2}$$

since, residues at poles on imaginary axis i.e. $s = \pm j$ are negative. So, condition 2 is not satisfied.

$\therefore Z(s)$ is not positive real function (PRF)

Example 2 $Z(s) = \frac{s^2 + 2s + 6}{s(s+3)}$ (~~incorrect~~)

$$Z(s) = \frac{s^2 + 2s + 6}{s(s^2 + 3)}$$

For given function, $D(s) = s^3 + 3s$

Then, even polynomial $= s^2$

odd polynomial $= 3s$

Then, continued fraction is, $3s \left(\frac{s^2 + \frac{1}{3}s}{s^2} \right)$

$$D(s) = s^3 + 3s$$

$$D'(s) = 3s^2 + 3$$

Condition 1 $3s^2 + 3 \overline{s^3 + 3s} \left(\frac{1}{3}s \right)$

$$\frac{s^3 + s}{2s} \overline{3s^2 + 3} \left(\frac{2}{3}s \right)$$

Since, the quotients is positive. $D(s)$ is Hurwitz polynomial.

Condition 2

$Z(s)$ has poles at $s=0$ and $s=-3$

$s=0$ lies on imaginary axis.

For residue test, taking partial fraction

$$\text{Here, } \frac{s^2 + 2s + 6}{s^2 + 3s} \text{ so, } \frac{s^2 + 2s + 6}{s^2 + 3s} \left(\frac{1}{s^2 + 3s} \right)$$

$$\frac{s^2 + 2s + 6}{s(s+3)} = 1 + \frac{6-s}{s(s+3)}$$

$$\text{Now, } \frac{6-s}{s(s+3)} = \frac{A}{s} + \frac{B}{s+3}$$

since, the quotients are positive. $D(s)$ is Hurwitz polynomial.

Condition 2
 $Z(s)$ has poles at

$s=0, s = \pm j\sqrt{3}$

for residue test

$$\frac{s^2 + 2s + 6}{s(s^2 + 3)} = \frac{A}{s} + \frac{B}{s-j\sqrt{3}} + \frac{C}{s+j\sqrt{3}}$$

$$A = \left. \frac{s^2 + 2s + 6 \times s}{s^3 + 3s} \right|_{s=0} \Rightarrow 2 = -ve$$

$$B = \left. \frac{s^2 + 2s + 6 \times (s-j\sqrt{3})}{s(s^2 + 3)} \right|_{s=j\sqrt{3}} \Rightarrow 3 + 2j\sqrt{3} = -ve$$

$$\text{Expt, } A = \left. \frac{6-s}{s(s+3)} \times s \right|_{s=0} = 2$$

$$B = \left. \frac{6-s}{s(s+3)} \times (s+3) \right|_{s=-3} = -3$$

Since, the residue of pole at $s=0$ is positive. So, condition 2 is satisfied.

Condition 3:

$$A(\omega^2) = M_1(j\omega) \cdot M_2(j\omega) - N_1(j\omega) \cdot N_2(j\omega) \geq 0$$

For given polynomial,

$$M_1(s) = s^2 + 6 \quad N_1(s) = 2s$$

$$M_2(s) = s^2 \quad N_2(s) = 3s$$

$$\text{Now, } M_1(s) \cdot M_2(s) - N_1(s) \cdot N_2(s)$$

$$(s^2 + 6)s^2 - 2s \cdot 3s$$

$$= s^4 + 6s^2 - 6s^2 = s^4$$

∴ in $j\omega$,

$$M_1(j\omega) \cdot M_2(j\omega) - N_1(j\omega) \cdot N_2(j\omega) = (j\omega)^4 = \omega^4$$

which is positive for all values of ω . So, condition 3 is verified.

Thus, the $z(s)$ is positive real function (PRF).

Example 3

$$z(s) = \frac{(s+2)(s+4)}{(s+1)(s+3)}$$

$$\text{Here, } z(s) = \frac{(s+2)(s+4)}{(s+1)(s+3)} = \frac{s^2 + 6s + 8}{s^2 + 4s + 3}$$

Condition 1:

Since, the poles for above function are at $s = -1, s = -3$. So, the above function satisfies condition 1 i.e. all poles are at left half side of s -plane.

Condition 2:

No roots on $j\omega$ axis. So, condition 2 is not exist.

Condition 3:

$$A(\omega^2) = M_1(j\omega) \cdot M_2(j\omega) - N_1(j\omega) \cdot N_2(j\omega) \geq 0$$

$$\begin{aligned} M_1(s) &= s^2 + 6 \\ M_2(s) &= 0 \\ N_1(s) &= 2s \\ N_2(s) &= s^2 + 3s \\ A(s) &= 0 - 2s(2s + 3s) \\ &= -4s^4 + 6s^2 \\ A(\omega^2) &= -4(j\omega)^4 + 6(j\omega)^2 \\ &= -4\omega^4 + 6\omega^2 \\ A(\omega^2) &\geq 0 \text{ for all } \omega \\ z(s) &\text{ is not PRF} \end{aligned}$$

given polynomial,

$$N_1(s) = s^2 + 8 \quad N_1(s) = 6s$$

$$N_2(s) = s^2 + 3 \quad N_2(s) = 4s$$

$$H(s^2) = \{(j\omega)^2 + 8\} \{(\omega)^2 + 3\} - (6j\omega)(4j\omega)$$

$$= (8 - \omega^2)(3 - \omega^2) + 24\omega^2$$

$$= 24 - 8\omega^2 - 3\omega^2 + \omega^4 + 24\omega^2$$

$$= \omega^4 + 13\omega^2 + 24, \text{ This is positive for all value of } \omega.$$

condition 3 is satisfied.

Hence, the $Z(s)$ is positive Real function (PRF)

$$Z(s) = \frac{s^3 + 5s^2 + 9s + 3}{s^3 + 4s^2 + 7s + 9}$$

Condition 1

$$\text{Here, } D(s) = s^3 + 4s^2 + 7s + 9$$

$$\text{odd polynomial} = s^3 + 7s$$

$$\text{even polynomial} = 4s^2 + 9$$

Then, continued fraction is,

$$\begin{aligned} & 4s^2 + 9 \overline{)s^3 + 7s} \left(\frac{1}{4}s \right. \\ & \quad \overline{- s^3 + \frac{9}{4}s} \\ & \quad \overline{\frac{19}{4}s} \Big) 4s^2 + 9 \left(\frac{16}{19}s \right. \\ & \quad \overline{- 4s^2} \\ & \quad \overline{9} \Big) \frac{19}{4}s \left(\frac{19}{36}s \right. \\ & \quad \overline{- \frac{19}{4}s} \\ & \quad \overline{x} \end{aligned}$$

Since, all the quotients are

+ve. $D(s)$ is Hurwitz polynomial.

so, condition 1 is satisfied.

Condition 2 By using calculator, poles are at $s = -2.64, -0.68 \pm j1.71$

∴ None of the poles lies on imaginary axis. so, condition 2 does not exist.

Condition 3:

$$A(\omega^2) = M_1(j\omega) \cdot M_2(j\omega) - N_1(j\omega) N_2(j\omega) \geq 0$$

$$M_1(s) = 5s^2 + 3 \quad N_1(s) = s^3 + 9s$$

$$M_2(s) = 4s^2 + 9 \quad N_2(s) = s^3 + 7s$$

NOW, $M_1(s)N_2(s) - N_1(s)N_2(s)$

$$(5s^2 + 3)(4s^2 + 9) - (s^3 + 9s)(s^3 + 7s)$$

$$= 20s^4 + 45s^2 + 12s^2 + 27 - s^6 - 7s^4 - 9s^4 - 63s^2$$

$$= -s^6 + 4s^4 - 6s^2 + 27$$

NOW,

$$A(\omega^2) = M_1(j\omega)M_2(j\omega) - N_1(j\omega)N_2(j\omega)$$

$$= -(\omega)^6 + 4(\omega)^4 - 6(\omega)^2 + 27$$

$$= \omega^6 + 4\omega^4 + 6\omega^2 + 27. \text{ This is positive for all values of } \omega.$$

so, condition 3 is satisfied.

Hence, $Z(s)$ is PRF.

Synthesis of one port network

Methods of synthesising network are:

① Foster I

- Series combination of parallel components.
- use of partial fraction expansion for $Z(s)$

② Foster II

- Parallel combination of series components
- use of partial fraction expansion for $Y(s)$

③ Cauer I

- Continued fraction expansion of $Z(s)$ by arranging numerator and denominator in descending order

④ Cauer II


- Continued fraction expansion of $Z(s)$ by arranging numerator and denominator in ascending order.

R-C circuit

R-C series

$$Z(s) = LS + \frac{1}{Cs}$$
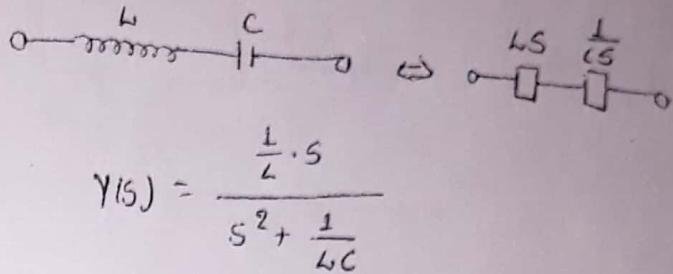
$$= \frac{Ls^2 + 1}{sC} = \frac{s^2 + \frac{1}{LC}}{\frac{1}{L} \cdot s}$$



R-C parallel

$$Z(s) = LS \parallel \frac{1}{Cs}$$

$$= \frac{LS \times \frac{1}{Cs}}{LS + \frac{1}{Cs}} = \frac{\frac{L}{C} \times Cs}{LCS^2 + 1} = \frac{LS}{LCS^2 + 1} = \frac{\frac{1}{C}s}{s^2 + \frac{1}{LC}}$$

$$V(s) = \frac{s^2 + \frac{1}{LC}}{\frac{1}{C}s}$$

R-L circuit

R-L series

$$Z(s) = R + LS = L \left[s + \frac{R}{L} \right]$$



$$V(s) = \frac{\frac{1}{L}}{s + \frac{R}{L}}$$

R-L parallel

$$Z(s) = R \parallel LS = \frac{RLS}{R+LS}$$

$$= \frac{RS}{s + \frac{R}{L}}$$

$$(s) = \frac{s + \frac{R}{L}}{RS}$$

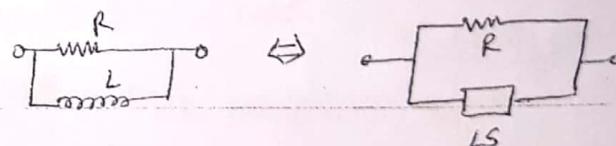
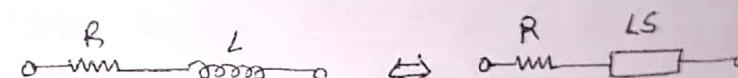


R-C circuit

R-C series

$$Z(s) = R + \frac{1}{Cs} = \frac{RCS + 1}{Cs} = \frac{s + \frac{1}{RC}}{\frac{1}{R}s}$$
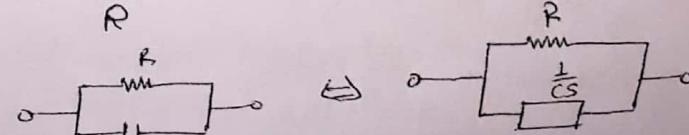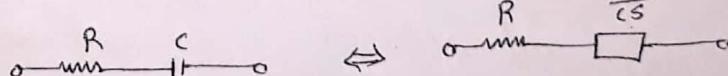
$$V(s) = \frac{\frac{1}{R}s}{s + \frac{1}{RC}}$$




R-C parallel

$$Z(s) = R \parallel \frac{1}{Cs} = \frac{R \times \frac{1}{Cs}}{R + \frac{1}{Cs}} = \frac{R}{RCS + 1} = \frac{\frac{1}{C}}{s + \frac{1}{RC}}$$


Foster I:

General form:

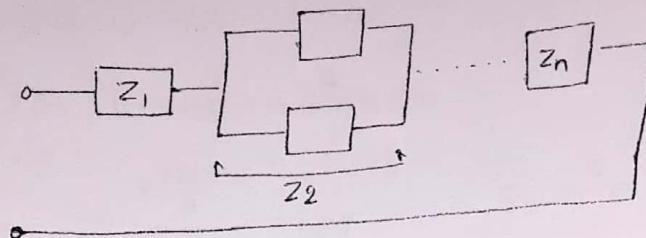

Foster II:

General form:

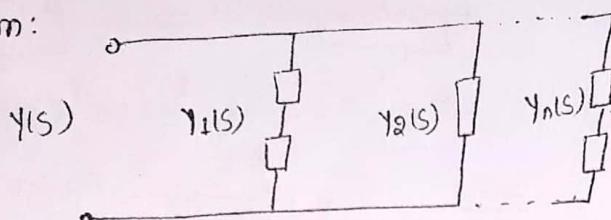

sample

The driving point impedance of one port L-C network is given

$$z(s) = \frac{4(s^2+4)(s^2+25)}{s(s^2+16)}$$

obtain Foster I and Foster II form of equivalent networks.

? We have,

$$z(s) = \frac{4(s^2+4)(s^2+25)}{s(s^2+16)}$$

For Foster I:

Since, order of numerator polynomial is greater than denominator polynomial so we need to divide before partial fraction.

$$\begin{array}{r} s^3 + 16s \\ \overline{s^3 + 16s} \end{array} \left| \begin{array}{r} 4s^4 + 116s^2 + 400 \\ - 4s^4 - 64s^2 \\ \hline 52s^2 + 400 \end{array} \right. (4s)$$

$$\text{i.e. } z(s) = \frac{4(s^2+4)(s^2+25)}{s(s^2+16)} = 4s + \frac{52s^2+400}{s(s^2+16)}$$

Now, using partial fraction,

$$z(s) = 4s + \frac{52s^2+400}{s(s^2+16)} = 4s + \frac{A}{s} + \frac{Bs+C}{s^2+16}$$

$$\text{Now, } \frac{52s^2+400}{s(s^2+16)} = \frac{A}{s} + \frac{Bs+C}{s^2+16}$$

$$s^2 + 400 = As^2 + 16A + Bs^2 + Cs$$

$$s^2 + 400 = (A+B)s^2 + Cs + 16A$$

$$A=400 \Rightarrow A=25$$

$$\therefore 0 \Rightarrow C=0$$

$$B=52 \Rightarrow B=27$$

$$Z(s) = 45 + \frac{25}{s} + \frac{27s}{s^2 + 16} = 45 + \frac{\frac{1}{25}s}{s^2 + \frac{1}{25}} + \frac{\frac{1}{27}s}{s^2 + \frac{27}{16}}$$

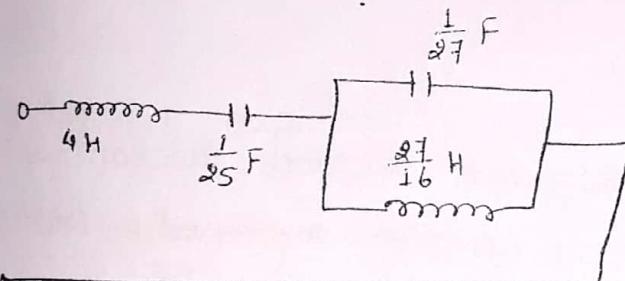


Fig: Foster I

Foster II :

$$V(s) = \frac{1}{Z(s)} = \frac{s(s^2 + 16)}{4(s^2 + 4)(s^2 + 25)}$$

Using partial fraction

$$\frac{1}{4} \frac{s^3 + 16s}{(s^2 + 4)(s^2 + 25)} = \frac{1}{4} \left[\frac{As + B}{s^2 + 4} + \frac{Cs + D}{s^2 + 25} \right]$$

$$\frac{s^3 + 16s}{(s^2 + 4)(s^2 + 25)} = \frac{(As + B)(s^2 + 25) + (Cs + D)(s^2 + 4)}{(s^2 + 4)(s^2 + 25)}$$

$$s^3 + 16s = As^3 + 25As + Bs^2 + 25Bs + Cs^3 + 4Cs + Ds^2 + 4D$$

$$s^3 + 16s = (A+C)s^3 + (B+D)s^2 + (25A+4C)s + 25B+4D$$

Equating coefficient

$$+C=1 \quad \dots \dots \textcircled{1}$$

$$+D=0 \Rightarrow B=-D \quad \dots \dots \textcircled{2}$$

$$A+4C=16 \Rightarrow 25A+4(1-A)=16 \Rightarrow 25A+4-4A=16 \Rightarrow 21A=12$$

$$\therefore 1-A = 1 - \frac{12}{21} = \frac{9}{21}$$

$$A = \frac{12}{21}$$


$$B+4D=0 \quad \dots \dots \textcircled{3}$$

from $\textcircled{2}$ and $\textcircled{3}$, we have
 $B=0, D=0$

Thus,

$$Y(s) = \frac{s(s^2 + 16)}{4(s^2 + 4)(s^2 + 25)} = \frac{\frac{1}{4} s}{s^2 + 4} + \frac{\frac{9}{4} s}{s^2 + 25}$$
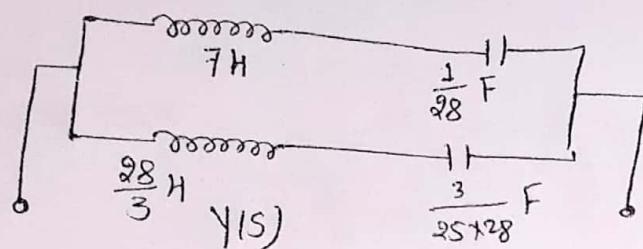
$$= \frac{\frac{1}{7} s}{s^2 + 4} + \frac{\frac{3}{28} s}{s^2 + 25}$$




$$Y_1(s) = \frac{\frac{1}{7} s}{s^2 + 4} \text{ with } \frac{\frac{1}{L} \cdot s}{s^2 + \frac{1}{LC}}$$

$$Y_2(s) = \frac{\frac{3}{28} s}{s^2 + 25} \text{ with } \frac{\frac{1}{E} \cdot s}{s^2 + \frac{1}{LC}}$$

Cauer Method

Cauer method is based on fact that reactance function may be represented by two different network configuration expressed by continued fraction expansion.
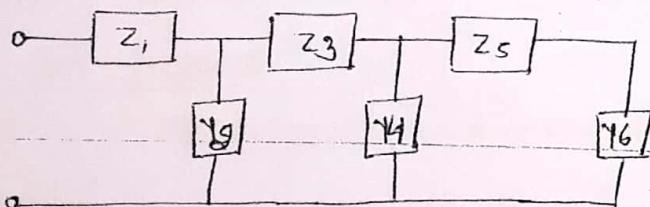
$$\text{Cauer I : } Z_1(s) + \frac{1}{Y_2(s) + \frac{1}{Z_3(s) + \frac{1}{Y_4(s) + \frac{1}{Z_5(s) + \dots}}}}$$



- ① If number of $Z(s)$ is of higher order than denominator divide as usual.
- ② If number of $Z(s)$ is equal order than denominator divide as usual.
- ③ If number of $Z(s)$ is lower order than denominator take inverse and divide.

Example 1

Find Cauer I form of


$$Z(s) = \frac{12s^4 + 10s^2 + 1}{4s^3 + 2s}$$

Soln: Using continued fraction:

$$\begin{aligned} & \frac{12s^4 + 10s^2 + 1}{12s^4 + 6s^2} \left(3s = Z_1(s) \right); L = 3H \\ & \frac{4s^2 + 1}{4s^2 + s} \left(4s^3 + 2s \left(s = Y_2(s) \right); C = 1F \right) \end{aligned}$$

$$\begin{aligned} & \frac{s}{4s^2 + 1} \left(4s = Z_3(s) \right); L = 4H \\ & \frac{1}{s} \left(s = Y_4(s) \right); C = 1F \end{aligned}$$

Circuit expression is,

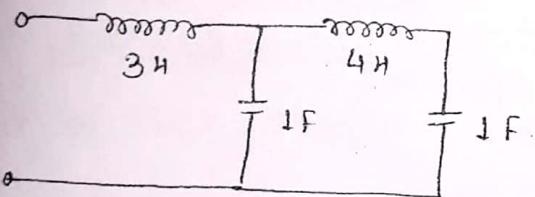

Ex 2

Synthesise the given RC impedance using coupler method.

$$Z(s) = \frac{s^2 + 4s + 3}{s^2 + 2s}$$

Given, $Z(s) = \frac{s^2 + 4s + 3}{s^2 + 2s}$

Now, using coupler method:

$$\begin{aligned} & s^2 + 2s \left(\frac{s^2 + 4s + 3}{s^2 + 2s} \right) \left(1 \Rightarrow Z_1(s) \right) \Rightarrow R = 1\Omega \\ & \frac{s^2 + 2s}{s^2 + 2s} \left(2s + 3 \right) \left(\frac{1}{2}s \Rightarrow Y_2(s) \right) \Rightarrow C = \frac{1}{2}F \\ & \frac{-s^2 - \frac{3}{2}s}{-2s} \left(2s \right) \left(4 \Rightarrow Z_3(s) \right) \Rightarrow R = 4\Omega \\ & \frac{-2s}{\frac{3}{2}s} \left(\frac{1}{6}s \Rightarrow Y_4(s) \right) \Rightarrow C = \frac{1}{6}F \end{aligned}$$

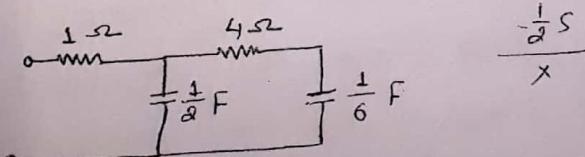


Fig: coupler circuit

Cauer II

We take the given polynomial in reverse order and take continued fraction i.e. $Z(s) = \frac{3+4s+s^2}{2s+s^2}$

NOW, taking long division method

$$2s+s^2 \overline{) 3+4s+s^2} \left(\frac{3}{2s} \Rightarrow Z_1(s) \Rightarrow C_1 = \frac{2}{3} F$$

$$\frac{3 + \frac{3}{2}s}{2s+s^2} \overline{) 2s+s^2} \left(\frac{4}{5} \Rightarrow Y_2(s) \Rightarrow R_1 = \frac{5}{4} \Omega$$

$$\frac{2s + \frac{9}{2}s^2}{\frac{s^2}{5}} \overline{) \frac{5}{2}s+s^2} \left(\frac{25}{2s} \Rightarrow Z_3(s) \Rightarrow C_2 = \frac{2}{25} F,$$

$$\frac{-\frac{s}{2}}{s^2} \overline{) \frac{s^2}{5}} \left(\frac{1}{5} \Rightarrow Y_2(s) \Rightarrow R_2 = 5 \Omega$$

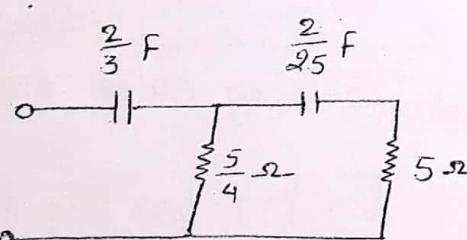


Fig. Cauer II circuit representation.

DEFINITION

MOST often we have seen that the networks with terminals are connected in pairs to other networks. If the current entering one terminal of a pair is equal and opposite to the current leaving the other terminal of the pair, then this type of terminal pair is known as a "port."

and v_1 : Current and voltage at port 1

and v_2 : Current and voltage at port 2

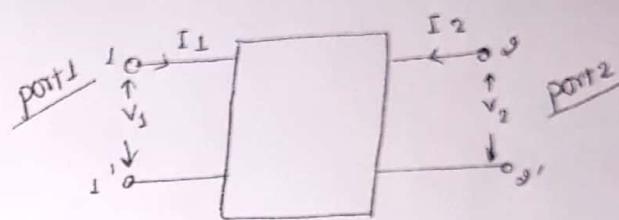


Fig: Two port nw

Out of four variable two are independent variables and remaining two depends on two independent variables and network parameters of that network.

Example

$$\begin{aligned} v_1 &= Z_{11}I_1 + Z_{12}I_2 \\ v_2 &= Z_{21}I_1 + Z_{22}I_2 \end{aligned} \quad \left. \begin{array}{l} \\ \end{array} \right\} z\text{-parameter equation}$$

Here,

I_1 and I_2 are independent parameters variables

v_1 and v_2 are dependent variables

Z_{11}, Z_{12}, Z_{21} and Z_{22} are network parameters (z-parameters)

Two port Network parameters:

There are six combination of network parameters as listed below:

z-parameter $\Rightarrow Z_{11}, Z_{12}, Z_{21}, Z_{22} \Rightarrow$ Open circuit impedance parameter

y-parameter $\Rightarrow Y_{11}, Y_{12}, Y_{21}, Y_{22} \Rightarrow$ short circuit impedance parameter

t-parameter $\Rightarrow T_{11}, T_{12}, T_{21}, T_{22} \Rightarrow$ transmission parameter

$A'B'C'D'$ parameter $\Rightarrow A', B', C', D' \Rightarrow$ inverse transmission parameter

h-parameter $\Rightarrow H_{11}, H_{12}, H_{21}, H_{22} \Rightarrow$ hybrid parameter


f-parameter $\Rightarrow F_{11}, F_{12}, F_{21}, F_{22} \Rightarrow$ inverse-hybrid parameter

Relationship of Two port variables:


Name	Function Express in terms of	Matrix equation
open-circuit impedance [Z]	V_1, V_2 I_1, I_2	$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$
short-circuit admittance [Y]	I_1, I_2 V_1, V_2	$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$
Transmission or chain [T]	V_1, I_1 $V_2, -I_2$	$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$
Inverse transmission [T]	V_2, I_2 $V_1, -I_1$	$\begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix} \begin{bmatrix} V_1 \\ -I_1 \end{bmatrix}$
Hybrid (h)	V_1, I_2 I_1, V_2	$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$
Inverse hybrid	I_1, V_2 V_1, I_2	$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$

Reciprocity and Symmetry:

A two port network is said to be reciprocal, if the ratio of the excitation to response is invariant to an interchange of the position of the excitation and response in the network. Networks containing resistors, inductors and capacitors are generally reciprocal. Networks that additionally have dependent sources are generally non-reciprocal. Mathematically, $\frac{V_S}{I_2'} = \frac{V_S}{I_1}$ or $I_2' = I_1'$

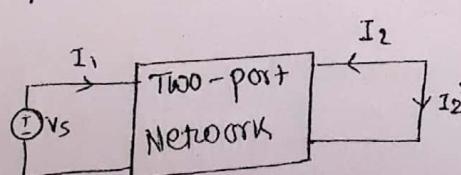

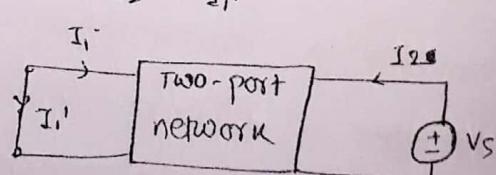
$$[V_1 = V_S, I_1 = I_1, V_2 = 0, I_2 = -I_2']$$



$$[V_2 = V_S, I_2 = I_2, V_1 = 0, I_1 = -I_1']$$

fig: Determination of condition for reciprocity.

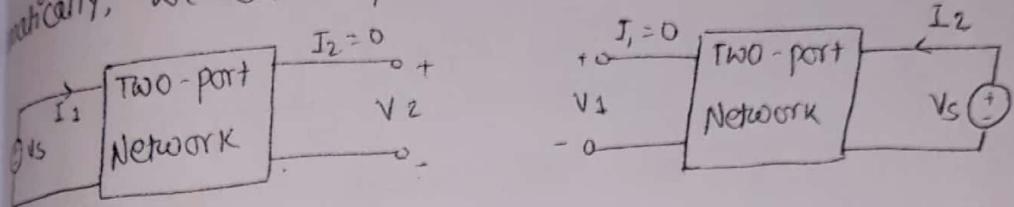A two port network is said to be symmetrical if the ports can be interchanged without changing the port voltage and currents. Mathematically, we can say from figure:




$$(V_1 = V_S, I_1 = I_1, I_2 = 0, V_2 = V_2) \quad (V_2 = V_S, I_2 = I_2, I_1 = 0, V_1 = V_1)$$

fig. Determination the condition for symmetry.


$$\frac{V_S}{I_1} \Big|_{I_2=0} = \frac{V_S}{I_2} \Big|_{I_1=0}$$

Ex 1

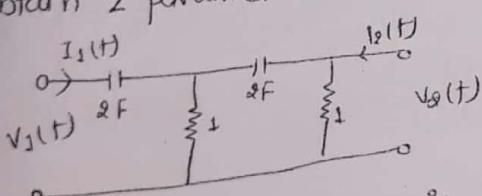Obtain Z parameter of given two port netw.



The transform circuit is,

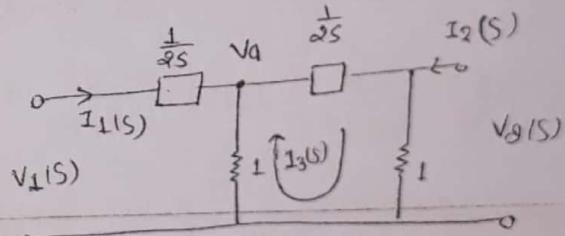

Apply KCL at Va

$$\frac{V1(s) - Va}{1/(2s)} + \frac{Va - V2(s)}{1/(2s)} = I1(s) - I3(s)$$

$$(V2(s) - Va)/2s = Va + (V2(s) - Va)/2s$$

$$V1(s) = \frac{1}{2s} I1(s) + I1(s) - I3(s) \quad \textcircled{A}$$

$$V2(s) = I2(s) + I3(s) \quad \textcircled{B}$$

$$I3(s) - I1(s) + \frac{1}{2s} I3(s) + I3(s) + I2(s) = 0$$

$$I3(s) \left[2 + \frac{1}{2s} \right] = I1(s) - I2(s)$$

$$I3(s) = \frac{I1(s) - I2(s)}{\left(\frac{4s+1}{2s} \right)} = \left(\frac{2s}{4s+1} \right) [I1(s) - I2(s)] \quad \textcircled{C}$$

from ④ and ⑤

$$V_1(S) = \frac{1}{2S} I_1(S) + I_1(S) - \frac{2S}{4S+1} I_1(S) + \frac{2S}{4S+1} I_2(S)$$

$$V_1(S) = I_1(S) \left[\frac{1}{2S} + 1 - \frac{2S}{4S+1} \right] + \frac{2S}{4S+1} I_2(S)$$

$$V_1(S) = I_1(S) \left[\frac{4S+1+8S^2+2S-2S^2}{8S^2+2S} \right] + \frac{2S}{4S+1} I_2(S)$$

Now,

$$Z_{11} = \frac{V_1(S)}{I_1(S)} \Big|_{I_2(S)=0} = \frac{4S^2+6S+1}{2S(4S+1)}$$

$$Z_{12} = \frac{V_1(S)}{I_2(S)} \Big|_{I_1(S)=0} = \frac{2S}{4S+1}$$

from ⑥ and ⑦

$$V_2(S) = I_2(S) + \frac{2S}{4S+1} I_1(S) - \frac{2S}{4S+1} I_2(S)$$

$$V_2(S) = \left(1 - \frac{2S}{4S+1}\right) I_2(S) + \frac{2S}{4S+1} I_1(S)$$

~~$$V_2(S) = \left(\frac{2S+1}{4S+1}\right) I_2(S) + \left(\frac{2S}{4S+1}\right) I_1(S)$$~~

Now,


$$Z_{21} = \frac{V_2(S)}{I_1(S)} \Big|_{I_2(S)=0} = \frac{2S}{4S+1}$$

$$Z_{22} = \frac{V_2(S)}{I_2(S)} \Big|_{I_1(S)=0} = \frac{2S+1}{4S+1}$$

$$\therefore Z_{11} = \frac{4S^2+6S+1}{2S(4S+1)}, \quad Z_{12} = \frac{2S}{4S+1}$$

$$Z_{21} = \frac{2S}{4S+1}, \quad Z_{22} = \frac{2S+1}{4S+1}$$

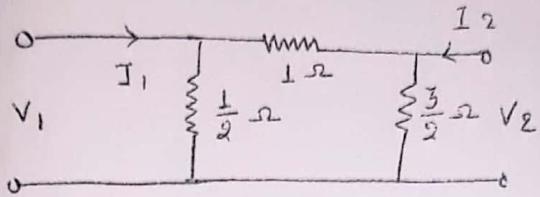(P2) Find ABCD parameter for following resistive net.




The required equation for ABCD parameter are:

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

NOW, transformed circuit is,

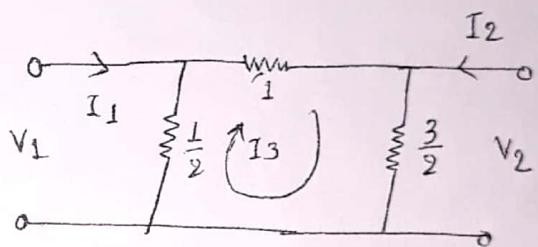

$$= \frac{1}{2} (I_1 - I_3)$$

$$= \frac{1}{2} I_1 - \frac{1}{2} I_3 \quad \dots \dots \textcircled{1}$$

$$= \frac{3}{2} (I_2 + I_3) = \frac{3}{2} I_2 + \frac{3}{2} I_3 \quad \dots \dots \textcircled{2}$$

$$-I_1 \left(\frac{1}{2} + I_3 + \frac{I_2 + I_3}{\frac{3}{2}} \right) = 0$$

$$[3 \left(\frac{1}{2} + I_3 + \frac{I_2}{\frac{3}{2}} \right)] = \frac{1}{2} I_1 - I_2 + \frac{3}{2} I_3 \Rightarrow I_3 \left(\frac{6}{2} \right) = \frac{1}{2} I_1 - \frac{3}{2} I_2$$

$$I_3 = \frac{1}{6} I_1 - \frac{3}{6} I_2 = \frac{1}{6} I_1 - \frac{1}{2} I_2 \quad \dots \textcircled{3}$$

From eqⁿ. ① and ③

$$1 = \frac{1}{2} I_1 - \frac{1}{2} \left(\frac{1}{6} I_1 - \frac{1}{2} I_2 \right)$$

$$1 = \frac{1}{2} I_1 - \frac{1}{12} I_1 + \frac{1}{4} I_2$$

$$1 = \frac{5}{12} I_1 + \frac{1}{4} I_2 \quad \dots \dots \textcircled{4}$$

From eqⁿ. ② and ③

$$1 = \frac{3}{2} I_2 + \frac{3}{2} \left[\frac{1}{6} I_1 - \frac{1}{2} I_2 \right]$$

$$1 = \frac{3}{2} I_2 + \frac{1}{12} I_1 - \frac{3}{4} I_2 = \frac{1}{4} I_2 + \frac{1}{12} I_1 \quad \textcircled{5}$$

Now, from ④ and ⑤

$$\frac{1}{A} = \frac{V_2}{V_1} \Big|_{I_2=0} = \frac{\frac{1}{4} I_1}{\frac{5}{12} I_1}$$

$$A = \frac{5}{12} \times 4 = \frac{5}{3}$$

Now, when, $V_2 = 0$ eq? 5 becomes,

$$I_1 = -3I_2 \quad \dots \quad ⑥$$

from 4,

$$V_1 = \frac{5}{12} \times (-3I_2) + \frac{1}{4} I_2 = -\frac{5}{4} I_2 + \frac{1}{4} I_2 = -I_2$$

$$\therefore -\frac{V_1}{I_2} = B = 1$$

from ⑥

$$\frac{I_1}{I_2} = D = 3$$



~~when~~ when, $I_2 = 0$ from eq? ⑤

$$V_2 = \frac{1}{4} I_1$$

$$\frac{I_1}{V_2} = 4 \doteq C$$

$$\therefore A = \frac{5}{3}, B = 1, C = 4, D = 3$$

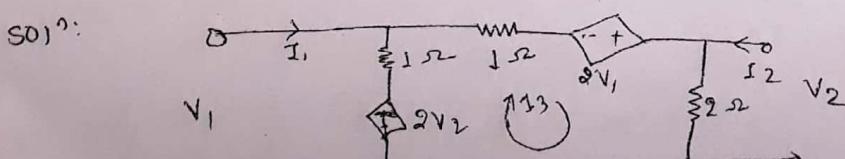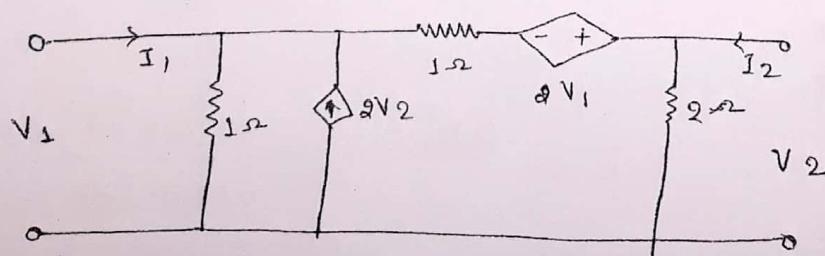Example 3 Find Y parameter for the following resistance n/w.



tion of γ parameter are:

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \quad \text{i.e.} \quad \begin{aligned} I_1 &= Y_{11}V_1 + Y_{12}V_2 \\ I_2 &= Y_{21}V_1 + Y_{22}V_2 \end{aligned}$$

circuit.

$$V_1 = I_1 - I_3 + 2V_2$$

$$I_3 = I_1 + 2V_2 - V_1 \quad \dots \quad (1)$$

$$I_3 - 2V_1 + 2(I_3 + I_2) - 2V_2 + I_3 - I_1 = 0$$

$$4I_3 - 2V_1 - 2V_2 + 2I_2 = -I_1 = 0$$

$$2V_1 + 2V_2 = -I_1 + 2I_2 + 4I_3 \quad \dots \quad (2)$$

$$V_2 = 2(I_2 + I_3) \quad \dots \quad (3)$$

ing value of I_3 from (1) into (2) and (3) we have,

$$2V_1 + 2V_2 = -I_1 + 2I_2 + 4(I_1 + 2V_2 - V_1)$$

$$2V_1 + 2V_2 = -I_1 + 2I_2 + 4I_1 + 8V_2 - 4V_1$$

$$6V_1 - 6V_2 = 3I_1 + 2I_2 \quad \dots \quad (4)$$

$$V_2 = 2I_2 + 2(I_1 + 2V_2 - V_1)$$

$$V_2 = 2I_2 + 2I_1 + 4V_2 - 2V_1$$

$$2V_1 - 3V_2 = 2I_2 + 2I_1 \quad \dots \quad (5)$$

Subtracting (4) from (5), we have

$$-I_1 = -4V_1 + 3V_2$$

$$I_1 = 4V_1 - 3V_2 \quad \dots \quad (6)$$

W, eq (5) becomes

$$2V_1 - 3V_2 = 2I_2 + 8V_1 - 6V_2$$

$$\begin{aligned} I_2 &= \frac{3V_2 - 6V_1}{2} \\ &= -3V_1 + \frac{3}{2}V_2 \end{aligned} \quad \dots \quad (7)$$

From eq (6) and (7), required γ -parameter are

$$\gamma = \begin{bmatrix} 4 & -3 \\ -3 & \frac{3}{2} \end{bmatrix}$$

Relationship among parameters:

If we want to express α -parameter in terms of β -parameter, we have to write β -parameter equation then by algebraic manipulation we transform it to the form of α -parameter.

Example

Z-parameter in terms of T-parameter

Equations of T-parameters are:

$$V_1 = AV_2 - BI_2 \quad \dots \dots \dots \quad (1)$$

$$I_1 = CV_2 - DI_2 \quad \dots \dots \dots \quad (2)$$

$$\text{From equation, (2)} \quad CV_2 = I_1 + DI_2$$

$$V_2 = \frac{1}{C} I_1 + \frac{D}{C} I_2 \quad \dots \dots \dots \quad (3)$$

Comparing it with,

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$\text{We have, } Z_{21} = \frac{1}{C}, \quad Z_{22} = \frac{D}{C}$$

From equation (1) and (3)

$$V_1 = \frac{A}{C} I_1 + \frac{AD}{C} I_2 - BI_2 = \frac{A}{C} I_1 + \frac{AD-BC}{C} I_2$$

$$\text{Comparing it with, } V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$\therefore Z_{11} = \frac{A}{C}, \quad Z_{12} = \frac{AD-BC}{C}$$

Y-parameters in terms of Z

$$[V] = [Z][I]$$

$$\text{For, } \frac{[I]}{[V]} = [Z]^{-1} [V]$$

$$[Y] = [Z]^{-1}$$

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}^{-1} = \frac{1}{DZ} \begin{bmatrix} Z_{22} & -Z_{12} \\ -Z_{21} & Z_{11} \end{bmatrix}$$


Table for relationship among parameter

Z	Y	T
$Z_{11} \quad Z_{12}$	$\frac{Y_{22}}{\Delta Y} \quad -\frac{Y_{12}}{\Delta Y}$	$\frac{A}{C} \quad \frac{AD-BC}{C}$
$Z_{21} \quad Z_{22}$	$-\frac{Y_{21}}{\Delta Y} \quad \frac{Y_{11}}{\Delta Y}$	$\frac{1}{C} \quad \frac{D}{C}$
$\frac{Z_{22}}{\Delta Z} \quad -\frac{Z_{12}}{\Delta Z}$	$Y_{11} \quad Y_{12}$	$\frac{D}{B} \quad -\frac{AD-BC}{B}$
$\frac{Z_{21}}{\Delta Z} \quad \frac{Z_{11}}{\Delta Z}$	$Y_{21} \quad Y_{22}$	$-\frac{1}{B} \quad \frac{A}{B}$
$\frac{Z_{11}}{Z_{21}} \quad \frac{\Delta Z}{Z_{21}}$	$-\frac{Y_{22}}{Y_{21}} \quad -\frac{1}{Y_{21}}$	$A \quad B$
$\frac{1}{Z_{21}} \quad \frac{Z_{22}}{Z_{21}}$	$-\frac{\Delta Y}{Y_{21}} \quad -\frac{Y_{11}}{Y_{21}}$	$C \quad D$

T and Π representation of 2-port network:

T-Network

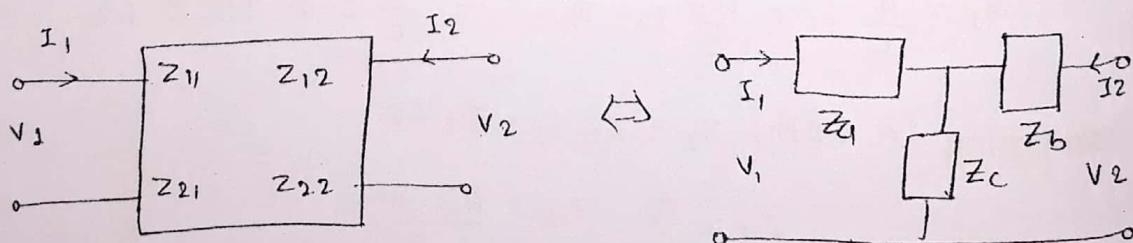Any two port network can be represented by an equivalent T network as shown in figure below.



Equation for 2-parameter are

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

For above netw, for $I_2 = 0$

$$V_1 = (Z_a + Z_c)I_1 \Rightarrow \frac{V_1}{I_1} = Z_a + Z_c = Z_{11}$$

$$I_1 Z_C \Rightarrow \frac{V_2}{I_1} = Z_C = Z_{21}$$

$$I_1 = 0$$

$$Z_C I_2 \Rightarrow \frac{V_1}{I_2} = Z_C = Z_{12}$$

$$V_2 = (Z_b + Z_C) I_2 \Rightarrow \frac{V_2}{I_2} = Z_b + Z_C = Z_{22}$$


$$= Z_{12} = Z_{21}$$

$$+ Z_C = Z_{11} \Rightarrow Z_a = Z_{11} - Z_C = Z_{11} - Z_{12}$$

$$+ Z_C = Z_{22} \Rightarrow Z_b = Z_{22} - Z_C = Z_{22} - Z_{21}$$

WORK

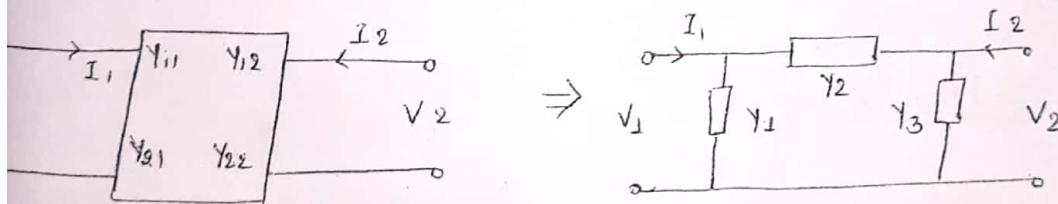Any two port n/w can be represented by an equivalent π is shown in figure below:



Equation for γ -parameter

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

or, above n/w, for $V_2 = 0$

$$\Rightarrow I_1 = (Y_1 + Y_2) V_1 \quad \dots \dots \textcircled{a}$$


$$\frac{I_1}{Y_1} = Y_1 + Y_2 = Y_{11}$$

$$\therefore \frac{I_1 + I_2}{Y_2} + \frac{I_2}{Y_2} = 0$$

$$\therefore Y_2 (I_1 + I_2) + I_2 Y_1 = 0$$

$$\therefore (Y_1 + Y_2) I_2 + Y_2 I_1 = 0$$
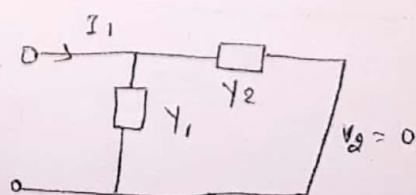
$$\therefore I_1 = -\frac{I_2 (Y_1 + Y_2)}{Y_2}$$



Now, from ①


$$-\frac{I_2(Y_1+Y_2)}{Y_2} = (Y_1+Y_2)V_2$$

$$\frac{I_2}{V_1} = -Y_2 = Y_{21}$$

For $V_1 = 0$

$$I_2 = (Y_2 + Y_3)V_2 \quad \dots \textcircled{b}$$

$$\frac{I_2}{V_2} = Y_2 + Y_3 = Y_{22}$$

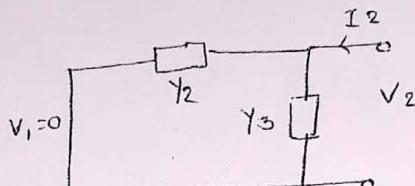

$$\text{and, } \frac{I_1}{Y_2} + \frac{I_1 + I_2}{Y_3} = 0$$

$$I_2 = -\frac{I_1(Y_2 + Y_3)}{Y_2}$$


NOW, ⑤ becomes

$$-\frac{I_1(Y_2 + Y_3)}{Y_2} = (Y_2 + Y_3)V_2$$


$$\Rightarrow \frac{I_1}{V_2} = -Y_2 = Y_{12}$$

J to T and T to D transfer

II-network

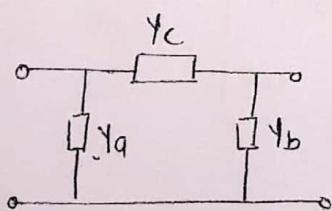

T-network

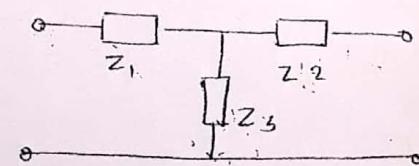

Delta to star (II to T)

$$Z_1 = \frac{\frac{1}{Y_a} \times \frac{1}{Y_c}}{\frac{1}{Y_a} + \frac{1}{Y_b} + \frac{1}{Y_c}} = \frac{\frac{1}{Y_a Y_c}}{\frac{1}{Y_a Y_b} + \frac{1}{Y_b Y_c} + \frac{1}{Y_c Y_a}} = \frac{Y_b}{Y_a Y_b + Y_b Y_c + Y_c Y_a}$$




$$Z_2 = \frac{Y_a}{Y_a Y_b + Y_b Y_c + Y_c Y_a}$$

$$Y_a Y_b + Y_b Y_c + Y_c Y_a$$

to delta (Δ to Π)

$$\begin{aligned}
 &= \frac{\frac{1}{Z_1} \times \frac{1}{Z_3}}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}} = \frac{\frac{1}{Z_1 Z_3}}{Z_2 Z_3 + Z_1 Z_3 + Z_2 Z_1} = \frac{Z_2}{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1} \\
 &= \frac{Z_1}{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1} \\
 &= \frac{Z_3}{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}
 \end{aligned}$$

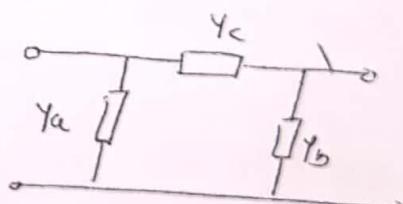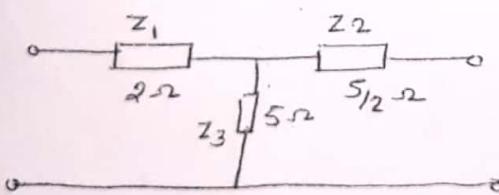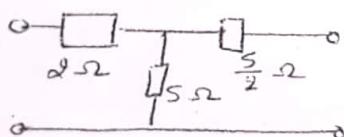
Example Find equivalent Π n/w for given Δ n/w.




$$\begin{aligned}
 Y_a &= \frac{S_{12}}{2 \times S_{12} + \frac{5}{2} \times 5 + 2 \times 5} = \frac{S_{12}}{S + \frac{25}{2} + 10} = \frac{\frac{5}{2}}{\frac{5}{2} (2 + 5 + 4)} = \frac{1}{11} \text{ S} \\
 Y_b &= \frac{Z_1}{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1} = \frac{2}{\frac{5}{2} (11)} = \frac{4}{55} \text{ S}
 \end{aligned}$$

$$Y_c = \frac{Z_3}{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1} = \frac{5}{\frac{5}{2} \times 11} = \frac{2}{11} \text{ S}$$

Obtain an equivalent T-network

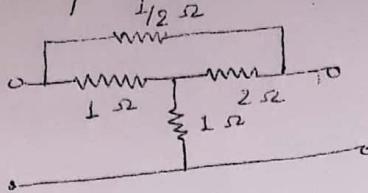

Soln: Here,

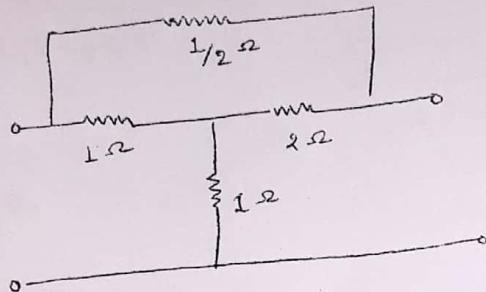

$$\text{Here, } Y_a = \frac{1}{1} \Omega$$

$$Y_b = \frac{1}{2} \Omega$$


$$Y_c = \frac{1}{2} \Omega$$

$$\text{Then, } Z_2 = \frac{Y_a}{Y_a Y_b + Y_a Y_c + Y_b Y_c} = \frac{1}{2 + 1 + \frac{1}{2}} = \frac{2}{7} \Omega$$


$$Z_3 = \frac{Y_a}{Y_a Y_b + Y_a Y_c + Y_b Y_c} = \frac{2}{\frac{7}{2}} = \frac{4}{7} \Omega$$

$$Z_{B,L} = \frac{Y_b}{Y_a Y_b + Y_a Y_c + Y_b Y_c} = \frac{\frac{1}{2}}{\frac{7}{2}} = \frac{1}{7} \Omega$$

Now,

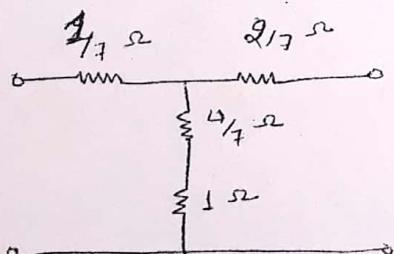

D

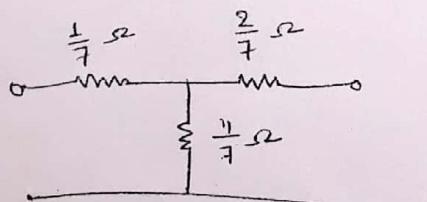

Equivalent T-n/w.