

EXAMPLE 12.38 Find the open circuit impedance parameter of the circuit shown in Fig. E12.56. Also find the Y parameters.

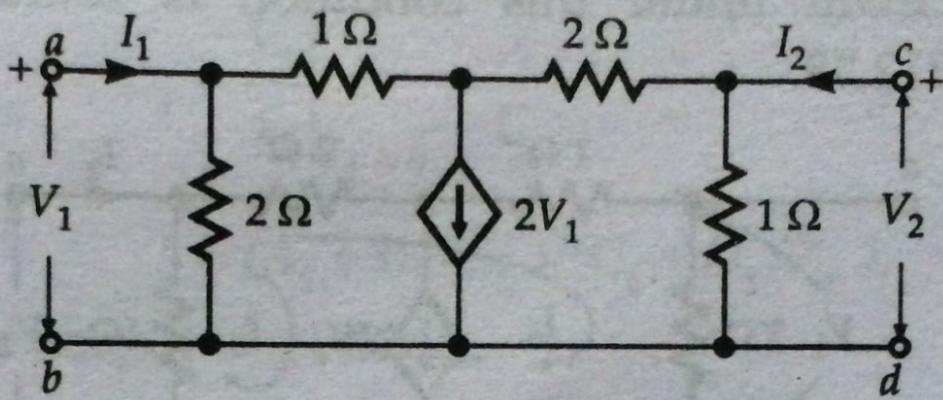


Fig. E12.56

SOLUTION. Assuming the output port (port *cd*) to the open-circuited, $I_2 = 0$. The circuit configuration alongwith loop currents has been shown in Fig. E12.57.

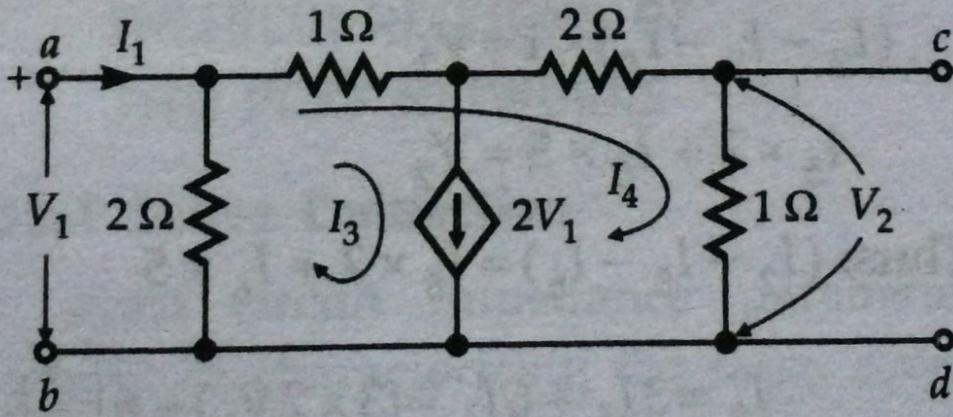


Fig. E12.57

Here,

$$I_4 \times 1 = V_2 ; (I_1 - I_3 - I_4)2 = V_1 ;$$

$$I_3 \times 1 + I_4 \times 4 = V_1 .$$

Thus,

$$2I_1 - 2I_3 - 2I_4 = I_3 + 4I_4 \quad \text{or}$$

$$\text{or, } I_1 = 1.5 I_3 + 3 I_4 = 1.5 \times 2V_1 + 3 \times V_2$$

$$= 3V_1 + 3\left(-\frac{1}{4}V_1\right) = \frac{9}{4}V_1 \quad \text{or}$$

$$\left[\because V_1 = 4I_4 + I_3 = 4V_2 + 2V_1 \text{ or } V_2 = -\frac{1}{4}V_1 \right] \quad \text{or}$$

$$\therefore \frac{V_1}{I_1} = Z_{11} = \frac{4}{9}\Omega \quad \text{or}$$

$$\text{Also, } (2+1)I_4 + I_3 + V_2 = V_1$$

$$\text{or } 3I_4 + I_3 + V_2 = V_1$$

$$\text{or } \left(\frac{V_2}{1}\right)3 + I_3 + V_2 = V_1 \quad \left[\because I_4 = \frac{V_2}{1\Omega}\right]$$

$$\text{or } 4V_2 + 2V_1 = V_1 \quad [\because I_3 = 2V_1]$$

$$\text{or } 4V_2 = -V_1 = -\frac{4}{9}I_1 \quad [\because 4I_1 = 9V_1] \quad i.e.,$$

$$\text{or } Z_{21} = \left.\frac{V_2}{I_1}\right|_{I_2=0} = -\frac{1}{9}\Omega$$

Let us now open the circuit of Fig. E12.58 and apply voltage at input port (port *a-b*). With $I_1 = 0$, the circuit under this condition is redrawn in Fig. E12.58.

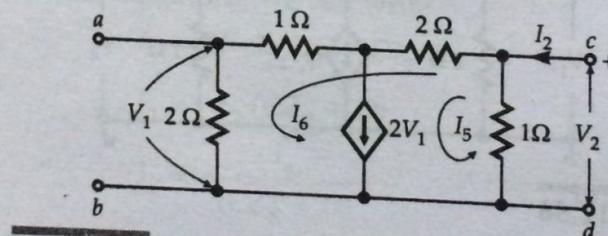


Fig. E12.58

$$\text{Here, } I_5 = 2V_1; 2 \times I_6 = V_1$$

Also utilising KVL,

$$(I_2 - I_5 - I_6) \times 1 = V_2$$

$$\text{and } I_5 \times 2 + I_6 \times 5 = V_2$$

$$\text{Thus, } (I_2 - I_5 - I_6) = I_5 \times 2 + I_6 \times 5$$

$$\text{or } I_2 = 3I_5 + 6I_6 = (3 \times 2V_1) + 6\left(\frac{V_1}{2}\right)$$

$$= 6V_1 + 3V_1 = 9V_1 \quad [\because I_5 = 2V_1 \text{ and } 2I_6 = V_1] \quad \text{and}$$

$$\therefore Z_{12} = \left.\frac{V_1}{I_2}\right|_{I_1=0} = \frac{1}{9}\Omega \quad \text{or}$$

Again, $5I_6 + 2I_5 = V_2$
 or $\frac{5}{2}V_1 + 4V_1 = V_2$

$[\because I_5 = 2V_1 \text{ and } 2I_6 = V_1]$

or $\frac{5}{2} \times \frac{I_2}{9} + 4 \frac{I_2}{9} = V_2$

$\left[\because \frac{V_1}{I_2} = \frac{1}{9} \right]$

or $\frac{13}{18}I_2 = V_2$

or $\left. \frac{V_2}{I_2} \right|_{I_1=0} = Z_{22} = \frac{13}{18} \text{ ohm}$

\therefore Z parameters are given by,

$$Z = \begin{bmatrix} (4/9) & (1/9) \\ (-1/9) & (13/18) \end{bmatrix}$$

i.e., $\text{Det}[Z] = \left(\frac{4}{9} \right) \left(\frac{13}{18} \right) + \left(\frac{1}{9} \right) \left(\frac{1}{9} \right) = \frac{1}{3}$

Thus Y parameters are given as

$$Y_{11} = \frac{Z_{22}}{\text{Det}[Z]} = \frac{13/18}{1/3} = \frac{13}{6} \text{ mho.}$$

$$Y_{21} = -\frac{Z_{21}}{\text{Det}[Z]} = \frac{1/9}{1/3} = \frac{1}{3} \text{ mho}$$

$$Y_{12} = -\frac{Z_{12}}{\text{Det}[Z]} = -\frac{(1/9)}{1/3} = -\frac{1}{3} \text{ mho}$$

$$Y_{22} = \frac{Z_{11}}{\text{Det}[Z]} = \frac{4/9}{1/3} = \frac{4}{3} \text{ mho.}$$

EXAMPLE 12.39 The Z-parameters of a circuit are given by

EXAMPLE 12.61 Obtain short circuit parameters of the network shown in Fig. E12.89.

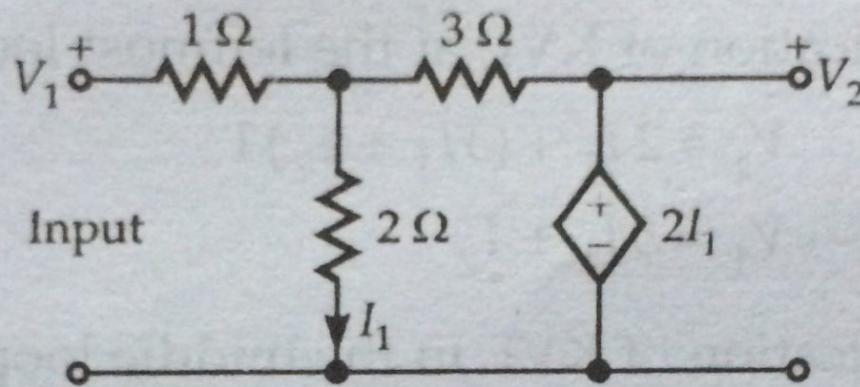


Fig. E12.89

SOLUTION. To obtain the short circuit parameters (*i.e.*, Y -parameters), short circuit is applied at the output port. (Fig. E12.90). Under this condition,

$$2I_1 = 0$$

i.e.,

$$I_1 = 0$$

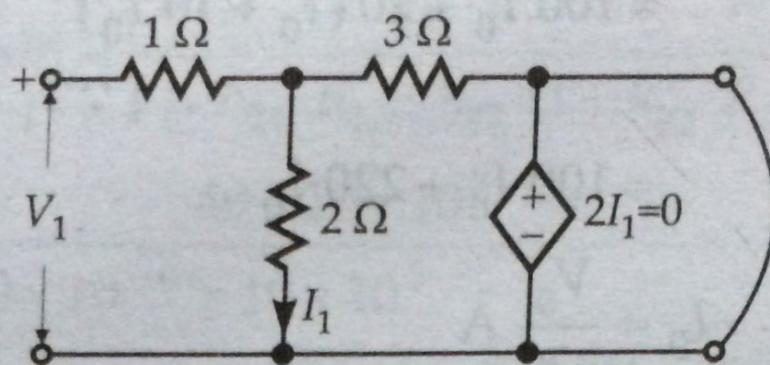


Fig. E12.90

However, I_1 should be a finite quantity as V_1 , the voltage applied at the input port is a nonzero quantity. This apparent paradox indicates that the solution of the network though Y-parameter concept is not possible and *it can be concluded that the Y-parameters of the network do not exist.*

EXAMPLE 12.62 Find Z-parameters of the network shown in Fig. E12.91.

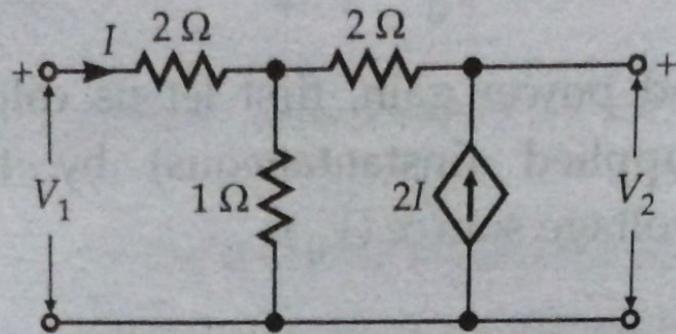


Fig. E12.91

SOLUTION. Let us redraw the given circuit with respective branch currents (Fig. E12.92).

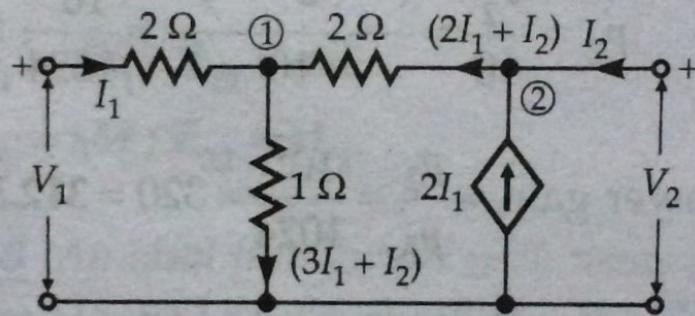


Fig. E12.92

Application of KVL at the leftmost loop yields

$$V_1 = 2I_1 + (3I_1 + I_2)1 \quad \text{or} \quad V_1 = 5I_1 + I_2 \quad \dots(A)$$

Application of KVL in the middle loop [*i.e.*, the loop involving the nodes (1) and (2)] gives

$$+2(2I_1 + I_2) + (3I_1 + I_2)1 - V_2 = 0 \quad \text{or} \quad V_2 = +7I_1 + 3I_2 \quad \dots(B)$$

From equations (A) and (B),

$$Z_{11} = 5\Omega, Z_{12} = 1\Omega, Z_{21} = 7\Omega, Z_{22} = 3\Omega.$$

EXAMPLE 12.62 Find Z-parameters of the network shown in Fig. E12.91.

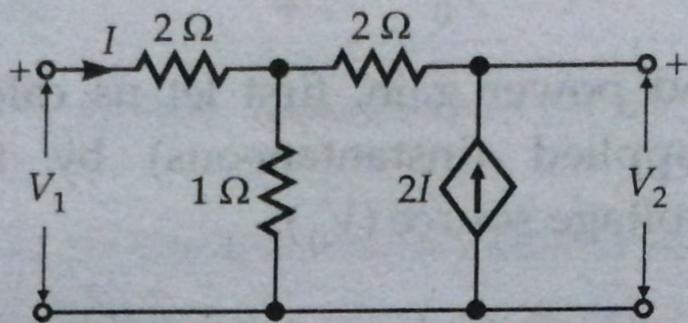


Fig. E12.91

SOLUTION. Let us redraw the given circuit with respective branch currents (Fig. E12.92).

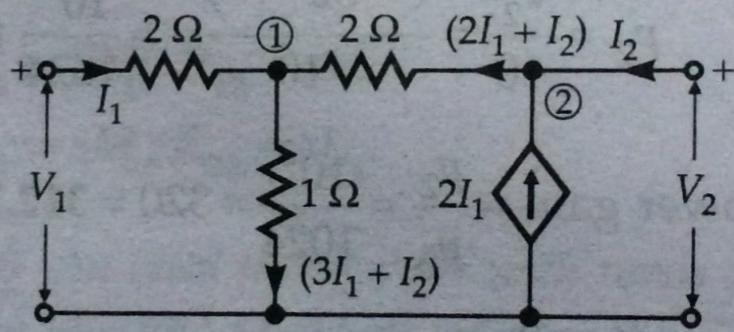


Fig. E12.92

Application of KVL at the leftmost loop yields

$$V_1 = 2I_1 + (3I_1 + I_2)1 \quad \text{or} \quad V_1 = 5I_1 + I_2 \quad \dots(A)$$

Application of KVL in the middle loop [i.e., the loop involving the nodes (1) and (2)] gives

$$+2(2I_1 + I_2) + (3I_1 + I_2)1 - V_2 = 0 \quad \text{or} \quad V_2 = +7I_1 + 3I_2 \quad \dots(B)$$

From equations (A) and (B),

$$Z_{11} = 5\Omega, Z_{12} = 1\Omega, Z_{21} = 7\Omega, Z_{22} = 3\Omega.$$

EXAMPLE 12.66 Find Z parameters of the following circuit (Fig. E12.95).

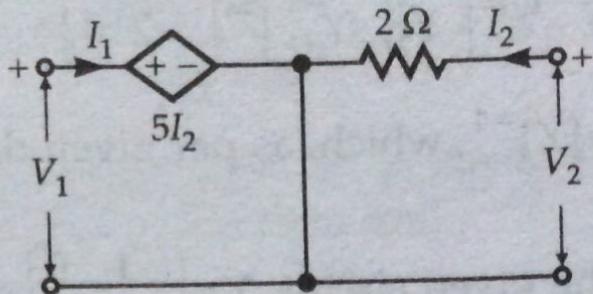


Fig. E12.95

SOLUTION. Applying KVL in the left handed loop,

$$V_1 = 0 \cdot I_1 + 5I_2 \quad \dots(1)$$

Applying KVL in the right handed loop,

$$\begin{aligned} V_2 &= 2I_2 + 0 \cdot (I_1 + I_2) \\ &= 0 \cdot I_1 + 2I_2 \end{aligned} \quad \dots(2)$$

From (1) and (2), we get

$$Z_{11} = 0 \Omega, Z_{12} = 5 \Omega$$

$$Z_{21} = 0, Z_{22} = 2 \Omega$$

It may be noted that for this circuit,

$$Z = \begin{bmatrix} 0 & 5 \\ 0 & 2 \end{bmatrix} \text{ and } Y = [Z]^{-1}$$

However, it is evident that with the given values of $Z, Y (= [Z]^{-1})$ does not exist.

\therefore For the given circuit, Y parameter does not exist. Also, it can be observed that in this circuit, V_1 and V_2 can not be chosen independently justifying the absence of Y parameter.

2. Find Y parameters of the network shown in Fig. P12.2.

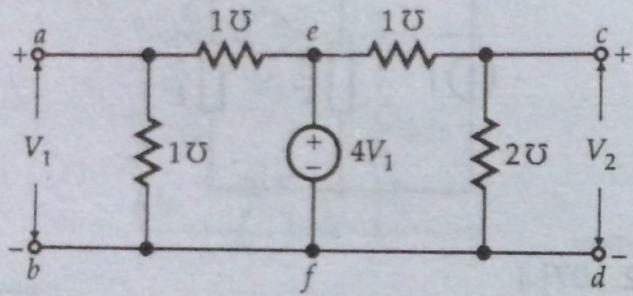


Fig. P12.2

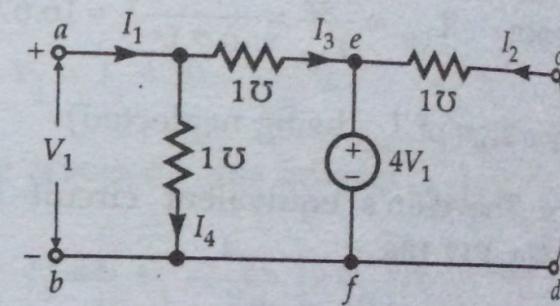


Fig. P12.3

[Hint. In the first step $c-d$ is short-circuited (Refer to Fig. P12.3)]

$$4V_1 = -(I_2) / 1 \text{ mho} \quad \text{or, } I_2 = -4V_1$$

$$V_1 = 4V_1 + \frac{I_3}{1\Omega} \quad \text{or, } I_3 = -3V_1$$

$$I_1 = I_3 + I_4 = -3V_1 + V_1 / 1 = -2V_1$$

$$\therefore Y_{11} = -2 \text{ mho}$$

$$Y_{21} = -4 \text{ mho}$$

Next, short terminal $a-b$ (refer to Fig. P12.4)

Note that $4V_1 = 0$ as $V_1 = 0$ due to s.c. at terminal $(a-b)$

$$V_2 = I_2 (2 + 1) = 3I_2 \quad \therefore Y_{22} = 3 \text{ mho}$$

$$\text{also } V_2 = -I_1 \times 1 \quad \therefore Y_{12} = -1 \text{ mho}$$

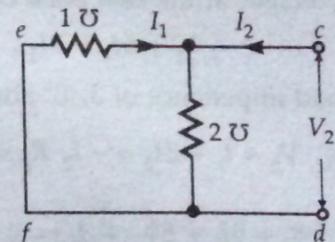


Fig. P12.4

3. Find Z-parameters for the attenuator network shown in Fig. P12.5.

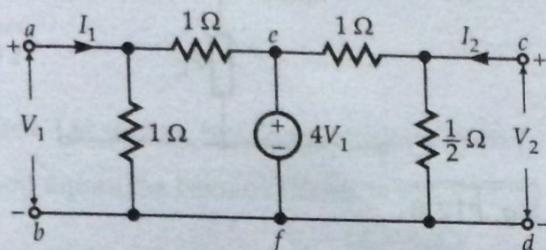


Fig. P12.5

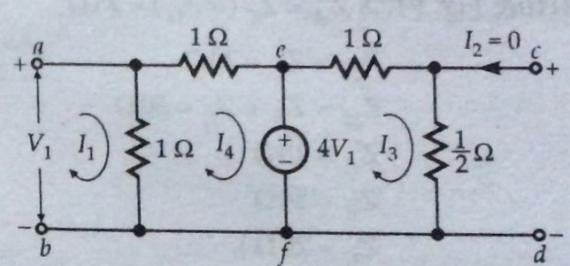


Fig. P12.6

[Hint. Open circuit output port (Fig. P12.6)]

$$V_2 = \frac{1}{2} \times I_3 \quad \text{or} \quad V_2 = \frac{I_3}{2} - 4V_1 + I_3 \left(1 + \frac{1}{2}\right) = 0$$

$$\text{or} \quad I_3 = \frac{4}{1.5} V_1$$

$$4V_1 + I_4 (1 + 1) - I_1 \times 1 = 0 \quad \text{or} \quad 4V_1 + 2I_4 - I_1 = 0$$

$$V_1 = I_1 \times 1 - I_4 \times 1 \quad \text{or} \quad V_1 = I_1 - I_4$$

From the above four equations find Z_{11} and Z_{21} .

Next make terminal $a-b$ open (Fig. P12.7),

$$V_1 = I_5 \times 1$$

$$2I_5 = 4V_1$$

$$\frac{1}{2}(I_6 - I_2) + I_6 \times 1 + 4V_1 = 0$$

$$\frac{1}{2}(I_2 - I_6) = V_2$$

From these equations, Z_{22} and Z_{12} can be found out.]

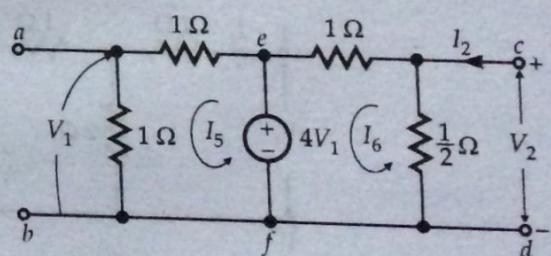


Fig. P12.7

12. Determine Y parameters of the network shown in Fig. P12.12.

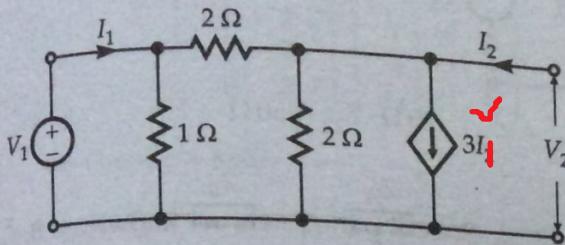


Fig. P12.12

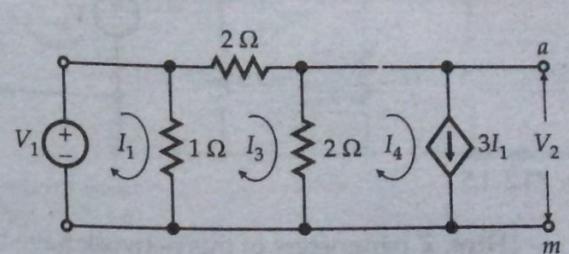


Fig. P12.13

[Hint. Let us first find Z parameters, With $I_2 = 0$,

Loop equations become (Refer to Fig. P12.13)

$$V_1 = (I_1 - I_3) 1 \quad \dots(1)$$

$$0 = (I_3 - I_1) 1 + 2 I_3 + (I_3 - I_4) 2 \quad \dots(2)$$

$$V_2 = 2(I_3 - I_4) \quad \dots(3)$$

$$I_4 = 3 I_1 \quad \dots(4)$$

From (2), utilising (4),

$$0 = I_3 - I_1 + 2 I_3 + 2 I_3 - 6 I_1 \quad \text{or} \quad 5 I_3 = 7 I_1$$

$$\therefore I_3 = \frac{7}{5} I_1$$

$$\therefore \text{From (1)} \quad V_1 = I_1 - \frac{7}{5} I_1 = -\frac{2}{5} I_1$$

$$\therefore Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = -0.4 \Omega$$

Also, from (3) and (4),

$$V_2 = 2(I_3 - 3 I_1) = 2\left(\frac{7}{5} I_1 - 3 I_1\right) = -\frac{16}{5} I_1 \quad \therefore Z_{21} = -3.2 \Omega$$

Next input port is opened (Fig. P12.14), $I_1 = 0$,

$$V_2 = (I_2 - I_5) 2 \quad \dots(5)$$

$$\text{and} \quad 0 = 2(I_5 - I_2) + 3 I_5 \quad \dots(6)$$

$$\text{or} \quad I_5 = \frac{2}{5} I_2$$

$$\text{Thus from (5), } V_2 = \left(I_2 - \frac{2}{5} I_2\right) 2 = 2 I_2 - \frac{4}{5} I_2 = \frac{6}{5} I_2$$

$$\therefore Z_{22} = \frac{6}{5} = 1.2 \Omega$$

$$\text{Also, } V_1 = I_5 \times 1 = \frac{2}{5} I_2 \quad \therefore \quad \frac{V_1}{I_2} = Z_{12} = \frac{2}{5} = 0.4 \Omega$$

$$\text{Thus } \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} -0.4 & 0.4 \\ -3.2 & 1.2 \end{bmatrix}$$

From these values of Z , referring to Art 12.11, the value of Y parameters can be determined].

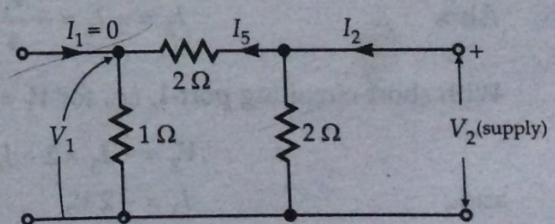


Fig. P12.14

EXAMPLE 12.54 Find Y-parameters of the network shown in Fig. E12.80.

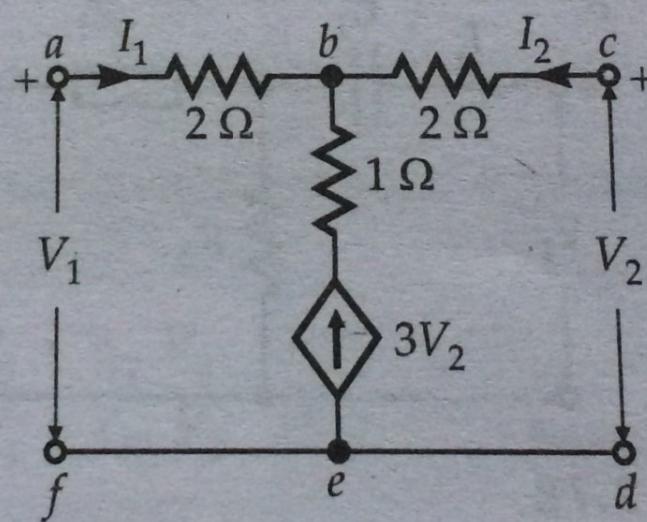


Fig. E12.80

SOLUTION. Let us first apply KVL at the outer loop of the given circuit (*abcdef*), assuming the currents I_1 and I_2 entering the circuit from the input and output sides with application of voltages V_1 and V_2 at the input and output respectively.

We thus obtain,

$$-V_1 + 2I_1 - 2I_2 + V_2 = 0 \quad \dots(a)$$

Applying KCL at node (b),

$$I_1 + I_2 + 3V_2 = 0$$

or $I_1 = -I_2 - 3V_2 \quad \dots(b)$

i.e., $I_2 = -I_1 - 3V_2 \quad \dots(c)$

Substituting the value of I_2 from (c) in (a),

$$-V_1 + 2I_1 - 2(-I_1 - 3V_2) + V_2 = 0$$

or $-V_1 + 4I_1 + 7V_2 = 0$

or $I_1 = -\frac{7}{4}V_2 + \frac{1}{4}V_1 \quad \dots(d)$

Again substituting the value of I_1 from (b) in (a),

$$-V_1 + 2(-I_2 - 3V_2) - 2I_2 + V_2 = 0$$

or $-V_1 - 2I_2 - 6V_2 - 2I_2 + V_2 = 0$

or $-V_1 - 4I_2 - 5V_2 = 0$
 $\therefore I_2 = -\frac{1}{4}V_1 - \frac{5}{4}V_2 \quad \dots(e)$

Rearranging equations (d) and (e),

$$I_1 = \frac{1}{4}V_1 - \frac{7}{4}V_2$$

$$I_2 = -\frac{1}{4}V_1 - \frac{5}{4}V_2$$

Comparing these equations with the standard form of the Y -parameter equation,

$$Y_{11} = \frac{1}{4} \text{ mho}$$

$$Y_{12} = -\frac{7}{4} \text{ mho}$$

$$Y_{21} = -\frac{1}{4} \text{ mho}$$

$$Y_{22} = -\frac{5}{4} \text{ mho.}$$

EXAMPLE 12.55 Find Z -parameters of the circuit shown

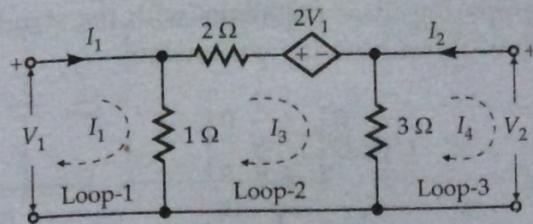


Fig. E12.81

For loop-1

$$I_1 - I_3 = V_1 \quad \dots(a)$$

For loop-2

$$2I_3 + 2V_1 + 3(I_3 - I_4) + 1(I_3 - I_1) = 0$$

$$\text{or} \quad -I_1 + 2V_1 + 6I_3 - 3I_4 = 0$$

$$\text{or} \quad -I_1 + 3I_2 + 6I_3 = -2V_1 \quad \dots(b)$$

 $[\because I_4 \equiv -I_2]$

For loop-3

$$3(I_4 - I_3) + V_2 = 0$$

$$\text{or} \quad V_2 = 3(I_3 - I_4)$$

$$\text{or} \quad V_2 = 3I_3 + 3I_2 \quad \dots(c)$$

Thus the equations are rearranged as

$$I_1 + 0.1I_2 - I_3 = V_1 \quad \dots(a)$$

$$-I_1 + 3I_2 + 6I_3 = -2V_1 \quad \dots(b)$$

$$0.1I_1 + 3I_2 + 3I_3 = V_2 \quad \dots(c)$$

$$\text{From (a), } I_3 = I_1 - V_1$$

Then from (b),

$$-I_1 + 3I_2 + 6(I_1 - V_1) = -2V_1$$

$$\text{or} \quad 5I_1 + 3I_2 = 4V_1$$

$$\text{or} \quad V_1 = \frac{5}{4}I_1 + \frac{3}{4}I_2 \quad \dots(d)$$

Again, using (a) in (c),

$$+3I_2 + 3(I_1 - V_1) = V_2$$

$$\text{or} \quad +3I_2 + 3I_1 - 3V_1 = V_2$$

$$\text{or} \quad V_2 = 3I_2 + 3I_1 - 3\left[\frac{5}{4}I_1 + \frac{3}{4}I_2\right]$$

$$\therefore V_2 = 3I_1 - \frac{15}{4}I_1 + 3I_2 - \frac{9}{4}I_2$$

$$\text{or} \quad V_2 = -\frac{3}{4}I_1 + \frac{3}{4}I_2 \quad \dots(e)$$

Comparing (d) and (e) with the standard equations of Z-parameter,

$$Z_{11} = \frac{5}{4}\Omega; \quad Z_{12} = \frac{3}{4}; \quad Z_{21} = -\frac{3}{4}; \quad Z_{22} = \frac{3}{4}$$