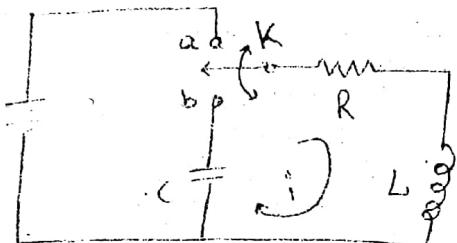


- In the network of the figure, K is changed from position a to b at $t=0$. Solve for i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t=0^+$ if $R=1000\Omega$, $L=14$, $C=0.1\mu F$ and $V=100V$.




Ans:

$$i(0^+) = 0.1 \text{ amp}$$

$$\frac{di(0^+)}{dt} = -100 \text{ amp/sec}$$

$$\frac{d^2i(0^+)}{dt^2} = -9 \times 10^5 \text{ A/sec}^2$$

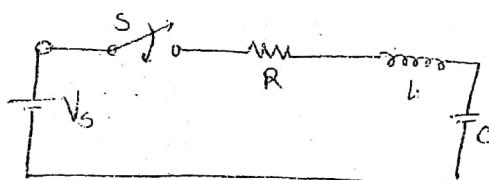- Consider the RLC series circuit shown in figure below. $V_s = 2V$; $R = 6\Omega$, $L = 2H$, $C = 0.25F$. Determine $i(0^+)$, $\frac{di(0^+)}{dt}$, $\frac{d^2i(0^+)}{dt^2}$ and $v(t)$.




Ans:

$$i(0^+) = 0 \text{ amp} \quad \frac{d^2i(0^+)}{dt^2} = -3 \text{ A/sec}^2$$

$$\frac{di(0^+)}{dt} = 1 \text{ A/sec}$$

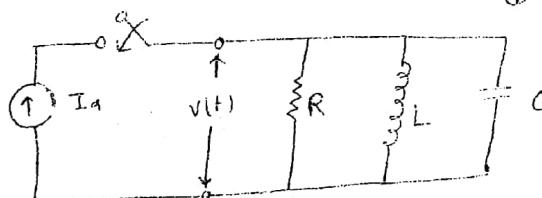- Consider the RLC parallel circuit shown in figure below. $I_s = 2A$, $R = \frac{1}{16}\Omega$, $L = \frac{1}{16}H$, $C = 4F$. Determine $v(0^+)$, $\frac{dv(0^+)}{dt}$, $\frac{d^2v(0^+)}{dt^2}$ and $v(t)$.




Ans:

$$v(0^+) = 0 \quad \frac{d^2v(0^+)}{dt^2} = -2 \text{ V/sec}^2$$

$$\frac{dv(0^+)}{dt} = \frac{1}{2} \text{ V/sec}$$

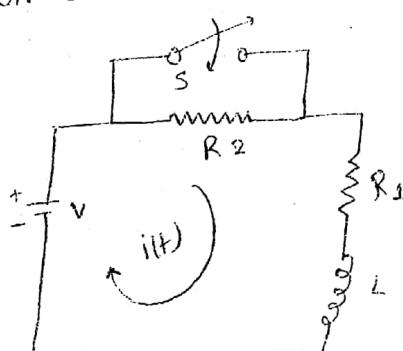
- In the network shown in figure below, switch S is closed at $t=0$, a steady state current having previously been attained. solve for the current as a function of time.



Ans:

$$i(t) = \frac{V}{R_1} \left[1 - \frac{R_2}{R_1 + R_2} e^{-\frac{R_1}{L}t} \right]$$

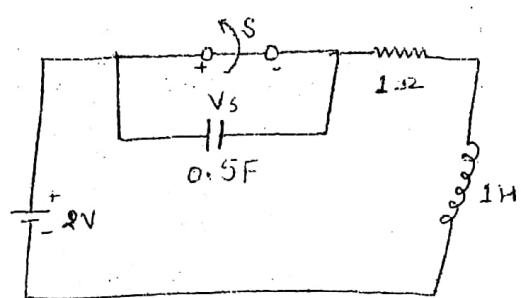- The circuit shown in figure is in the steady state with the switch S closed. This switch is opened at $t=0$. Determine voltage across the switch, v_s and $\frac{dv_s}{dt}$ at $t=0^+$.




Ans:

$$V_S(0^+) = 0$$

$$\frac{dV_S(0^+)}{dt} = 4 \text{ V/sec.}$$

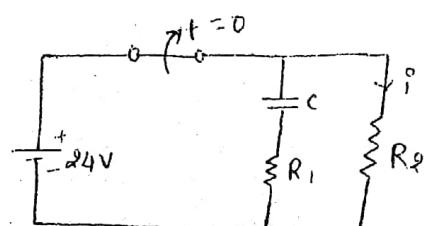- 6/ The circuit was under steady state before the switch was opened.
If $R_1 = 1\Omega$, $R_2 = 2\Omega$ and $C = 0.167 \text{ F}$, determine $V_C(0^-)$, $V_C(0^+)$ and $i(0^+)$.




Ans:

$$V_C(0^-) = 24 \text{ V}$$

$$V_C(0^+) = 24 \text{ V}$$

$$i(0^+) = 8 \text{ A}$$

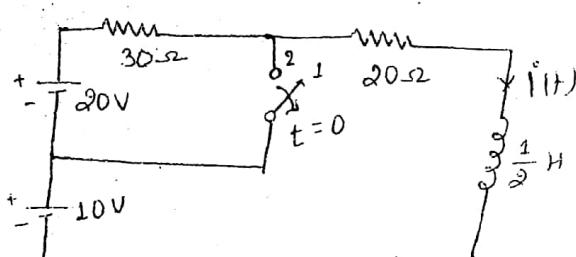
- 7/ The circuit of given figure reaches a steady state in position 2 and at $t = 0$ the switch S is moved to position 1. find it.



Ans:

$$i(t) = 0.6 - 0.1e^{-100t} \text{ A}$$

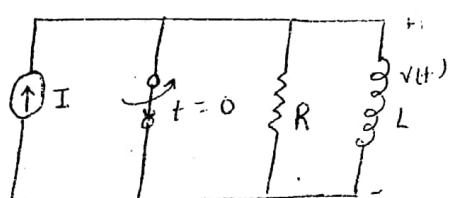- 8/ The circuit shown in figure below has the switch S opened at $t = 0$. Solve for v , $\frac{dv}{dt}$ and $\frac{d^2v}{dt^2}$ at $t = 0^+$ if $I = 1 \text{ amp}$, $R = 100 \Omega$ and $L = 1 \text{ H}$. Also find the expression for $v(t)$.




Ans:

$$v(0^+) = 100 \text{ V} \quad \frac{d^2v(0^+)}{dt^2} = 10^6 \text{ V}$$


$$\frac{dv(0^+)}{dt} = -10^4 \text{ V/sec}$$

$$v(t) = 100 e^{-100t} \text{ V}$$

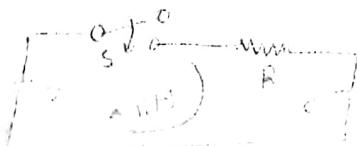- 9/ In the circuit of the given figure, the switch S is closed at $t = 0$ with the capacitor uncharged. Find values for i , $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$ at $t = 0^+$ for given values as follows: $V = 100 \text{ V}$, $R = 1000 \Omega$ and $C = 0.1 \text{ F}$.



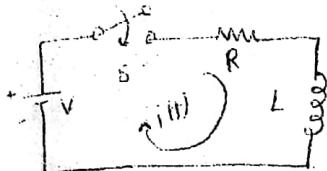- Q.10 In the given circuit, S is closed at $t=0$ with zero current in the inductor. Find the values of i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t=0^+$, if $R = 10\Omega$, $L = 1H$ and $V = 100V$.




Ans:

$$i(0^+) = 0 \quad \frac{d^2i(0^+)}{dt^2} = -1000 \text{ A/sec.}$$


$$\frac{di(0^+)}{dt} = 100 \text{ A/sec.}$$

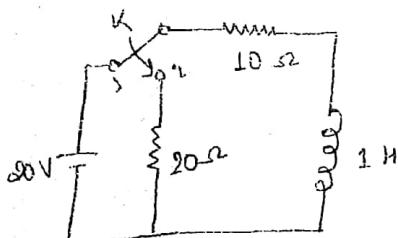- Q.11 In the given circuit switch K is changed from position 1 to 2 at $t=0$, steady state condition having reached before switching. Find, i , $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$ at $t=0^+$. [2007 Fall]




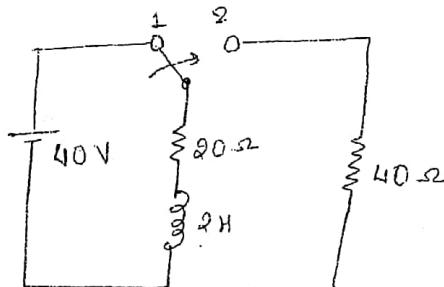- Q.12 In the given circuit the switch is changed from position 1 to 2 at time $t=0$, steady state having reached previously. Find:

$$i(0^+), \frac{di(0^+)}{dt}, \frac{d^2i(0^+)}{dt^2} \quad [2008 Fall]$$



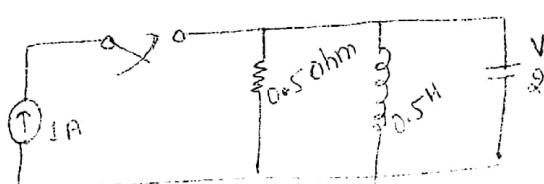
- Q.13 In the given RLC parallel circuit, determine $v(0^+)$, $\frac{dv(0^+)}{dt}$, $\frac{d^2v(0^+)}{dt^2}$.




[2009 Fall]

Assume no initial energy is stored

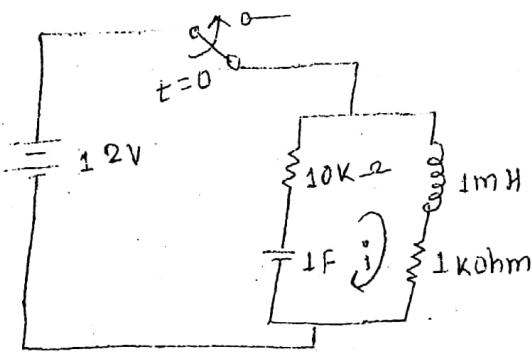- Q.14 The switch S in the given circuit is opened at time $t=0$. Determine the current in the inductor at $t=0^+$. [2013 Fall]



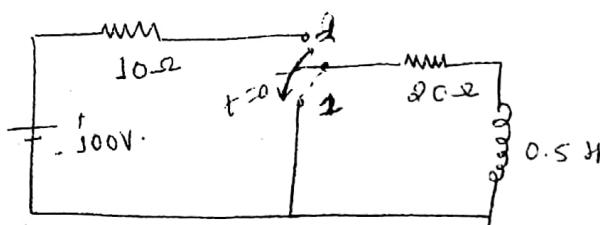3.15 Switch κ is kept at position 2 and steady state condition is reached. At $t = 0$, the switch is moved to position 1. find, i. $\frac{di}{dt}$ and, $\frac{d^2i}{dt^2}$ at $t = 0$.




chapter: 3

Assignment: 2

- Q1 : A series circuit containing $R = 7\Omega$, $L = 1H$ and $C = 0.1F$ is connected to 20V DC supply at $t = 0$ sec. Find the expression of voltage across capacitor at any time using classical method considering inductor has zero current and capacitor has zero voltage initially.

[2009 Fall 1.a]

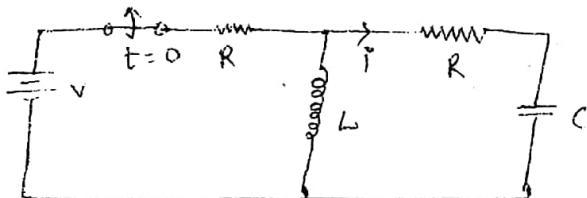
- Q2 : In the given circuit, switch opens at $t = 0$.



Solve $i(t)$ for $V = 12V$, $R = 4\Omega$, $C = \frac{1}{3}F$ and $L = 1H$.

[2009 Spring 1.a]

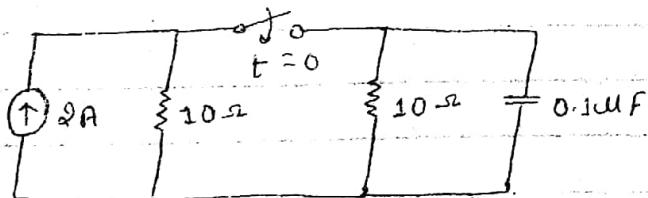- Q3 : Find the total response $v_c(t)$ for the voltage across the capacitor in circuit given below using classical method. The switch s is closed at $t = 0$.




[2008 S 1.b]

- Q4 : A DC current of $5A$ is suddenly connected to a parallel RLC network at $t = 0$. Obtain the particular solution for voltage $v(t)$ across the circuit elements. Given that $R = \frac{1}{5}\Omega$, $L = 0.1H$ and $C = 4F$. Assume zero initial charge across capacitor and zero initial current through inductor. (2008 S 2.a)


- Q5 : An R-L circuit is connected to an AC voltage $e = 100\sin(50\pi t)$ Volts at $t = 0$. If $R = 5\Omega$ and $L = 0.01H$. Find the equation for the current using classical method. (2008 S 2.b)

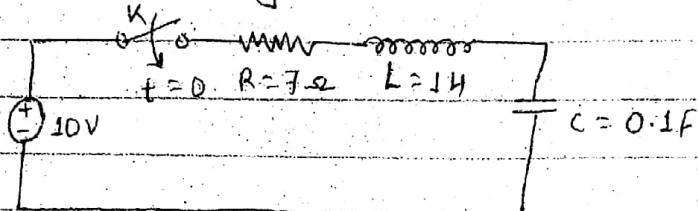Q.6 At $t=0$, switch K is closed. Find the value of current at $t=0.1$ sec. Using classical approach.




[2010 S 1b]

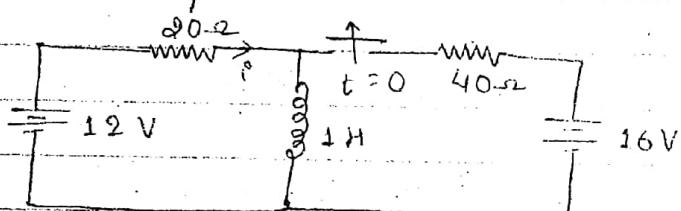Q.7 Find $i(t)$ for $t > 0$ in the circuit shown in figure below. Switch is opened at $t = 0$.




[2010 S 2b]

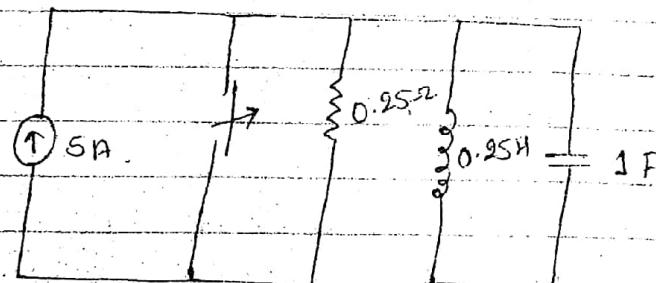Q.8 For the network shown in figure below, determine the voltage response of the circuit when switch is opened at $t = 0$.



[2011 F 1(a)]

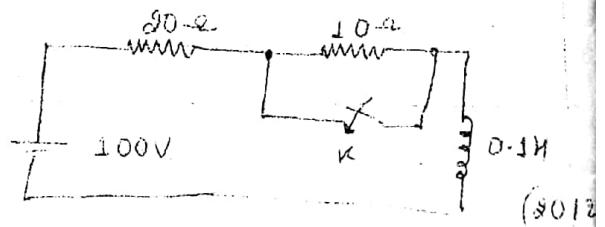Q.9 A dc voltage 100V is applied in the adjoining circuit and switch K is open. The switch K is closed at $t = 0$. Find the complete expression for current.



(s012)

Q.10 In the series RLC network, $V = 100V$, $L = 0.2H$, $R = 30\Omega$ and $C = 40\mu F$. Obtain the expression for $i(t)$ using classical approach. Assume there is no initial charge on the capacitor or current in the inductor.

[2014 F 1 9]

• ✓



Name _____


Roll _____

Subject _____

Date _____


Assignment : 3

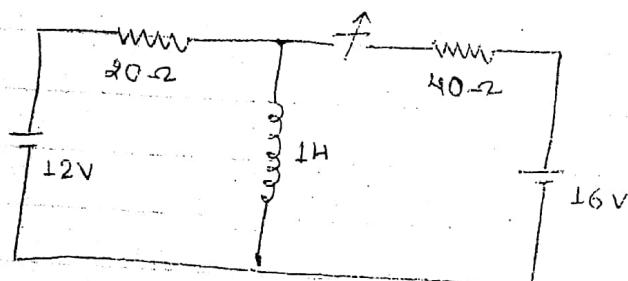1. Find $i(t)$ for $t > 0$ in the circuit shown in figure below using Laplace transform. Switch is opened at $t = 0$.



(2014 Fall)

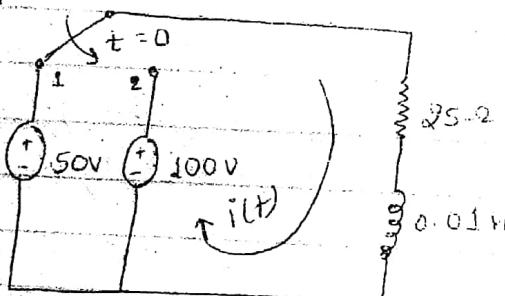2. In the series R-L circuit shown below, Switch K is in position 1 for a long time and moved to position 2 at time $t = 0$. Find the resulting current $i(t)$ using Laplace transform method.



(2013 Fall)

3. ~~90/2~~ What are the conditions necessary for the existence of Laplace Transform? Prove that the Laplace Transform of Delta function is unity

(2012 Spring)


4. An exponential voltage $V(t) = 4e^{-2t}$ is suddenly at time $t=0$

~~90/2~~
Spring

to a series RL circuit consisting of $R = 4\Omega$ and $L = 1H$ using Laplace transform method, find the particular solution for $i(t)$ through the circuit. Assume the current through the inductor is 3A before switching.


[2012 spring]

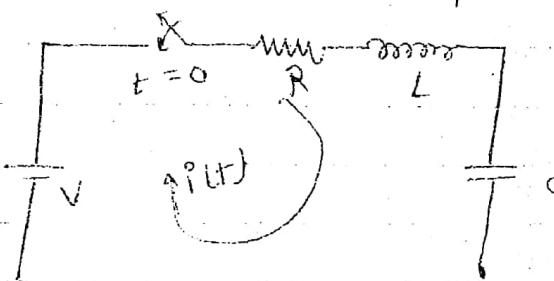5. In the circuit below, $V_0 = 10V$, $R = 5\Omega$, $L = 1H$ and $C = 0.25F$, the switch is closed at time $t = 0$, using Laplace technique to obtain the particular solution for $i_C(t)$ through the circuit. Assume that there is zero current through inductor and zero charge across capacitor before switching.



[2012 Fall]

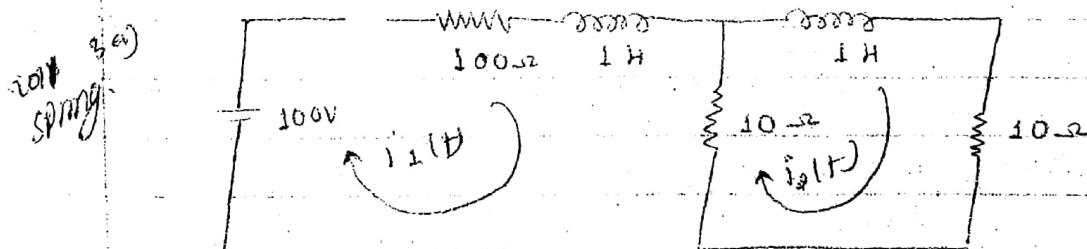6. Using Laplace transform in the given network, find $i_L(t)$. Assume zero current through inductor initially.




[2011 spring]

7. State initial and final value theorems for Laplace transform. Find $i(a)$ and steady state value $i(t)$ for the function:

$$I(s) = \frac{(s+1)}{s(s+2)}$$


[2011 Spring]

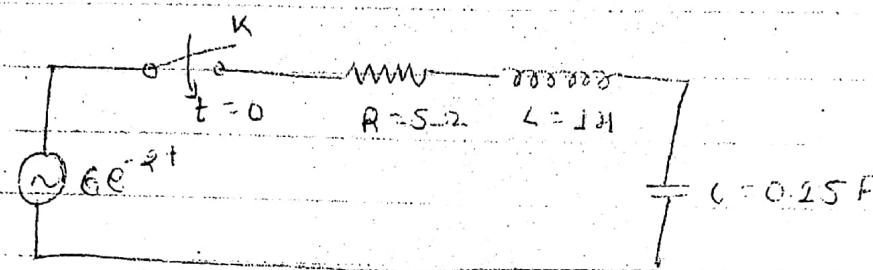8. Switch K is closed at $t = 0$. Find the time domain circuit current using Laplace transform for the following circuit



[2011 Fall]

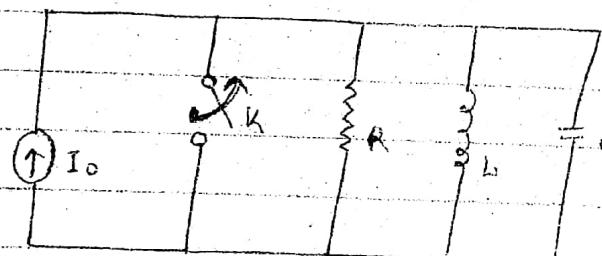9. In the circuit shown below $C = 1F$, $R = \frac{1}{2}\Omega$, $L = \frac{1}{2}H$ and the switch K is opened at $t = 0$. Obtain particular solution for $v(t)$, calculate the value of voltage V at $t = 0 +$ and 0.2 second (use Laplace transform)



[2008 Fall]

10. A sinusoidal voltage $\sin \omega t$ is applied at time $t = 0$ to a series R-L circuit comprising $R = 5\Omega$ and $L = 1H$. By the method of Laplace transformation, find current $i(t)$. Assume zero current through inductor before application of voltage.

[2007 Spring]

90
3
Spring

Subject:

Date:

Page:

Chapter: 5

Assignment: 4

1. From pole zero plot, obtain the time response for

$$I(s) = \frac{4s}{(s+1)(s+3)}$$
 also determine the value of $i(t)$ for $t = 1$ sec.

[2014 Fall] [2010 Spring]

2. Check the stability of the system whose characteristic equation is given by $s^5 + s^4 + 2s^3 + 2s^2 + 3s + 5 = 0$. Using Routh - Hurwitz criteria.

[2013 Fall]

3. Determine the range of 'k' for which the system is stable using Routh - Hurwitz criteria;

$$g(s) = s^4 + s^3 + s^2 + s + k$$

[2012 Spring]

4. Plot the poles and zeroes in s-plane and obtain T(s) for the transfer function of a network given by

$$T(s) = \frac{3s}{(s+2)(s^2+2s+2)}$$

[2012 Fall]

5. Check the stability of the following system expressed in polynomial as $g(s) = s^3 + 2s^2 + 2s + 40$ using Routh Hurwitz criteria.


[2012 Fall]

6. Show the pole-zero plot of the given network function
 $H(s) = \frac{10s}{(s+1)(s+3)}$, and obtain $h(t)$ using pole-zero plot

[2011 Spring]

7. Define transfer function for the network shown below
determine $V_2(s)$

$$V_1(s)$$

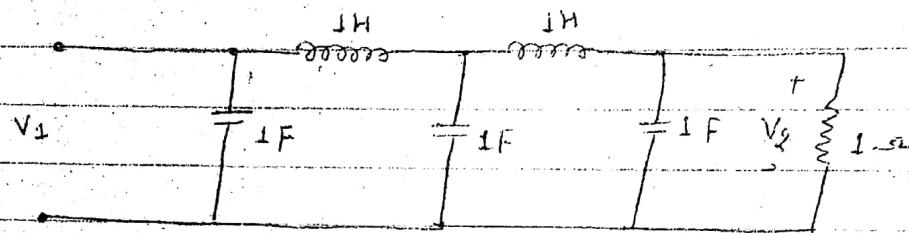


[2011 Fall]

8. The denominator polynomial of a network is given as $s^3 + 7s^2 + 10s + 10k = 0$. Determine the range of k for which the system is stable using Routh-Hurwitz criterion

[2010 Fall]

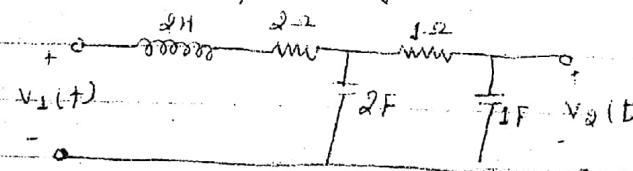9. Find $V_2(s)/V_1(s)$ for the following network:



[2009 Fall]

10. What does Routh-Hurwitz criteria state? Form Routh array for the following characteristic equation and state whether the system is stable or not.

$$G(s) = 5s^5 + 3s^4 + 2s^3 + 2s^2 + s + 1$$


[2008 Fall]

Name _____
Roll _____
Subject _____

CHAPTER 6

Assignment 5

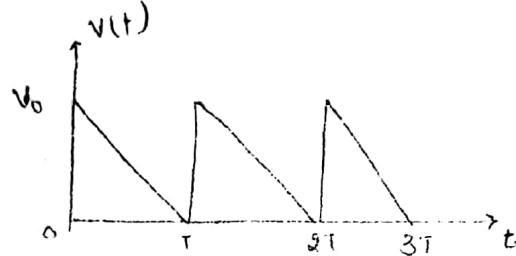
1. for the following periodic waveform, find the fourier series expansion.



[2012 spring]


[2014 Fall]

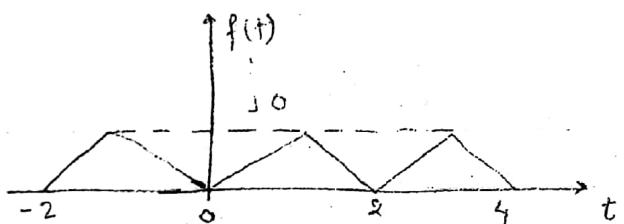2. Find the trigonometric fourier series for the waveform shown.




[2013 Fall]

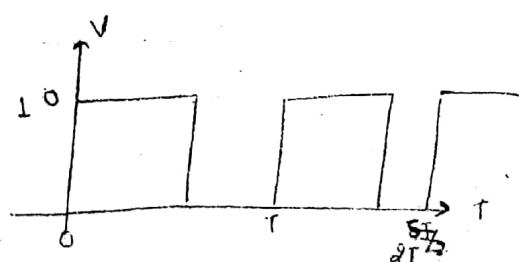3. Determine the fourier series of the wave form given by




[2012 Fall]

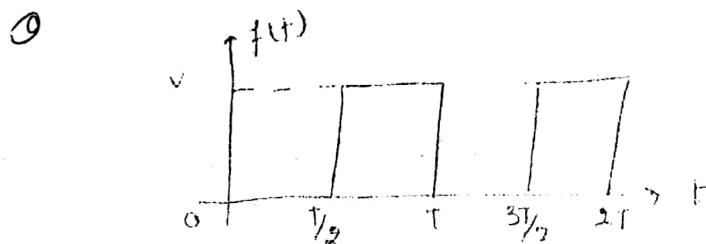4. find the fourier series of the given waveform.




[2011 spring]

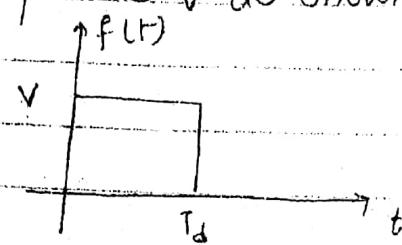5. Determine the fourier transform of a pulse of duration T_d and amplitude V as shown in figure below:




[2011 Fall]

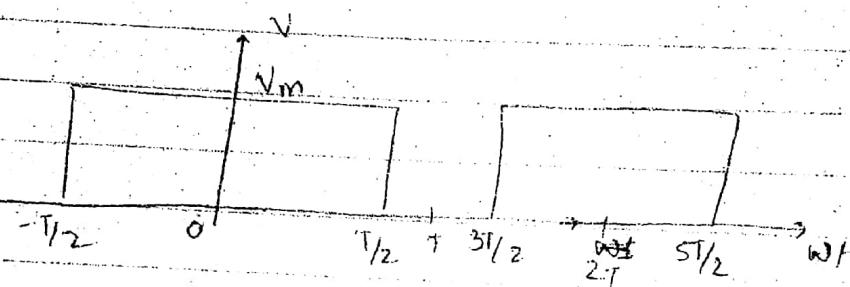6. Obtain the trigonometric form of the fourier series for following function.




[2010 Spring]

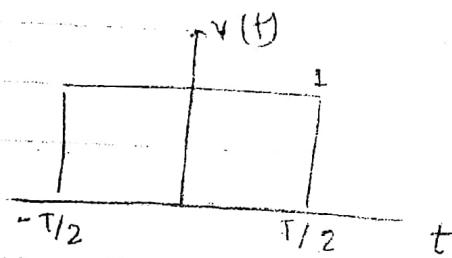7. Obtain the fourier transform of the given waveform.



[2009 Fall]

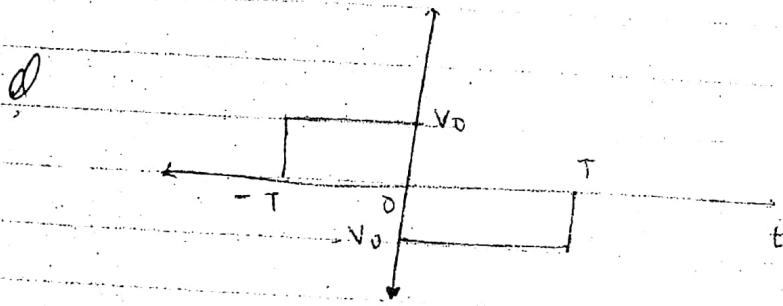
8. Determine the fourier transform of the function shown below.



[2008 Spring]

Assignments

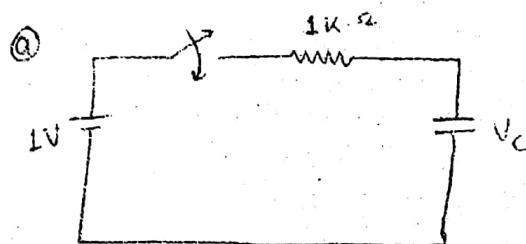
Find, $v(0^-)$, $v(0^+)$, $v(\infty)$ and $i(0^-)$, $i(0^+)$ and $i(\infty)$



$$v_C(0^-) = 0 \quad i(0^-) = 0$$

$$v_C(0^+) = 0, \quad i(0^+) = 1\text{mA}$$
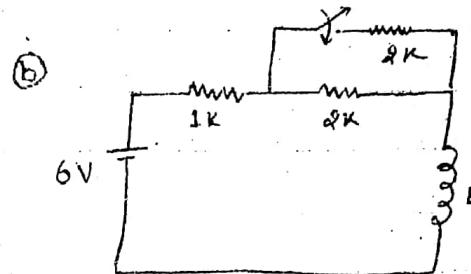
$$v_C(\infty) = 1\text{V} \quad i(\infty) = 0$$




$$v_L(0^-) = 0 \quad i_L(0^-) = 2\text{mA}$$

$$v_L(0^+) = 2\text{V} \quad i_L(0^+) = 2\text{mA}$$

$$v_L(\infty) = 0 \quad i_L(\infty) = 3\text{mA}$$

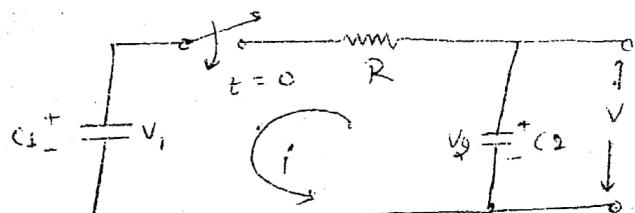- (c) In the given circuit C_1 has initial voltage v_1 and C_2 has initial voltage v_2 . At time $t=0$, switch K is closed. Find the expression for voltage 'v' across capacitor C_2 at $t > 0$.



Soln: For $t > 0$, apply KV2

$$v_{C_1} + v_R + v_{C_2} = 0$$

$$\text{or, } \frac{1}{C_1} \int_{-\infty}^t i dt + iR + v = 0 \Rightarrow \frac{1}{C_1} \int_{-\infty}^0 i dt + \frac{1}{C_1} \int_0^t i dt + iR + v = 0$$

$$\text{or, } -v_1 + \frac{1}{C_1} \int_0^t i dt + iR + v = 0 \quad \dots \textcircled{1}$$

$$\text{Since, } i = C_2 \frac{dv}{dt} \quad \text{and when } t=0, v=v_2 \quad \dots \textcircled{2}$$

$$t \rightarrow t, v = V$$

from $\textcircled{1}$ and $\textcircled{2}$

$$\text{or}, -V_1 + \frac{C_2}{C_1} \int_{V_2}^V dV + R C_2 \frac{dV}{dt} + V = 0$$

$$\text{or}, -V_1 + \frac{C_2}{C_1} [V - V_2] + R C_2 \frac{dV}{dt} + V = 0 \quad \text{--- (11)}$$

$$\text{or}, R C_2 \frac{dV}{dt} + V + \frac{C_2}{C_1} V = V_1 + \frac{C_2}{C_1} V_2$$

$$\text{or}, R C_1 C_2 \frac{dV}{dt} + C_1 V + C_2 V = C_1 V_1 + C_2 V_2$$

Since source is constant, force response is obtained by placing $P=0$ i.e. $\frac{dV}{dt}=0$

$$\text{or}, (C_1 + C_2) V_f = C_1 V_1 + C_2 V_2$$

$$V_f = \frac{C_1 V_1 + C_2 V_2}{C_1 + C_2} \quad \text{--- (12)}$$

To find transient response, corresponding homogeneous equation is,

$$R C_2 C_1 \frac{dV}{dt} + (C_1 + C_2) V = 0$$

$$\text{or}, R C_2 C_1 s + (C_1 + C_2) = 0$$

Let, $V = K e^{st}$ be the form of solution

$$R C_2 C_1 \frac{d(K e^{st})}{dt} + (C_1 + C_2) K e^{st} = 0$$

$$\text{or}, R C_2 C_1 s K e^{st} + (C_1 + C_2) K e^{st} = 0$$

$$\text{or}, K e^{st} (R C_2 C_1 s + (C_1 + C_2)) = 0$$

Since, $K e^{st} \neq 0$

$$\text{so}, R C_2 C_1 s + (C_1 + C_2) = 0$$

$$\therefore V_f(t) = K e^{-\left(\frac{C_1 + C_2}{R C_1 C_2}\right)t}$$

The complete voltage response is given by,

$$V_t = V_p(t) + V_f(t)$$

$$\text{i.e. } V_t = \frac{C_1 V_1 + C_2 V_2 + K e^{-\left(\frac{C_1 + C_2}{R C_1 C_2}\right)t}}{C_1 + C_2}$$

using initial condition,

$$\text{for } V(0^+) \text{ at } t = 0^+ \quad V(0^+) = V_2 \text{ so, } V(0^+) = V_2$$

[Since Voltage across capacitor can not change instantaneously]

$$\text{so, } V(0^+) = \frac{C_1 V_1 + C_2 V_2 + K e^{-\left(\frac{C_1 + C_2}{R C_1 C_2}\right)(0^+)}}{C_1 + C_2}$$


$$\text{or, } V_2 = \frac{C_1 V_1 + C_2 V_2 + K}{C_1 + C_2}$$

$$\text{or, } K = \frac{C_1 V_2 + C_2 V_2 - C_1 V_1 - C_2 V_1}{C_1 + C_2} = \frac{C_1 (V_2 - V_1)}{C_1 + C_2}$$

Total solution is

$$V(t) = \frac{C_1 V_1 + C_2 V_2}{C_1 + C_2} + \frac{C_1 (V_2 - V_1)}{C_1 + C_2} e^{-\left(\frac{C_1 + C_2}{R C_1 C_2}\right)t}$$

Q.1

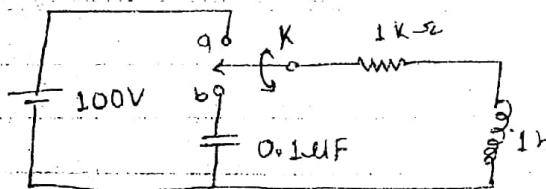


At $t = 0^-$

Initially switch is at position 'a'

The steady state value of current,
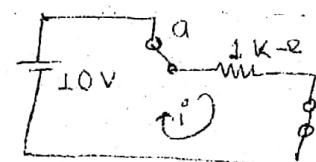
$$i(0^-) = \frac{100}{1000} = 0.1 \text{ A}$$



$i(0^+) = i(0^-) = 0.1 \text{ A}$ [∴ Current through Inductor can not change instantaneously]

For $t > 0$, apply KVL

$$1000 i(t) + \frac{di(t)}{dt} + \frac{1}{0.1 \times 10^{-6}} \int_{-\infty}^t i(t') dt = 0 \quad \text{--- (1)}$$

Equivalent circuit for $t > 0$

$$\text{or}, 1000 i(t) + \frac{di(t)}{dt} + V_c(t) = 0$$

At $t = 0^+$

$$1000 i(0^+) + \frac{di(0^+)}{dt} + V_c(0^+) = 0$$

$$\frac{di(0^+)}{dt} = -100 \text{ amp/sec.}$$

[∴ $V_c(0^-) = 0 = V_c(0^+)$ since voltage across capacitor can not change instantaneously]

Now, differentiating Equation (1), we get

$$1000 \frac{di(t)}{dt} + \frac{d^2i(t)}{dt^2} + \frac{1}{0.1 \times 10^{-6}} i(t) = 0$$


at $t = 0^+$

$$1000 \frac{d^2i(0^+)}{dt^2} + \frac{d^2i(0^+)}{dt^2} + \frac{i(0^+)}{0.1 \times 10^{-6}} = 0$$

$$\frac{di(0^+)}{dt} = -10^6 + 10^5 = -9 \times 10^5 \text{ Amp/sec}^2$$

Thus,
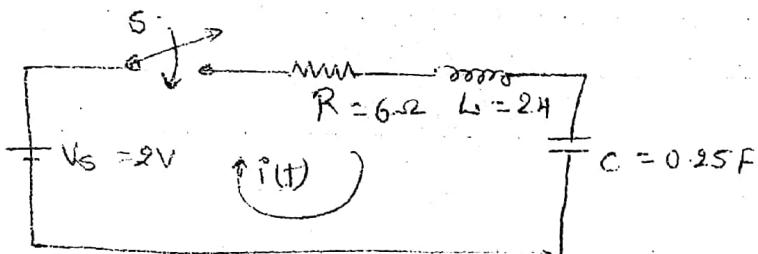
$$i(0^+) = 0 \text{ Amp}, \frac{di(0^+)}{dt} = -100 \text{ amp/sec} \& \frac{d^2i(0^+)}{dt^2} = -9 \times 10^5 \text{ Amp/sec}^2$$



At $t = 0^-$

$$i(0^-) = 0 \text{ and } V_C(0^-) = 0$$

so, $i(0^+) = i(0^-) = 0$ [∴ Current through inductor can not change instantaneously]

and, $V_C(0^+) = V_C(0^-) = 0$ [∴ Voltage across capacitor can not change instantaneously]

Now, Apply KVL for $t > 0$

$$\delta V = 6i(t) + \frac{1}{2} \frac{di(t)}{dt} + \frac{1}{0.25} \int_0^t i(t) dt \quad \text{①}$$

At, $t = 0^+$

$$\delta = 6i(0^+) + \frac{1}{2} \frac{di(0^+)}{dt} + \frac{1}{0.25} \int_0^{0^+} i(t) dt \quad \left[\because V_C = \frac{1}{2} \int_0^t i(t) dt \right]$$

$$\delta = 6 \times 0 + \frac{1}{2} \frac{di(0^+)}{dt} + V_C(0^+) \rightarrow 0$$

$$\frac{di(0^+)}{dt} = 1 \text{ amp/sec.}$$

Now, Differentiating equation ① w.r.t to t ,

at, $t = 0^+$

$$0 = 6 \frac{di(0^+)}{dt} + 2 \frac{d^2i(0^+)}{dt^2} + \frac{i(0^+)}{0.25}$$


$$\Rightarrow 0 = 6 \times 1 + 2 \frac{d^2i(0^+)}{dt^2}$$

$$\text{or, } \frac{d^2i(0^+)}{dt^2} = -\frac{6}{2} = -3 \text{ amp/sec}^2$$

Thus,


$$i(0^+) = 0, \frac{di(0^+)}{dt} = 1 \text{ A/sec}, \frac{d^2i(0^+)}{dt^2} = -3 \text{ A/sec}^2$$

Q.3

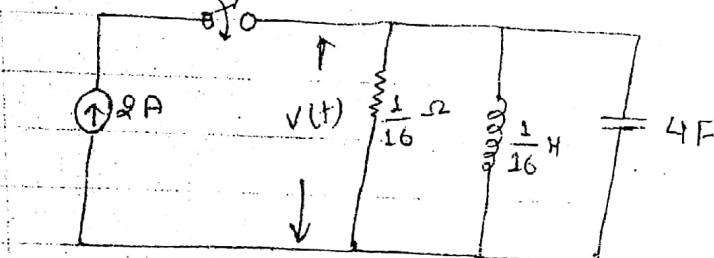


Here, at, $t = 0^-$ switch is opened. $i_R(0) = 0, i_L(0) = 0, i_C(0) = 0$

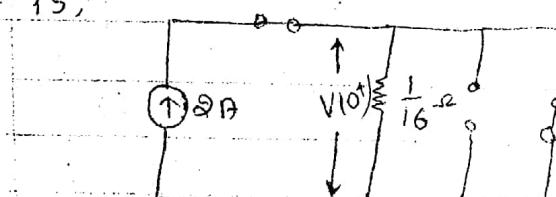at, $t = 0^+$, switch is closed and equivalent circuit is



$V(0^+) = 0$ and, $i_L(0^+) = 0$ [\because Current through inductor can not change instantaneously]

At $t > 0$, equivalent circuit is

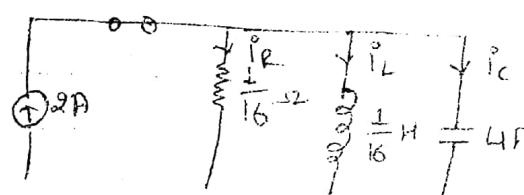

Now, using KCL

$$\phi^0 = i_R + i_L + i_C$$

at, t = 0⁺

$$\alpha = 16 \frac{V(0^+)}{E_0} + 4 \frac{dV(0^+)}{dt} + i_L(0^+)$$

$$\phi = 0 + \frac{4dv(0^+)}{dt} + \dots$$

$$\therefore \frac{dv(0^+)}{dt} = \frac{1}{\alpha^0} \text{ V/sec.}$$

Now, Differentiating equation ① w.r.t t

$$0 = \frac{4c d V(t)}{\pi R^2} + 4 \frac{d^2 V(t)}{dt^2} + \frac{dV}{dt}$$

$$0 = \frac{16}{55} \frac{dV(t)}{dt} + 4 \frac{d^2V(t)}{dt^2} + \frac{VL}{L} \quad \left[\because i_L = \frac{1}{L} \int V_L dt \right]$$

at, t = 0+


$$0 = \frac{16}{60} \frac{dv(0t)}{dt} + 4 \frac{d^2v(0t)}{dt^2} + \frac{v_L(0t)}{L}$$

$$0 = \frac{16}{48} \times \frac{1}{2} + 4 \frac{d^2 v(0^+)}{dt^2} + 0 \quad [v_L(0^+) = v(0^+)]$$


$$\therefore \frac{d^2 v(0+)}{dt^2} = -2 \cdot v / \sec^2$$

Thus,
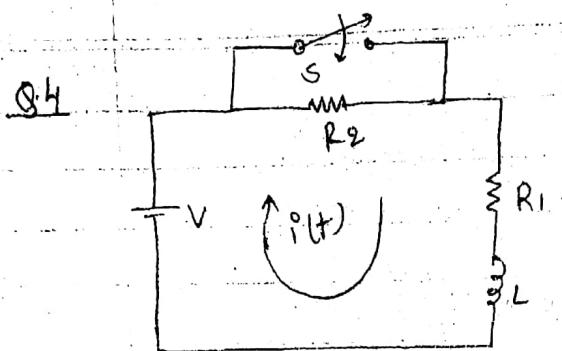
$$\therefore V(0^+) = 0 \quad \frac{dv(0^+)}{dt} = \frac{1}{2} V \text{ l/sec.} \quad \text{and} \quad \frac{d^2v(0^+)}{dt^2} = -2V \text{ l/sec.}^2$$



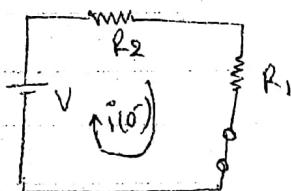At, $t = 0^-$, steady state is reached. Equivalent circuit is,



$$i(0^+) = \frac{V}{R_1 + R_2}$$

and,

$$i(0^+) = i(0^-) = \frac{V}{R_1 + R_2} \quad [\because \text{current through inductor can not change instantaneously}]$$

for $t > 0$, equivalent circuit is,


$$V = R_1 i(t) + L \frac{di(t)}{dt} \quad \dots \textcircled{1}$$

In p-operator form

$$V = R_1 i(t) + L P i(t)$$

$$i(t) = \frac{V}{R_1 + LP} \quad \dots \textcircled{2}$$

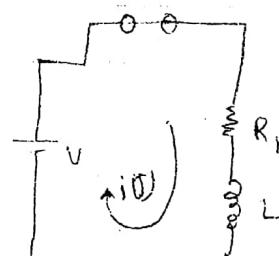Here, equation $\textcircled{1}$ is non-homogeneous equation. It contains two parts of solution.



$$i(t) = \frac{V}{R_1 + Lp}$$

Here, source is constant so put $p=0$ for forced response

$$i_f(t) = \frac{V}{R_1}$$

② Transient solution

Homogeneous version of equation ① is,

$$R_1 i(t) + L \frac{di(t)}{dt} = 0$$

Characteristic equation is, $R_1 + LS = 0$

$$\Rightarrow S = -\frac{R_1}{L}$$

∴ Transient solution, $i_t(t) = Ke^{St} = Ke^{-\frac{R_1}{L}t}$

Total solution $i(t) = i_f(t) + i_t(t)$

$$= Ke^{-\frac{R_1}{L}t} + \frac{V}{R_1}$$

Now, to find value of K , use initial conditions

$$i(0^+) = K + \frac{V}{R_1}$$


$$\frac{V}{R_1 + R_2} - \frac{V}{R_1} = K \Rightarrow K = \frac{VR_1 - VR_1 - VR_2}{R_1(R_1 + R_2)} = -\frac{VR_2}{R_1(R_1 + R_2)}$$

Now,

$$P(t) = \frac{V}{R_1} - \frac{V}{R_1} \left(\frac{R_2}{R_1 + R_2} \right) e^{-\frac{R_1}{L}t}$$

$$i(t) = \frac{V}{R_1} \left[1 - \frac{R_2}{R_1 + R_2} e^{-\frac{R_1}{L}t} \right]$$

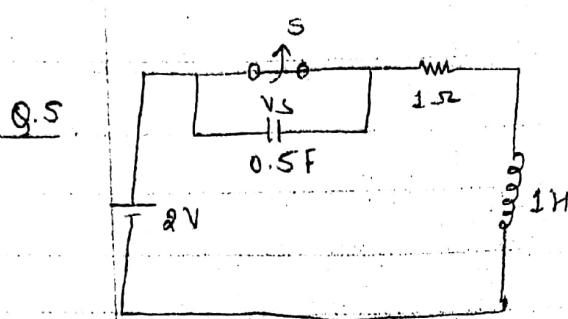
This is the required expression for $i(t)$



At, $t=0^-$, steady state is reached. Equivalent circuit is,

$$i(0^-) = \frac{2}{1} = 2 \text{ A}$$
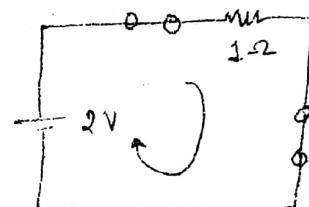
$$\therefore i(0^+) = i(0^-) = 2 \text{ A} \quad [\because \text{Current through inductor can not change instantaneously}]$$



Circuit is in steady state with

When, \wedge Switch is closed, Capacitor is short circuited so,

$$v_s(0^+) = 0$$

$\therefore v_s(0^+) = v_s(0^-) = 0$ [Voltage across capacitor can not change instantaneously]

Now, at $t > 0$, equivalent circuit is,


$$v_s(t) = \frac{1}{C} \int i(t) dt$$

$$\text{or } i(t) = C \frac{dv_s(t)}{dt}$$

at, $t=0^+$

$$i(0^+) = 0.5 \frac{dv_s(0^+)}{dt}$$


$$2 = \frac{dv_s(0^+)}{dt}$$

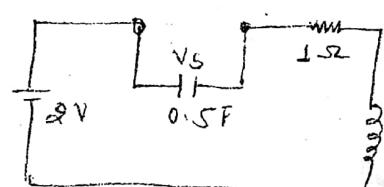

$$2 = \frac{1}{0.5} \int i(t) dt + (2) + \frac{dv_s(t)}{dt}$$

$$2 = i(t) + \frac{dv_s(t)}{dt}$$
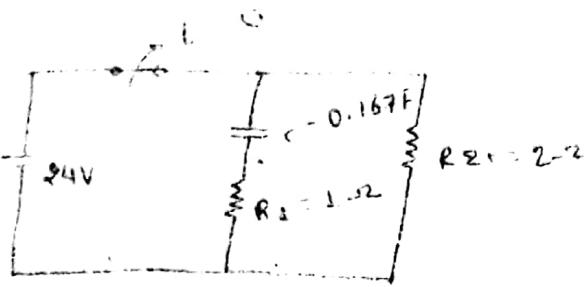
$$\therefore \frac{dv_s(t)}{dt} = 4 \text{ V/sec.}$$



Since At steady state capacitor behaves as an open circuit
(i.e capacitor is fully charged)

so,

$$V_c(0^-) = 24V$$

$\therefore V_c(0^+) = V_c(0^-) = 24$ [: Voltage across capacitor can not change instantaneously]

At, $t > 0$, Apply KVL

$$V_c = V_{R_1} + V_{R_2}$$


$$V_c = i(t) R_1 + i(t) R_2$$

$$\text{or, } i(t) = \frac{V_c}{R_1 + R_2}$$

at, $t = 0^+$


$$i(0^+) = \frac{V_c(0^+)}{1+2} = \frac{24}{3} = 8 \text{ amp.}$$

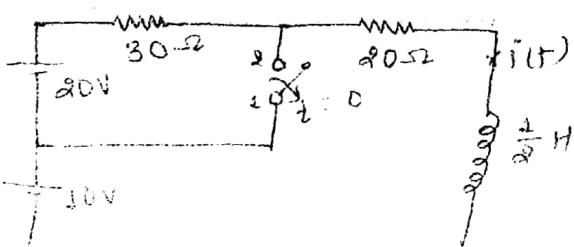$\therefore V_c(0^-) = 24V, V_c(0^+) = 24V \text{ and } i(0^+) = 8 \text{ Amp.}$



At position t , steady state is reached. Equivalent circuit:
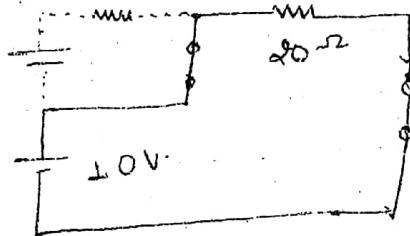
$$i(0^-) = \frac{10}{30} \cdot \frac{10}{20} = 0.5 \text{ amp}$$



$\therefore i(0^+) = i(0^-) = 0.5 \text{ amp}$ [current through inductor can not change instantaneously].

At, $t > 0$, apply KVL

$$30 = 50i(t) + \frac{1}{2} \frac{di(t)}{dt} \quad \dots \dots \dots \textcircled{1}$$

Equation ① is non-homogeneous equation. It contains two parts of solution.

① Forced solution

Equation ① in p-operator form

$$30 = 50i(t) + \frac{1}{2} pi(t)$$

$$\text{or, } i(t) = \frac{30}{50 + \frac{1}{2} p}$$

Here, source is constant so put $p=0$ to find forced response,

$$i_f(t) = \frac{30}{50} = 0.6 \text{ amp.}$$

② Transient solution

Homogeneous version of equation ① is,

$$\frac{1}{2} \frac{di(t)}{dt} + 50i(t) = 0$$

∴ Transient solution, $i_t(t) = Ke^{st} = Ke^{-100t}$

$$\begin{aligned}\text{Total solution, } i(t) &= i_f(t) + i_t(t) \\ &= 0.6 + Ke^{-100t}\end{aligned}$$


at, $t = 0^+$

$$i(0^+) = 0.6 + K$$

$$0.5 = 0.6 + K$$

$$K = -0.1$$

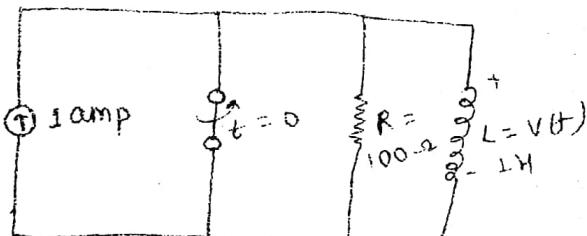
∴ Total solution, $\boxed{i(t) = 0.6 - 0.1 e^{-100t}}$



At, $t = 0^+$,

Equivalent circuit is,

$$V(0^+) = IR = 100 \text{ V.}$$

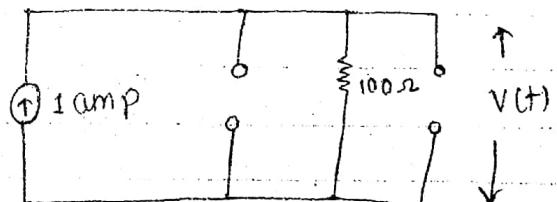

At $t > 0$, Apply KCL

$$I = i_R + i_L$$

$$\text{or, } I = \frac{V(t)}{R} + \frac{1}{L} \int V(t) dt \quad \dots \textcircled{1}$$

Differentiating w.r.t. t , we get

$$0 = \frac{1}{L} \frac{dV(t)}{dt} + V(t) \quad \dots \textcircled{2}$$

at, $t = 0^+$

$$0 = \frac{1}{100} \frac{dV(0^+)}{dt} + V(0^+)$$

$$\text{or, } \frac{dV(0^+)}{dt} = -100 \times 100 = -10^4 \text{ V/sec.}$$

Differentiating eq. ② w.r.t. t , we get

$$0 = \frac{1}{100} \frac{d^2V(t)}{dt^2} + \frac{dV(t)}{dt}$$

at, $t = 0^+$

$$0 = \frac{1}{100} \frac{d^2V(0^+)}{dt^2} + \frac{dV(0^+)}{dt}$$

$$\text{or, } \frac{d^2V(0^+)}{dt^2} = -(-10^4) \times 100 = 10^6 \text{ V/sec}^2$$

$$\text{Thus, } V(0^+) = 100 \text{ V}, \frac{dV(0^+)}{dt} = -10^4 \text{ V/sec. and } \frac{d^2V(0^+)}{dt^2} = 10^6 \text{ V/sec}^2$$

Here, equation ② is homogeneous equation. So, its forced response will be zero i.e. $V_f(t) = 0$

For transient solution:

Characteristic equation is,

$$\frac{1}{100} s + 1 = 0$$


$$s = -100$$

$$\therefore \text{Transient solution, } V_t(t) = K e^{st} = K e^{-100t}$$

$$\therefore \text{Total solution, } V(t) = V_f(t) + V_t(t) \\ = K e^{-100t}$$

To find value of K , use initial conditions,
at $t = 0^+$
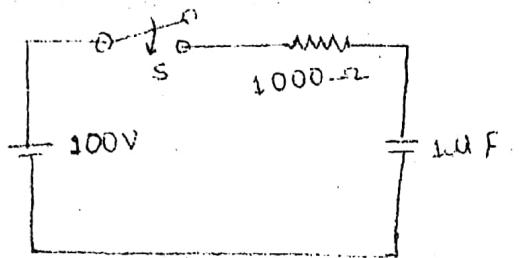
$$\therefore \text{At } t = 0^+, V(0^+) = 100 \text{ V} \quad \boxed{V(0^+) = 100 e^{-100t}}$$



At. $t = 0^-$

$$V_c(0^-) = 0$$

$\therefore V_c(0^+) = V_c(0^-) = 0$ [Voltage across capacitor can not change instantaneously].

Apply KVL for $t > 0$, we get


$$100V = 1000 i(t) + \frac{1}{10^6} \int i(t) dt \quad \textcircled{1}$$

Differentiating w.r.t. t , we get

$$0 = 1000 \frac{di(t)}{dt} + \frac{i(t)}{10^6} \quad \textcircled{2}$$

At. $t = 0^+$, Equivalent circuit is,
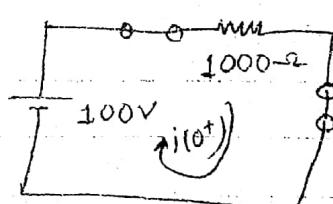
$$i(0^+) = \frac{100}{1000} = 0.1 \text{ Amp.}$$



Now, equation $\textcircled{2}$ at, $t = 0^+$

$$0 = 1000 \frac{di(0^+)}{dt} + i(0^+) \times 10^6$$

$$\text{or, } \frac{di(0^+)}{dt} = -\frac{0.1 \times 10^6}{1000} = -100 \text{ amp/sec.}$$

Differentiating eqⁿ. $\textcircled{2}$ w.r.t. t , we get

$$0 = 1000 \frac{d^2 i(t)}{dt^2} + 10^6 \frac{di(t)}{dt}$$


at, $t = 0^+$

$$0 = 1000 \frac{d^2 i(0^+)}{dt^2} + 10^6 \frac{di(0^+)}{dt}$$

$$\text{or, } \frac{d^2 i(0^+)}{dt^2} = -\frac{10^6 \times (-100)}{1000} = 10^5 \text{ amp/sec.}^2$$

$\therefore i(0^+) = 0$. \perp Amp, $\frac{di(0^+)}{dt} = -100$ Amp/sec. and $\frac{d^2 i(0^+)}{dt^2} = 10^5$ amp/sec.

Q.10

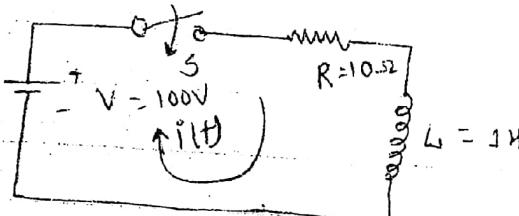

At, $t = 0^-$

$$i(0^-) = 0$$

$i(0^+) = i(0^-) = 0$ [Current through inductor can not change instantaneously]

Apply KVL for $t > 0$

$$V = R i(t) + L \frac{di(t)}{dt}$$

$$\text{or, } 100 = 10i(t) + 1 \frac{di(t)}{dt} \quad \dots \dots \dots \textcircled{1}$$

at, $t = 0^+$

$$100 = 10i(0^+) + \frac{di(0^+)}{dt}$$

$$\therefore \frac{di(0^+)}{dt} = 100 \text{ Amp/sec.}$$


Differentiating $\textcircled{1}$ w.r.t t +

$$0 = 10 \frac{di(t)}{dt} + \frac{d^2 i(t)}{dt^2}$$

Name : _____


$i(0) = 0$, $\frac{di(0)}{dt} = 100 \text{ Amp/sec}$ and $\frac{d^2i(0)}{dt^2} = -1000 \text{ Amp/sec}^2$

3.11.

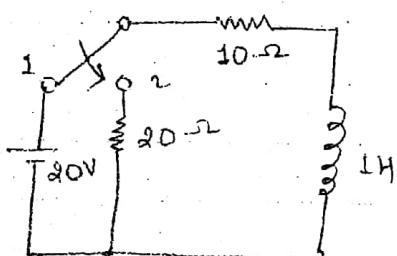

At, $t = 0$, steady state is reached. Equivalent circuit is,

$$i(0) = \frac{20V}{10^{-2}} = 2A$$

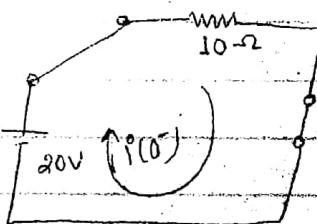

$$\therefore i(0^+) = i(0^-) = 2A$$

(Current through inductor can not change instantaneously)

Now, Apply KVL at $t > 0$, we get

$$30i(t) + 10i(t) + \frac{di(t)}{dt} = 0$$

$$\text{or, } 30i(t) + \frac{di(t)}{dt} = 0 \quad \textcircled{1}$$

at, $t = 0^+$

$$30i(0^+) + \frac{di(0^+)}{dt} = 0$$

$$\frac{di(0^+)}{dt} = -30 \times 2 = -60 \text{ Amp/sec}$$

Now, Differentiating equation $\textcircled{1}$ w.r.t t , we get

$$30 \frac{di(t)}{dt} + \frac{d^2i(t)}{dt^2} = 0$$


at, $t = 0^+$

$$30 \frac{di(0^+)}{dt} + \frac{d^2i(0^+)}{dt^2} = 0$$

$$\frac{d^2i(0^+)}{dt^2} = -30 \times -60 = 1800 \text{ Amp/sec}^2$$

$$\therefore i(0^+) = 2 \text{ Amp}, \frac{di(0^+)}{dt} = -60 \text{ Amp/sec} \text{ and } \frac{d^2i(0^+)}{dt^2} = 1800 \text{ Amp/sec}^2$$


Q.12

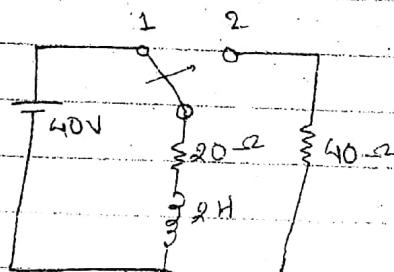

At, $t = 0^-$ Steady state is reached. Equivalent circuit.

$$i(0^-) = \frac{40V}{20\Omega} = 2 \text{ Amp}$$
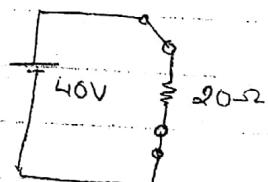
$$\therefore i(0^+) = i(0^-) = 2 \text{ Amp}$$



[Current through inductor can not change instantaneously.]

Now, apply KVL at $t > 0$, we get

$$20i(t) + 40i(t) + 2 \frac{di(t)}{dt} = 0$$

$$60i(t) + \frac{d}{dt} i(t) = 0 \quad \textcircled{1}$$

at, $t = 0^+$

$$60i(0^+) + \frac{d}{dt} i(0^+) = 0$$

$$\frac{d}{dt} i(0^+) = -60 \times 2 = -120$$

$$\therefore \frac{di(0^+)}{dt} = -60 \text{ Amp/sec.}$$

Now, Differentiating equation ① w.r.t t,

$$60\frac{di(t)}{dt} + \frac{d^2i(t)}{dt^2} = 0$$


at, $t = 0^+$

$$60\frac{di(0^+)}{dt} + \frac{d^2i(0^+)}{dt^2} = 0$$

$$\frac{d^2i(0^+)}{dt^2} = -60 \times (-60) = 3600$$

$$\therefore \frac{d^2i(0^+)}{dt^2} = 1800 \text{ Amp/sec}^2$$

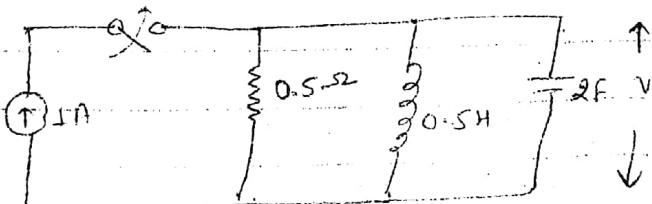$i(0^+) = 2 \text{ Amp}$, $\frac{di(0^+)}{dt} = -60 \text{ Amp/sec}$ and $\frac{d^2i(0^+)}{dt^2} = 1800 \text{ amp/sec}^2$




Here, at, $t = 0^-$ switch is opened so, $i_R(0^-) = 0$, $i_L(0^-) = 0$ and $i_C(0^-) = 0$

$i_L(0^+) = i_L(0^-) = 0$ [∴ Current through inductor can not change instantaneously.]


at, $t = 0^+$. Equivalent circuit

$$V(0^+) = 0.$$

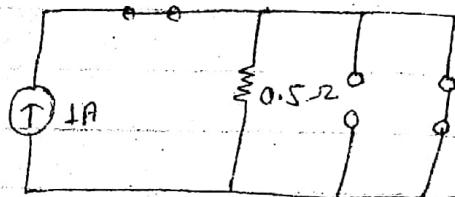

Now, at $t > 0$, Equivalent circuit

Apply KCL, we have

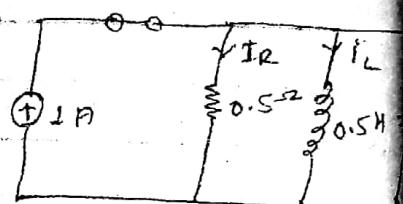

$$I = i_R + i_L + i_C$$

$$\text{or, } I = \frac{V(t)}{R} + i_L + \frac{CdV(t)}{dt} \quad \text{①}$$

$$\text{or, } I = \frac{V(t)}{R} + \frac{1}{L} \int V(t) dt + \frac{CdV(t)}{dt} \quad \text{②}$$

Now,

at, $t = 0^+$ equation ① becomes

$$I = \frac{V(0^+)}{0.5} + i_L(0^+) + \frac{2}{0.5} \frac{dV(0^+)}{dt}$$

$$I = 0 + 0 + 2 \frac{dV(0^+)}{dt}$$

$$\frac{dV(0^+)}{dt} = \frac{1}{2} \frac{V}{\cancel{0.5}} \text{ V/sec.}$$

Now, Differentiating equation ② w.r.t t we get

No. 3

Time : _____

Suggested by _____

$$L \cdot \frac{dV(t)}{dt} + \frac{V(t)}{R} + C \frac{d^2V(t)}{dt^2}$$

at, $t = 0^+$


$$0 = \frac{1}{0.5} \frac{dV(0^+)}{dt} + \frac{V(0^+)}{0.5} + 2 \frac{d^2V(0^+)}{dt^2}$$

$$\text{or, } 0 = 2 \times \frac{1}{2} + 0 + 2 \frac{d^2V(0^+)}{dt^2}$$

$$\text{or, } \frac{d^2V(0^+)}{dt^2} = -\frac{1}{2} \text{ Volt/sec}^2$$

$\therefore V(0^+) = 0$, $\frac{dV(0^+)}{dt} = \frac{1}{2} \text{ Volt/sec}$ and, $\frac{d^2V(0^+)}{dt^2} = -\frac{1}{2} \text{ V/sec}^2$

Q. 14

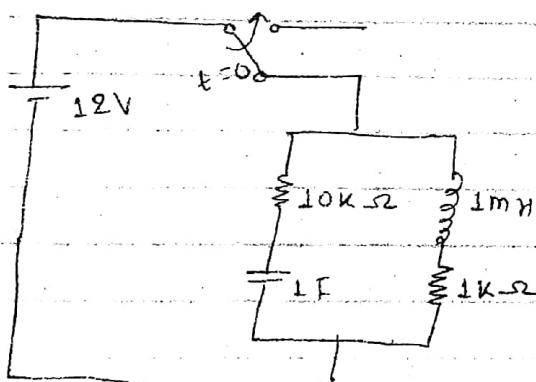


At $t = 0^+$, steady state is reached. Equivalent circuit is

$$i(0^-) = \frac{12V}{1k\Omega} = 0.012 \text{ Amp}$$

$$= 0.012 \text{ Amp.}$$

$$i(0^+) = i(0^-) = 0.012 \text{ Amp}$$

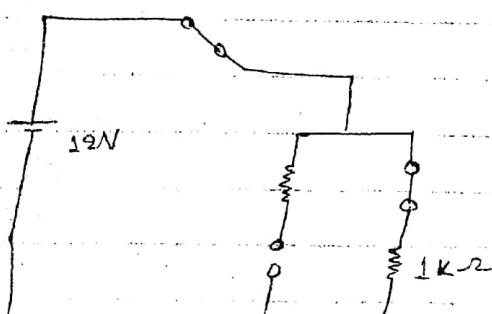[\because Current through inductor
can not change instantaneously.]



$V_c(0) = 12V \Rightarrow V_c(0^+) \quad (\because \text{Voltage across capacitor can not change instantaneously})$

Apply KVL for $t > 0$, we get:

$$10k i(t) + 1m \frac{di(t)}{dt} + 1k i(t) + \frac{1}{2} \int i(t) dt = 0$$

$$11,000 i(t) + 10^{-3} \frac{di(t)}{dt} + \int i(t) dt = 0 \quad \dots \textcircled{1}$$

$$11,000 i(t) + 10^{-3} \frac{di(t)}{dt} - V_c = 0 \quad \dots \textcircled{2}$$

$$\text{at, } t = 0^+$$

$$11,000 i(0^+) + 10^{-3} \frac{di(0^+)}{dt} - V_c(0^+) = 0$$

$$11,000 \times 0.012 + 10^{-3} \frac{di(0^+)}{dt} - 12 = 0$$

$$11 \times 12 + 10^{-3} \frac{di(0^+)}{dt} = 12$$

$$\frac{di(0^+)}{dt} = \frac{-12 - 132}{10^{-3}} = -\frac{120}{10^{-3}} \text{ amp/sec.}$$

Differentiating eq $\textcircled{1}$ w.r.t t

$$11,000 \frac{di(t)}{dt} + 10^{-3} \frac{d^2 i(t)}{dt^2} + i(t) = 0$$

$$\text{at, } t = 0^+$$

$$11,000 \frac{di(0^+)}{dt} + 10^{-3} \frac{d^2 i(0^+)}{dt^2} + i(0^+) = 0$$

$$\therefore 11,000 \times (-\frac{120}{10^{-3}}) + 10^{-3} \frac{d^2 i(0^+)}{dt^2} + 0.012 = 0$$


$$\frac{d^2i(0^+)}{dt^2} = \frac{13.2}{10^{-3}} + 0.012$$

$$= 132 \times 10^3 \text{ amp/sec}^2$$

$$= 132 \times 10^{10}$$


$$i(0^+) = 0.012 \text{ amp}, \frac{di(0^+)}{dt} = -132 \times 10^3 \text{ amp/sec}$$

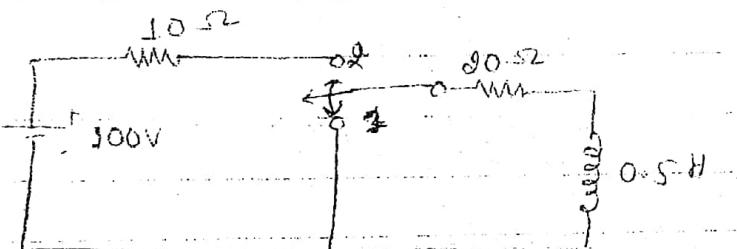and, $\frac{d^2i(0^+)}{dt^2} = \frac{132 \times 10^9}{132 \times 10^{10}}$ amp/sec²



at, $t = 0^+$, steady state is reached at position ②
equivalent circuit is,
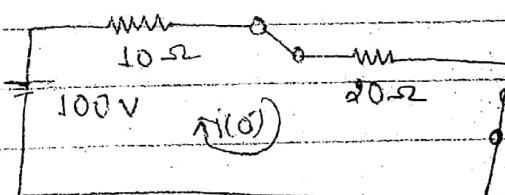
$$\therefore i(0) = \frac{100V}{10+20} = \frac{10}{3} \text{ amp.}$$



$$i(0^+) = i(0^-) = \frac{10}{3} \text{ Amp} \quad [\because \text{Current through inductor can not change instantaneously.}]$$

Apply KVL at $t > 0$.

$$20i(t) + 0.5 \frac{di(t)}{dt} = 0 \quad \dots \dots \textcircled{1}$$

at, $t = 0^+$

$$20i(0^+) + 0.5 \frac{di(0^+)}{dt} = 0$$

$$\frac{20 \times 10}{3} + 0.5 \frac{di(0^+)}{dt} = 0$$

$$\frac{di(0^+)}{dt} = -\frac{200}{3} = -\frac{400}{3} \text{ amp/sec.}$$

Differentiating eq. ① w.r.t. t , we get

$$20 \frac{di(t)}{dt} + 0.5 \frac{d^2i(t)}{dt^2} = 0$$

$$\text{at } t = 0^+$$

$$\frac{20 di(0^+)}{dt} + 0.5 \frac{d^2i(0^+)}{dt^2} = 0$$

$$0.5 \frac{d^2i(0^+)}{dt^2} = -20 \times -\frac{400}{3} = \frac{800}{3}$$

$$\therefore \frac{d^2i(0^+)}{dt^2} = \frac{1600}{3} \text{ amp/sec}^2$$

$$\therefore i(0^+) = \frac{10}{3} \text{ amp.} \quad \frac{di(0^+)}{dt} = -\frac{1600}{3} \text{ amp/sec.}$$


$$\text{and } \frac{d^2i(0^+)}{dt^2} = \frac{1600}{3} \text{ amp/sec}^2.$$

11.

Solution (Assignment 2) Ch.3

①

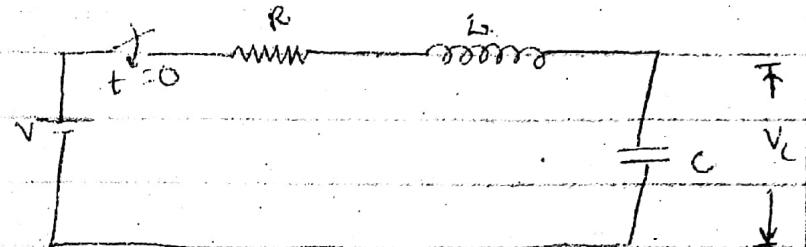Q.1 Here, $R = 7\Omega$, $L = 1H$ and $C = 0.1F$
 $V = 20V$



Initially, $i_L(0^-) = 0 = i_L(0^+)$ [Current through inductor can not change instantaneously.]

$V_C(0^-) = 0 = V_C(0^+)$ [Voltage across capacitor can not change instantaneously.]

Now, at $t > 0$, Using KVL

$$V = Ri + L \frac{di}{dt} + \frac{1}{C} \int idt \quad ①$$

$$20 = 7i + \frac{di}{dt} + 10 \int_{-\infty}^t idt \quad ①$$

$$20 = 7i + \frac{di}{dt} + 10 \int_{-\infty}^0 idt + 10 \int_0^t idt$$

$$20 = 7i + \frac{di}{dt} + 10 \int_0^t idt$$

Differentiating with respect to t

$$0 = 7 \frac{di}{dt} + \frac{d^2i}{dt^2} + 10i$$

$$\frac{d^2i}{dt^2} + 7 \frac{di}{dt} + 10i = 0 \quad ②$$

Equation ② is homogeneous second order differential

↗

2.

equation. so, forced response becomes zero.

$$\text{Thus, } i(t) = i_f(t) + i_t(t)$$

$$= i_t(t)$$

Now, for transient response $i_t(t)$:

characteristic equation is, $s^2 + 7s + 10 = 0$

$$s_1, s_2 = \frac{-7 \pm \sqrt{49 - 40}}{2}$$

$$= \frac{-7 \pm 3}{2} = -2, -5$$

$$\text{Thus, } i_t(t) = K_1 e^{st} + K_2 e^{-st}$$
$$= K_1 e^{-2t} + K_2 e^{-5t}$$

③

Now, Using initial condition at $t = 0^+$

$$i(0^+) = K_1 e^0 + K_2 e^0 \Rightarrow 0 = K_1 + K_2$$

$$\therefore K_1 = -K_2$$

Now, Equation ① at $t = 0^+$

$$20 = 7i(0^+) + \frac{di(0^+)}{dt} + v_c(0^+)$$

$$\underline{\frac{di(0^+)}{dt}} = 20$$

Differentiating eq. ③ we get

$$\frac{di(t)}{dt} = -2K_1 e^{-2t} - 5K_2 e^{-5t}$$

at $t = 0^+$

$$\underline{\frac{di(0^+)}{dt}} = -2K_1 e^0 - 5K_2 e^0$$

$$\Delta O = -2K_1 - 5K_2$$

$$\text{or, } \Delta O = -2K_1 + 5K_1$$

$$\therefore K_1 = \frac{\Delta O}{3} \quad \text{and, } K_2 = -\frac{\Delta O}{3}$$

$$\text{Thus, } q(t) = \frac{\Delta O}{3} e^{-2t} - \frac{\Delta O}{3} e^{-5t}$$

$$\therefore V_C(t) = \frac{1}{C} \int_{-\infty}^t i(t) dt$$

$$= \frac{1}{C} \int_{-\infty}^0 i(t) dt + \frac{1}{C} \int_0^t i(t) dt$$

$$= \frac{1}{C} \int_0^t \left[\frac{\Delta O}{3} e^{-2t} - \frac{\Delta O}{3} e^{-5t} \right] dt$$

$$= 10 \left\{ \frac{\Delta O}{3} \left[\frac{e^{-2t}}{-2} \right]_0^t - \frac{\Delta O}{3} \left[\frac{e^{-5t}}{-5} \right]_0^t \right\}$$


$$= \frac{200}{3} \left\{ \frac{e^{-2t} - 1}{-2} \right\} - \frac{200}{3} \left\{ \frac{e^{-5t} - 1}{-5} \right\}$$

$$= -\frac{200}{3} e^{-2t} + \frac{100}{3} + \frac{40}{3} e^{-5t} - \frac{40}{3}$$


$$= -\frac{100}{3} e^{-2t} + \frac{40}{3} e^{-5t} + 20$$

$$\therefore V_C(t) = -\frac{100}{3} e^{-2t} + \frac{40}{3} e^{-5t} + 20$$

Q.2 Give circuit is,

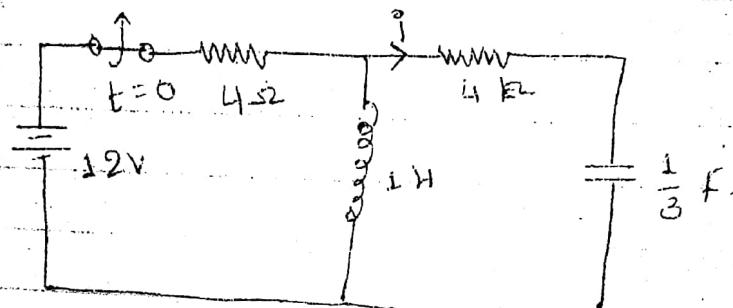

At, $t = 0^-$ equivalent circuit is,

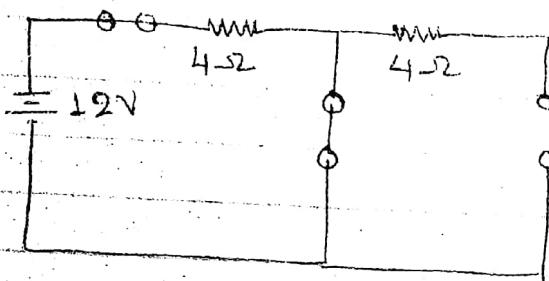


$$i(0^-) = \frac{12V}{4\Omega} = 3A$$

$i(0^+) = i(0^-) = 3A$ (\because current through inductor can not change instantaneously.)

$V_C(0^-) = 0 = V_C(0^+)$ (\because Voltage across capacitor can change instantaneously.)

At $t > 0$, equivalent circuit is,

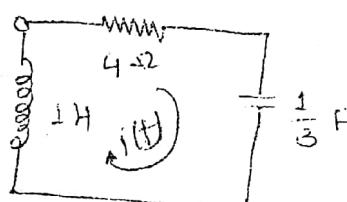

Using KVL,

\dots

$$i) \quad 4i(t) + \frac{di(t)}{dt} + 3v(t) = 0 \quad \textcircled{1}$$

$$\text{or, } 4il(t) + \frac{di(t)}{dt} + 3 \int_0^t i(t) dt = 0 \quad \textcircled{2}$$

Differentiating w.r.t. t,

$$4\frac{di(t)}{dt} + \frac{d^2i(t)}{dt^2} + 3i(t) = 0 \quad \textcircled{3}$$

Characteristic equation is,

$$s^2 + 4s + 3 = 0$$

$$s_1, s_2 = \frac{-4 \pm \sqrt{16 - 12}}{2} = \frac{-4 \pm 2}{2} = -3, -1$$

Equation $\textcircled{3}$ is homogeneous equation so, it has forced response if $f(t) = 0$.

$$i(t) = i_t(t) + i_f(t)$$

$$= i_t(t)$$

$$\therefore \text{Transient response, } i_t(t) = K_1 e^{s_1 t} + K_2 e^{s_2 t}$$

$$i_t(t) = K_1 e^{-3t} + K_2 e^{-t}$$

$$\therefore i(t) = K_1 e^{-3t} + K_2 e^{-t} \quad \textcircled{4}$$

at, $t = 0^+$

$$i(0^+) = K_1 e^0 + K_2 e^0$$

$$\Rightarrow 3K_2 = K_1 + K_2$$

$$\Rightarrow K_1 = 2K_2$$

⑤

Now, differentiating at $t = 0^+$, eqⁿ $\textcircled{1}$ becomes

$$4i(0^+) + \frac{di(0^+)}{dt} + 3v_e(0^+) = 0$$

$$\frac{di(0^+)}{dt} = 6 \times 3 = -12 \text{ amp/sec}$$

③

6

Differentiating eqⁿ (4)

$$\frac{di(t)}{dt} = -3K_1 e^{-3t} - K_2 e^{-t}$$

at, $t = 0^+$

$$\frac{di(0^+)}{dt} = -3K_1 e^0 - K_2 e^0$$

$$-12 = -3K_1 - K_2$$

$$\alpha, -q_2 = -3(3-K_2) - K_2$$


$$\alpha, -q_2 = -9 + 3K_2 - K_2$$

$$\therefore K_2 = \frac{3}{2} \quad \text{and, } K_1 = 3 + \frac{3}{2} = \frac{9}{2}$$

Thus,


$$i(t) = -\frac{3}{2} e^{-3t} + \frac{9}{2} e^{-t} - \frac{3}{2} e^{-t}$$

Q.3. Here,

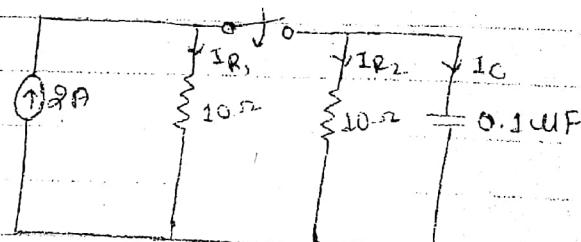

From figure

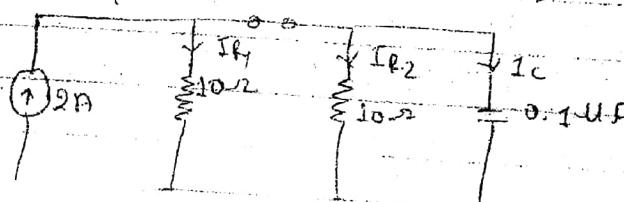$V_C(0^-) = 0 = V_C(0^+)$ [∴ Capacitor can not change instantaneous
at, $t > 0$. equivalent circuit is,



Using KCL we have,

$$\delta A = \cancel{V} I_{R1} + I_{R2} + I_{C1}$$

$$\delta = \frac{V}{10} + \frac{V}{10} + C \frac{dV}{dt}$$

$$\delta = \frac{V}{5} + 0.1 \frac{dV}{dt} \quad \textcircled{1}$$

Equation ① is non-homogeneous equation. It has two parts of solution.

① forced solution

from ① in operator form

$$\delta = \frac{V}{5} + 0.1 P V$$

$$V(t) = \frac{2}{\left(\frac{1}{5} + 0.1 P\right)}$$

Here, source is constant so put $P=0$ to find $V_f(t)$

$$V_f(t) = \frac{2}{15} = 10 \text{ V.}$$

② Transient solution : Homogeneous version of ① is,

from ①, characteristic equation is, $0.1 \frac{dV}{dt} + \frac{V}{5} = 0$

$$0.1 S + \frac{1}{5} = 0$$

$$S = -\frac{1}{0.1 \cdot 5} = -2$$

Transient solution, $V_t(t) = K_1 e^{-2t}$

8

$$\text{complete response, } V(t) = V_f(t) + V_t(t)$$

$$= 10 + K_1 e^{-2t}$$

at, $t = 0^+$

$$V(0^+) = 10 + K_1 e^{-2 \cdot 0}$$

$$0 = 10 + K_1 e^{-2 \cdot 0}$$

$$K_1 = -10$$

$$\text{Thus, } V(t) = 10 - 10 e^{-2t}$$


$$= 10 (1 - e^{-2t})$$

Q.4 Here,

$$I = 5 \text{ A}, R = \frac{1}{5} \Omega, L = 0.1 \text{ H}, C = 4 \text{ F}$$


At, $t = 0^+$, $V_C(0^+) = 0$

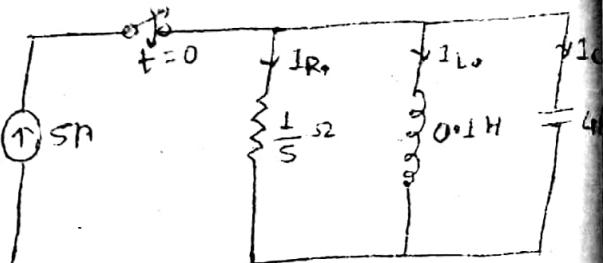$V_C(0^+) = 0 = V_C(0^-)$ (\because Voltage across capacitor can not change instantaneously.)



for $t > 0$, equivalent circuit is,
using KCL,

$$5\text{A} = I_R + I_L + I_C$$

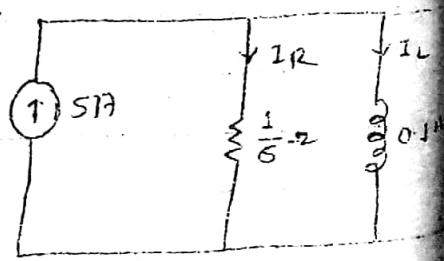

Differentiating w.r.t. t

$$0 = 5 \frac{dv(t)}{dt} + 10v(t) + 4d^2v(t) \quad \dots \textcircled{2}$$

Equation $\textcircled{2}$ is homogeneous equation. It has forced response zero. So,

$$\begin{aligned} v(t) &= V_f(t) + V_t(t) \\ &= V_t(t) \end{aligned}$$

for transient response,

characteristic equation is,

$$\begin{aligned} 4s^2 + 5s + 10 &= 0 \\ s_1, s_2 &= -\frac{5 \pm \sqrt{25 - 160}}{8} = -\frac{5 \pm \sqrt{-135}}{8} \end{aligned}$$

$$s_1 = -\frac{5 + j\sqrt{135}}{8}$$

$$s_2 = -\frac{5 - j\sqrt{135}}{8}$$

$$(s + \frac{5 + j\sqrt{135}}{8})t \quad (-s + \frac{5 - j\sqrt{135}}{8})t \quad \dots \textcircled{3}$$

Transient response, $v_t(t) = K_1 e^{(-s + j\sqrt{135}/8)t} + K_2 e^{(-s - j\sqrt{135}/8)t}$

$$v(t) = v_f(t) + v_t(t)$$

NOW, at $t = 0^+$

$$v(0^+) = K_1 e^0 + K_2 e^0$$

$$0 = K_1 + K_2$$

$$\therefore K_1 = -K_2$$

From eq? $\textcircled{1}$ at $t = 0^+$

$$s = \frac{v(0^+)}{R} + i\omega(0^+) + c \frac{dv(0^+)}{dt} \Rightarrow \frac{dv(0^+)}{dt} = \frac{5}{4} \quad \textcircled{4}$$

10

Now, differentiating eq? ③

$$\frac{dV(t)}{dt} = \left(\frac{-5+j\sqrt{135}}{8} \right) K_1 e^{\left(\frac{-5+j\sqrt{135}}{8} \right)t} + \left(\frac{-5-j\sqrt{135}}{8} \right) K_2 e^{\left(\frac{-5-j\sqrt{135}}{8} \right)t}$$

at, $t=0^+$

$$\frac{dV(0^+)}{dt} = \left(\frac{-5+j\sqrt{135}}{8} \right) K_1 + \left(\frac{-5-j\sqrt{135}}{8} \right) K_2$$

$$\frac{5}{4} = -\frac{5}{8}K_1 + j\sqrt{135}K_1 + \frac{5}{8}K_1 + j\sqrt{135}K_2$$

$$\frac{5}{4} = j\sqrt{135}K_2$$

$$K_2 = \frac{5}{j\sqrt{135}} = -\frac{j5}{\sqrt{135}} = -K_1$$

$$\therefore V(t) = \frac{5j}{\sqrt{135}} e^{\left(\frac{-5+j\sqrt{135}}{8} \right)t} - \frac{5j}{\sqrt{135}} e^{\left(\frac{-5-j\sqrt{135}}{8} \right)t}$$

Q.5. Here,


$$e = 100\sin(500t + 30)$$

$$R = 5\Omega$$

$$L = 0.01H$$

At $t = 0^-$

$$i(0^-) = 0$$

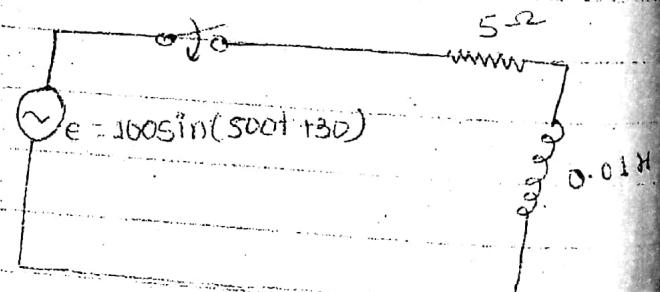

$\therefore i(0^+) = i(0^-) = 0$ (Current through Inductor can not change instantaneously)

Now, at $t > 0$, apply KVL

$$e = iR + L \frac{di}{dt}$$

$$100\sin(500t + 30^\circ) = 5i(t) + 0.01 \frac{di(t)}{dt} \quad \textcircled{1}$$

Equation ① is non-homogeneous equation so, it has two parts of solution.

① Forced solution

from eq: ① in p-operator form

$$5i(t) + 0.01pi(t) = 100\sin(500t + 30^\circ)$$

$$i(t) [5 + 0.01P] = 100\sin(500t + 30^\circ)$$

$$i(t) = \text{Im} \left[\frac{j(500t + 30^\circ)}{5 + 0.01P} \right]$$

Here, source is exponential so replace P by s and

s by $j500$

$$i_f(t) = \text{Im} \left[\frac{j(500t + 30^\circ)}{5 + j5} \right]$$

$$= \text{Im} \left[\frac{100 e^{j(500t + 30^\circ)}}{7.07445} \right]$$

$$= \text{Im} \left[14.14 e^{j(500t - 15^\circ)} \right]$$

$$= 14.14 \sin(500t - 15^\circ)$$

② Transient response

⑤

Q2

Homogeneous version of equation ① PS,

$$0.01 \frac{di(t)}{dt} + si(t) = 0$$

characteristic equation PS, $0.01s + s^2 = 0$

$$s = -500$$

transient solution, $i_f(t) = K_1 + K_2 e^{-500t}$

$$= K_2 e^{-500t}$$

Total solution, $i(t) = i_f(t) + i_p(t)$

$$= 14.14 \sin(500t - 15^\circ) + K_2 e^{-500t}$$

$$\text{at, } t = 0^+$$

$$i(0^+) = 14.14 \sin(0 - 15^\circ) + K_2 e^0$$

$$0 = -3.7 + K_2$$

$$K_2 = 3.7$$


$$\text{Thus, } i(t) = 14.14 \sin(500t - 15^\circ) + 3.7 e^{-500t}$$


Q6. Same as Q1

Hints: Find, $i(t)$ only, and $i(0^+)$ by putting $t = 0^+$

Q7

Here,

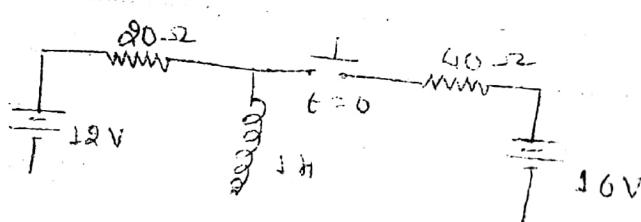

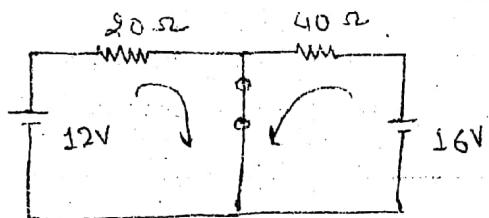
At, $t = 0^-$ 

$$i(0^-) = \frac{12}{20} + \frac{16}{40} = \frac{40}{40} = 1 \text{ A.}$$

so, $i(0^+) = i(0^-) = 1 \text{ Amp}$ [∴ Current through inductor cannot change instantaneously.]

At, $t > 0$, equivalent circuit
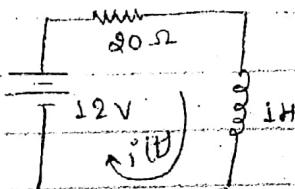
$$12 = 20i(t) + \frac{di(t)}{dt} \quad \dots \textcircled{1}$$



Equation ① is non-homogeneous equation. It has two parts of solution.

① forced solution

Equation ① in P operator form

$$12 = 20 \dot{i}(t) + Pi(t)$$

$$i(t) = \frac{12}{20+P}$$

Here, source is constant. So, put $P=0$ for forced response.

$$i_f(t) = \frac{12}{20} = \frac{3}{5} \text{ Amp.}$$

② Transient solution

Homogeneous version of equation ① is,

$$\frac{di(t)}{dt} + 20 \dot{i}(t) = 0$$

14

characteristic equation is,

$$s + 20 = 0$$

$$s = -20$$

$$\therefore \text{transient solution, } i_f(t) = Ke^{st} \\ = Ke^{-20t}$$

Thus, total solution,

$$i(t) = i_f(t) + i_t(t) \\ = \frac{3}{5} + Ke^{-20t}$$

at, $t = 0^+$

$$i(0^+) = i_f(0^+) + i_t(0^+)$$

$$1 = \frac{3}{5} + Ke^0$$

$$K = 1 - \frac{3}{5} = \frac{2}{5}$$


$$\therefore i(t) = \frac{3}{5} + \frac{2}{5} e^{-20t}$$


Q.8

Same as Q.4.

Q.9

Here,

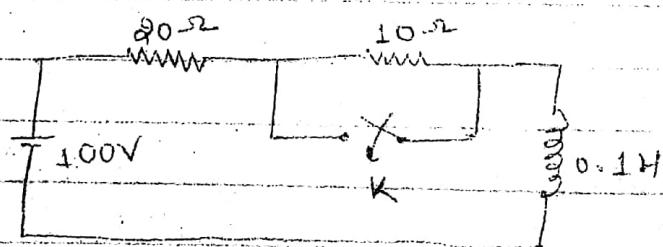

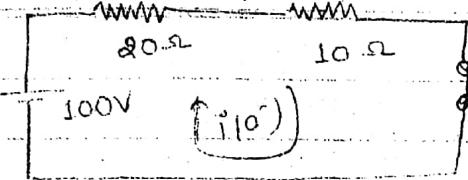


$$i(0^+) = \frac{100}{30} = \frac{10}{3} \text{ Amp.}$$

$$i(0^+) = i(0^-) = \frac{10}{3} \quad (\because \text{Current through inductor can not change instantaneously.})$$

At $t > 0$, equivalent circuit
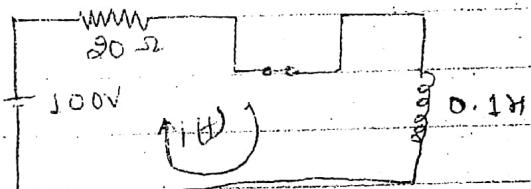
$$20i(t) + 0.1\frac{di(t)}{dt} = 100 \quad \text{①}$$



equation ① is non-homogeneous equation. It has two parts of solution.

① Forced solution

from eq. ① in p-operator form

$$20i(t) + 0.1Pi(t) = 100$$

$$i(t) = \frac{100}{20 + 0.1P} \quad \text{Here Source is constant, so}$$

put $P=0$ for forced response.

$$i_f(t) = \frac{100}{20} = 5 \text{ Amp.}$$

② Transient solution

Homogeneous Version of eq. ① is,

$$20i(t) + 0.1\frac{di(t)}{dt} = 0$$

A

16

Characteristic equation is,

$$20 + 0.1s = 0$$

$$s = -200$$

$$\therefore \text{transient response } i_f(t) = Ke^{st} \\ = Ke^{-200t}$$

$$\therefore \text{Total response } i(t) = i_f(t) + i_s(t)$$

$$\text{at, } t = 0^+ \\ = 5 + Ke^{-200t}$$

$$i(0^+) = 5 + Ke^0$$

$$\frac{10}{3} = 5 + K \Rightarrow K = \frac{10}{3} - 5 = -\frac{5}{3}$$

$$\therefore i(t) = 5 - \frac{5}{3} e^{-200t}$$


Q.10.

Same as Q. 6

only values are different.


do yourself  !!

Ch-4
Assignment 3: Solution

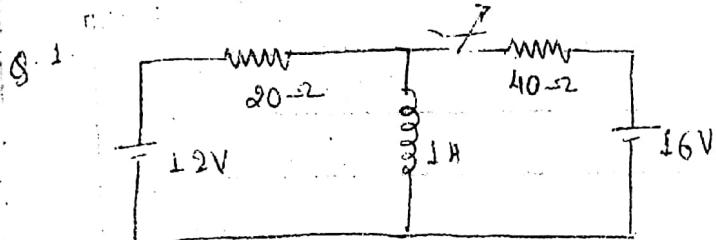

At, $t = 0^-$, Equivalent circuit is

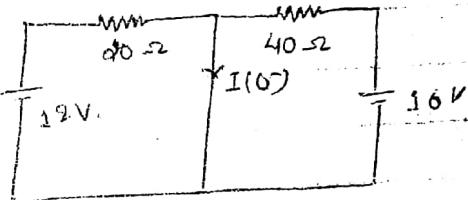
$$I(0) = \frac{12}{20} + \frac{16}{40} = 1 \text{ Amp.}$$



$I(0^+) = I(0^-) = 1$ (As current through inductor can not change instantaneously)

Now, equivalent circuit at $t > 0$

$$20 I(t) + \frac{dI(t)}{dt} = 12$$

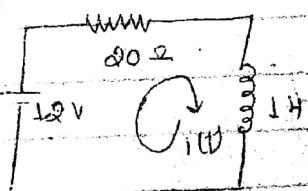

Taking Laplace transform on both side, we get

$$20 I(s) + s I(s) - I(0) = \frac{12}{s}$$

$$I(s)(s+20) = \frac{12}{s} + 1 = \frac{(12+s)}{s}$$

$$I(s) = \frac{12+s}{s(s+20)}$$

Using partial fraction expansion,

$$I(s) = \frac{12+s}{s(s+20)} = \frac{A}{s} + \frac{B}{s+20}$$


$$A = \left. \frac{12+s}{s(s+20)} \times s \right|_{s=0} = \frac{12}{20} = \frac{3}{5}$$

$$B = \left. \frac{12+s}{s(s+20)} \times (s+20) \right|_{s=-20} = \frac{12-20}{-20} = \frac{-8}{-20} = \frac{2}{5}$$

$$\therefore I(s) = \frac{3}{5s} + \frac{2}{5(s+20)}$$

Taking Inverse laplace transform, we have
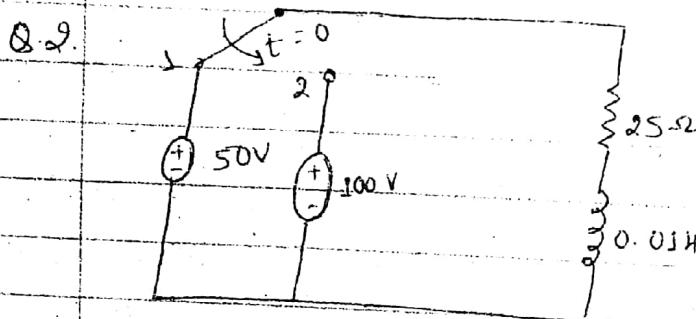
$$i(t) = \frac{3}{5} + \frac{2}{5} e^{-20t}$$




At $t = 0^-$

Equivalent circuit is,


$$i(0^-) = \frac{50}{25} = 2 \text{ Amp.}$$

NOW,

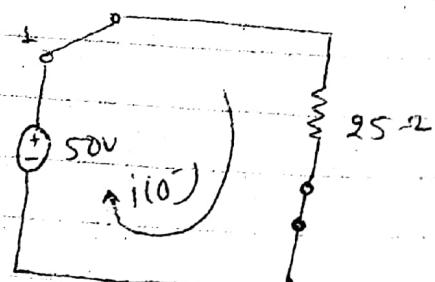$i(0^+) = i(0^-) = 2 \text{ Amp.}$ [Current through inductor can not change instantaneously.]



19

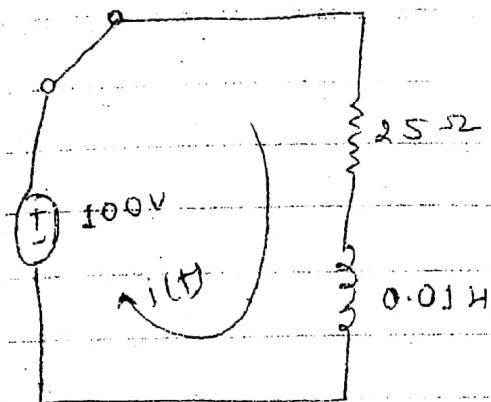

$$25i(t) + 0.01 \frac{di(t)}{dt} = 100$$

Taking Laplace transform on both sides we get

$$25I(s) + 0.01sI(s) - 0.01i(0) = \frac{100}{s}$$

$$\text{or, } I(s)[0.01s + 25] = \frac{100 + 0.02}{s}$$

$$\text{or, } I(s) = \frac{0.02s + 100}{s(0.01s + 25)}$$

$$\text{or, } I(s) = \frac{0.02[s + 5000]}{0.01s[s + 2500]} = \frac{2(s + 5000)}{s(s + 2500)}$$

Using partial fraction expansion

$$I(s) = \frac{2(s + 5000)}{s(s + 2500)}$$

$$\Rightarrow \frac{2s + 10000}{s(s + 2500)} = \frac{A}{s} + \frac{B}{s + 2500}$$

$$A = 2(s + 5000) \times s \Big|_{s=0} = 2 \cdot 5000 = 10000$$

$$B =$$

6

Q9

$$B = \frac{2(s+500)}{s(s+2500)} \times (s+2500) \Big|_{s=-2500} = \frac{2(-2500+5000)}{-2500} = -2500$$

$$= -2$$

$$I(s) = \frac{4}{s} - \frac{2}{s+2500}$$

Taking Inverse Laplace transform we get

$$i(t) = 4 - 2e^{-2500t}$$


Q4 Here,

$$V(t) = 4e^{-2t}$$

$$R = 2\Omega$$

$$L = 1H$$

$$i_L(0^-) = 3A$$

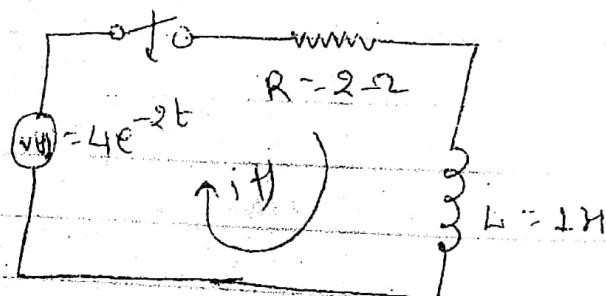

$\therefore i(0^+) = i(0^-) = 3A$ [Current through inductor can not change instantaneously.]

Now, at $t > 0$, apply KVL

$$\frac{di(t)}{dt} + \frac{i(t)}{2} = 4e^{-2t}$$

Using Laplace transform on both sides, we get

~~S F T G E~~

L1

$$I(s) [s+2] - 3 = \frac{4}{s+2}$$

$$I(s) = \frac{4+3s+6}{(s+2)^2}$$

$$I(s) = \frac{10+3s}{(s+2)^2}$$

using partial fraction expansion:

$$I(s) = \frac{10+3s}{(s+2)^2} = \frac{A}{s+2} + \frac{B}{(s+2)^2}$$

$$\Rightarrow \frac{10+3s}{(s+2)^2} = \frac{A(s+2)+B}{(s+2)^2}$$

$$\Rightarrow 10+3s = As + (2A+B)$$

Comparing coefficient,

$$A = 3$$

$$B = 10 - 2 \times 3 = 4$$

Thus,

$$I(s) = \frac{3}{s+2} + \frac{4}{(s+2)^2}$$

Taking inverse Laplace transform

$$i(t) = 3e^{-2t} + 4te^{-2t}$$


85

Here,

$$V_0 = 10V, R = 5\Omega, L = 1H \text{ and } C = 0.25F$$

(3)

22

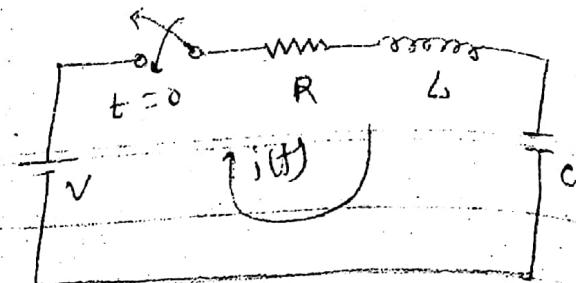

$$i(0^-) = 0 \text{ and } v_c(0^-) = 0$$

$\therefore i(0^+) = i(0^-) = 0$ (\because Current through inductor can not change instantaneously)

$\therefore v_c(0^+) = v_c(0^-) = 0$ (\because Voltage across capacitor can not change instantaneously.)

Now, applying KVL at $t > 0$

$$Ri(t) + \frac{Ldi(t)}{dt} + \frac{1}{C} \int_{-\infty}^t i(t) dt = V$$

$$\text{or, } Ri(t) + \frac{Ldi(t)}{dt} + \frac{1}{C} \int_{-\infty}^0 i(t) dt + \frac{1}{C} \int_0^t i(t) dt = V$$

$$\text{or, } 5i(t) + \frac{di(t)}{dt} + v_c(0^+) + 4 \int_0^t i(t) dt = 10 \quad \text{①}$$

Differentiating w.r.t t we get

$$5\frac{di(t)}{dt} + \frac{d^2i(t)}{dt^2} + 4i(t) = 0 \quad \text{②}$$

from ①

$$5i(t) + \frac{di(t)}{dt} + 4v_c(t) = 10$$

at $t = 0^+$

$$5i(0^+) + \frac{di(0^+)}{dt} + 4v_c(0^+) = 10$$

$$\frac{di(0^+)}{dt} = 10 \text{ amp/Sec.}$$

Now, Taking Laplace transform of equation ②,

we get

$$5S I(S) - I(0) + S^2 I(S) - 5I(0) - i'(0) + 4 I(S) = 0$$

$$\text{or, } I(S) [5S + S^2 + 4] - 0 - 5 \cdot 0 - 10 = 0$$

$$\text{or, } I(S) [S^2 + 5S + 4] = 10$$

$$\text{or, } I(S) = \frac{10}{S^2 + 5S + 4} = \frac{10}{(S+4)(S+1)}$$

Now, using partial fraction expansion.

$$I(S) = \frac{10}{S^2 + 5S + 4} = \frac{10}{(S+4)(S+1)} = \frac{A}{S+4} + \frac{B}{S+1}$$

Now,

$$A = \left. \frac{10}{(S+4)(S+1)} \times (S+4) \right|_{S=-4} = -\frac{10}{3}$$

$$B = \left. \frac{10}{(S+4)(S+1)} \times (S+1) \right|_{S=-1} = \frac{10}{3}$$

$$\text{Thus, } I(S) = -\frac{10}{3(S+4)} + \frac{10}{3(S+1)}$$


Taking inverse Laplace transform, we get

$$i(t) = -\frac{10}{3} e^{-4t} + \frac{10}{3} e^{-t}$$

Q7

Q.6 Here

$$i_L(0) = 0$$

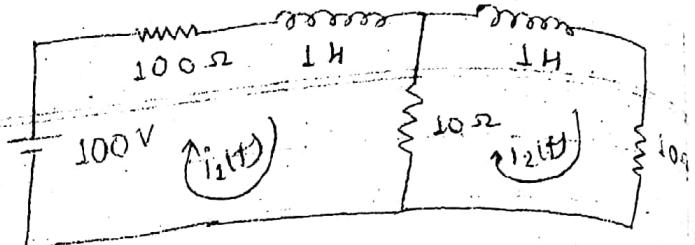

$i_L(0^+) = i_L(0^-) = 0$ (Current through inductor cannot change instantaneously.)

Applying KVL at loop 1:

$$100i_1(t) + 1 \frac{di_1(t)}{dt} + 10(i_1(t) - i_2(t)) = 100$$

Taking Laplace transform

$$100I_1(S) + S I_1(S) - I_1(0) + 10I_1(S) - 10I_2(S) = \frac{100}{S}$$

$$\text{or, } I_1(S)[100 + S + 10] - I_1(0) - 10I_2(S) = \frac{100}{S}$$

$$\text{or, } (110 + S)I_1(S) - 10I_2(S) = \frac{100}{S} \quad \dots \textcircled{1}$$

Applying KVL at loop 2:

$$10i_2(t) + 1 \frac{di_2(t)}{dt} + 10(i_2(t) - i_1(t)) = 0$$

Taking Laplace transform,

$$10I_2(S) + S I_2(S) - I_2(0) + 10I_2(S) - 10I_1(S) = 0$$

$$\text{or, } I_2(S)[10 + S + 10] = 10I_1(S)$$

from eqⁿ ① and ②

$$(110+s)(20+s) I_2(s) - 10 I_2(s) = \frac{100}{s}$$

$$\text{or, } I_2(s) [(110+s)(20+s) - 100] = \frac{1000}{s}$$

$$\text{or, } I_2(s) [2200 + 130s + s^2 - 100] = \frac{1000}{s}$$

$$\text{or, } I_2(s) [s^2 + 130s + 2100] = \frac{1000}{s}$$

$$\text{or, } I_2(s) = \frac{1000}{s(s+18.9)(s+111.1)}$$

Now, taking Partial fraction expansion.

$$I_2(s) = \frac{1000}{s(s+18.9)(s+111.1)} = \frac{A}{s} + \frac{B}{s+18.9} + \frac{C}{s+111.1}$$

$$A = \frac{1000}{s(s+18.9)(s+111.1)} \Big|_{s=0} = \frac{1000}{18.9 \times 111.1} = 0.48$$

$$B = \frac{1000}{s(s+18.9)(s+111.1)} \Big|_{s=-18.9} = \frac{1000}{-18.9 \times (-18.9 + 111.1)} = -0.57$$

$$C = \frac{1000}{s(s+18.9)(s+111.1)} \Big|_{s=-111.1} = \frac{1000}{-111.1 \times (-111.1 + 18.9)} = 0.097$$

26

$$\text{Thus, } I(s) = \frac{0.48}{s} - \frac{0.57}{s+18.9} + \frac{0.097}{s+111.1}$$

Taking Inverse Laplace transform

$$i(t) = 0.48 - 0.57 e^{-18.9t} + 0.097 e^{-111.1t}$$

Q 1 Initial value theorem

If $f(t)$ and its first derivative $f'(t)$ Laplace transformable then,

$$f(0) = \lim_{t \rightarrow 0} f(t) = \lim_{s \rightarrow \infty} sF(s)$$

Final value theorem

If $f(t)$ and its first derivative $f'(t)$ Laplace transformable then,

$$f(\infty) = \lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} sF(s)$$

Numerical part

Given,

$$I(s) = \frac{(s+1)}{s(s+2)}$$

For $i(0)$

use Initial value theorem

27

$$= \lim_{s \rightarrow \infty} \frac{s(1 + \frac{1}{s})}{s(1 + \frac{2}{s})}$$

$$= \lim_{s \rightarrow \infty} \frac{1 + \frac{1}{s}}{1 + \frac{2}{s}}$$

$$= \frac{1}{1} = 1$$

for steady state value of $i(t)$ i.e $i(\infty)$


use final value theorem,

$$i(\infty) = \lim_{s \rightarrow 0} sI(s) = \lim_{s \rightarrow 0} \frac{8(s+1)}{8(s+2)}$$

$$= \frac{1}{2}$$

$$\therefore i(0) = 1 \text{ amp and } i(\infty) = \frac{1}{2} \text{ amp}$$

Q8 Given, circuit

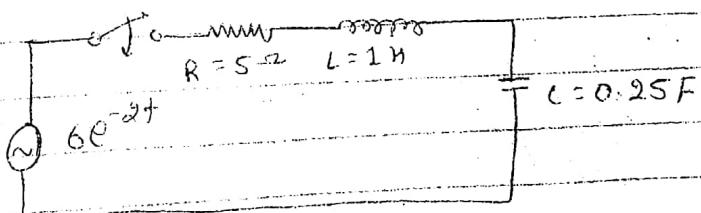

$$\text{Here, } i(0^+) = 0$$

$$v_e(0^+) = 0$$

so, $i(0^+) = i(0^-) = 0$ [Current through inductor can not change instantaneously.]

⑥

28

$$V_c(0^+) = V_c(0^-) = 0$$

[Voltage across capacitor can not be instantaneous]

Now, using KVL at $t > 0$, we get

$$5i(t) + \frac{di(t)}{dt} + 4 \int_{-\infty}^t i(t) dt = 6e^{-st}$$

$$\text{or, } 5i(t) + \frac{di(t)}{dt} + 4 \int_{-\infty}^0 i(t) dt + 4 \int_0^t i(t) dt = 6e^{-st}$$

$$\text{or, } 5i(t) + \frac{di(t)}{dt} + 4V_c(0^+) + 4 \int_0^t i(t) dt = 6e^{-st}$$

at, $t = 0^+$

$$5i(0^+) + \frac{di(0^+)}{dt} + 4V_c(0^+) = 6e^0$$

$$\frac{di(0^+)}{dt} = 6$$

Now, Differentiating eq. ① w.r.t. t, we get

$$5\frac{di(t)}{dt} + \frac{d^2i(t)}{dt^2} + 4i(t) = -12e^{-st}$$

Now, Taking Laplace transform we get

$$5I(s) - i(0) + s^2 I(s) - sI(0) - i'(0) + 4I(s) = \frac{-12}{(s+2)}$$

$$\text{or, } I(s) [5s + s^2 + 4] - 0 - 0 - 6 = \frac{-12}{(s+2)}$$

$$I(s) [(s+4)(s+1)] = \frac{6s}{(s+2)}$$

$$I(s) = \frac{6s}{(s+1)(s+2)(s+4)}$$

Now, using partial fraction expansion, we have

$$I(s) = \frac{6s}{(s+1)(s+2)(s+4)} = \frac{A}{s+1} + \frac{B}{s+2} + \frac{C}{s+4}$$

$$A = \frac{6s}{(s+1)(s+2)(s+4)} \times (s+1) \Big|_{s=-1} = \frac{-6}{3} = -2$$

$$B = \frac{6s}{(s+1)(s+2)(s+4)} \times (s+2) \Big|_{s=-2} = \frac{-12}{-1 \times 2} = 6$$

$$C = \frac{6s}{(s+1)(s+2)(s+4)} \times (s+4) \Big|_{s=-4} = \frac{-24}{-3 \times -2} = -4$$

Thus,

$$I(s) = -\frac{2}{s+1} + \frac{6}{s+2} - \frac{4}{s+4}$$

Now, taking inverse Laplace transform we get

$$i(t) = -2e^{-t} + 6e^{-2t} - 4e^{-4t}$$

Q9 Here,

$$C = 1F, R = \frac{1}{2} \Omega, L = \frac{1}{2} H \text{ and } I_0 = 2A$$

30

Here,

$$\dot{i}_R(0^-) = i_R(0^+) \pm i_c(0^-) = 0$$

$$V_c(0^-) = 0$$

$V_c(0^+) = V_c(0^-) = 0$ (\because Voltage across capacitor can not change instantaneously)

NOW, USE KCL at $t > 0$.

$$2A = i_R + i_L + i_C$$

$$\text{or, } 2 = \frac{V}{R} + \frac{1}{L} \int v dt + \frac{dv}{dt}$$

$$\text{or, } 2 = 2V(t) + 2 \int_{-\infty}^t v(t) dt + \frac{dv(t)}{dt}$$

$$\text{or, } 2 = 2V(t) + 2 \int_{-\infty}^0 v(t) dt + 2 \int_0^t v(t) dt + \frac{dv(t)}{dt}$$

$$\text{or, } 2V(t) + i_L(0^+) + 2 \int_0^t v(t) dt + \frac{dv(t)}{dt} = 2$$

Since, $i_L(0^+) = i_L(0^-) = 0$ (\because current through inductor can change instantaneously.)


so,

$$2V(t) + 2 \int_0^t v(t) dt + \frac{dv(t)}{dt} = 2 \quad (1)$$

at, $t = 0^+$

$$2V(0^+) + 2i_L(0^+) + \frac{dv(0^+)}{dt} = 2$$

$$\underline{\underline{dv(0^+)} = 2}$$

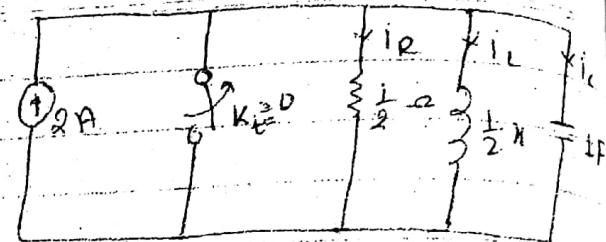

On differentiating equation ① we get

$$\int \frac{dv(t)}{dt} + 2v(t) + \frac{d^2v(t)}{dt^2} = 0$$

on taking Laplace transform, we get

$$2SV(s) - 2V(0) + 2V(s) + s^2V(s) - SV(0) - V'(0) = 0$$

$$V(s)[2s+2+s^2] - 0 - 0 - 2 = 0$$

$$V(s)[s^2+2s+2] = 2$$

$$V(s) = \frac{2}{s^2+2s+2}$$

$$V(s) = \frac{2}{(s+1)^2 + 1^2}$$

$$V(s) = \frac{2}{(s+1)^2 + 1^2}$$

Now, taking inverse Laplace transform, we get

$$v(t) = 2e^{-t} \sin t$$

Here, $V = 25 \sin 10t$, $R = 5\Omega$ and $L = 1H$.

$$i(0^-) = 0$$

$i(0^+) = i(0^-) = 0$ [Current through inductor can not change instantaneously]

Apply KVL at $t > 0$

$$v(t) + \frac{di(t)}{dt} = 25 \sin 10t$$

at $t = 0$ $v(0) = 50$
 $\therefore 50 + \frac{dI(0)}{dt} = 25 \sin 10t$

32

using Laplace transform we get,

$$5I(s) + sI(s) - I(0) = 25 \cdot \frac{10}{s^2 + 100}$$

$$I(s)[s+5] = \frac{250}{s^2 + 100}$$

$$I(s) = \frac{250}{(s+5)(s^2 + 100)}$$

Using partial fraction expansion

$$I(s) = \frac{250}{(s+5)(s^2 + 100)} = \frac{A}{s+5} + \frac{Bs+C}{s^2 + 100}$$

$$\text{or, } \frac{250}{(s+5)(s^2 + 100)} = \frac{As^2 + 100A + Bs^2 + Cs + 5B}{(s+5)(s^2 + 100)}$$

$$\text{or, } 250 = (A+B)s^2 + (Cs + 5B)s + (5C + 100A)$$

Comparing coefficient.

$$A + B = 0 \Rightarrow A = -B$$

$$C + 5B = 0 \Rightarrow C = -5B$$

$$5C + 100A = 250$$

$$\text{or, } -25B - 100B = 250$$

$$\Rightarrow B = -2$$

$$\Rightarrow A = 2$$

$$\Rightarrow C = 10$$

$$\therefore I(s) = \frac{2}{s+5} + \frac{2s-10}{s^2 + 100}$$

$$= \frac{2}{s+5} - 2 \cdot \frac{s}{s^2 + 10^2} + \frac{10}{s^2 + 10^2}$$


Taking inverse Laplace transform we get

$$i(t) = 2e^{-st} - 2 \cos 10t + 5 \sin 10t$$

Assignment 4: Solution

Q① Given, $I(s) = \frac{4s}{(s+1)(s+3)}$

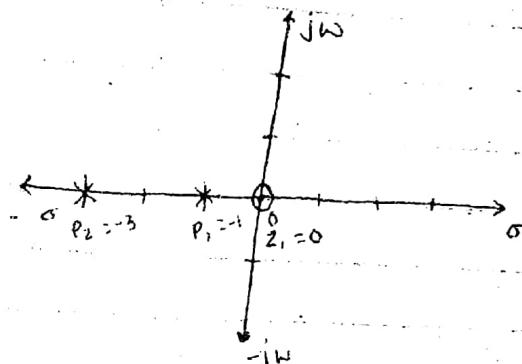It has zeros at $s=0$
and poles at $s=-1, -3$



NOW,

$$I(s) = \frac{K_1}{(s+1)} + \frac{K_2}{(s+3)}$$

For pole at $s=-1$

$$K_1 = \frac{K(P_1 - Z_1)}{(P_1 - P_2)} = \frac{4(-1-0)}{(-1+3)} = \frac{-4}{2} = -2$$

For pole at $s=-3$

$$K_2 = \frac{K(P_2 - Z_1)}{(P_2 - P_1)} = \frac{4(-3-0)}{(-3+1)} = \frac{-12}{2} = 6$$

$$\therefore I(s) = \frac{-2}{s+1} + \frac{6}{s+3}$$

Taking inverse Laplace transform

$$i(t) = -2e^{-t} + 6e^{-3t}$$

$$i(1) = -2e^{-1} + 6e^{-3} = -0.44 \quad \therefore |i(1)| = 0.44 \text{ SEC}$$

Q② Given, characteristic equation:

$$s^5 + s^4 + 2s^3 + 2s^2 + 3s + 5 = 0$$

34

R-H array

s^5	1	2	3	
s^4	1	2	5	$b_1 = -\frac{1}{1} \begin{vmatrix} 1 & 2 \\ 1 & 2 \end{vmatrix} = 0$
s^3	$b_1 = 0$	$b_2 = -2$	0	
s^2	can not determine			$b_2 = -\frac{1}{1} \begin{vmatrix} 1 & 3 \\ 1 & 5 \end{vmatrix} = -2$
s^1				
s^0				

Here, First column of third row has value zero. So, other values below third row can not be determined. In such case we replace 0 by small valued number near to zero, say ϵ .

Then, stability depends of ϵ .

Now, R-H array becomes

s^5	1	2	3	
s^4	1	2	5	$c_1 = -\frac{1}{\epsilon} \begin{vmatrix} 1 & 2 \\ \epsilon & -2 \end{vmatrix} = -\frac{1}{\epsilon} (-2-2\epsilon) = \frac{2\epsilon+2}{\epsilon} = 2 + \frac{2}{\epsilon}$
s^3	ϵ	-2	0	
s^2	$c_1 = 2 + \frac{2}{\epsilon}$	5		
s^1	$d_1 = -\frac{s\epsilon^2 + 4\epsilon + 4}{2\epsilon + 2}$			$d_1 = -\frac{\epsilon}{2\epsilon+2} \begin{vmatrix} \epsilon & -2 \\ 2+\frac{2}{\epsilon} & 5 \end{vmatrix}$
s^0	5			

For -ve value of ϵ , 1st column of 3rd row has -ve value

so sign changes occurs and system is unstable.

For +ve value of ϵ , 1st

$$= -\left(\frac{5\epsilon^2 + 4\epsilon + 4}{2\epsilon+2} \right)$$

Hence, above system is unstable.

(3) Here,

$$Q(s) = s^4 + s^3 + s^2 + s + k$$

R-H array

$$\begin{array}{ccccc} s^4 & 1 & 1 & k \\ s^3 & 1 & 1 & 0 \\ s^2 & b_2 = 0 & k \end{array}$$

$$b_1 = -\frac{1}{1} \quad \left| \begin{array}{cc} 1 & 1 \\ 1 & 1 \end{array} \right| = 0$$

s^1 : can not determine

s^0

Here, First column of third row has value 0. So, fourth and fifth row can not be determined. so, we replace 0 by small number near to zero. say ϵ .

Now, R-H array becomes

$$\begin{array}{ccccc} s^4 & 1 & 1 & k \\ s^3 & 1 & 1 & 0 \\ s^2 & \epsilon & k \\ s^1 & c_1 = 1 - \frac{k}{\epsilon} & 0 \end{array}$$

$$c_1 = -\frac{1}{\epsilon} \quad \left| \begin{array}{cc} 1 & 1 \\ \epsilon & k \end{array} \right|$$

$$= -\frac{1}{\epsilon} (k - \epsilon) = 1 - \frac{k}{\epsilon}$$

s^0 : k

For stability, first column has same sign i.e. it has no sign changes.

(a) if ϵ is positive

$$\text{so, } 1 - \frac{k}{\epsilon} > 0 \Rightarrow \epsilon - k > 0 \Rightarrow \epsilon > k$$

and $k > 0$

(b) if ϵ is negative

$$\text{so, } \epsilon > k > 0 \quad 1 + \frac{k}{\epsilon} > 0 \Rightarrow -\epsilon < k$$

Here, ϵ should be positive value.

so, $\epsilon > 0$

(2)

36

Q.4 Given,

$$\begin{aligned}
 T(s) &= \frac{8s}{(s+2)(s^2+2s+2)} \\
 &= \frac{3s}{(s+2)\{(s+1)^2 + 1\}} \\
 &= \frac{3s}{(s+2)\{(s+1)^2 - j^2\}} \quad = \frac{3s}{(s+2)\cdot(s+1+j)}
 \end{aligned}$$

Poles are at, $s = -2, -1 \pm j$ Zero at, $s = 0$

Now,


$$T(s) = \frac{k_1}{s+2} + \frac{k_2}{(s+1+j)} + \frac{k_3}{(s+1-j)}$$

For pole at $P_1 = -2$

$$\begin{aligned}
 k_1 &= \frac{k(-2 - z_1)}{(P_1 - P_2)(P_1 - P_3)} = \frac{3(-2 - 0)}{(-2 + 1 + j)(-2 + 1 - j)} \\
 &= \frac{-6}{(-1 + j)(-1 - j)(1 + j)(1 - j)} = \frac{-6}{1 + 1} = -3
 \end{aligned}$$

For pole at $P_2 = -1 + j$
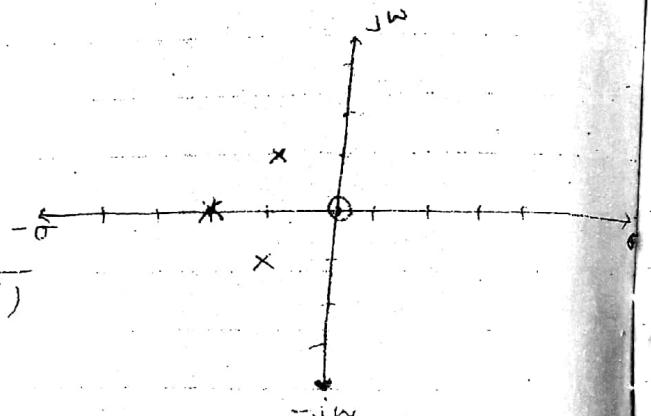
$$\begin{aligned}
 k_2 &= \frac{k(P_2 - z_1)}{(P_2 - P_1)(P_2 - P_3)} = \frac{3(-1 - j - 0)}{(-1 - j + 2)(-1 - j + 1 - j)} \\
 &= \frac{-3 - 3j}{(1 - j)(-2j)} = \frac{3 + 3j}{2j + 2} \\
 &= \frac{3 + 3j}{2j + 2} \times \frac{2 - 2j}{2 - 2j} = \frac{6 - 6j + 6j + 6}{4} = \frac{12}{4} = 3
 \end{aligned}$$



For pole at $P_3 = -1+j$

$$\begin{aligned}
 K_3 &= \frac{K(P_3 - Z_1)}{(P_3 - P_1)(P_3 - P_2)} = \frac{3(-1+j-0)}{(-1+j+2)(-1+j+1+j)} \\
 &= \frac{-3+3j}{(1+j)2j} = \frac{-3+3j}{-2+2j} \\
 &= \frac{-3+3j}{-2+2j} \times \frac{-2-2j}{-2-2j} = \frac{6+6j-6j+6}{4+4} = \frac{12}{8} = 1.5
 \end{aligned}$$

$$\therefore OT(s) = -\frac{3}{s+2} + \frac{1.5}{s+1+j} + \frac{1.5}{s+1-j}$$

Taking inverse Laplace transform:

$$T(t) = -3e^{-2t} + 1.5e^{-(1+j)t} + 1.5e^{-(1-j)t}$$

[NOTE: K_3 can be calculated directly as,

$$K_3 = K_2 = 1.5$$

(K_2 and K_3 are complex conjugate.)]

Q.5 Given:

$$Q(s) = s^3 + 2s^2 + 2s + 40$$

R-H array

$$\begin{array}{ccc}
 s^3 & 1 & 2 \\
 s^2 & 2 & 40 \\
 s^1 & b_1 = -18 & 0 \\
 s^0 & 40
 \end{array}$$

$$b_1 = -\frac{1}{2} \begin{vmatrix} 1 & 2 \\ 2 & 40 \end{vmatrix}$$

$$= -\frac{1}{2} (40-4) = -18$$

Here, 1st column has two sign changes. Therefore (3)


38

two poles are lies on Right half of s plane so, the system is unstable.

Q.6 Here, $H(s) = \frac{10s}{(s+1)(s+3)}$

Poles are at, $s = -1, -3$

zero at, $s = 0$

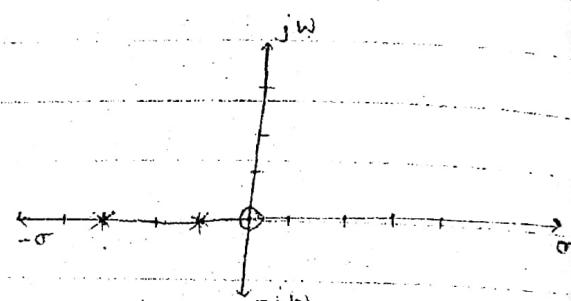

Now,

$$H(s) = \frac{K_1}{s+1} + \frac{K_2}{s+3}$$

For pole at, $s = -1$

$$K_1 = \frac{K(P_1 - Z_1)}{(P_1 - P_2)} = \frac{10(-1-0)}{(-1+3)} = -5$$

For pole at, $s = -3$

$$K_2 = \frac{K(P_2 - Z_1)}{(P_2 - P_1)} = \frac{10(-3-0)}{(-3+1)} = 15$$

$$H(s) = \frac{-5}{s+1} + \frac{15}{s+3}$$

Taking inverse Laplace transform

$$h(t) = -5e^{-t} + 15e^{-3t}$$

Blender note

Graphs of 3/4 of chapter 5.

Q.8 Given,

$$s^3 + 7s^2 + 10s + 10K = 0$$

R-H array

$$\begin{array}{ccc} s^3 & 1 & 10 \\ s^2 & 7 & \end{array}$$

$$b_1 = -\frac{1}{7} \quad | \quad 1 \quad 10$$

$$s^1 \quad b_2 = \frac{10-10K}{7} \quad 0$$

$$= \frac{1}{7}(70-10K) = \frac{10-10K}{7}$$

$$s^0 \quad c_1 = 10K$$

The system to be stable, first column should have same sign. for this, $10K > 0$ i.e. $K > 0$

and, $10 - \frac{10K}{7} > 0$ i.e. $70 > 10K$
 $7 > K$

Required Range of K's

$$0 < K < 7$$

Now, check for $A = 7$

R-H array

$$\begin{array}{ccc} s^3 & 1 & 10 \\ s^2 & 7 & \end{array}$$

$$s^1 \quad 0$$

s^0 can not determine

Replace 0 by small number ϵ then,

R-H array

$$\begin{array}{ccc} s^3 & 1 & 10 \\ s^2 & 7 & 70 \\ s^1 & \epsilon & 0 \end{array}$$


$$s^0 \quad 70$$

(4)


40

stability depends on ϵ . If $\epsilon > 0$, system is stable for A_2
 if $\epsilon < 0$, system is unstable for $A = 7$.

Q.9 Given circuit,

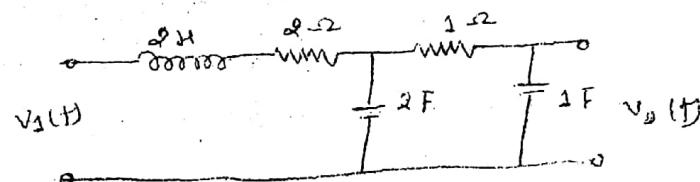

Transformed circuit is,

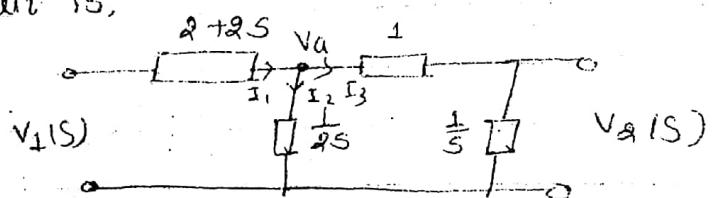

Applying KCL

$$I_1 = I_2 + I_3$$

$$\frac{V_1(s) - V_a}{2+2s} = V_a \times 2s + V_a - V_2(s)$$

$$\frac{V_1(s) - V_a}{2+2s} = V_a \times 2s + V_a - V_2(s)$$

$$V_a \left[\frac{1}{2+2s} + 2s + 1 \right] = \frac{V_1(s) + V_2(s)}{2+2s}$$

$$V_a \left[\frac{1 + 4s + 4s^2 + 2 + 2s}{2+2s} \right] = \frac{V_1(s) + (2+2s)V_2(s)}{(2+2s)}$$

$$V_a = \frac{V_1(s) + (2+2s)V_2(s)}{(4s^2 + 6s + 3)}$$

$$V_2(s) = \frac{\frac{1}{s} \times V_a(s)}{1 + \frac{1}{s}} \quad \therefore \quad \frac{V_a(s)}{(s+1)}$$

$$V_a(s) = V_1(s) + 1.9 + 9s \quad (1.1)$$

$$\frac{V_2(s)}{V_1(s)} \left[1 - \frac{2+2s}{(s+1)(4s^2+6s+3)} \right] = \frac{V_1(s)}{(s+1)(4s^2+6s+3)}$$

$$\frac{V_2(s)}{V_1(s)} \left[\frac{4s^3+6s^2+3s+1s^2+6s+3 - 2 - 2s}{(s+1)(4s^2+6s+3)} \right] = \frac{V_1(s)}{(s+1)(4s^2+6s+3)}$$

$$\frac{V_2(s)}{V_1(s)} = \frac{1}{4s^3+10s^2+7s+1}$$

S.10: R-H criteria states "The network or system described by a transfer function for which $P(s)$ is the denominator polynomial, is stable if there are no changes of sign in first column of the array."

Given,

$$Q(s) = 5s^5 + 3s^4 + 2s^3 + 2s^2 + s + 1$$

R-H array

$$\begin{array}{ccccc} s^5 & 5 & 2 & 1 & \\ s^4 & 3 & 2 & 1 & \\ s^3 & b_1 = -\frac{4}{3} & b_2 = -\frac{2}{3} & 0 & \\ s^2 & 4 = \frac{1}{3} & 1 & & \\ s^1 & d_1 = 2 & 0 & & \\ s^0 & 1 & & & \end{array}$$

$$\begin{aligned} b_1 &= -\frac{1}{3} \begin{vmatrix} 5 & 2 \\ 3 & 2 \end{vmatrix} \\ &= -\frac{1}{3} (10 - 6) = -\frac{4}{3} \end{aligned}$$

$$\begin{aligned} b_2 &= -\frac{1}{3} \begin{vmatrix} 5 & 1 \\ 3 & 1 \end{vmatrix} = -\frac{2}{3} \end{aligned}$$

$$c_1 = \frac{3}{4} \begin{vmatrix} 3 & 2 \\ -4 & -\frac{2}{3} \end{vmatrix}$$

First column of R-H array

has two sign changes. So,


two poles are lies on

right half of s -plane so the system is unstable.

$$\begin{aligned} &= \frac{3}{4} \left(-2 + \frac{8}{3} \right) = \frac{3}{4} \times \frac{2}{3} = \frac{1}{2} \\ d_1 &= -2 \begin{vmatrix} -4 & 2 \\ 1 & 1 \end{vmatrix} = -2 \left(-\frac{4}{3} + \frac{2}{3} \right) \\ &= -2 \times \frac{-6}{6} = 2 \quad (5) \end{aligned}$$

42

Q7. Transformed circuit is,

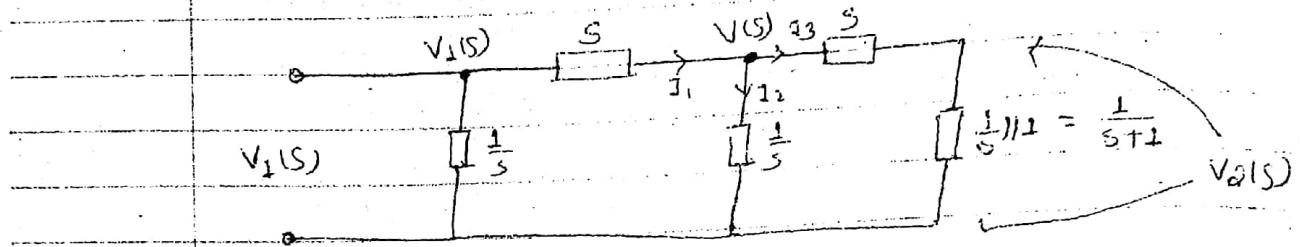

Apply KCL,

$$I_1 = I_2 + I_3$$

$$\frac{V_1(s) - V(s)}{s} = \frac{V(s)}{1/s} + \frac{V(s) - V_2(s)}{s}$$

$$\frac{V(s)}{(s)} + sV(s) + \frac{V(s)}{s} = \frac{V_1(s) + V_2(s)}{s}$$

$$V(s) \left[\frac{1}{s} + s + \frac{1}{s} \right] = \frac{V_1(s) + V_2(s)}{s}$$

$$V(s) = \frac{V_1(s) + V_2(s)}{(s^2 + 2)}$$

NOW,

$$V_2(s) = \frac{\left(\frac{1}{s+1} \right) V(s)}{s + \frac{1}{(s+1)}} = \frac{1}{(s^2 + s + 1)} V(s)$$

$$V_2(s) = \frac{1}{(s^2 + s + 1)} \frac{V_1(s) + V_2(s)}{(s^2 + 2)}$$

$$V_2(s) = \frac{1}{s^4 + 2s^3 + 3s^2 + 2s + 2} [V_1(s) + V_2(s)]$$

$$V_2(s) = \frac{1}{s^4 + 3s^3 + 3s^2 + 2s + 2} [V_1(s) + V_2(s)]$$

$$V_2(s) \left[1 - \frac{1}{s^4 + s^3 + 3s^2 + 2s + 2} \right] = \frac{V_1(s)}{(s^4 + s^3 + 3s^2 + 2s + 2)}$$

$$V_2(s) \left[\frac{s^4 + s^3 + 3s^2 + 2s + 2 - 1}{s^4 + s^3 + 3s^2 + 2s + 2} \right] = \frac{V_1(s)}{(s^4 + s^3 + 3s^2 + 2s + 2)}$$

$$\frac{V_2(s)}{V_1(s)} = \frac{1}{s^4 + s^3 + 3s^2 + 2s + 1}$$




Name:

Roll:

Subject:

U6

Assignment 5: Solution

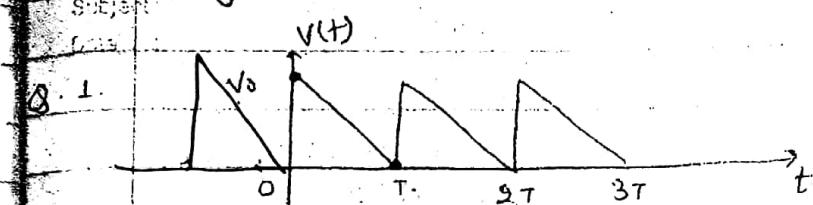

(0, V₀)

(T, 0)

$$v - V_0 = \frac{0 - V_0}{T - 0} (t - 0)$$

$$v = -\frac{V_0}{T} t + V_0$$

Here Period, T = T

$$\omega_0 = \frac{2\pi}{T}$$

$$\text{and, } v(t) = \begin{cases} -\frac{V_0}{T} t + V_0 & \text{for } 0 \leq t < T \\ \dots & \end{cases}$$

Correct as

Now, Trigonometric Fourier series expansion is given as,

$$v(t) = a_0 + \sum_{n=1}^{\infty} [a_n \cos n\omega_0 t + b_n \sin n\omega_0 t]$$

$$\begin{aligned} \text{Where, } a_0 &= \frac{1}{T} \int_0^T v(t) dt = \frac{1}{T} \int_0^T -\frac{V_0}{T} t dt \\ &= -\frac{V_0}{T^2} \left[\frac{t^2}{2} \right]_0^T = -\frac{V_0}{T^2} \left[\frac{T^2}{2} - 0 \right] \\ &= -\frac{V_0}{2} \end{aligned}$$

$$\begin{aligned} a_n &= \frac{2}{T} \int_0^T v(t) \cos n\omega_0 t dt = \frac{2}{T} \int_0^T -\frac{V_0}{T} t \cos n\omega_0 t dt \\ &= -\frac{2V_0}{T^2} \left[\frac{t \sin n\omega_0 t}{n\omega_0} + \frac{\cos n\omega_0 t}{n^2\omega_0^2} \right]_0^T \\ &= -\frac{2V_0}{T^2} \left[\frac{T \sin n\frac{2\pi}{T}}{n \frac{2\pi}{T}} + \frac{\cos n\frac{2\pi}{T}}{n^2 \left(\frac{2\pi}{T}\right)^2} - 0 - \frac{\cos 0}{n^2 \left(\frac{2\pi}{T}\right)^2} \right] \\ &= -\frac{2V_0}{T^2} \left[\frac{T \sin n\frac{2\pi}{T}}{n \frac{2\pi}{T}} + \frac{(cos n\frac{2\pi}{T}) - 1}{n^2 \left(\frac{2\pi}{T}\right)^2} \right] \end{aligned}$$

15

$$= -\frac{2V_0}{T} \left[\frac{1}{n^2 \omega_0^2} - \frac{1}{n^2 \omega_0^2} \right]$$

$$= 0$$

$$b_n = \frac{2}{T} \int_0^T v(t) \sin n \omega_0 t dt$$

$$= \frac{2}{T} \int_0^T \frac{-V_0 t}{T} \sin n \omega_0 t dt$$

$$= -\frac{2V_0}{T^2} \int_0^T t \sin n \omega_0 t dt$$

$$= -\frac{2V_0}{T^2} \left[-t \cos n \omega_0 t + \frac{\sin n \omega_0 t}{n \omega_0} \right]_0^T$$

$$= -\frac{2V_0}{T^2} \left[-\frac{T \cos 2n\pi}{n \omega_0} + \frac{\sin 2n\pi}{n^2 \omega_0^2} + 0 - \frac{\sin 0}{n^2 \omega_0^2} \right]$$

$$= -\frac{2V_0}{T^2} \left[-\frac{T}{n \omega_0} + 0 \right]$$


$$= \frac{2V_0}{T n \times 2\pi}$$

$$= \frac{V_0}{n \pi}$$

$$\therefore v(t) = \frac{-V_0}{2} \sum_{n=1}^{\infty} \left[\frac{V_0}{n \pi} \sin \frac{2\pi n t}{T} \right]$$

Q.2.

Given waveform:

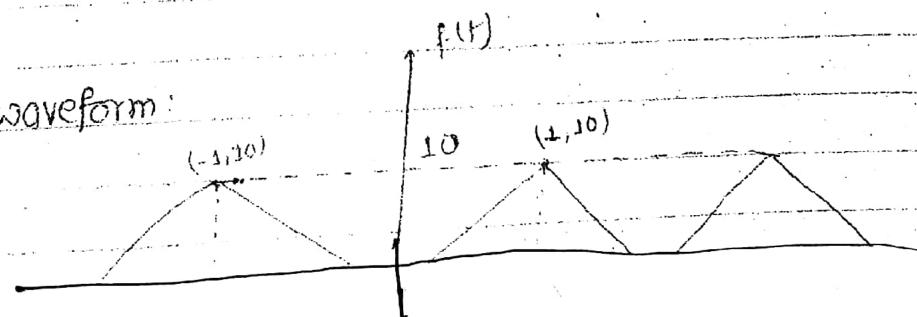

Time period, $T = 2$

$$\omega_0 = \frac{2\pi}{T} = \pi$$

$$f(t) = \begin{cases} -10t & \text{for } -1 \leq t < 0 \\ +10t & \text{for } 0 \leq t \leq 1 \end{cases}$$

Here function $f(t)$ is even function so, it has $b_m = 0$.

Now, trigonometric fourier series becomes,

$$f(t) = a_0 + \sum_{n=1}^{\infty} a_n \cos n\omega_0 t$$

$$\text{where } a_0 = \frac{2}{T} \int_0^{T/2} f(t) dt = \frac{2}{2} \int_0^1 10t dt = 10 \left[\frac{t^2}{2} \right]_0^1 = 5$$

$$\text{Now, } a_n = \frac{4}{T} \int_0^{T/2} f(t) \cos n\omega_0 t dt$$

$$= \frac{4}{2} \int_0^1 10t \cos nt dt$$

$$= 20 \int_0^1 t \cos nt dt$$

$$= 20 \left[\frac{t \sin nt}{n\pi} + \frac{\cos nt}{n^2\pi^2} \right]_0^1$$

$$= 20 \left[\frac{\sin n\pi}{n\pi} + \frac{\cos n\pi}{n^2\pi^2} - 0 - \frac{\cos 0}{n^2\pi^2} \right]$$

$$= \frac{20}{n^2\pi^2} \left[(-1)^n - 1 \right]$$

47

When n is odd,


$$a_n = -\frac{40}{n^2 \pi^2}$$

When n is even, $a_n = 0$

$$\therefore f(t) = 5 + \sum_{n=1}^{\infty} \left(-\frac{40}{n^2 \pi^2} \right) \cos(n\pi t) \quad \text{for } n \text{ is odd}$$

$$= 5 \quad \text{for } n \text{ is even}$$

Q.

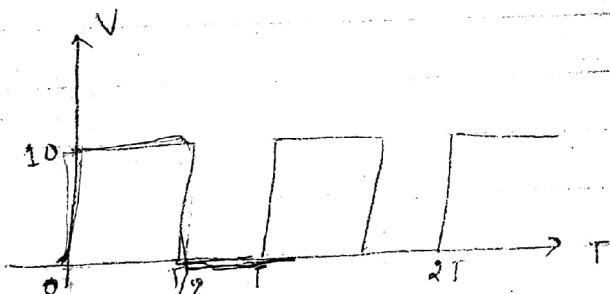

so? Here Time period, $T = T$

$$\omega_0 = \frac{2\pi}{T} \quad \text{and, } V(t) = \begin{cases} 10 & \text{for } 0 \text{ to } T/2 \\ 0 & \text{for } T/2 \text{ to } T \end{cases}$$

Trigonometric fourier series ps. given by

$$V(t) = a_0 + \sum_{n=1}^{\infty} a_n \cos(n\omega_0 t) + b_n \sin(n\omega_0 t)$$

$$\text{Where, } a_0 = \frac{1}{T} \int_0^T V(t) dt$$

$$= \frac{1}{T} \int_0^{T/2} 10 dt = \frac{10}{T} \left[t \right]_0^{T/2} = \frac{10}{T} \times \frac{T}{2} = 5$$



Everest

Engineering

College

Sil.

Name:

Roll:

$$a_n = \frac{2}{T} \int_0^T v(t) \cos n\omega_0 t dt$$

$$= \frac{2}{T} \int_0^{T/2} 10 \cos n\omega_0 t dt$$

$$= \frac{20}{T} \left[\frac{\sin n\omega_0 t}{n\omega_0} \right]_0^{T/2}$$

$$= \frac{20}{T \times 2\pi \times n} \left[\sin \frac{n\pi}{T} - \sin 0 \right]$$

$$= \frac{10}{n\pi} [\sin n\pi - 0] = 0$$

$$b_n = \frac{2}{T} \int_0^T v(t) \sin n\omega_0 t dt$$

$$= \frac{2}{T} \int_0^{T/2} 10 \sin n\omega_0 t dt$$

$$= \frac{20}{T} \left[- \frac{\cos n\omega_0 t}{n\omega_0} \right]_0^{T/2}$$

$$= \frac{20}{T \times 2\pi \times n} \left[- \cos \frac{n\pi}{T} + \cos 0 \right]$$

$$= \frac{10}{n\pi} \left[- \cos n\pi + 1 \right]$$

$$= \frac{10}{n\pi} [1 - (-1)^n]$$

when n is odd, $b_n = \frac{20}{n\pi}$

when n is even, $b_n = 0$

$$= \frac{2}{T} \cdot V \int_{T/2}^T \cos \omega_0 n t dt$$

$$= \frac{2V}{T} \left[\frac{\sin \omega_0 n t}{\omega_0 n} \right]_{T/2}^T$$

$$= \frac{2V}{T \times 2\pi \times n} \left[\frac{\sin 2\pi n \times T}{T} - \frac{\sin 2\pi n \times T/2}{T/2} \right]$$

$$= \frac{V}{n\pi} \left[\sin 2\pi n - \sin \pi n \right] = 0$$

$$b_n = \frac{2}{T} \int_0^T f(t) \sin \omega_0 n t dt$$

$$= \frac{2V}{T} \int_{T/2}^T \sin \omega_0 n t dt$$

$$= \frac{2V}{T} \left[-\frac{\cos \omega_0 n t}{\omega_0 n} \right]_{T/2}^T$$

$$= \frac{2V}{T} \left[-\frac{\cos 2\pi n \times T}{T} + \frac{(\cos 2\pi n \times T/2)}{T/2} \right]$$

$$= \frac{V}{n\pi} \left[-\cos 2\pi n + \cos \pi n \right]$$

$$= \frac{V}{n\pi} \left[-1 + (-1)^n \right]$$

$$= \frac{V}{n\pi} \left[(-1)^n - 1 \right]$$

When n is even, $b_n = 0$

When n is odd, $b_n = -\frac{2V}{n\pi}$


19

Thus

$$v(t) = 5 + \sum_{n=1}^{\infty} \left(\frac{a_0}{nn} \right) \sin n\omega_0 t \quad \text{when } n \text{ is odd}$$

$$= 5$$

when n is even

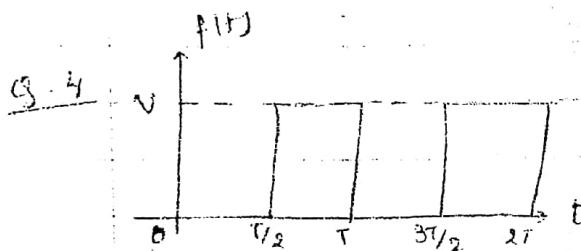

Sol: Time period, $T = T$

$$\omega_0 = \frac{2\pi}{T} \quad \text{and, } f(t) = \begin{cases} 0 & \text{for } 0 \leq t < T/2 \\ V & \text{for } T/2 \leq t < T \end{cases}$$

We have,

Trigonometric fourier series expansion,

$$f(t) = a_0 + \sum_{n=1}^{\infty} a_n \cos \omega_0 n t + b_n \sin \omega_0 n t$$

$$\text{where, } a_0 = \frac{1}{T} \int_0^T f(t) dt$$

$$= \frac{1}{T} \left[\int_0^{T/2} 0 dt + \int_{T/2}^T V dt \right]$$

$$= \frac{V}{T} \left[t \right]_{T/2}^T = \frac{V}{T} \left[T - \frac{T}{2} \right] = \frac{V}{T} \times \frac{T}{2}$$


$$= \frac{V}{2}$$

$$a_n = \frac{2}{T} \int_0^T f(t) \cos \omega_0 n t dt$$

5)

$$f(t) = 5 + \sum_{n=1}^{\infty} \left(-\frac{2V}{n\pi} \right) \sin(n\pi t) \quad \text{when } n \text{ is odd}$$

$$= 5$$

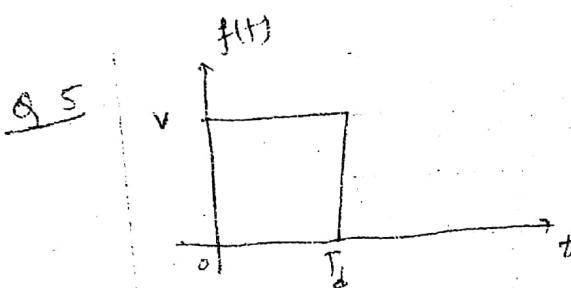when n is even:

so? Here,

$$f(t) = \begin{cases} V & \text{for } 0 < t < T_d \\ 0 & \text{otherwise} \end{cases}$$

we have

$$F(j\omega) = F[f(t)] = \int_{-\infty}^{\infty} f(t) e^{-j\omega t} dt$$

$$= \int_0^{T_d} V e^{-j\omega t} dt$$

$$= V \left[\frac{e^{-j\omega t}}{-j\omega} \right]_0^{T_d}$$

$$= -\frac{V}{j\omega} \left[e^{-j\omega T_d} - 1 \right]$$

$$= V \left(\frac{1 - e^{-j\omega T_d}}{j\omega} \right)$$

$$= V \left[\frac{e^{j\omega \frac{T_d}{2}} - e^{-j\omega \frac{T_d}{2}}}{j\omega} \right] = V \left[\frac{2 \sin(\omega \frac{T_d}{2})}{j\omega} \right]$$

$$= \frac{2V}{\omega} e^{-j\omega \frac{T_d}{2}}$$

$$\left[\frac{e^{j\omega \frac{T_d}{2}} - e^{-j\omega \frac{T_d}{2}}}{2j} \right]$$

$$= \frac{2V}{\omega} e^{-j\omega \frac{T_d}{2}} \sin(\omega \frac{T_d}{2})$$


i.e., $\omega = \pi / T_d$

$$= \frac{-j\omega \frac{T_d}{2}}{\omega} \sin(\omega \frac{T_d}{2})$$



Additional / not required in this question


Amplitude response:

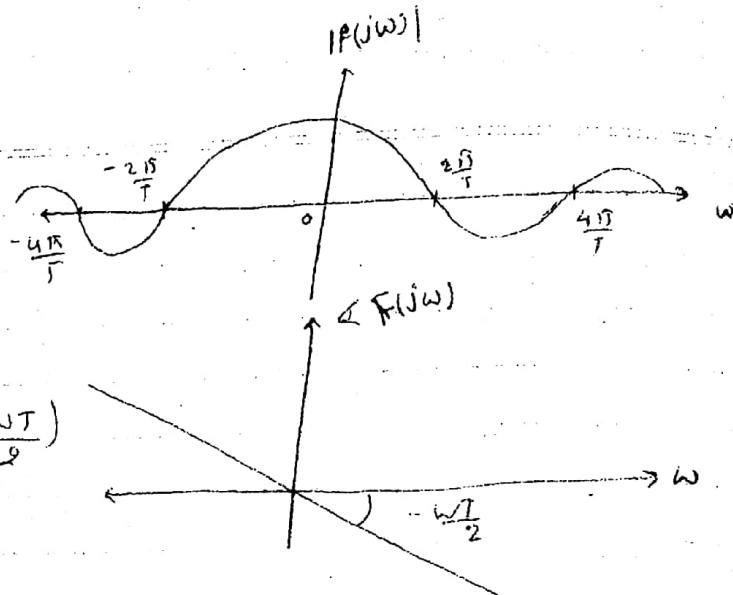

Phase response

$$\angle F(jw) = -\frac{(wT)}{2}$$

6. Given Signal.

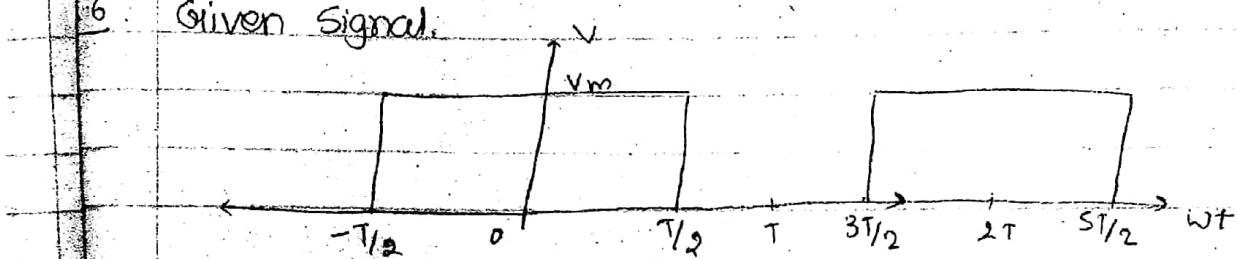

or Here, Time period, $T = 2T$

$$\omega = \frac{d\theta}{T} = \frac{\pi}{T}$$

$$v(t) = \begin{cases} V_m & \text{for } -T/2 \text{ to } T/2 \\ 0 & \text{otherwise } T/2 \text{ to } 3T/2 \end{cases}$$

Trigonometric Fourier Series expansion,

$$v(t) = a_0 + \sum_{n=1}^{\infty} a_n \cos n\omega t + b_n \sin n\omega t$$

$$\text{where, } a_0 = \frac{1}{T} \int_0^T v(t) dt$$

$$= \frac{1}{2T} \int_{-T/2}^{T/2} V_m dt$$

$$= \frac{V_m}{2T} \left[t \right]_{-T/2}^{T/2}$$

$$= \frac{V_m}{2T} \left[\frac{T}{2} + \frac{T}{2} \right] = \frac{V_m}{2}$$

$$a_n = \frac{2}{T} \int_0^T v(t) \cos \omega_0 n t dt$$

$$= \frac{2}{2T} \int_{-\frac{T}{2}}^{\frac{T}{2}} V_m \cos \omega_0 n t dt$$

$$= \frac{V_m}{T} \left[\frac{\sin \omega_0 n t}{\omega_0 n} \right]_{-\frac{T}{2}}^{\frac{T}{2}}$$

$$= \frac{V_m}{T \times \frac{\pi}{2} \times n} \left[\sin \frac{\pi}{T} n \frac{I}{2} - \sin \frac{\pi}{T} n * (-\frac{I}{2}) \right]$$

$$= \frac{V_m}{n \pi} \left[\sin \frac{n \pi}{2} + \sin \frac{n \pi}{2} \right]$$

$$= \frac{V_m}{n \pi} [2 \sin \frac{n \pi}{2}]$$

$$\text{when } n \text{ is odd, } a_n = \frac{2V_m}{n \pi} \left[\sin \frac{n \pi}{2} \right]$$

when n is even, $a_n = 0$

$$b_n = \frac{2}{T} \int_0^T v(t) \sin \omega_0 n t dt$$

$$= \frac{2}{2T} \int_{-\frac{T}{2}}^{\frac{T}{2}} V_m \sin \omega_0 n t dt$$

$$= \frac{V_m}{T} \left[\frac{-\cos \omega_0 n t}{\omega_0 n} \right]_{-\frac{T}{2}}^{\frac{T}{2}}$$

$$= \frac{V_m}{n \pi} \left[-\cos \frac{\pi}{T} n \times \frac{I}{2} + \cos \frac{\pi}{T} n \times -\frac{I}{2} \right] \Rightarrow \frac{V_m}{n \pi} \left[-\cos \frac{n \pi}{2} + \cos \frac{n \pi}{2} \right]$$


54

$$\therefore V(t) = \frac{V_m}{2} + \sum_{n=1}^{\infty} \left(\frac{a V_m}{n \pi} \sin \frac{n \pi t}{T} \right) \cos \omega_0 n t \quad \text{for } n \text{ is odd}$$

$$= \frac{V_m}{2} \quad \text{for } n \text{ is even}$$

Q. 7 Refer note (same question as ques no. 2)

Q. 8

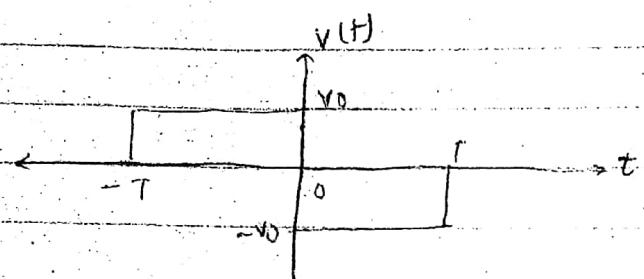

$$\text{Here, } v(t) = \begin{cases} v_0 & \text{for } -T \leq t < 0 \\ -v_0 & \text{for } 0 \leq t \leq T \end{cases}$$

We have fourier transform of $v(t)$

$$V(j\omega) = F(v(t)) = \int_{-\infty}^{\infty} v(t) e^{-j\omega t} dt$$

$$= \int_{-T}^{0} v_0 e^{-j\omega t} dt + \int_{0}^{T} -v_0 e^{j\omega t} dt$$

$$= v_0 \left[\frac{e^{-j\omega t}}{-j\omega} \right]_0^{-T} - v_0 \left[\frac{e^{j\omega t}}{j\omega} \right]_0^T$$

$$= v_0 \left[\frac{1 - e^{j\omega T}}{-j\omega} \right] - v_0 \left[\frac{e^{j\omega T} - 1}{j\omega} \right]$$

$$= \frac{v_0}{-j\omega} \left[1 - e^{j\omega T} - e^{-j\omega T} + 1 \right]$$

05.05
2

6

$$\begin{aligned}
 &= \frac{V_0}{-j\omega} \left[\alpha - \left(e^{j\omega T} + e^{-j\omega T} \right) \right] \\
 &= \frac{\alpha V_0}{-j\omega} + \frac{2V_0}{j\omega} \left[\frac{e^{j\omega T} + e^{-j\omega T}}{\alpha} \right] \\
 &= \frac{\alpha V_0}{j\omega} \left[-1 + \cos \omega T \right] \\
 &= \frac{\alpha V_0}{j\omega} \left[\cos \omega T - 1 \right].
 \end{aligned}$$