

Chapter 5

Small Signal Low Frequency Analysis model of BJT

Small Signal Parameters

The small signal current gains of BJT are;

$$\beta = \left. \frac{i_c}{i_b} \right|_{V_{CE} = \text{const}}$$

$$\alpha = \left. \frac{i_c}{i_e} \right|_{V_{CB} = \text{const}}$$

Emitter resistance (r_e):

It is the resistance offered by the base-emitter junction to the small signal i_b signal.

$$r_e = \left. \frac{v_e}{i_e} \right|_{V_{CE} = \text{const.}}$$

$$\alpha = \left. \frac{i_c}{i_b} \right|_{V_{CB} = \text{const}}$$

The small signal emitter-base resistance of BJT also called ~~also~~ called emitter resistance.

$$r_e = \left. \frac{V_{CE}}{i_c} \right|_{V_{CE} = \text{const.}}$$

Since BE junction of BJT resembles to a forward biased PN junction diode, we can calculate r_e in the similar way that we calculated dynamic resistance (r_d) of PN junction diode.

$$\text{i.e. } r_d = \frac{\eta V_T}{I}$$

taking $\eta = 1$ & $V_T = 0.026$ at room temp

$$r_d = \frac{0.026}{I}$$

$$\therefore r_e = \frac{0.026}{I_E}$$

Small signal collector-base resistance of BJT, also called collector resistance (r_c) is given by,

$$r_c = \left. \frac{V_{CB}}{i_c} \right|_{I_E = \text{const}}$$

Since collector-base junction is reverse-biased, the value of r_c is very high (M Ω).

re-model of Common-Base Configuration Small signal flow frequency Analysis of CB configuration

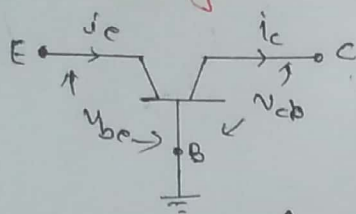


Fig: CB Configuration

Here, $V_{in} = V_{be}$
 $V_o = V_{cb}$
 $i_{in} = i_e$
 $i_o = i_c$

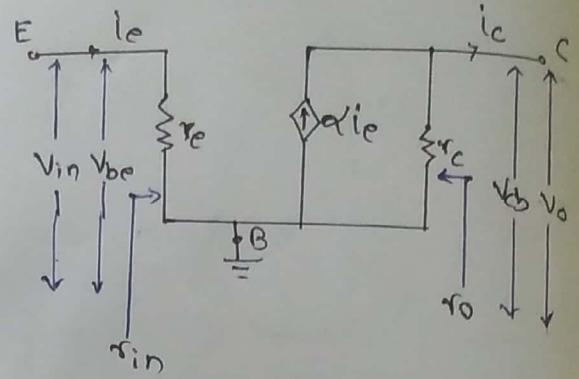


Fig: re-model of CB configuration.

i) I/P resistance (r_{in})

$$r_{in} = \frac{V_{in}}{i_{in}} = \frac{V_{be}}{i_e} = r_e$$

ii) O/P resistance

$$r_o = \frac{V_o}{i_o} = \frac{V_{cb}}{i_c} = r_c$$

When biasing resistor & voltage are connected to CB configuration, its re-model is as given below,

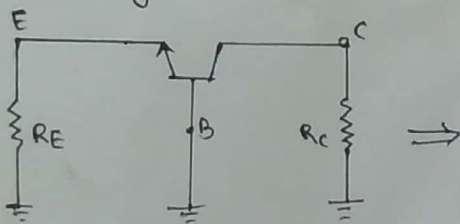


Fig: Biasing ckt

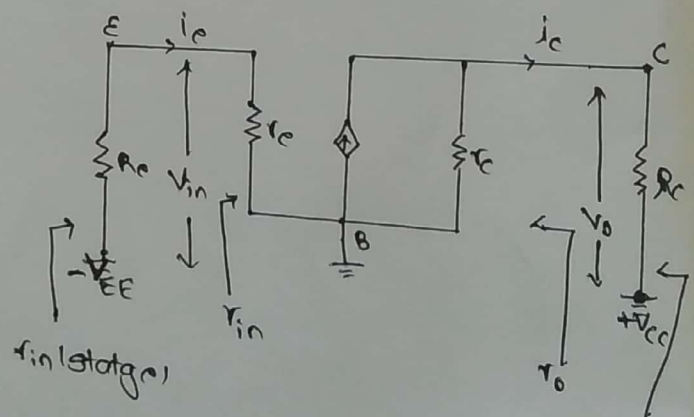


Fig: re-model of biasing ckt

iii) $r_{in(stage)} = R_E // r_e$

iv) $r_o(stage) = R_C // r_c \approx R_C$ ($\because r_c \gg R_C$)

v) Voltage Gain (A_v)

$$A_v = \frac{V_o}{V_{in}} = \frac{i_c R_C}{i_e r_e} = \frac{i_c}{i_e} \cdot \frac{R_C}{r_e} = \alpha \frac{R_C}{r_e}$$

Since $\alpha \approx 1$

$$\therefore A_v = \frac{R_C}{r_e}$$

vi) Current Gain (A_i) = $\frac{i_o}{i_{in}} = \frac{i_c}{i_e} = \alpha \approx 1$

When a transistor is driven by source voltage V_s with resistance r_s & load resistance R_L , then its r_e -model is,

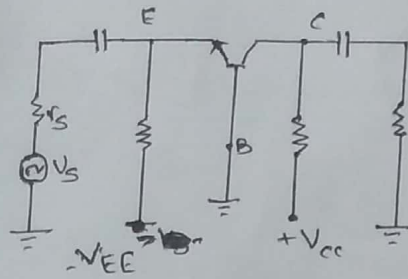


Fig: CE amplifier circuit


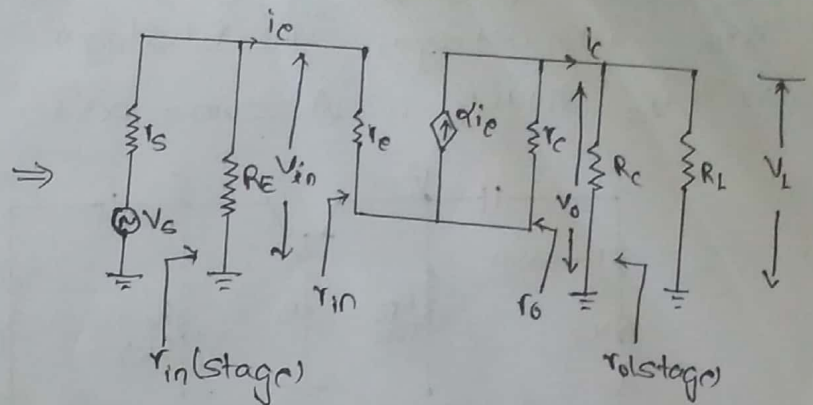


Fig: r_e -model of CE amplifier

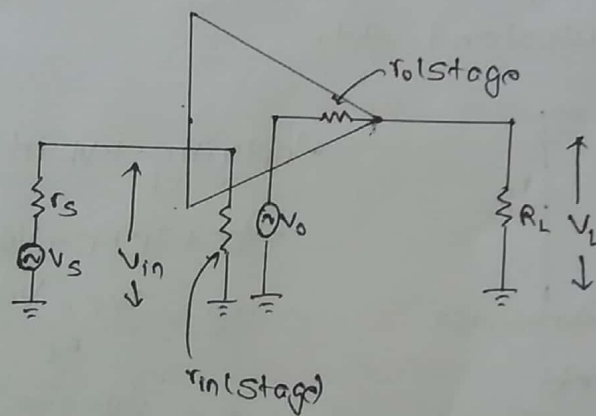The transistor amplifier can be represented by the transistor block as shown below,



Overall Gain (voltage) (V_L/V_s)

$$\frac{V_L}{V_s} = \frac{V_L}{V_0} \times \frac{V_0}{V_{in}} \times \frac{V_{in}}{V_s} = \frac{V_L}{V_0} \times A_v \times \frac{V_{in}}{V_s} = A_v \times \left(\frac{V_L}{V_0} \right) \times \left(\frac{V_{in}}{V_s} \right)$$

$$\therefore \frac{V_L}{V_s} = A_v \times \left(\frac{R_L}{r_{ol(stage)} + R_L} \right) \times \left(\frac{r_{in(stage)}}{r_{in(stage)} + r_s} \right)$$

Overall current Gain (i_L/i_s)


we have, $i_L = V_L/R_L$

$$\& i_s = \frac{V_s}{r_s + r_{in(stage)}}$$

$$\therefore \frac{i_L}{i_s} = \frac{V_L/R_L}{\frac{V_s}{r_s + r_{in(stage)}}} = \frac{V_L}{V_s} \times \frac{r_s + r_{in(stage)}}{R_L}$$

$$\therefore \frac{i_L}{i_s} = \frac{V_L}{V_s} \left(\frac{r_s + r_{in(stage)}}{R_L} \right)$$

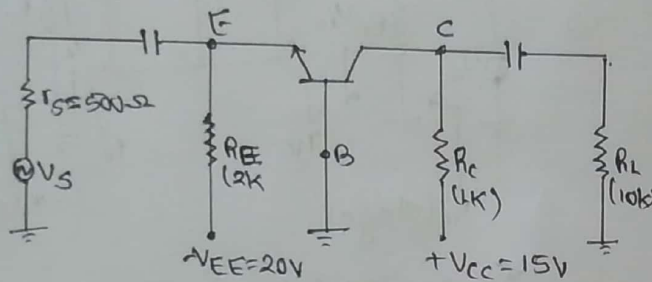For the transistor amplifier ckt shown below, draw r_e -model & find
 i) r_{in} ii) r_{in} (stage), iii) r_o (stage) iv) A_v
 v) V_L/V_S vi) i_L/i_S . Assume $\alpha = 1$.



Soln: We have, $r_e = \frac{0.026}{I_E}$

To find I_E , need to perform dc analysis of given ckt. For this, draw dc equivalent ckt.

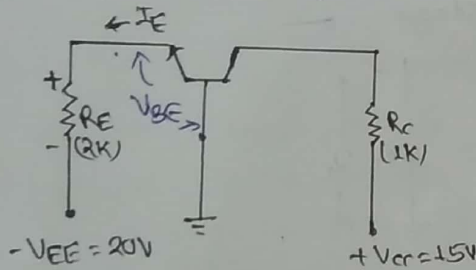


Fig: dc eqvt. ckt

Applying KVL at i/p loop,

$$-V_{EE} + I_E R_E + V_{BE} = 0$$


$$\Rightarrow I_E = \frac{V_{EE} - V_{BE}}{R_E}$$

$$\text{or, } I_E = \frac{20 - 0.7}{2 \times 10^3}$$

$$\therefore I_E = 9.65 \text{ mA}$$

$$\text{Thus, } r_e = \frac{0.026}{9.65 \times 10^{-3}} = 2.69 \Omega$$

Now r_e -model of given ckt is,

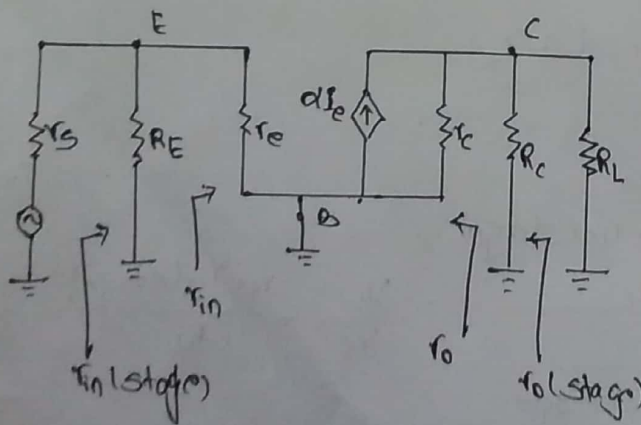

Here, i) $r_{in} = r_e$

$$\therefore r_{in} = 2.69 \Omega$$

$$ii) r_{in}(\text{stage}) = R_E // r_e = R_E // r_{in} = 2000 // 2.69$$

$$= \frac{2000 \times 2.69}{2000 + 2.69} = 2.68 \Omega$$

$$iii) r_o(\text{stage}) = R_C // r_c \approx R_C = 1K\Omega$$

$$iv) A_v = \alpha \left(\frac{R_C}{r_e} \right) = 1 \times \left(\frac{1000}{2.69} \right) = 371.74$$

$$v) \frac{V_L}{V_S} = A_v \left(\frac{r_{in}(\text{stage})}{r_s + r_{in}(\text{stage})} \right) \left(\frac{R_L}{R_L + r_o(\text{stage})} \right)$$

$$= 371.74 \times \left(\frac{2.68}{500 + 2.68} \right) \times \left(\frac{10}{10 + 1} \right)$$

$$= 1.798$$

$$vi) \frac{i_L}{i_s} = \frac{V_L}{V_S} \times \left(\frac{r_s + r_{in}(\text{stage})}{R_L} \right)$$

$$= 1.798 \times \left(\frac{2.68 + 500}{10,000} \right)$$

$$= 0.09$$

Small Signal Analysis of Common Emitter Configuration (re-model of CE configuration)

- 1) Emitter bypassed (with bypass capacitor)
- 2) Emitter unbypassed (without bypass capacitor)

1) Emitter Bypassed

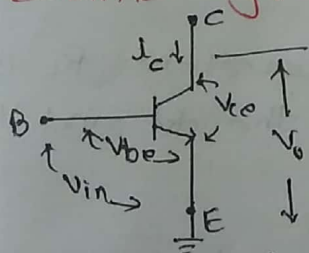


Fig: CE configuration

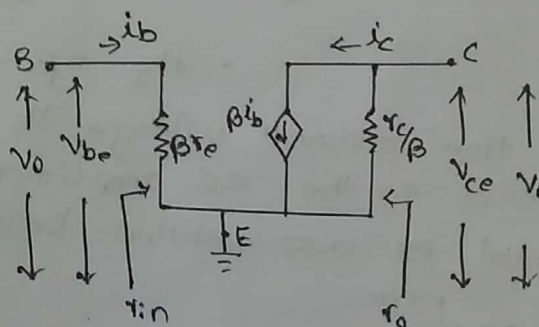


Fig: re-model of CE configuration

Here, $V_{in} = V_{be}$

$i_{in} = i_b$

$V_o = V_{ce}$

$i_o = -i_c$

$$\text{Input resistance, } r_{in} = \frac{V_{in}}{i_{in}} = \frac{V_{be}}{i_b} = \frac{V_{be}}{i_c/\beta} = \beta \frac{V_{be}}{i_c} = \beta \cdot r_e$$

$$\therefore r_{in} = \beta r_e$$

$$(\because i_c \approx i_e = \beta i_b \Rightarrow i_b = \frac{i_c}{\beta})$$

Output resistance, $r_o = \frac{V_o}{i_o} = \frac{V_{ce}}{I_c} = \frac{V_{ce}}{\beta I_b}$

$$r_o = \frac{r_c}{\beta}$$

If the CE transistor is biased by dc voltage then above ckt becomes,

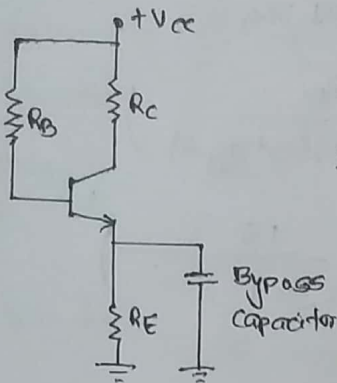


Fig: Emitter biased biasing ckt

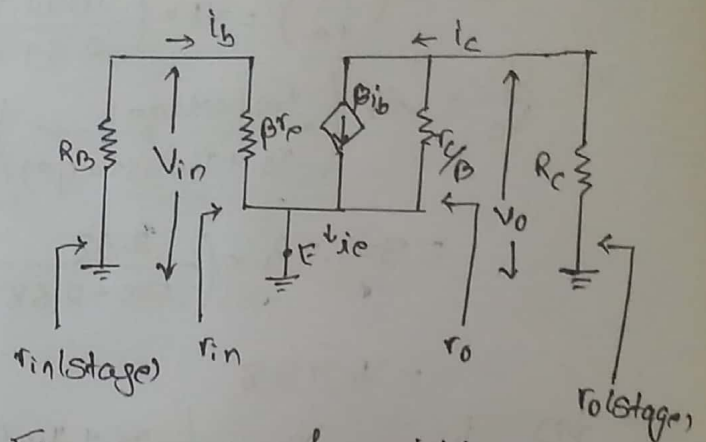


Fig: re-model of emitter bypassed CE configuration.

Here, $r_{in(stage)} = R_B // r_{in} = R_B // \beta r_e$

$$r_o(stage) = R_C // r_c \approx R_C \quad (r_c \gg R_C)$$

$$\text{Voltage gain } (A_v) = \frac{V_o}{V_{in}} = \frac{-i_c R_C}{i_b \beta r_e} = \frac{-\beta i_b R_C}{\beta r_e i_b} = -\frac{R_C}{r_e}$$

$$\therefore A_v = -\frac{R_C}{r_e}$$

(Here -ve sign indicates i_b & v_p are out of phase)

$$\text{Current gain } (A_i) = \frac{i_o}{i_{in}} = \frac{i_c}{i_b} \quad (\text{neglecting -ve sign i.e. } i_o = -i_c)$$

$$\therefore A_i = \beta$$

When the source voltage V_s & load resistance R_L is connected to the CE amplifier ckt then the ckt and its re-model is as shown below.

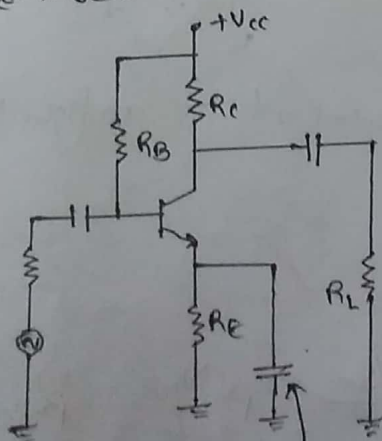


Fig: CE amplifier ckt.

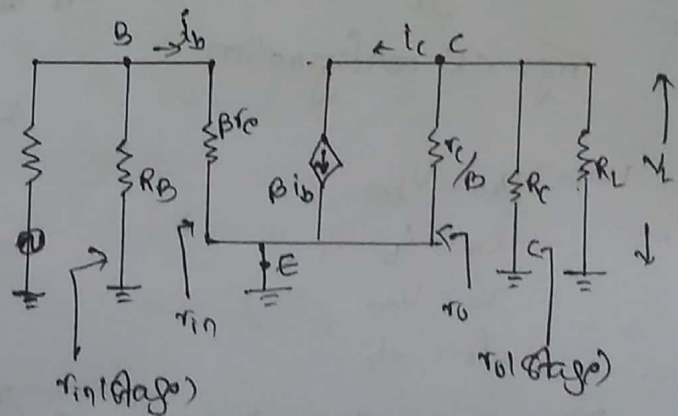



Fig: re-model of CE amplifier (Emitter bypassed)

Overall Voltage Gain (V_L/V_S)

Here,

$$\frac{V_L}{V_S} = \frac{V_L}{V_O} \times \frac{V_O}{V_{in}} \times \frac{V_{in}}{V_S}$$
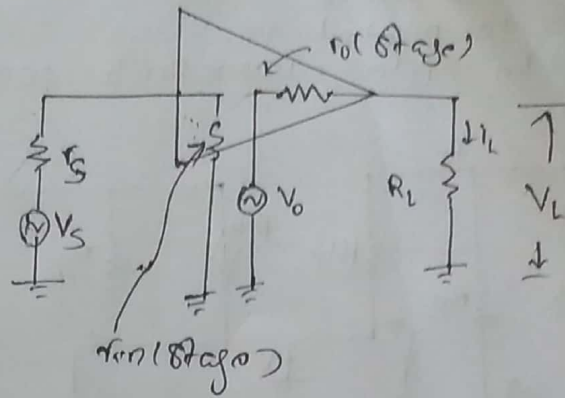
$$\therefore \frac{V_L}{V_S} = A_v \left(\frac{r_{in}(\text{Stage})}{r_s + r_{in}(\text{Stage})} \right) \times \left(\frac{R_L}{R_L + r_o(\text{Stage})} \right)$$




Overall Current Gain (I_L/I_S)

$$I_L = \frac{V_L}{R_L} \quad \& \quad I_S = \frac{V_S}{r_s + r_{in}(\text{Stage})} = \frac{V_S / R_L}{\left(\frac{r_s + r_{in}(\text{Stage})}{R_L} \right)}$$

$$\therefore \frac{I_L}{I_S} = \frac{V_L}{V_S} \left(\frac{r_s + r_{in}(\text{Stage})}{R_L} \right)$$

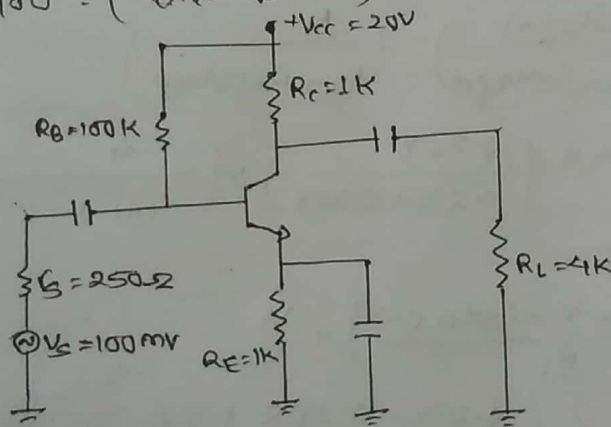For the transistor amplifier ckt shown below, find its r_o -model & r_{in} , $r_{in}(\text{Stage})$, A_v , V_L/V_S & Also find the value of V_L if $V_S = 100$ mV. (Take $\beta = 100$)



Soln: We know that,

$$r_o = \frac{0.026}{I_E}$$

To find I_E , we have to perform dc analysis of given ckt,

Applying KVL in i/p loop,

$$V_{cc} = I_B R_B + V_{BE} + I_E R_E$$

$$= \frac{I_E}{\beta} R_B + V_{BE} + I_E R_E$$

$$\Rightarrow I_E = \frac{V_{cc} - V_{BE}}{R_B/\beta + R_E}$$

$$= \frac{20 - 0.7}{\frac{100}{100} + 1} = \frac{19.3}{2} = 9.65 \text{ mA}$$

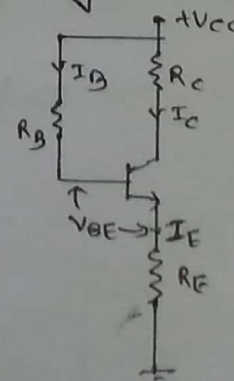


Fig: dc equivalent ckt

Thus, $r_e = \frac{0.026}{9.65 \times 10^3} = 2.69 \Omega$

Now, its r_e -model is,

i) $r_{in} = \beta r_e = 100 \times 2.69 = 269 \Omega = 0.269 \text{ K}\Omega$

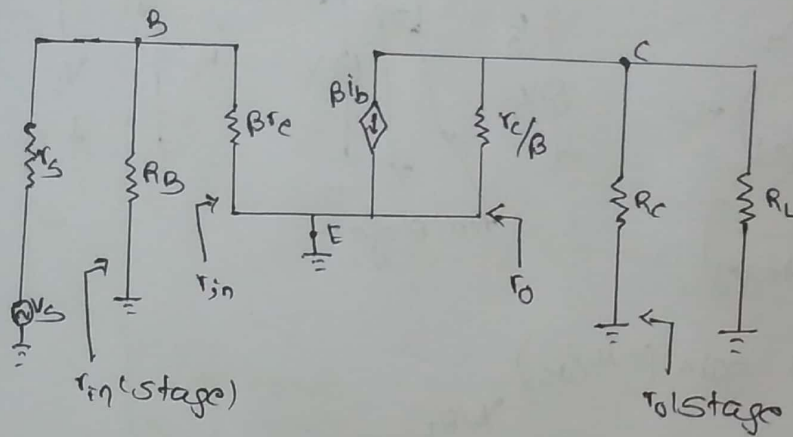


Fig: r_e -model of CE amplifier ckt

ii) $r_{in(stage)} = R_B // r_{in} = 100 // 0.269$
 $= 0.268 \text{ K}\Omega$

iii) $r_o(stage) = R_C // r_c/b \approx R_C = 1 \text{ K}$

iv) $A_v = -\frac{R_C}{r_e} = -\frac{1 \times 10^3}{2.69} = -371.74$

v) $\frac{V_L}{V_S} = A_v \left(\frac{r_{in(stage)}}{r_S + r_{in(stage)}} \right) \left(\frac{R_L}{R_L + R_o(stage)} \right)$
 $= -371.74 \times \left(\frac{0.268}{0.25 + 0.268} \right) \times \left(\frac{4}{4 + 1} \right)$
 $= -153.26$

vi) $\frac{i_L}{i_S} = \frac{A_v}{R_L} \left(\frac{r_S + r_{in(stage)}}{R_L} \right) \times \frac{V_L}{V_S}$
 $= \frac{-371.74}{4} \left(\frac{0.25 + 0.268}{4} \right) \times (-153.26)$
 $= -19.84$

vii) $V_S = 100 \text{ mV}$

We have, $\frac{V_L}{V_S} = -153.26$

$\Rightarrow V_L = -153.26 \times 100$
 $= -15.326 \text{ V}$

2) Emitter Unbypassed

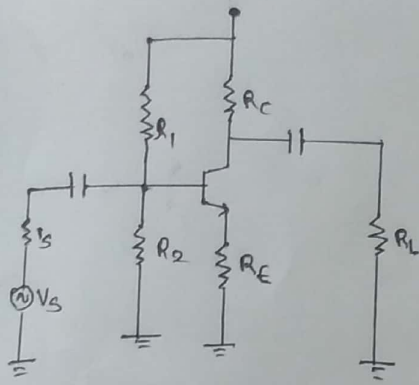


Fig: Emitter unbypassed CE configuration

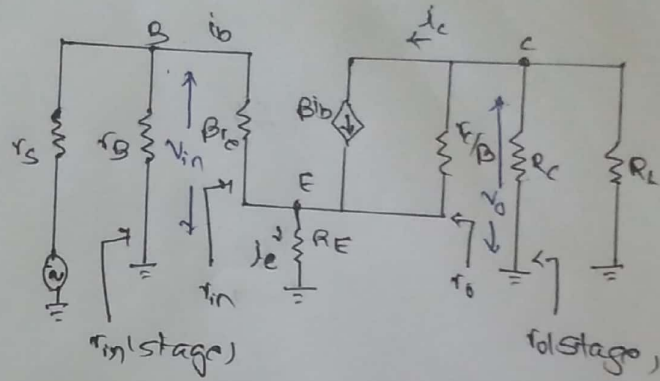


Fig: e-model of emitter unbypassed CE configuration.

Here, Input voltage (V_{in}) = $i_b \cdot \beta r_e + i_e R_E$

$$= \beta i_b r_e + \beta i_b R_E$$

$$= \beta i_b (r_e + R_E)$$

$$\text{Output voltage } (V_o) = -i_c R_C$$

$$\text{i) Input resistance } (r_{in}) = \frac{V_{in}}{i_{in}} = \frac{\beta i_b (r_e + R_E)}{i_b} = \beta (r_e + R_E)$$

$$\text{ii) Output resistance } (r_o) = r_c / \beta$$

$$\text{iii) } r_{o(stage)} = R_C \parallel r_o = R_C \parallel r_c / \beta \approx R_C$$

$$\text{iv) } r_{in(stage)} = R_B \parallel r_{in} = R_B \parallel \beta (r_e + R_E)$$

$$\text{v) Voltage gain, } A_v = \frac{V_o}{V_{in}} = \frac{-i_c R_C}{\beta i_b (r_e + R_E)} = -\frac{\beta i_b R_C}{\beta i_b (r_e + R_E)}$$

$$= -\frac{R_C}{r_e + R_E}$$


$$\text{vi) Current gain, } A_I = \frac{i_o}{i_{in}} = \frac{i_c}{i_b} \quad (\because i_o = -i_c, \text{ neglect negative sign})$$

$$= \beta$$

$$\text{vii) Overall voltage gain, } \frac{V_L}{V_S} = A_v \left(\frac{r_{in(stage)}}{r_s + r_{in(stage)}} \right) \times \left(\frac{R_L}{r_{o(stage)} + R_L} \right)$$

$$\text{viii) Overall Current gain, } \frac{i_L}{i_s} = \frac{V_L}{V_S} \times \left(\frac{r_s + r_{in(stage)}}{R_L} \right)$$

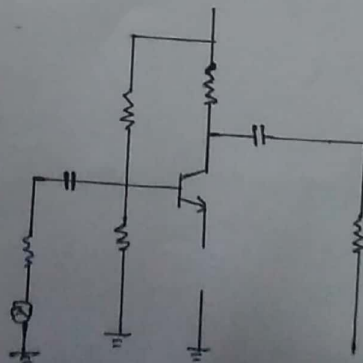For theckt diagram shown, find r_{in} , $r_{in(stage)}$, $r_{o(stage)}$ and $\frac{V_L}{V_S}$.
(Take $\beta = 100$)



$$i) \text{ Input resistance } (r_{in}) = \frac{V_{in}}{i_{in}}$$

$$\text{where, } V_{in} = i_b \cdot \beta r_e + i_o \cdot R_E = i_b \beta r_e + \beta i_b R_E \\ = \beta i_b (r_e + R_E)$$

$$\& i_{in} = i_b$$

$$\therefore r_{in} = \frac{\beta i_b (r_e + R_E)}{i_b} = \beta (r_e + R_E)$$

$$ii) r_{in}(\text{stage}) = R_B // r_{in} = R_B // \beta (r_e + R_E)$$

$$iii) r_o = r_c / \beta$$

$$iv) r_o(\text{stage}) = R_C // r_o = R_C // r_c / \beta \approx R_C \quad (R_C \ll r_c / \beta)$$

$$v) \text{ voltage gain } (A_v) = \frac{V_o}{V_{in}} = \frac{-i_c R_C}{\beta i_b (r_e + R_E)} = \frac{-\beta i_b R_C}{\beta i_b (r_e + R_E)}$$

$$\therefore A_v = \frac{-R_C}{r_e + R_E}$$


$$vi) \text{ Current gain } (A_i) = \frac{i_o}{i_{in}} = \frac{-i_c}{i_b} = \beta$$

$$vii) \text{ Overall voltage gain } \left(\frac{V_L}{V_S} \right) = A_v \left(\frac{r_{in}(\text{stage})}{r_s + r_{in}(\text{stage})} \right) \left(\frac{R_L}{R_L + r_o(\text{stage})} \right)$$

$$viii) \text{ Overall current gain, } \frac{i_L}{i_s} = \frac{V_L}{V_S} \left(\frac{r_s + r_{in}(\text{stage})}{R_L} \right)$$

For the ckt diagram given find r_{in} , $r_{in}(\text{stage})$, $r_o(\text{stage})$


A_v & V_L/V_S . | Take $\beta = 100$

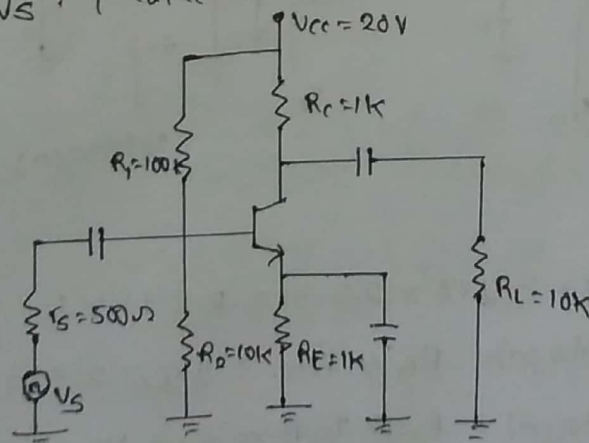

We know that,


$$r_e = \frac{0.026}{I_E}$$

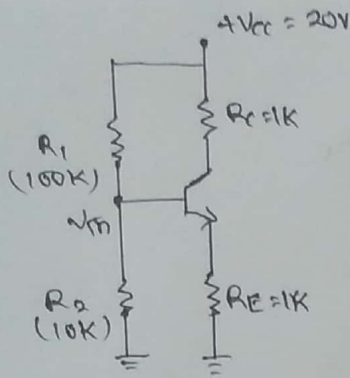To find I_E , we need to perform dc analysis of given ckt.



Thermin's
eqvt ckt \rightarrow

\Rightarrow i/p loop

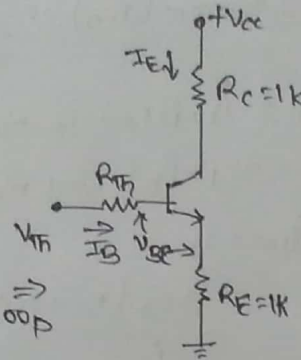

Here, $R_{Th} = R_1 // R_2 = 100 // 10 = 9.8 K\Omega$

$$V_{Th} = \frac{R_2}{R_1 + R_2} \times V_{cc} = \frac{10}{10 + 100} \times 20 = 1.81 V$$

Applying KVL at i/p loop,


$$V_{Th} = I_B R_{Th} + V_{BE} + I_E R_E$$

$$= \frac{I_E}{\beta} R_{Th} + V_{BE} + I_E R_E$$

$$\Rightarrow I_E = \frac{V_{Th} - V_{BE}}{\frac{R_{Th}}{\beta} + R_E} = \frac{1.81 - 0.7}{\frac{9.8}{100} + 1} = 1.01 mA$$

Thus, $r_e = \frac{0.026}{1.01 \times 10^{-3}} = 25.71 \Omega$

Now, the r_e -model of given ckt is,

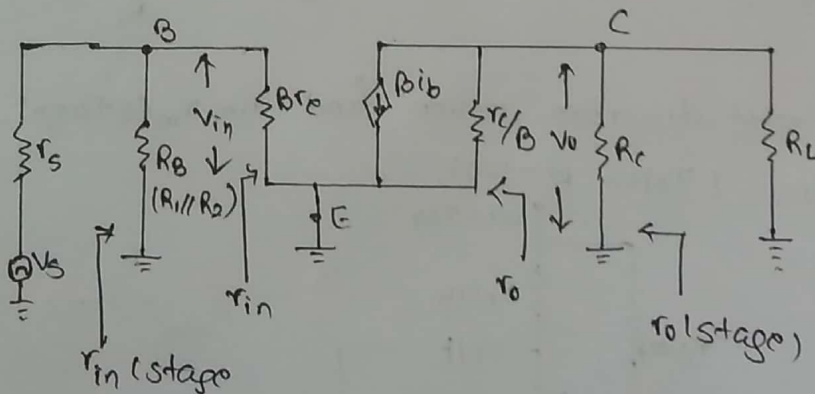

Here, i) $r_{in} = \beta r_e = 100 \times 25.71 = 2.571 K\Omega$

ii) $r_{in}(\text{stage}) = R_B // \beta r_e = 9.8 // 2.571 = 2.03 K\Omega$


iii) $r_o(\text{stage}) = R_C // r_c / \beta \approx R_C = 1 K\Omega$

iv) $A_v = -\frac{R_C}{r_e} = \frac{-1000}{25.71} = -38.8$

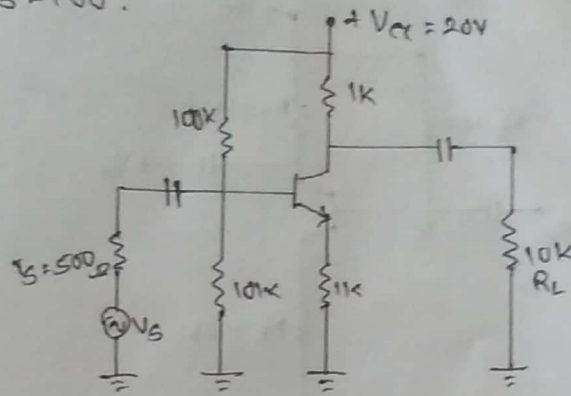
v) $\frac{V_L}{V_S} = A_v \left(\frac{r_{in}(\text{stage})}{r_s + r_{in}(\text{stage})} \right) \left(\frac{R_L}{R_L + r_o(\text{stage})} \right)$

$$= -38.8 \times \left(\frac{2.03}{0.5 + 2.03} \right) \times \left(\frac{10}{10 + 1} \right) = -28.98$$

Draw re-model & find r_{in} , $r_{in(stage)}$, $r_o(stage)$, A_v , V_L/V_S & i_L/i_S . Take $\beta = 100$.



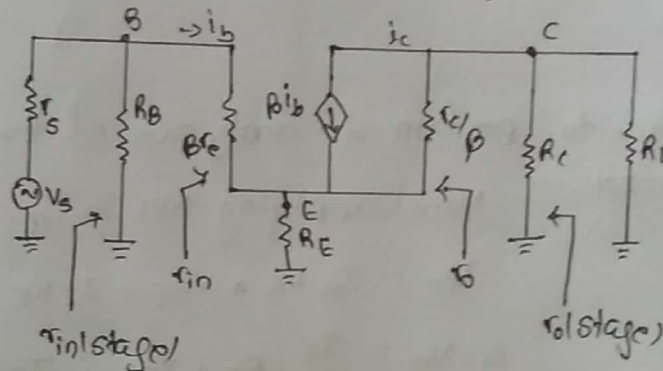Soln: Here, $r_e = \frac{0.026}{I_E} = \frac{0.026}{1.01 \times 10^{-3}} = 25.71 \Omega$



i) $r_{in} = \beta(r_e + R_E)$

$= 100 (25.71 + 1000) = 102.57 K\Omega$

ii) $r_{in(stage)} = R_B // r_{in} = (R_1 // R_2) // r_{in} = 9.8 K // 102.57$
 $= 8.94$

iii) $r_o(stage) = R_C // r_c/B \approx R_C = 1K$


iv) $A_v = \frac{-R_C}{r_e + R_E} = \frac{-1000}{25.71 + 1000} \approx -0.97$

v) $\frac{V_L}{V_S} = A_v \left(\frac{r_{in(stage)}}{r_s + r_{in(stage)}} \right) \times \left(\frac{R_L}{r_o(stage) + R_L} \right)$
 $= -0.97 \times \left(\frac{8.94}{0.5 + 8.94} \right) \times \left(\frac{10}{10 + 1} \right)$
 $= -0.83$

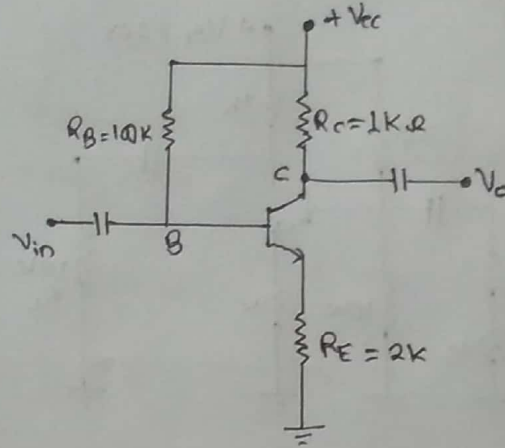vi) $\frac{i_L}{i_S} = \frac{V_L}{V_S} \left(\frac{r_s + r_{in(stage)}}{R_L} \right)$

$= -0.83 \left(\frac{0.5 + 8.94}{10} \right) = -0.78$


Draw r_e -model & find r_{in} , $r_{in(stage)}$, $r_{o(stage)}$, A_v . Take $\beta = 100$.



Soln: We know that,

$$r_e = \frac{0.026}{I_E}$$

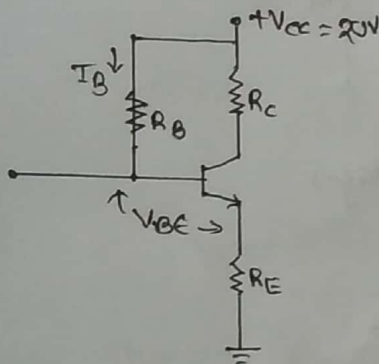To find I_E , we have to perform dc analysis of the ckt.



Now, applying KVL in i/p loop

$$V_{cc} = I_B R_B + V_{BE} + I_E R_E$$


$$\text{or, } V_{cc} = \frac{I_E}{\beta} R_B + V_{BE} + I_E R_E$$

$$\text{or, } I_E = \frac{V_{cc} - V_{BE}}{R_B/\beta + R_E}$$

$$\text{or, } I_E = \frac{20 - 0.7}{100/100 + 2}$$

$$= 6.43 \text{ mA}$$
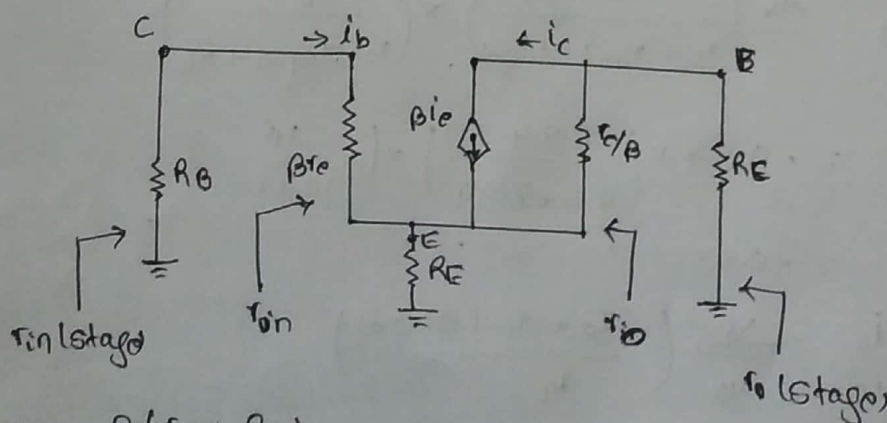
$$\therefore r_e = \frac{0.026}{6.43 \times 10^{-3}} = 4.04 \Omega$$



$$\begin{aligned} i) r_{in} &= \beta(r_e + R_E) \\ &= 100 \times (4.04 + 2000) \\ &= 200.404 \text{ k}\Omega \end{aligned}$$

$$\text{ii) } r_{in}(\text{stage}) = R_B // r_{in} = 1000 // 200.404 \\ = 66.71 \text{ K}\Omega$$

$$\text{iii) } r_{ol}(\text{stage}) \approx R_C // r_o / \beta = R_C = 1 \text{ K}\Omega$$

$$\text{iv) } A_v = - \frac{R_C}{r_o - R_E} = - \frac{1000}{4.04 + 2000} = -0.4989$$

r_e -model of Common Collector Configuration

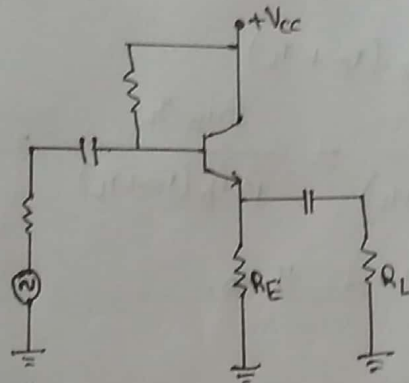


Fig: Common Collector Configuration

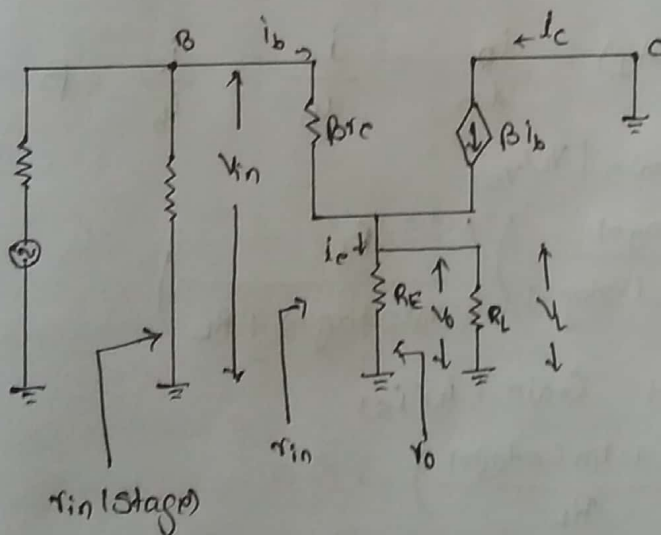


Fig: r_e -model

* If o/p is taken from R_E side if no resistor in V_{cc} side, then common collector configuration

i) Input resistance (r_{in})

$$r_{in} = \frac{V_{in}}{I_{in}}$$

$$V_{in} = i_b \cdot \beta r_e + i_e (R_E // R_L) \quad (\because r_L = R_E // R_L)$$

$$= i_b \beta r_e + i_e \cdot r_L$$

$$= i_b \beta r_e + \beta i_b r_L$$

$$V_{in} = \beta i_b (r_e + r_L)$$

$$I_{in} = i_b$$

$$\text{Thus, } r_{in} = \frac{\beta i_b (r_e + r_L)}{i_b} = \beta (r_e + r_L)$$

$$ii) r_{in}(\text{stage}) = R_B // r_{in} = R_B // \beta(r_e + r_L)$$

$$iii) r_{ol}(\text{stage}) = R_E // \left(\frac{r_s // R_B + \beta r_e}{\beta} \right)$$

$$iv) \text{Voltage Gain } (A_v) = \frac{V_o}{V_{in}} = \frac{i_e (R_E // R_L)}{i_e r_L} = \frac{\beta i_b r_L}{\beta i_b r_L} = \frac{r_L}{r_e + r_L}$$

$$V_o = i_e (R_E // R_L)$$

$$= i_e \cdot r_L$$

$$\& V_{in} = \beta i_b (r_e + r_L)$$

$$A_v = \frac{i_e \cdot r_L}{\beta i_b (r_e + r_L)} = \frac{\beta i_b \cdot r_L}{\beta i_b (r_e + r_L)} = \frac{r_L}{r_e + r_L}$$

If R_L is not connected then,

$$r_L = R_E$$

$$\therefore A_v = \frac{R_E}{r_e + R_E}$$

$$v) \text{Current Gain } (A_i) = \frac{i_o}{i_{in}} = \frac{i_e}{i_b} = \frac{i_c}{i_b} = \beta$$


vi) Overall Voltage Gain (V_L/V_S)

$$\frac{V_L}{V_S} = A_v \left(\frac{r_{in}(\text{stage})}{r_s + r_{in}(\text{stage})} \right) \left(\frac{R_L}{r_{ol}(\text{stage}) + R_L} \right)$$

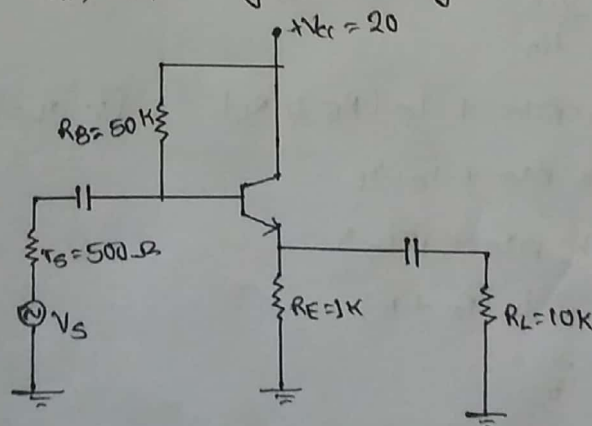vii) Overall Current Gain (i_L/i_s)

$$\frac{i_L}{i_s} = \frac{V_L}{V_S} \left(\frac{r_s + r_{in}(\text{stage})}{R_L} \right)$$


For the transistor amplifier ckt shown below, draw its re-model & find r_{in} , $r_{in}(\text{stage})$, $r_{ol}(\text{stage})$, A_v & V_L/V_S . ($\beta=100$)



Soln: We know that

$$r_e = \frac{0.026}{I_E}$$

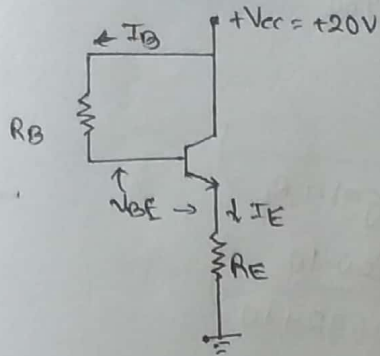To find I_E , we need to perform dc analysis of given ckt,



Applying KVL in i_p loop,


$$V_{CC} = I_B R_B + V_{BE} + I_E R_E$$

$$= \frac{I_E}{\beta} R_B + V_{BE} + I_E R_E$$

$$\Rightarrow I_E = \frac{V_{CC} - V_{BE}}{R_B/\beta + R_E} = \frac{20 - 0.7}{50/100 + 1}$$

$$= \frac{19.3}{1.5} = 12.86 \text{ mA}$$

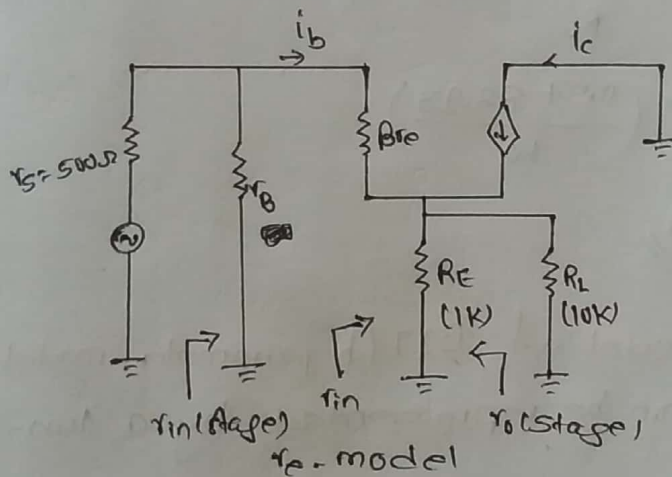Thus, $r_e = \frac{0.026}{12.86 \times 10^{-3}} = 2.02 \Omega$



Now,

i) $r_{in} = \beta(r_e + r_L)$

where, $r_L = R_E \parallel R_L = 1 \parallel 10 = 0.98 \text{ k}\Omega$

ii) $r_{in} = 100(2.02 + 980) = 98.202 \text{ k}\Omega$

iii) $r_{in(stage)} = R_B \parallel r_{in}$

$$= 50 \parallel 98.202 = 82.93 \text{ k}\Omega$$

iv) $r_o(stage) = R_E \parallel \left(\frac{r_s \parallel R_B + \beta r_e}{\beta} \right)$

$$= 1 \parallel \left(\frac{0.5 \parallel 50 + 100 \times 2.02 \times 10^{-3}}{100} \right)$$

$$= 1 \parallel \left(\frac{0.495 + 0.202}{100} \right)$$

$$= 1 \parallel 0.00697$$

$$= 0.00692 \text{ k}\Omega$$

$$v) \text{ Voltage gain } (A_v) = \frac{r_L}{r_o + r_L} = \frac{980}{2.02 + 980} = 0.9979 //$$


vi) Overall Voltage Gain (V_L/V_S)

$$\begin{aligned} \frac{V_L}{V_S} &= A_v \left(\frac{r_{in}(\text{stage})}{r_s + r_{in}(\text{stage})} \right) \left(\frac{R_L}{r_{o1}(\text{stage}) + R_L} \right) \\ &= 0.99 \left(\frac{82.93}{500\Omega + 82.93} \right) \left(\frac{980}{0.00692 + 980} \right) \\ &= 0.99 \left(\frac{82.93}{0.5 + 82.93} \right) \times \left(\frac{10}{10 + 0.00692} \right) \\ &= 0.983 // \end{aligned}$$

$$\begin{aligned} vii) \frac{i_L}{i_s} &= \frac{V_L}{V_S} \left(\frac{r_s + r_{in}(\text{stage})}{R_L} \right) \\ &= 0.983 \times \left(\frac{0.5 + 82.93}{10} \right) \\ &= 8.201 // \end{aligned}$$

Hybrid Parameter model of BJT (h-parameter model of BJT)

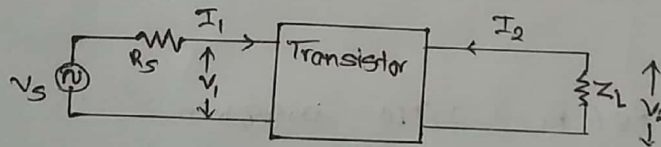A BJT amplifier ckt can be represented by a two-port n/w as shown below,



Here,
 V_1 = i/p voltage
 I_1 = i/p current
 V_2 = o/p voltage
 I_2 = o/p current
 Z_L = load impedance
 R_S = source resistance
 V_S = source voltage

The h-parameter eqn for above 2-port n/w is given by,

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

where,
 h_{11} = h_{ie} i/p impedance (resistance)
 h_{12} = h_{re} → reverse voltage gain
 h_{21} = h_{fe} → forward current gain
 h_{22} = h_{oe} → o/p admittance

Thus,
$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_i & h_r \\ h_f & h_o \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

i.e, $V_1 = h_i I_1 + h_r V_2$ — (i)

& $I_2 = h_f I_1 + h_o V_2$ — (ii)

From above two-port n/w,

$V_2 = -I_2 Z_L$ — (iii)

From above eqns we can draw h-parameter model of transistor as below:

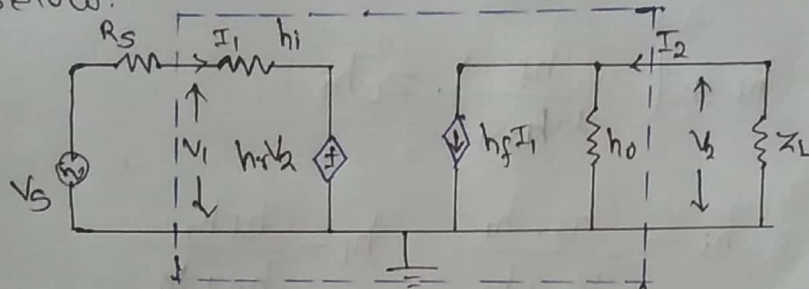


Fig: h-parameter model of transistor

Here, i) Current gain (A_I) = $-\frac{I_2}{I_1}$ — (iv)

From eqn (2), $I_2 = h_f I_1 + h_o V_2$

or, $I_2 = h_f I_1 + h_o (-I_2 Z_L)$

or, $I_2 = h_f I_1 - h_o I_2 Z_L$

or, $I_2 (1 + h_o Z_L) = h_f I_1$

or, $\frac{I_2}{I_1} = \frac{h_f}{1 + h_o Z_L}$ or, $\frac{I_2}{I_1} = \frac{h_f}{1 + h_o Z_L}$

$\therefore A_I = -\left(\frac{h_f}{1 + h_o Z_L}\right)$

2) Voltage Gain (A_V) = $\left(\frac{V_o}{V_{in}}\right) = \frac{V_2}{V_1} = \frac{-I_2 Z_L}{V_1}$

= $\frac{-(-A_I I_1) Z_L}{V_1}$ (∵ From eqn (iv))

= $\frac{A_I \cdot Z_L}{V_1 / I_1}$ $A_I = \frac{-I_2}{I_1}$

$\therefore A_V = \frac{A_I Z_L}{Z_i}$

where, $Z_i = \frac{V_1}{I_1} \Rightarrow$ i/p impedance.

iii) I/p impedance (Z_i)

$$Z_i = \frac{\text{i/p voltage}}{\text{i/p current}} = \frac{V_1}{I_1}$$

From eqn (2),

$$V_1 = I_1 h_i + h_r V_2 = I_1 h_i + h_r (-I_2 Z_L)$$

$$= I_1 h_i - h_r I_2 Z_L = I_1 h_i - h_r (-A_I I_1) Z_L$$

$$= I_1 h_i + A_I I_1 Z_L h_r$$

$$\text{or, } V_1 = I_1 (h_i + A_I Z_L h_r)$$

$$\text{or, } \frac{V_1}{I_1} = h_i + \left(\frac{-h_f}{1+h_o Z_L} \right) \cdot Z_L h_r$$

$$= h_i - \frac{h_f \cdot h_r}{\frac{1}{Z_L} + h_o} = h_i - \frac{h_f h_r}{h_o + Y_L}$$

$$\text{where, } Y_L = \frac{1}{Z_L}$$

$$\therefore Z_i = \frac{V_1}{I_1} = h_i - \frac{h_f h_r}{h_o + Y_L}$$

iv) O/p admittance (Y_o) & O/p impedance (Z_o)

$$Y_o = \frac{\text{o/p current}}{\text{o/p voltage}} \quad \text{with } V_s = 0$$

$$= \frac{I_2}{V_2} \quad \text{with } V_s = 0 \quad (\text{neglecting } -V_o \text{ sign})$$

$$\text{we have, } I_2 = h_f I_1 + h_o V_2$$

$$\text{So, } Y_o = \frac{h_f I_1 + h_o V_2}{V_2} = h_f \frac{I_1}{V_2} + h_o = h_o + h_f \frac{I_1}{V_2}$$

— To find I_1/V_2 , apply KVL in i/p side of the h-model.

$$V_s = I_1 R_s + I_1 h_i + h_r V_2$$

$$\text{or, } 0 = I_1 (R_s + h_i) + h_r V_2$$

$$\text{or, } I_1 (R_s + h_i) = -h_r V_2$$


$$\text{or, } \frac{I_1}{V_2} = -\frac{h_r}{R_s + h_i}$$

$$\therefore Y_o = h_o + h_f \left(-\frac{h_r}{R_s + h_i} \right)$$

$$\phi Z_0 = 1/Y_0$$

$$v) \text{ Overall Voltage Gain, } (A_{Vs}) = \frac{V_2}{V_S} = \frac{V_2}{V_1} \times \frac{V_1}{V_S} \\ = A_V \left(\frac{V_1}{V_S} \right)$$

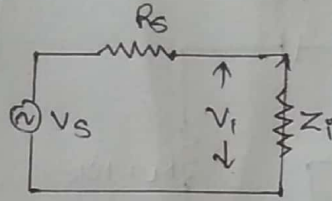→ To find V_1/V_S , let's draw Thevenin's equt ckt of i/p side.




$$\therefore V_1 = \frac{Z_i}{Z_i + R_S} \times V_S$$

$$\text{or, } \frac{V_1}{V_S} = \frac{Z_i}{Z_i + R_S}$$

$$\text{Thus, } A_{Vs} = A_V \times \left(\frac{Z_i}{Z_i + R_S} \right)$$

$$vi) \text{ Overall Current Gain } (A_{Is}) = \frac{-I_2}{I_S} = -\frac{I_2}{I_1} \times \frac{I_1}{I_S} \\ = A_I \times \frac{I_1}{I_S}$$

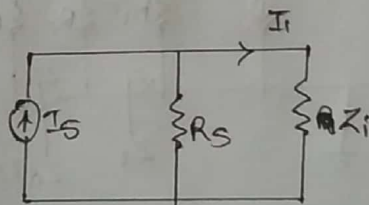→ To find I_1/I_S , draw Norton's - equt ckt




$$\text{Here, } I_1 = \frac{R_S}{R_S + Z_i} \times I_S$$

$$\text{or, } \frac{I_1}{I_S} = \frac{R_S}{R_S + Z_i}$$


$$\therefore A_{Is} = A_I \times \left(\frac{R_S}{R_S + Z_i} \right)$$

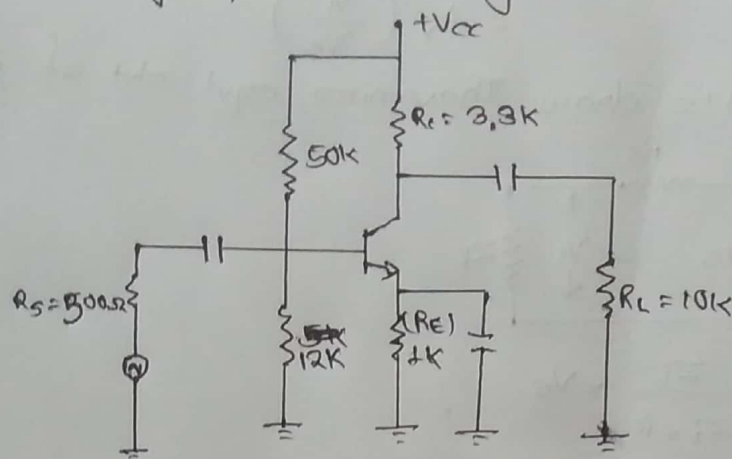For the given transistor amplifier ckt, the h-parameters are, $h_{ie} = 1600 \Omega$, $h_{fe} = 80$, $h_{re} = 20 \times 10^{-4}$ & $h_{oe} = 20 \mu S$.
Find Z_i , Z_i (stage), Z_o , Z_o (stage), A_i , A_v , A_{vs} & A_{is} .



Soln: Given, $h_{ie} = 1600 \Omega$
 $h_{fe} = 80$
 $h_{re} = 20 \times 10^{-4}$
 $h_{oe} = 20 \mu S$

The h-parameter model of given ckt is,

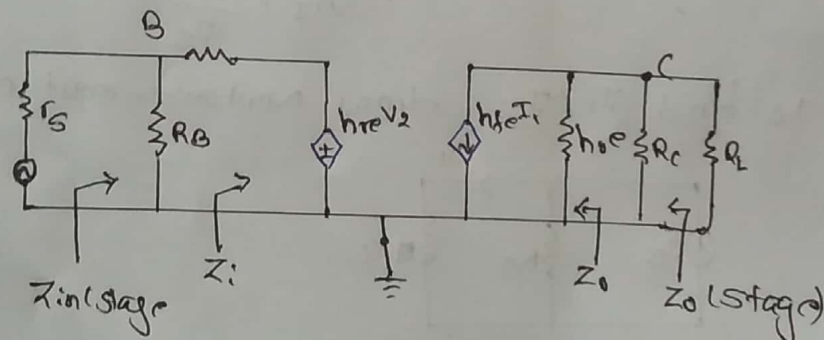

Here,

$$Z_L = R_C \parallel R_L = 3.3 \parallel 10 = 2.48 K\Omega$$

$$R_B = R_1 \parallel R_2 = 50 \parallel 12 = 9.8 K\Omega$$

Now, i) $Z_i = h_{ie} - \frac{h_{fe} * h_{re}}{h_{oe} + Y_L}$

where, $Y_L = \frac{1}{Z_L} = \frac{1}{2.48 \times 10^3} = 4.03 \times 10^{-4} S$

$$\therefore Z_i = 1600 - \frac{80 \times 20 \times 10^{-4}}{20 \times 10^{-6} + 4.03 \times 10^{-4}} = 1221.95 \Omega$$

ii) Z_i (stage) $= R_B \parallel Z_i$
 $= 9800 \parallel 1221.95$
 $= 1086.47 \Omega$

$$iii) Z_0 = 1/Y_0$$

$$\text{where, } Y_0 = h_{oe} - \frac{h_{fe} \cdot h_{re}}{h_{ie} + R_S // R_B}$$

$$= 20 \times 10^{-6} - \left(\frac{80 \times 20 \times 10^{-4}}{1600 + (500 // 9800)} \right)$$

$$= -5.7 \times 10^{-5} \text{ S}$$

$$= 5.7 \times 10^{-5} \text{ (neglecting -ve sign)}$$

$$\therefore Z_0 = \frac{1}{Y_0} = \frac{1}{5.7 \times 10^{-5}} = 17.518 \text{ k}\Omega$$

$$iv) Z_0 (\text{stage}) = R_C // Z_0$$

$$= 3.3 // 17.518$$

$$= 2.77 \text{ k}\Omega$$

$$v) A_I = \frac{-h_{fe}}{1 + h_{oe} Z_L} = \frac{-80}{1 + 20 \times 10^{-6} \times 2.48 \times 10^3} = -76.22$$

$$vi) A_v = \frac{A_I \cdot Z_L}{Z_i} = \frac{-76.22 \times 2480}{1221.95} = 154.67$$

$$vii) A_{vs} = -A_v \left(\frac{Z_i (\text{stage})}{Z_i (\text{stage}) + R_S} \right)$$